
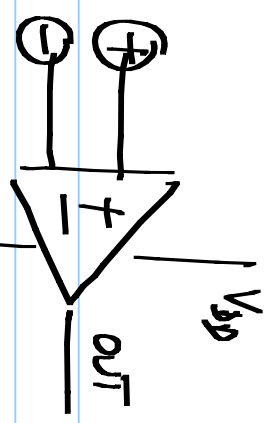


Two stage opamp:

single stage opamp

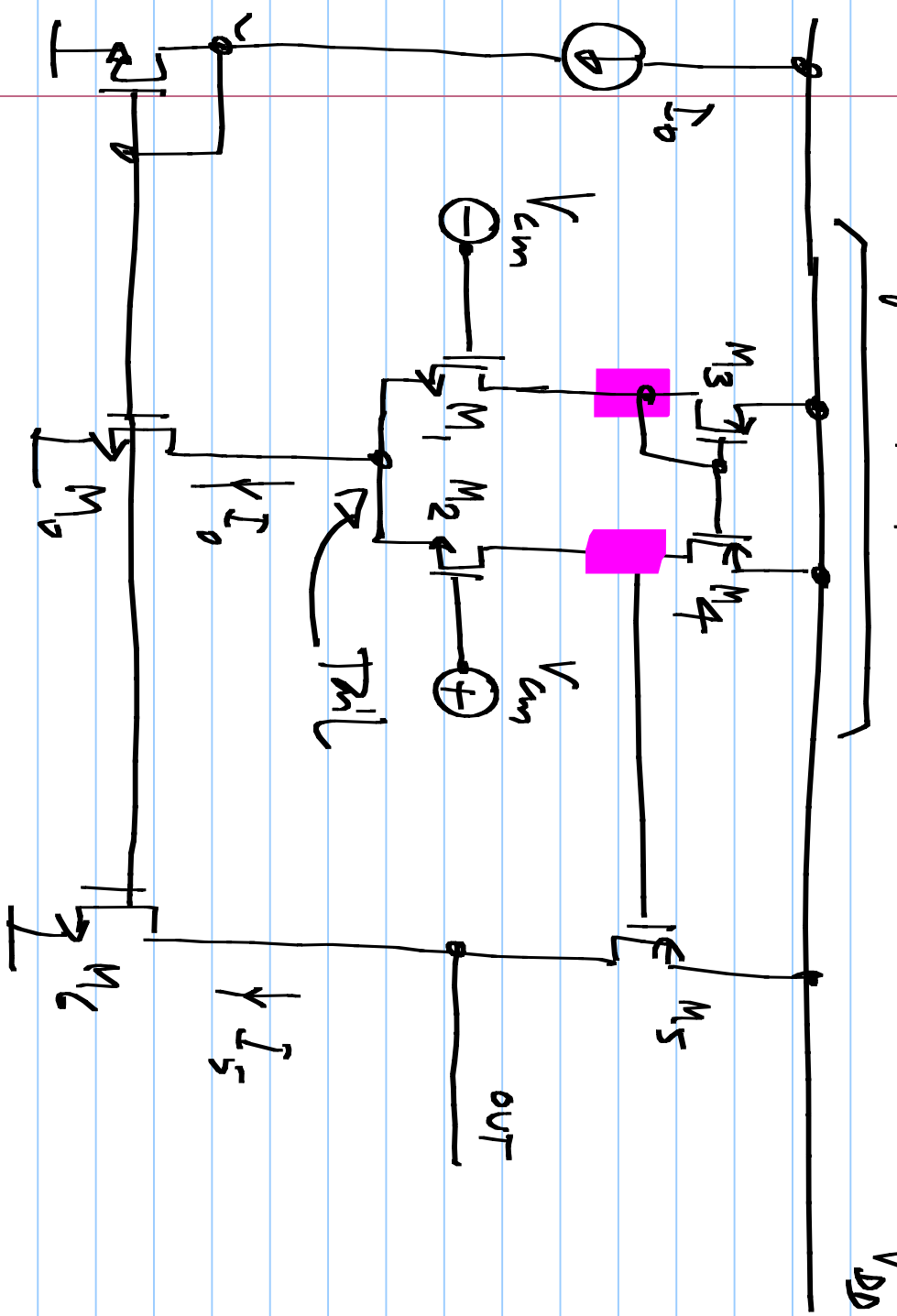


dc gain:

$$A_0 = \frac{g_{m1}}{g_{d1} + g_{d3}}$$

$$\frac{g_{m5}}{(g_{d5} + g_{d6})}$$


$$R_{out} = \frac{1}{g_{d5} + g_{d6}}$$

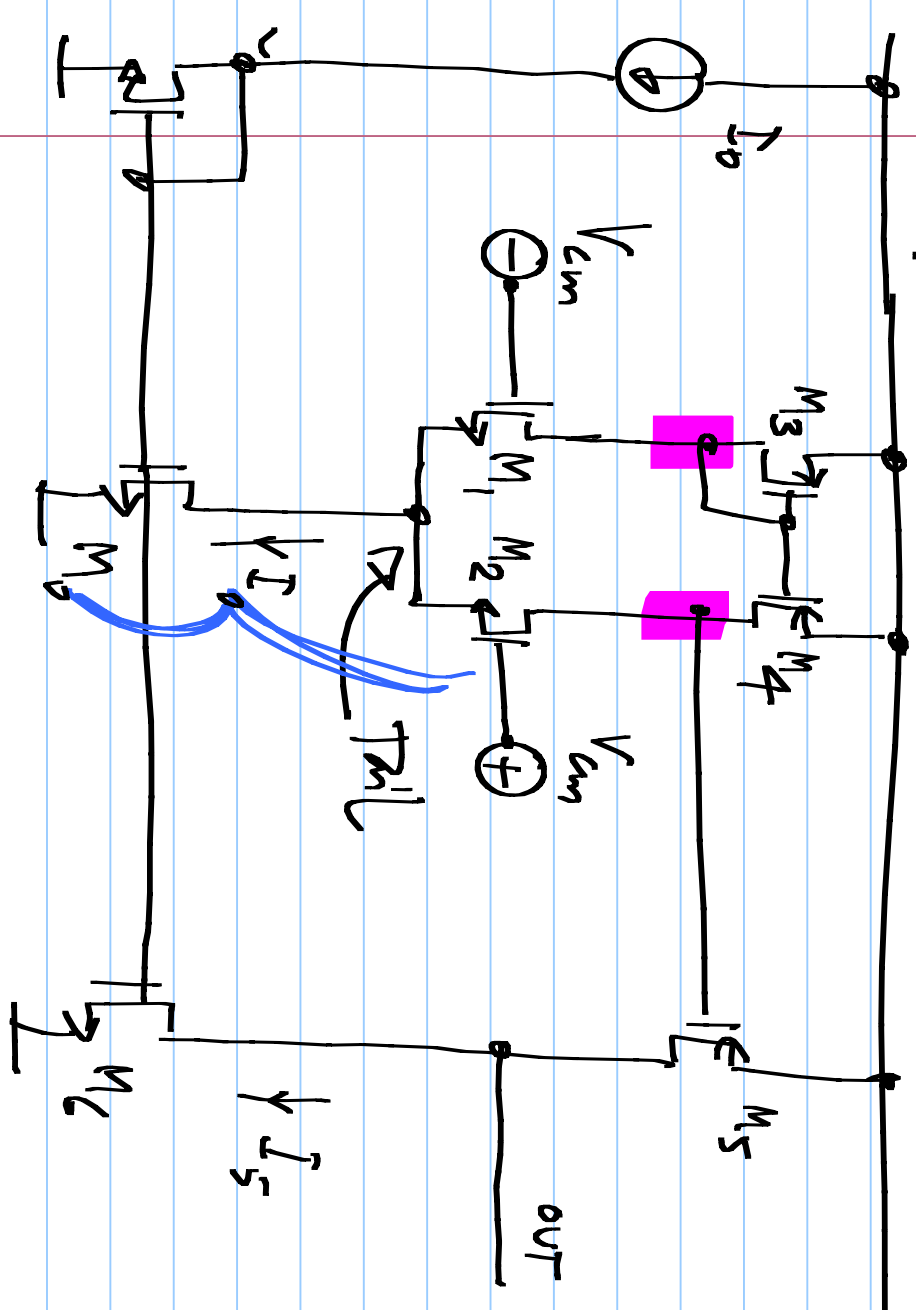
output: single  $V_{DSAT}$  away from  $V_{DD}$  and  $gnd$ : widest output swing





$$\left[ \begin{aligned} &V_{DSAT2} \left| \frac{I_D}{I_S} + V_{DSAT1} \right| + V_{TN} < V_{CM} \\ &< V_{DD} - V_{GS3} \left| \frac{I_D}{I_S} + V_{TN} \right| \end{aligned} \right]$$


$$V_{DSAT2} \left| \frac{I_D}{I_S} \right| < V_{out} < V_{DD} - V_{DSAT1} \left| \frac{I_D}{I_S} \right|$$

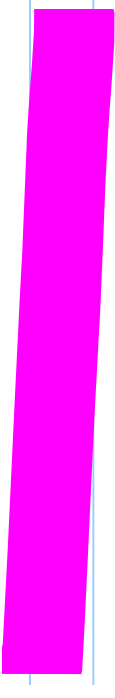

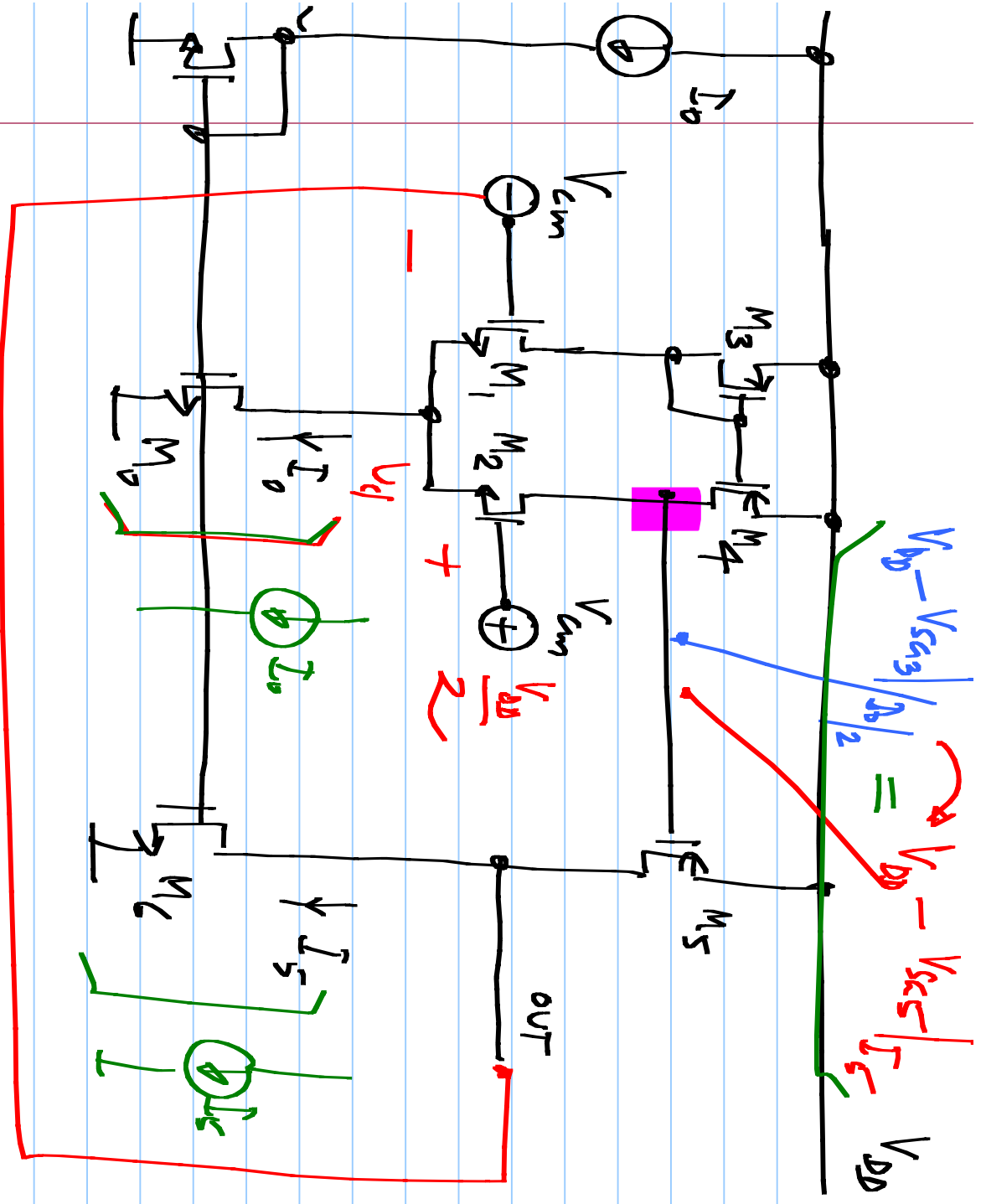
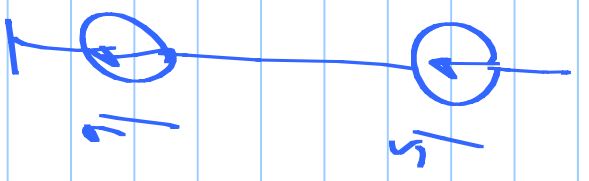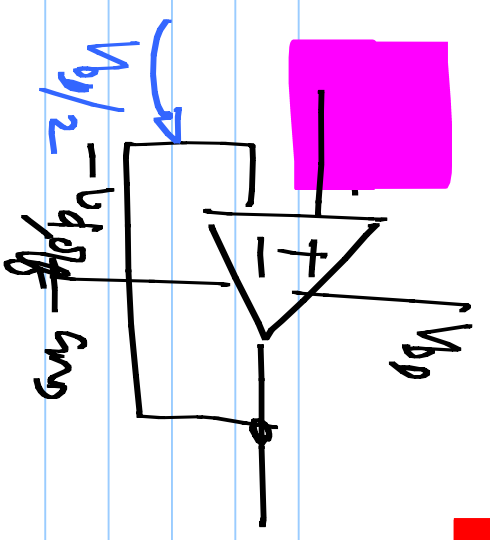
$$V_{DD} - V_{GS3} / \beta / 2 = V_{DD} - V_{GS5} / I_5$$




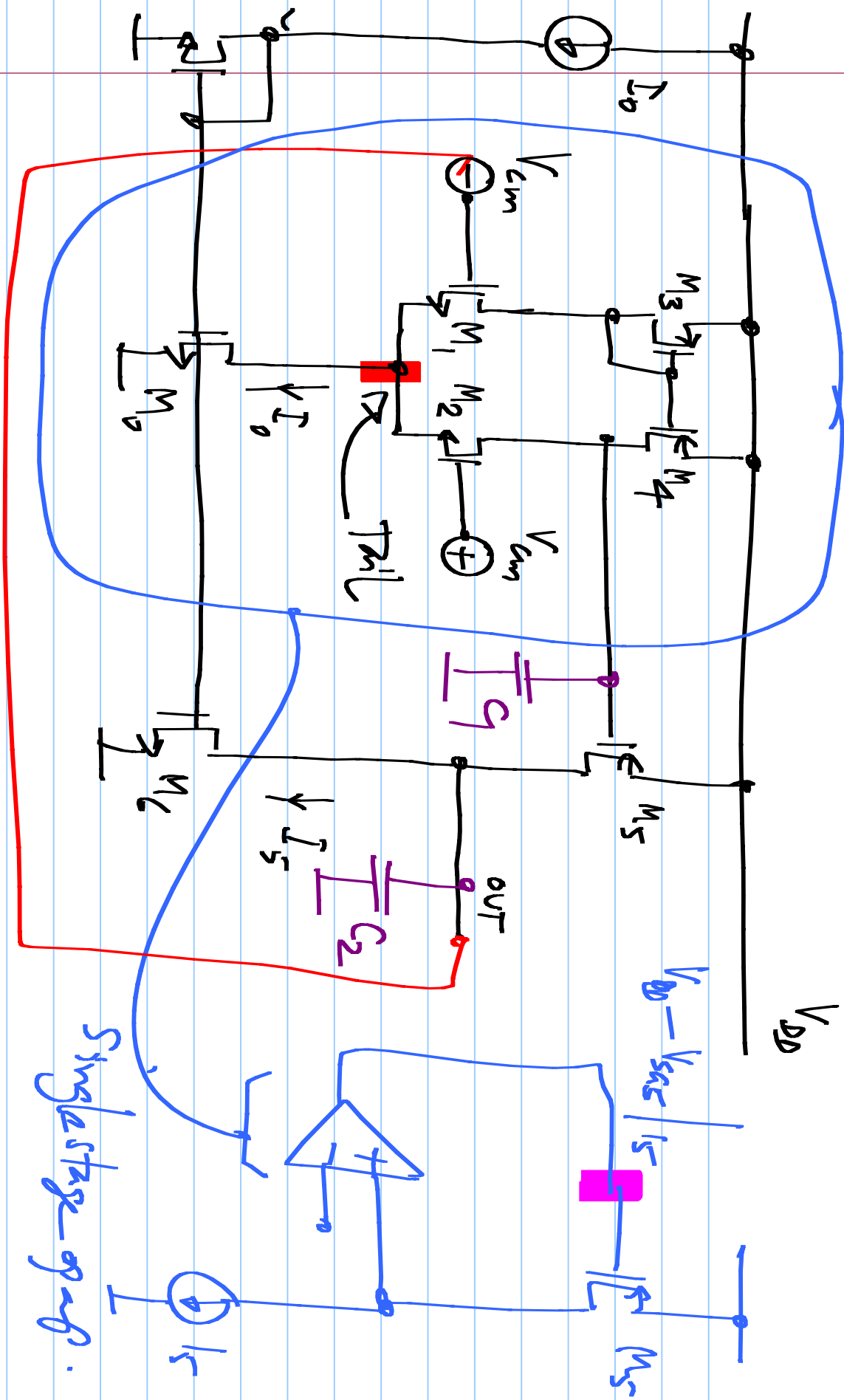

Single stage op-amp.



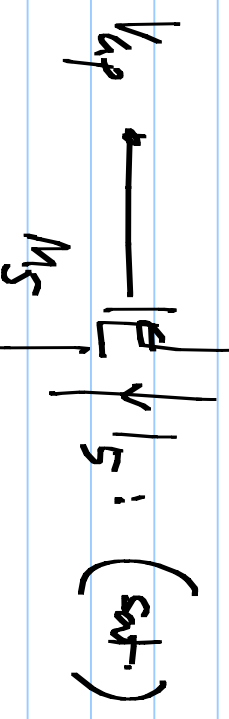
$$I_5 = \frac{\mu_n C_{ox}}{2} \frac{W_5}{L_5} (V_{GS} - V_{TP})^2$$



$$l_6 > l_5$$

$l_5$  flows through  $M_6$

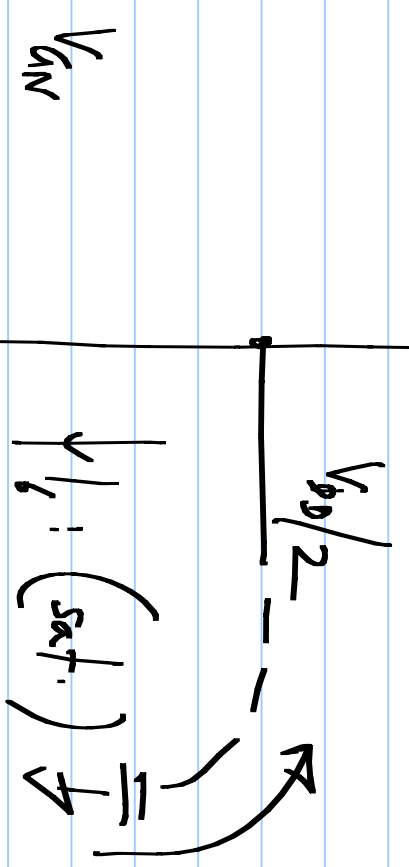

tride

$$l_6 = \frac{\mu_n C_{ox}}{2} \frac{W_6}{L_6} (V_{GS} - V_{TN})^2$$

## Systematic offset

In closed loop, the o/p of the first stage changes

to  $V_{DD} - V_{GS} / I_S$  (from  $V_{DD} - V_{GS} / I_{D/2}$ )

$$\Rightarrow V_{D/2}^{off} =$$

$$\frac{V_{GS3} / I_{D/2} - V_{GS5} / I_S}{A_1}$$


$$A_1 = \frac{g_{m1}}{g_{d1} + g_{d3}}$$

Fix: Design

$$V_{GS5} / I_S = V_{GS3} / I_{D/2}$$

$\Rightarrow$  systematic offset = 0

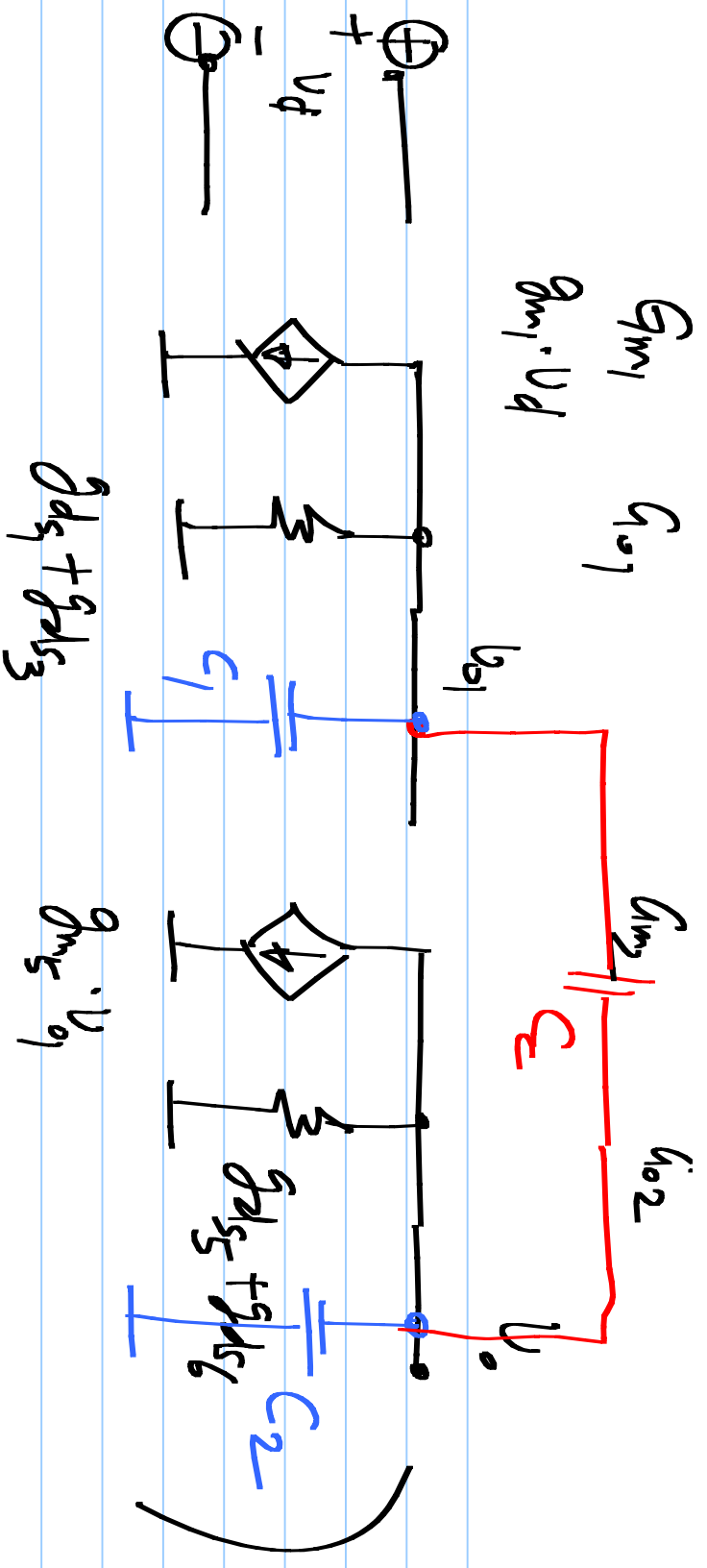May not need to do this if  $A_1$  is very large



$$A(s) = \frac{A_0 \left(1 - \frac{s}{z_1}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$$Z = \frac{g_{m5}}{C_c}, \quad p_1 \approx \frac{g_{ds1} + g_{ds3}}{g_c + (1 + \frac{g_{m5}}{C_c}) C_c}$$

$$p_2 = \frac{g_{m5} \cdot \frac{C_c}{C_c + C_1} + g_{ds5} + g_{ds6}}{C_2 + C_c \parallel C_1}$$

