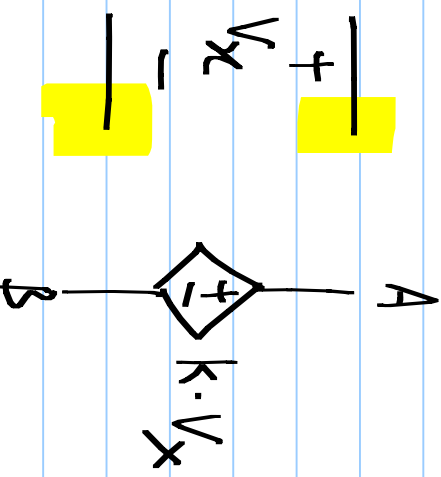


Dependant sources


EE 2015

Controlled sources

8/8/2017




Voltage controlled voltage source
(VCVS)

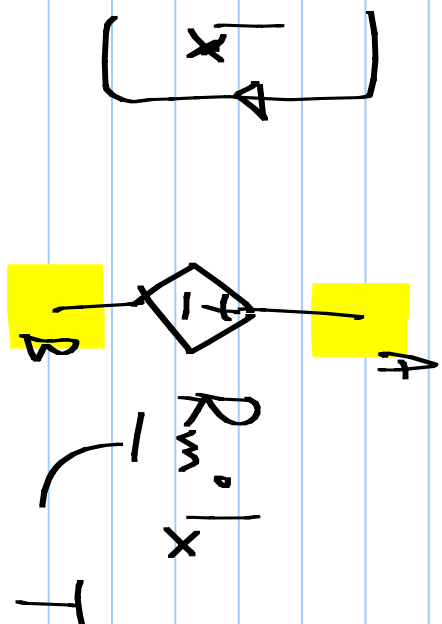


Current controlled voltage source
(CCVS)




Trans resistance

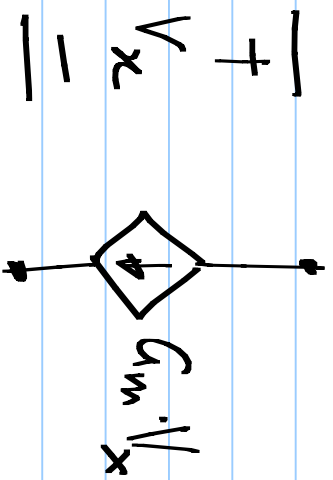


voltage controlled current source
(VCCS)

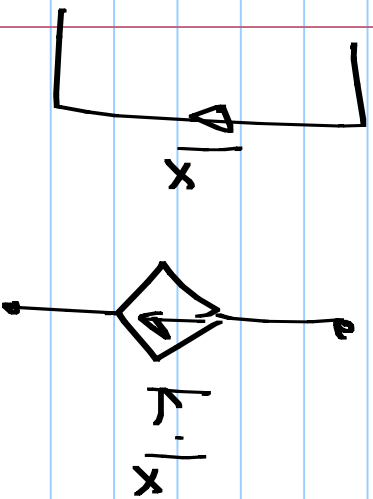

Current controlled current source
(CCCS)

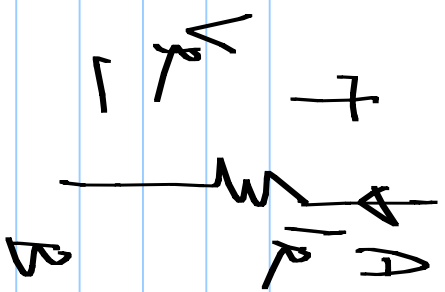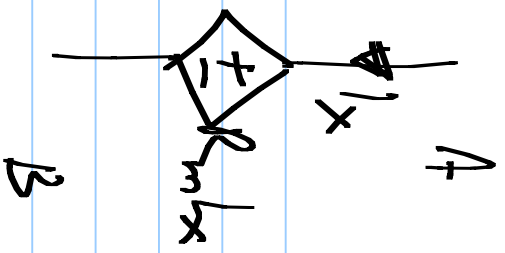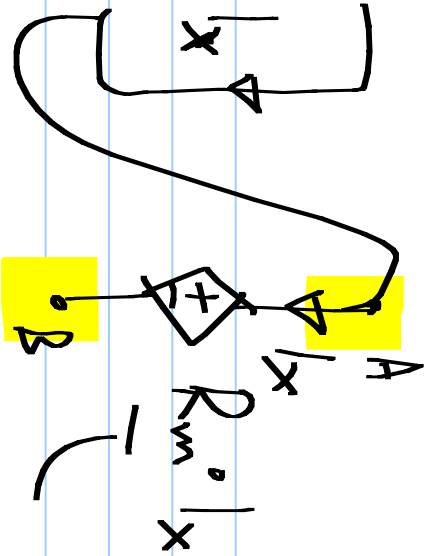


$$V_o = R \cdot I_o$$

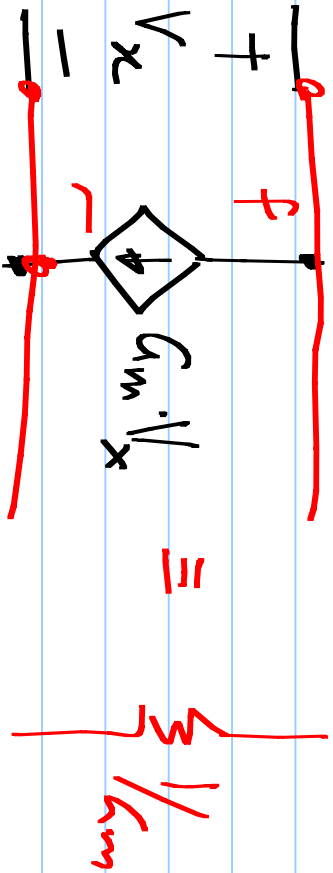

Power and energy:

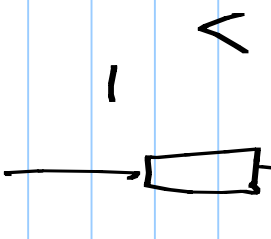+ \downarrow I $P = V \cdot I$: Power absorbed in the element




$$V \cdot I \geq 0$$

Passive element

$P_R \geq 0$ Dissipates

$E_R \geq 0$ power


Resistor:

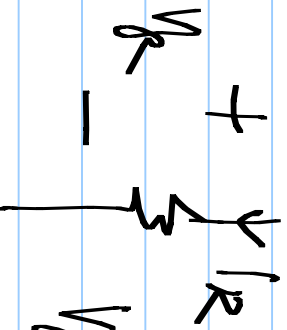

$$V_R = R \cdot I_R$$

$$E_R = \int_0^t P_R(t) \cdot dt$$


$$\frac{V_R^2}{R}$$

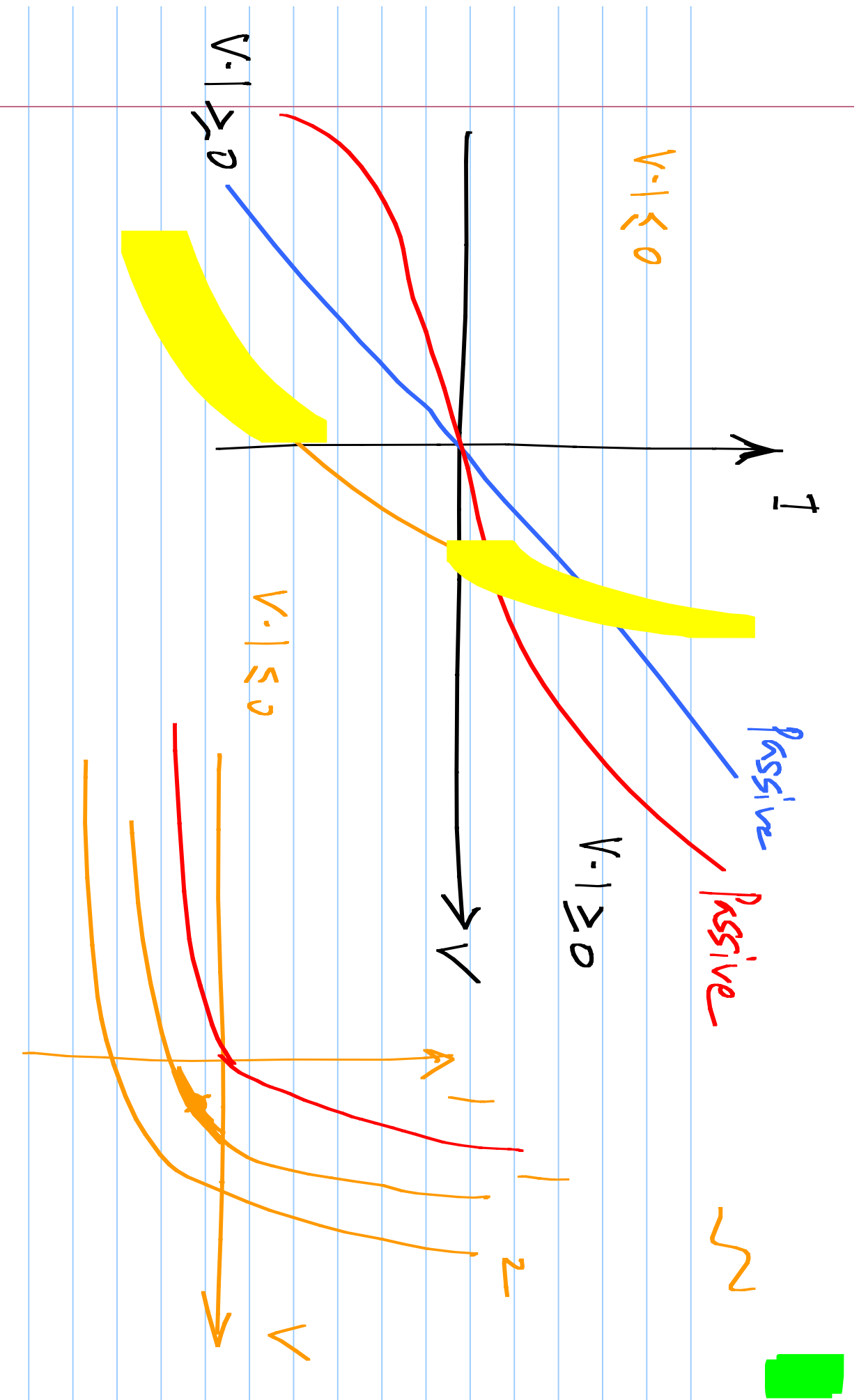

$E_c \geq 0$: passive

Capacitor:
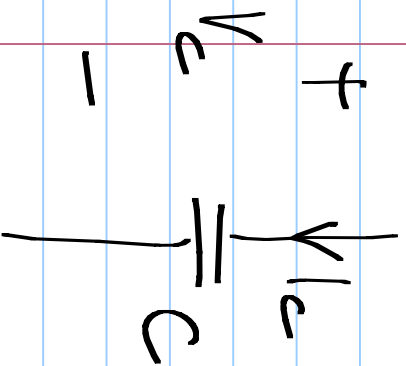
$$I_c = C \cdot \frac{dV_c}{dt} \quad P = C V_c \cdot \frac{dV_c}{dt}$$



$$P = \frac{C}{2} \frac{d}{dt} (V_c^2)$$


$$E_c = \int_{t_1}^{t_2} \frac{C}{2} \frac{d}{dt} (V_c^2) \cdot dt = \frac{C}{2} [V_c^2(t) - V_c^2(0)]$$

$$\text{at } t=0 \quad C \text{ is discharged} \quad \frac{V_c^2(t_2) - V_c^2(t_1)}{2}$$

Inductor:

Passive


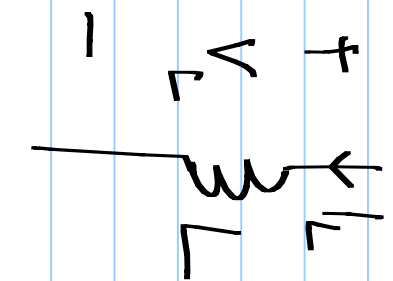
$$V_L = L \cdot \frac{dI_L}{dt} \quad P_L = I_L \cdot V_L \cdot \frac{dI_L}{dt} = \frac{L}{2} \frac{d}{dt} (I_L^2)$$






$$E_L = \int_0^{t_2} \frac{L}{2} \cdot \frac{d}{dt} (I_L^2) dt = \frac{L}{2} (I_L^2(t_2) - I_L^2(t_1))$$


Stored energy in an inductor: $\frac{1}{2} L I_L^2$

E_L

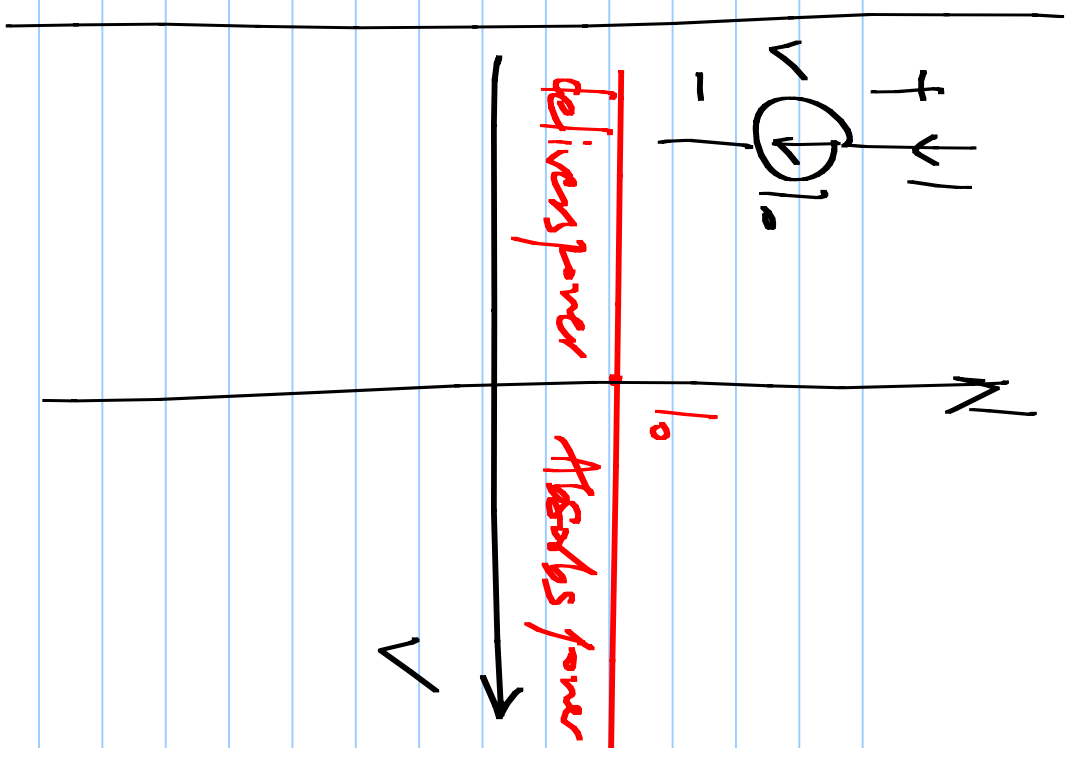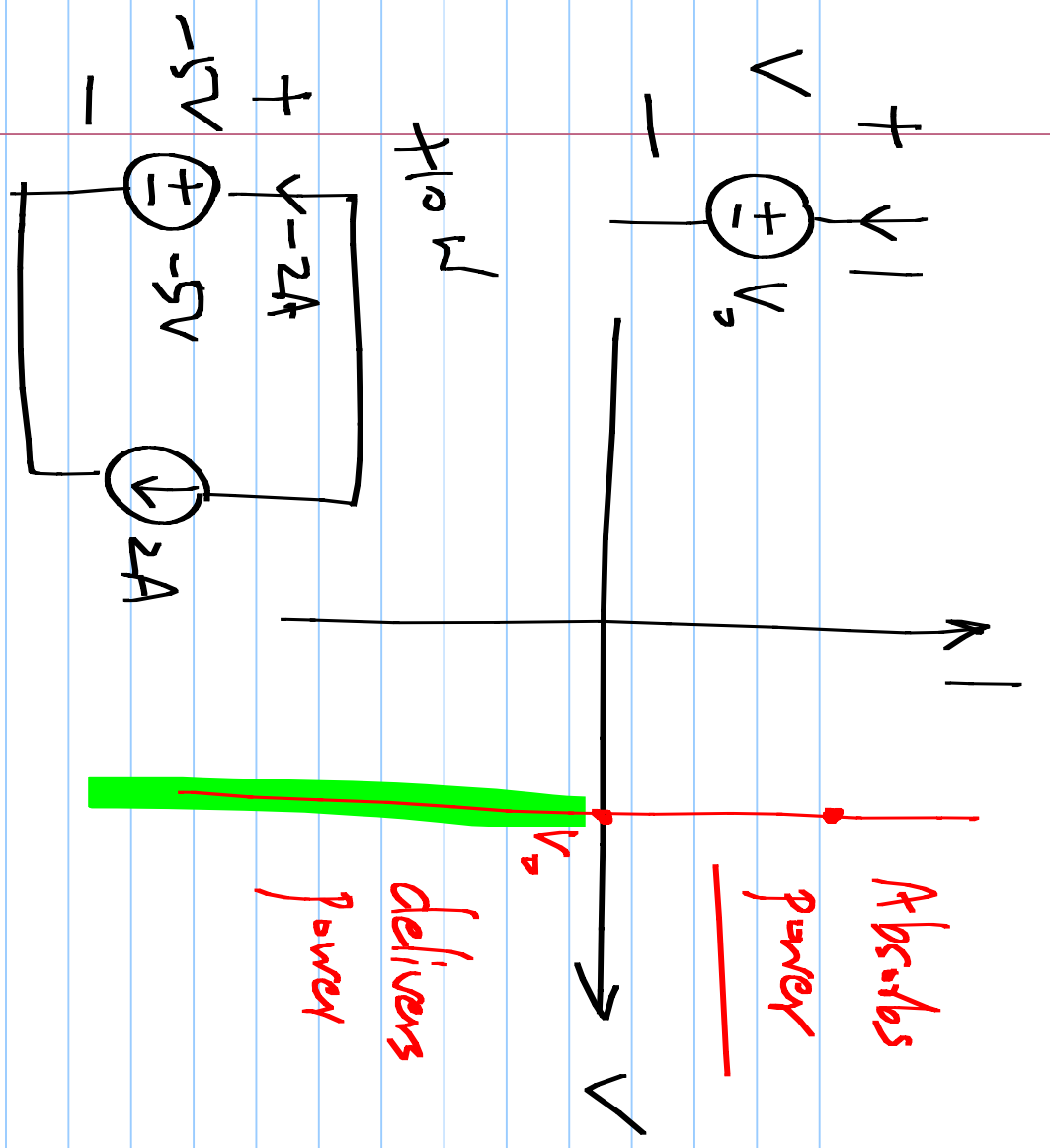


Elements in parallel & series

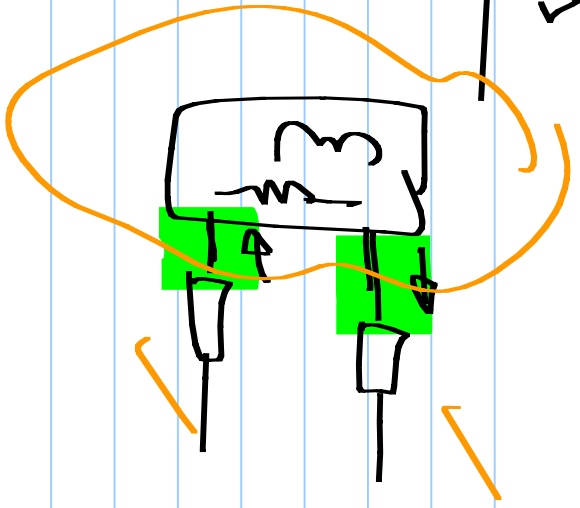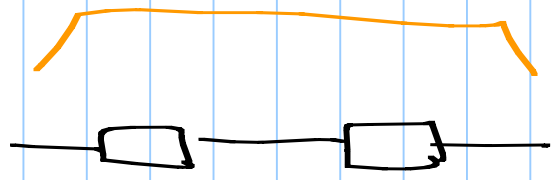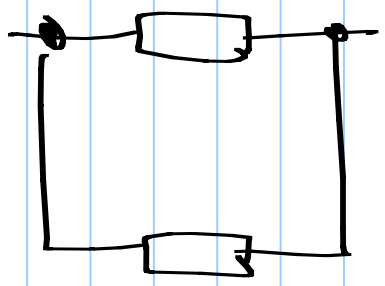

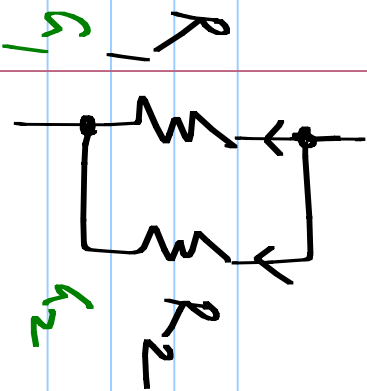


$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$r = r_1 + r_2$$

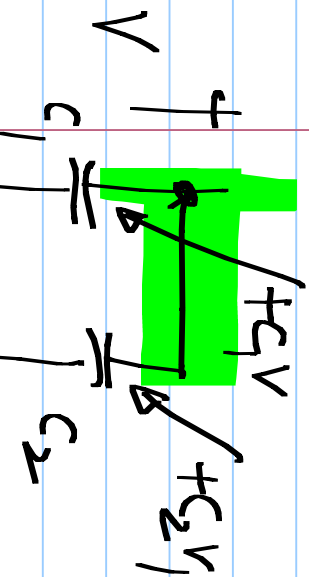


$$C = C_1 + C_2$$





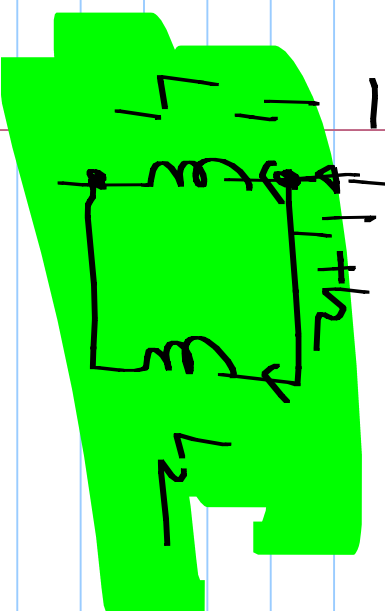



$$L = \frac{L_1 L_2}{L_1 + L_2}$$
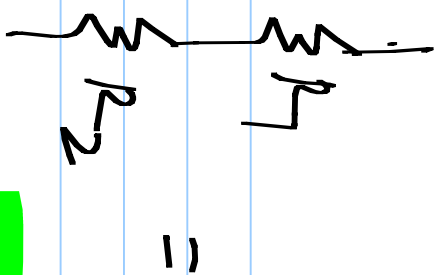
$$V_L = L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt}$$






=

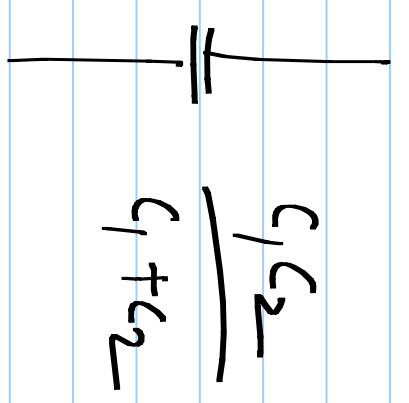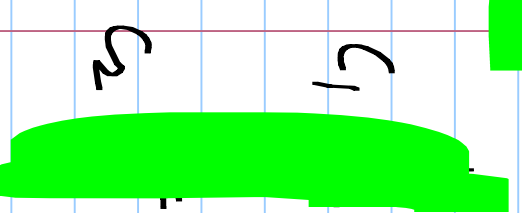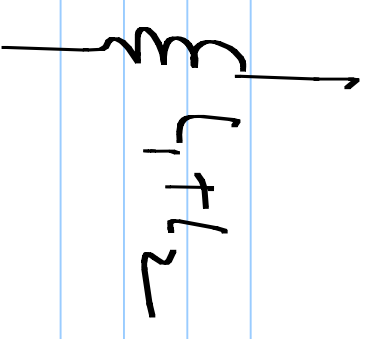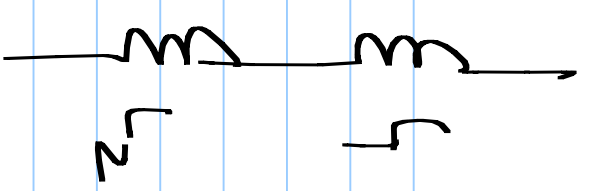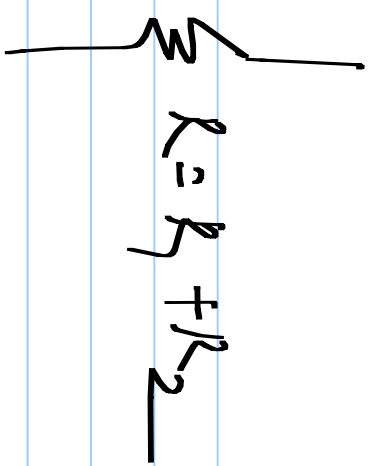

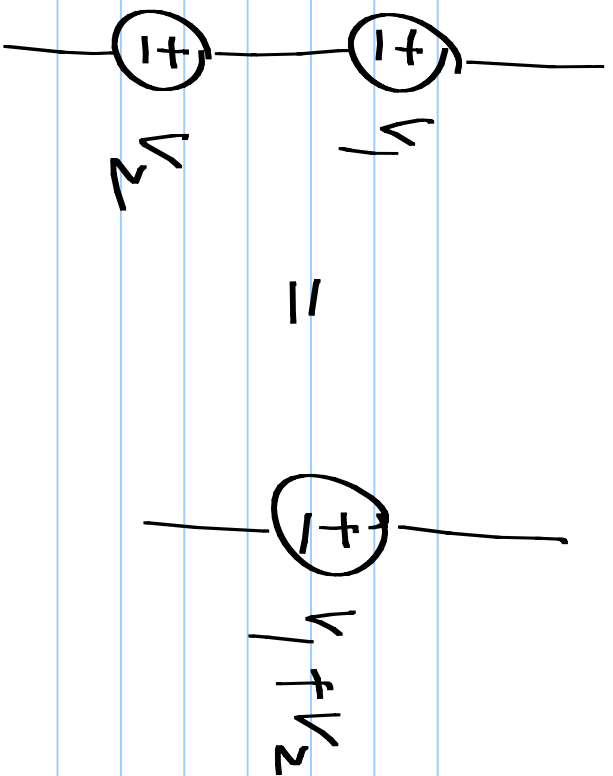


X violates KVL if $V_1 \neq V_2$

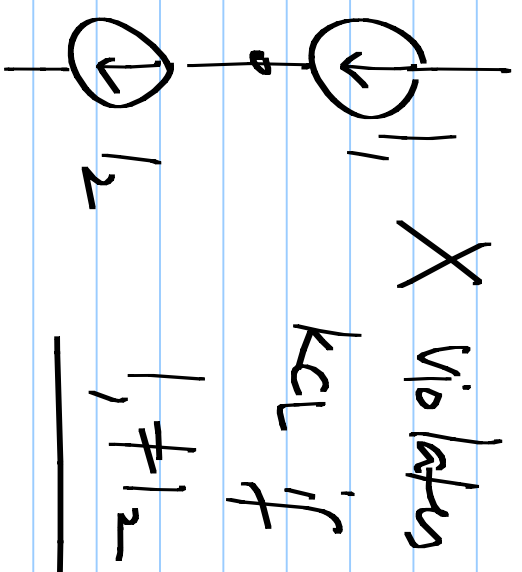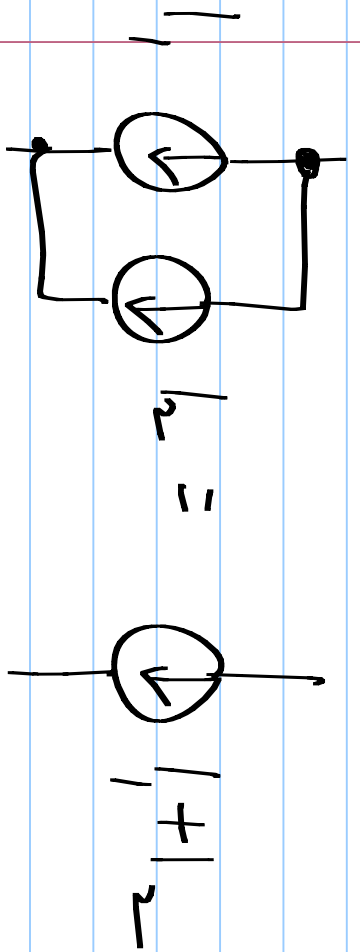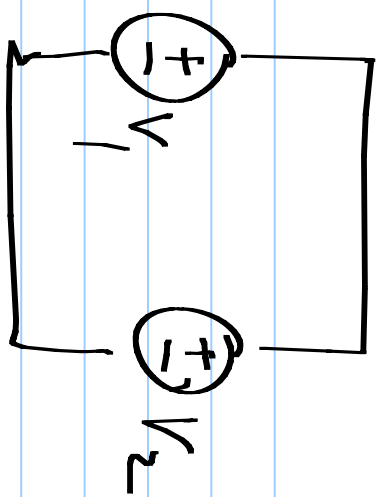



$I_1 \neq I_2$

Mutual inductance

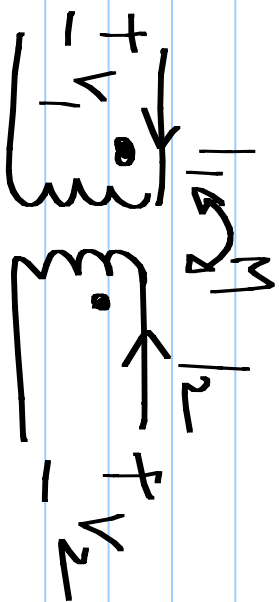

$$\sum_{k=1}^N V_k I_k$$

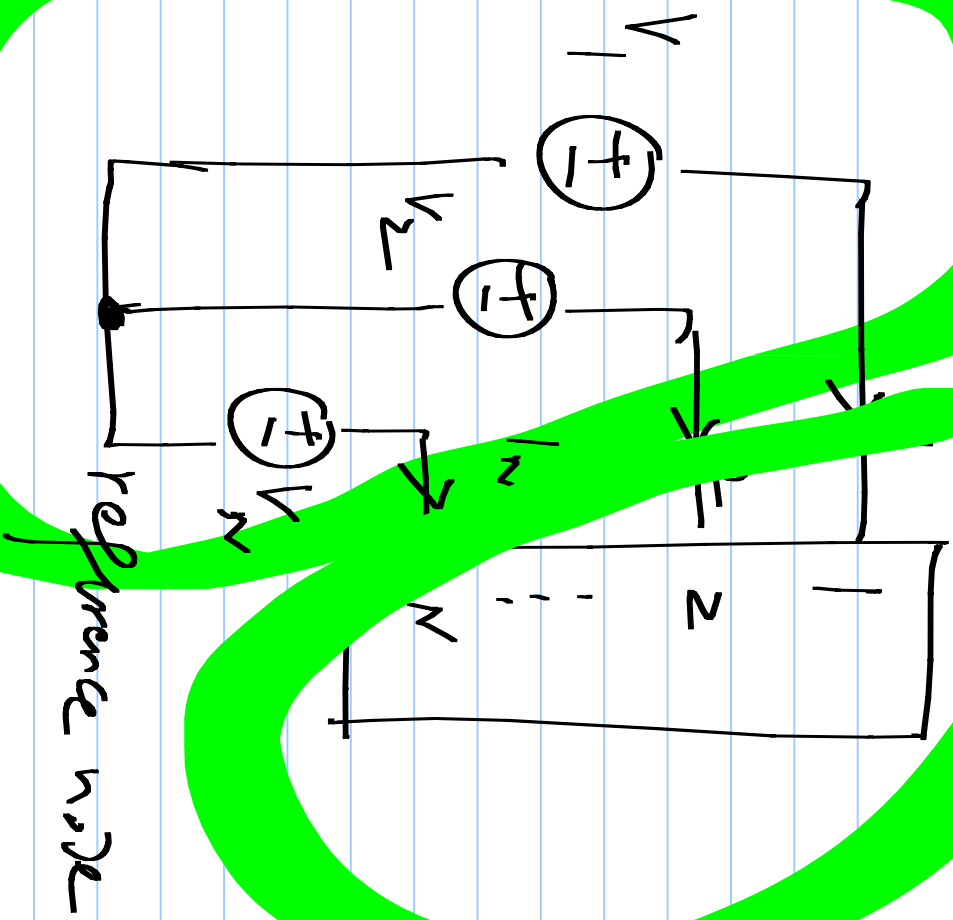

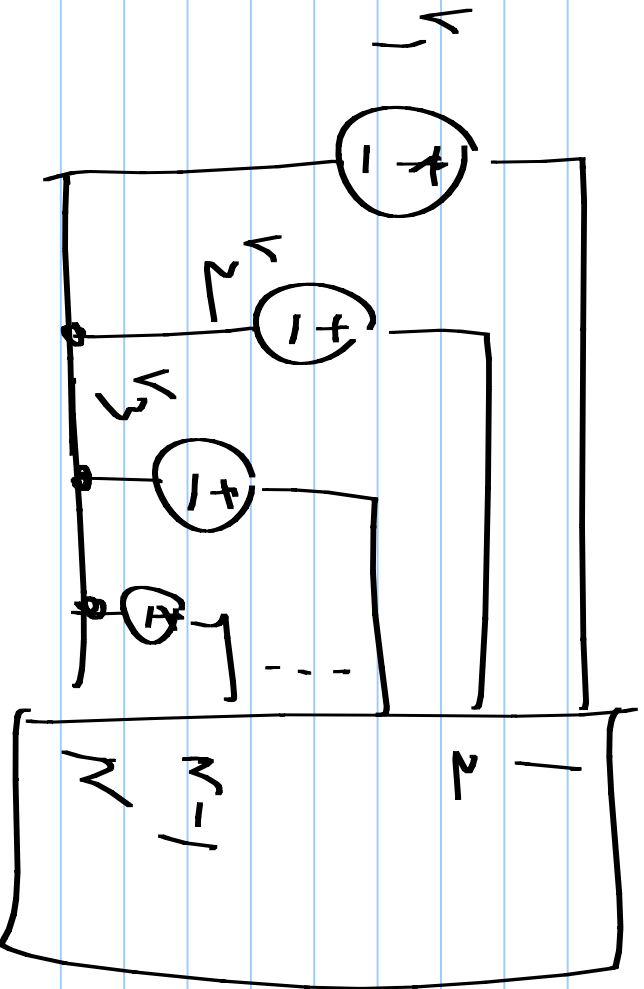

choose $V_N = 0$

$$\sum_{k=1}^{N-1} V_k |k$$