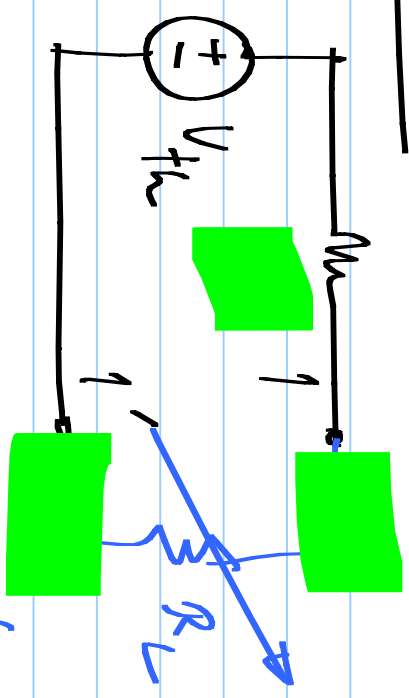


EE 2015 $R_{Th} > 0$




Vary R_L such that P_L is maximized

R_L should be equal to R_{Th} to maximize P_L

(matching for max. power transfer)


29/8/2017

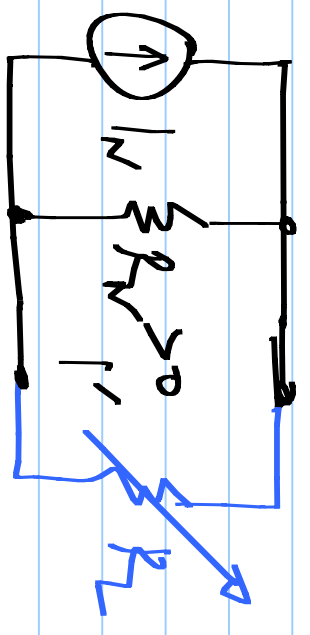

$$P_L = V_{Th}^2 \cdot \frac{R_L}{(R_L + R_{Th})^2}$$

$$P_{L,max} = \frac{V_{Th}^2}{4 \cdot R_{Th}} ; \text{ Available power}$$

($R_L = R_{Th}$)

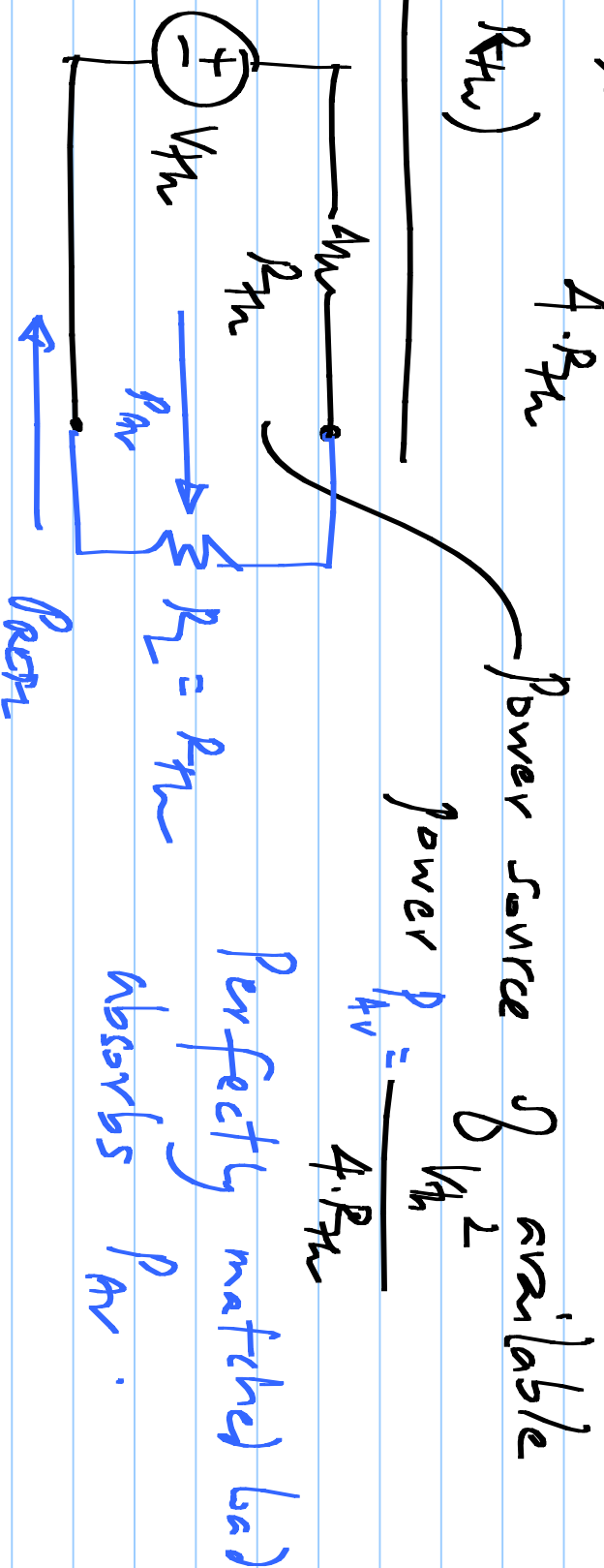

When $R_L \neq R_{th}$

Γ : reflection coefficient

$$P_L = P_{Av} - P_{refl}$$

Calculate P_{refl} & Γ

$$= P_{Av} (1 - \Gamma^2)$$

$$1 - \Gamma^2 =$$

$$\frac{4 \cdot R_{th} R_L}{(R_L + R_{th})^2}$$


$$V_{th}^2 \frac{R_L}{(R_L + R_{th})^2} = \frac{V_{th}^2}{4 R_{th}} \cdot (1 - \Gamma^2)$$

$$\Gamma^2 = 1 - \frac{4 R_{th} R_L}{(R_L + R_{th})^2} = \frac{(R_L - R_{th})^2}{(R_L + R_{th})^2}$$

Refl. coeff: $\Gamma = \left| \frac{R_L - R_{th}}{R_L + R_{th}} \right|$


$0 \leq \Gamma \leq 1$ $\Gamma = 0 \Rightarrow R_L = R_{th}$: Perfect matching

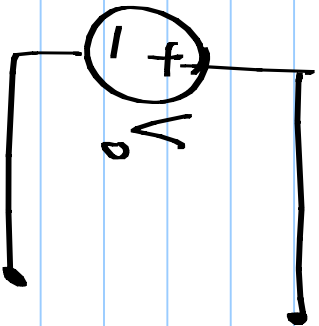$\Gamma = 1 \Rightarrow R_L = \infty$ or $R_L = 0$!




No independent sources

Two-terminal networks

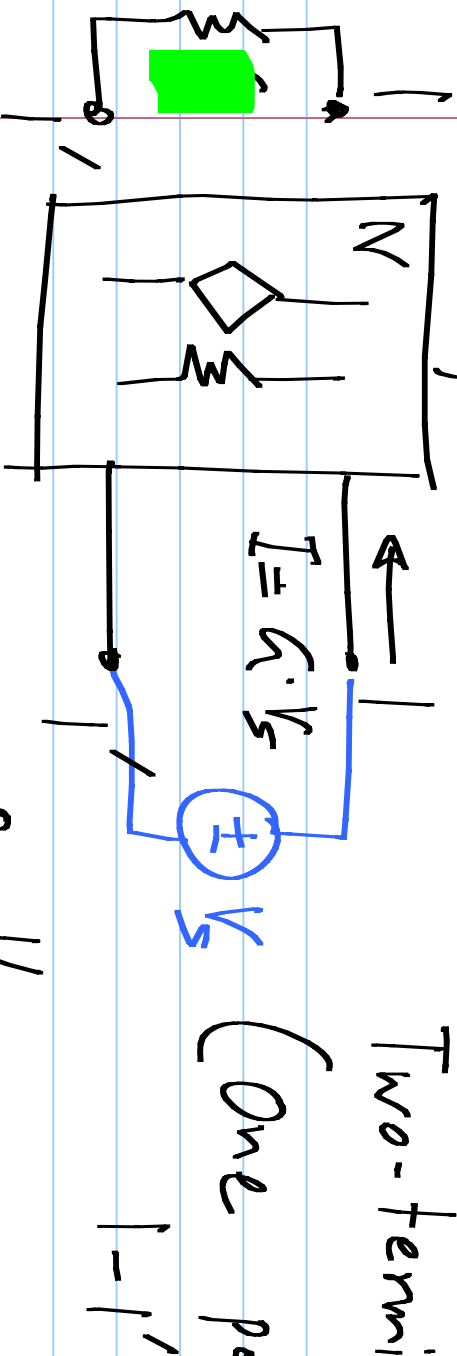


(One port network)

$$R = \frac{1}{G}$$

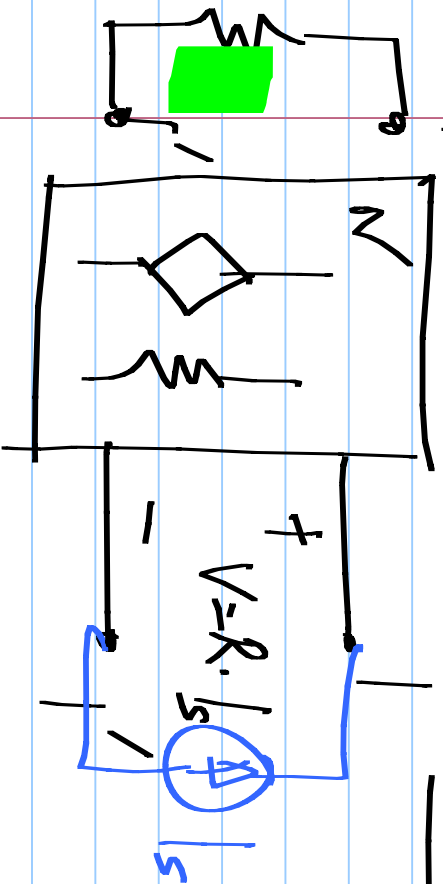
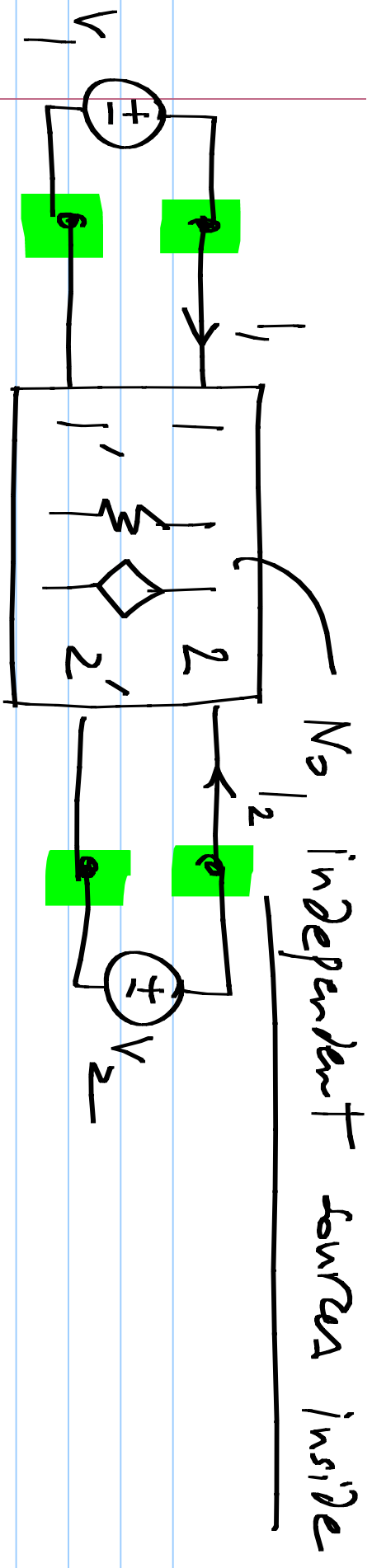
$$\begin{bmatrix} 0 & 1 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix} = z$$






$$I_1 = () \cdot V_1 + () \cdot V_2$$

$$I_2 = () \cdot V_1 + () \cdot V_2$$


Two-port Parameters

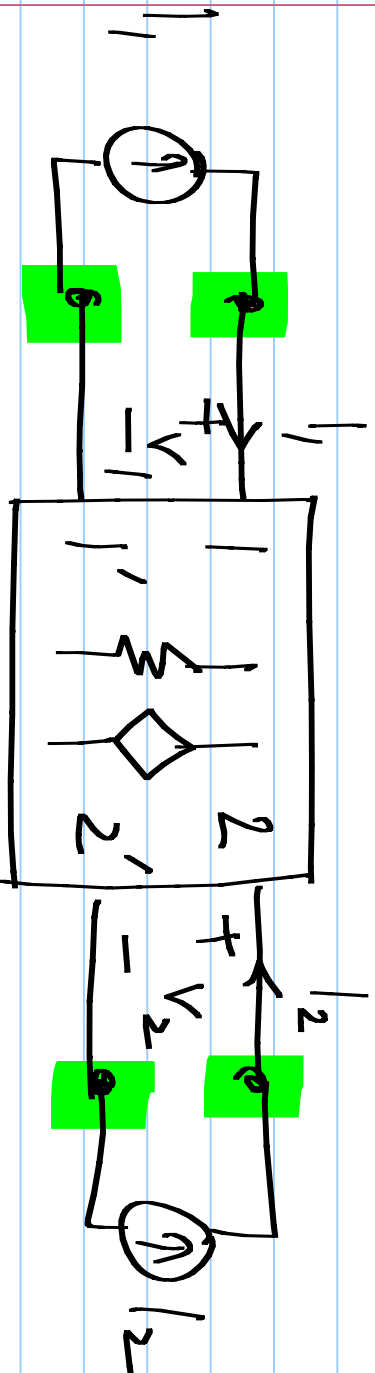

$$V_1 = () \cdot I_1 + () \cdot I_2$$

$$V_2 = () \cdot I_1 + () \cdot I_2$$

Two-port parameters

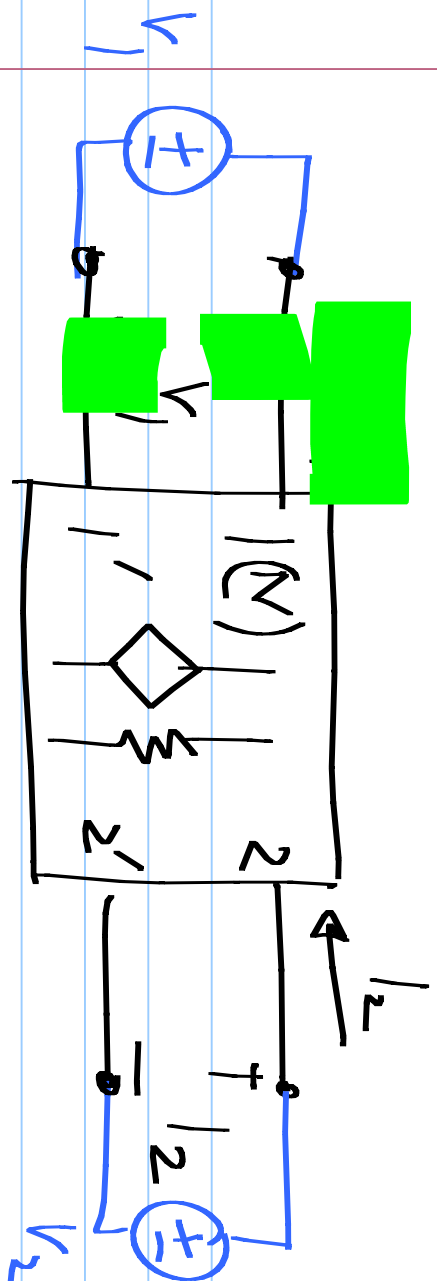

Relationship between $\{V_1, I_1\}$ & $\{V_2, I_2\}$
 2-port parameters


$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

short-circuit


y-parameters of N

Measuring 2-port Parameters

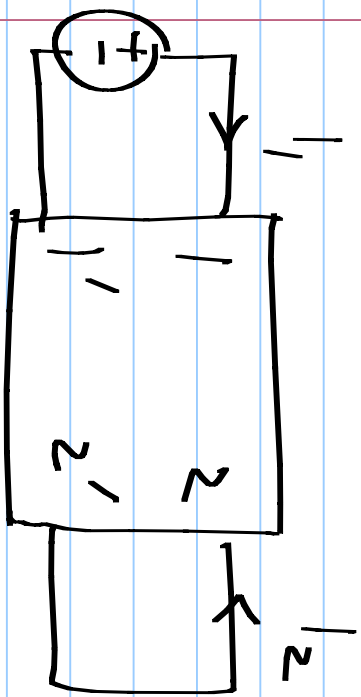

$V_1 \neq 0$
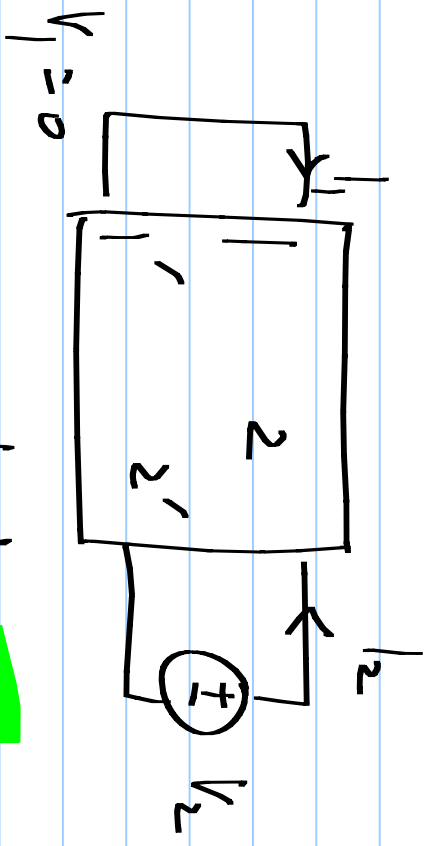
$$y_{11} = \frac{I_1}{V_1} \quad \text{or looking into } 1-1' \text{ with } 2-2' \text{ Shorted}$$



$$y_{22} = \frac{I_2}{V_2} \quad \text{or looking into } 2-2' \text{ with } 1-1' \text{ Shorted}$$

$$y_{21} = \frac{I_2}{V_1} \quad \text{with } V_2 = 0$$

$$y_{12} = \frac{I_1}{V_2} \quad \text{with } V_1 = 0$$

