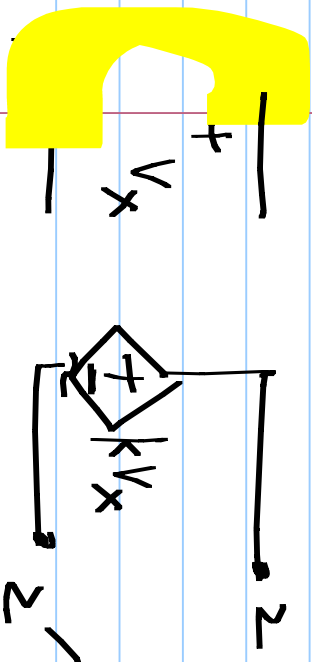


EE 2015

Two-port networks

8/9/2017

Controlled sources




$$g = \begin{bmatrix} 0 & 0 \\ k & 0 \end{bmatrix}$$

$$V_2 = k \cdot V_1$$

$$\left. \begin{matrix} V_2 \\ V_1 \end{matrix} \right|_{I_2=0}$$


$$Z = \infty$$

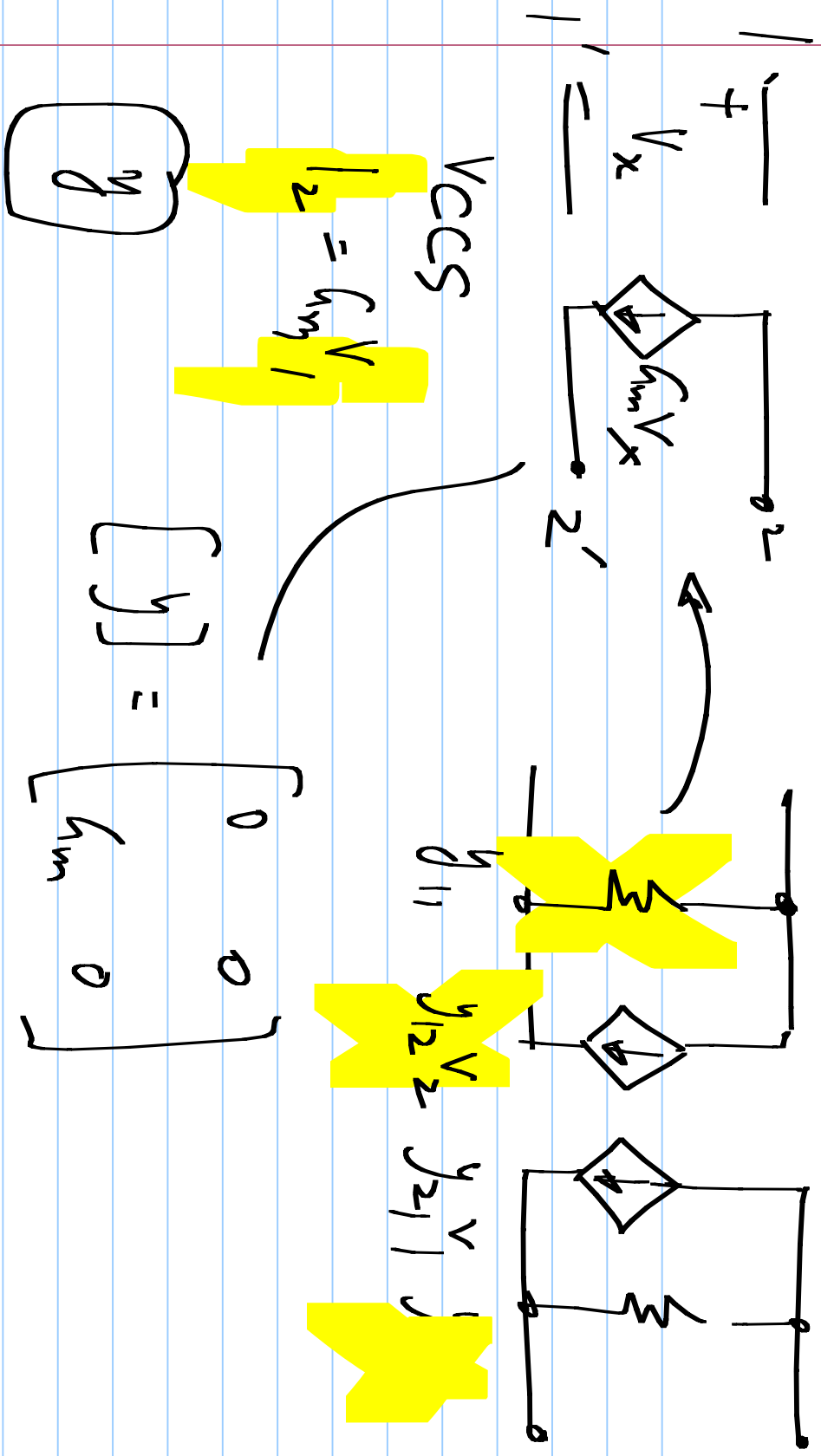


$$[y] =$$
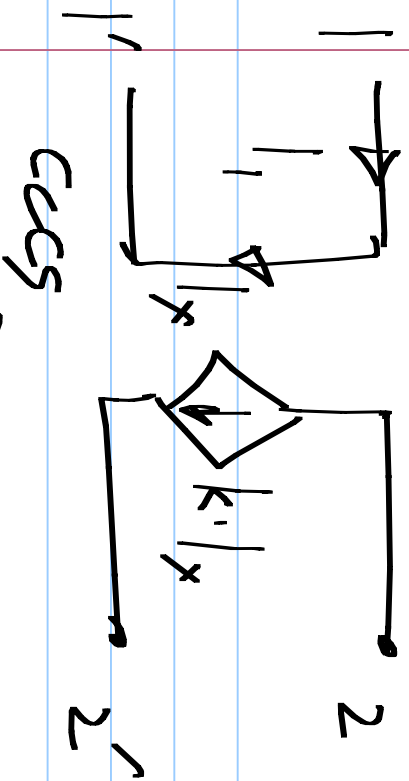
$$\begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$





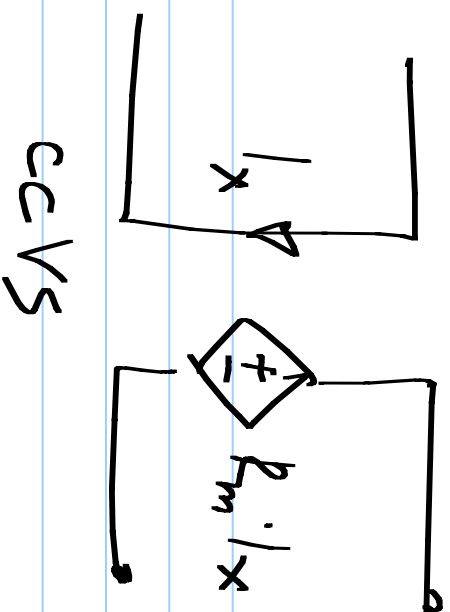
$$W = \begin{bmatrix} 0 & 0 \\ k & 0 \end{bmatrix}$$




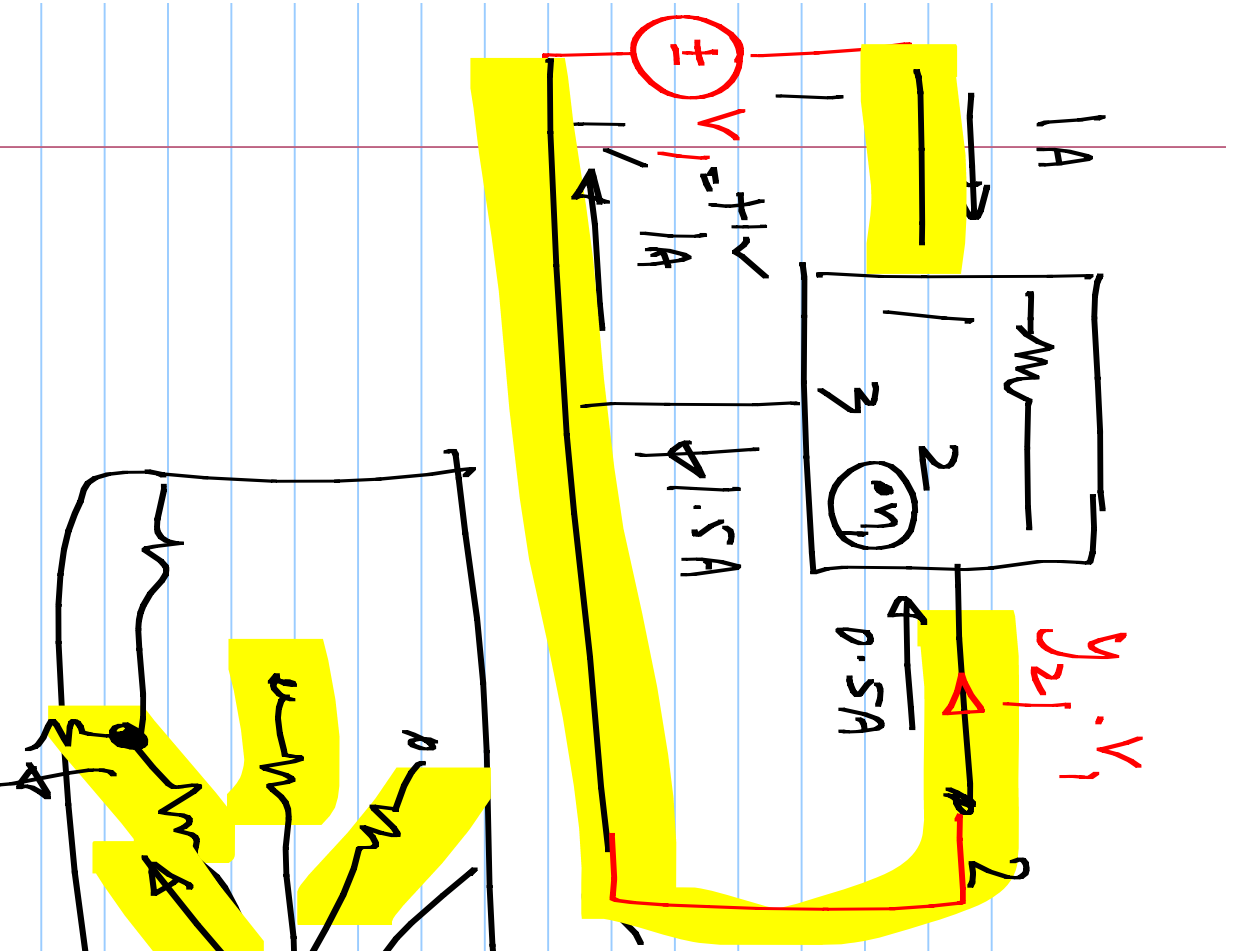
$$Z = \begin{bmatrix} 0 & 0 \\ R_m & 0 \end{bmatrix}$$




$$y = [\quad]$$

$$y_{12}, y_{21} < 0$$

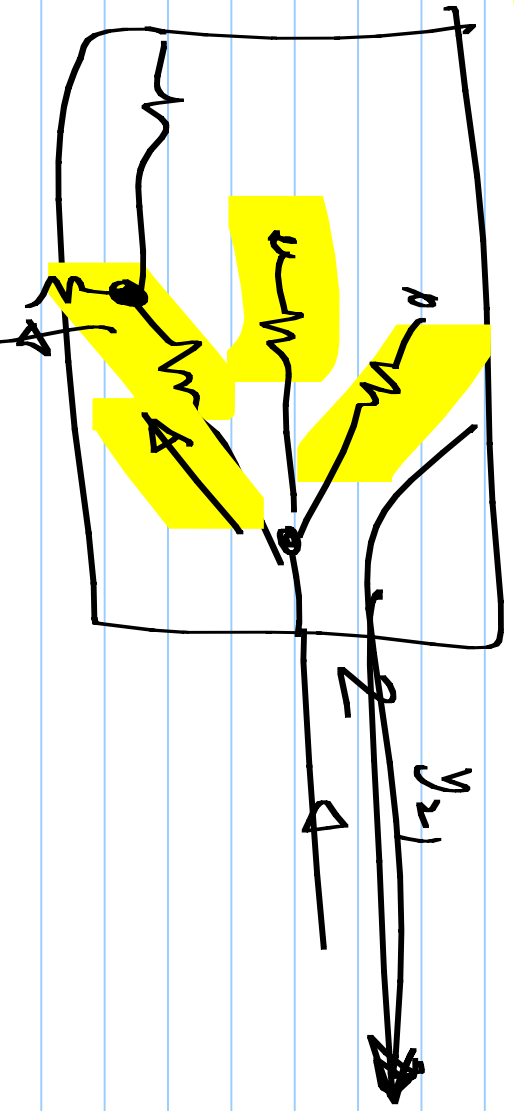

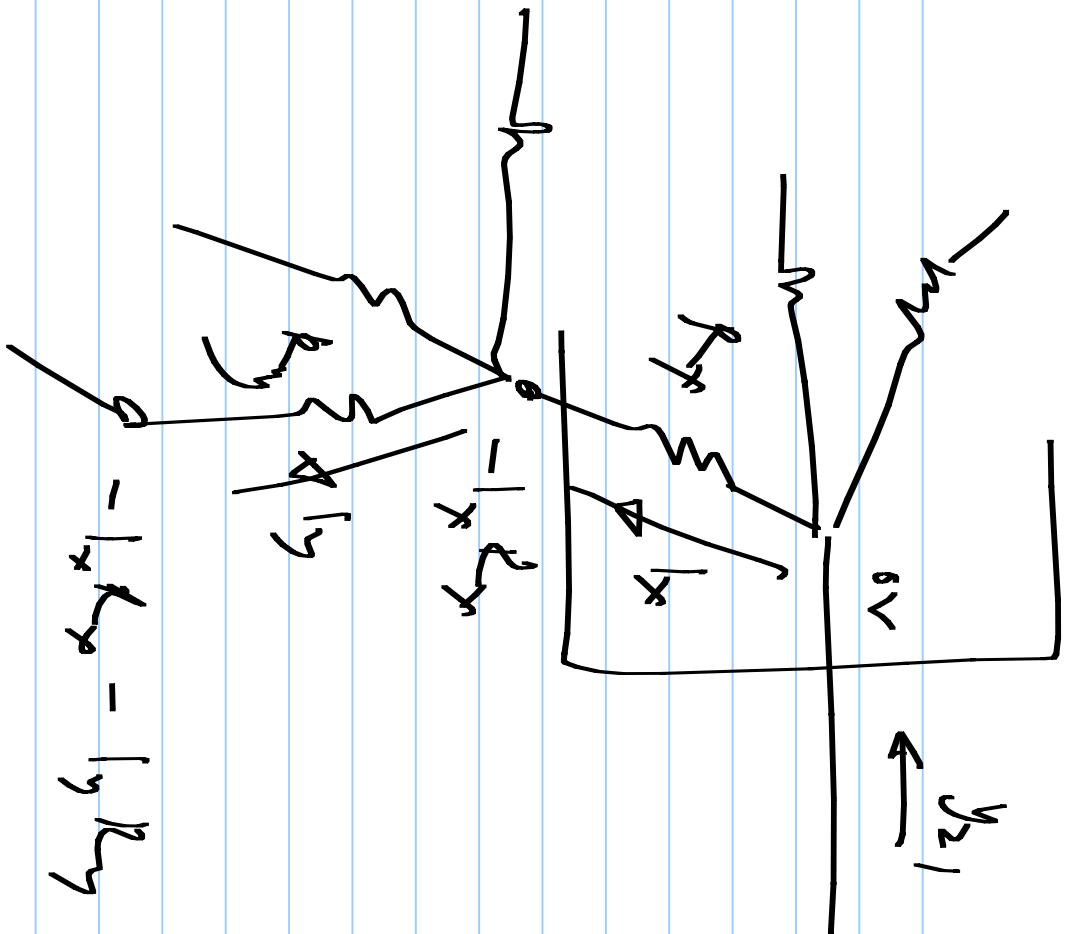



$$-k_p x - b \dot{x}$$

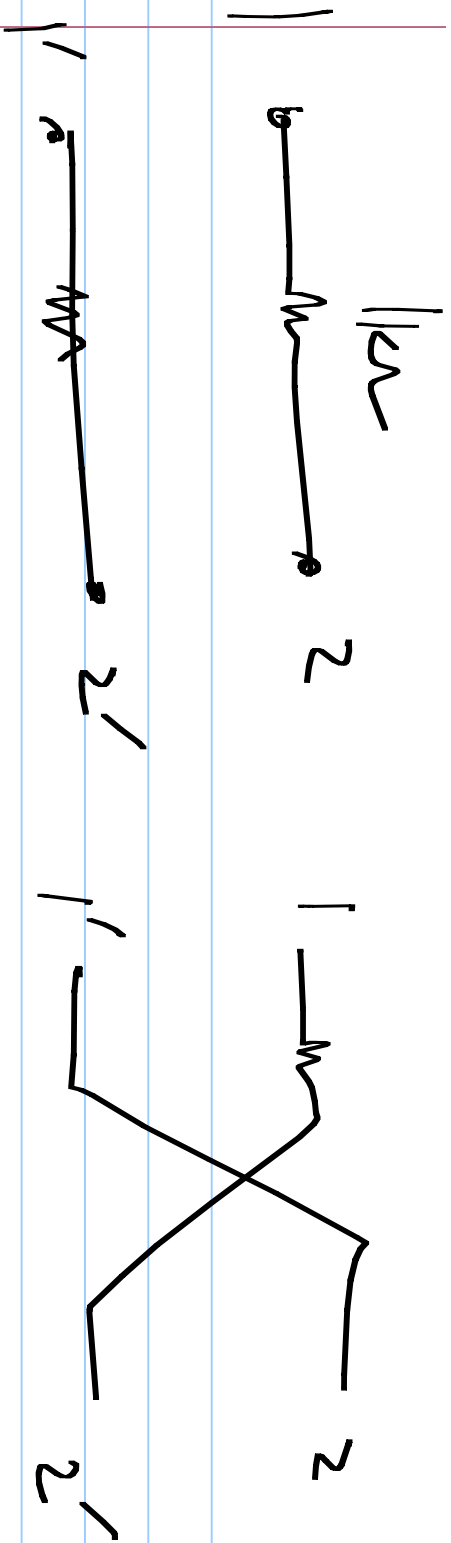

$$y = \begin{bmatrix} 1mS & -1mS \\ -1mS & 1mS \end{bmatrix}$$

Resistive 3-terminal 2 port

$$y_{12} \leq 0$$

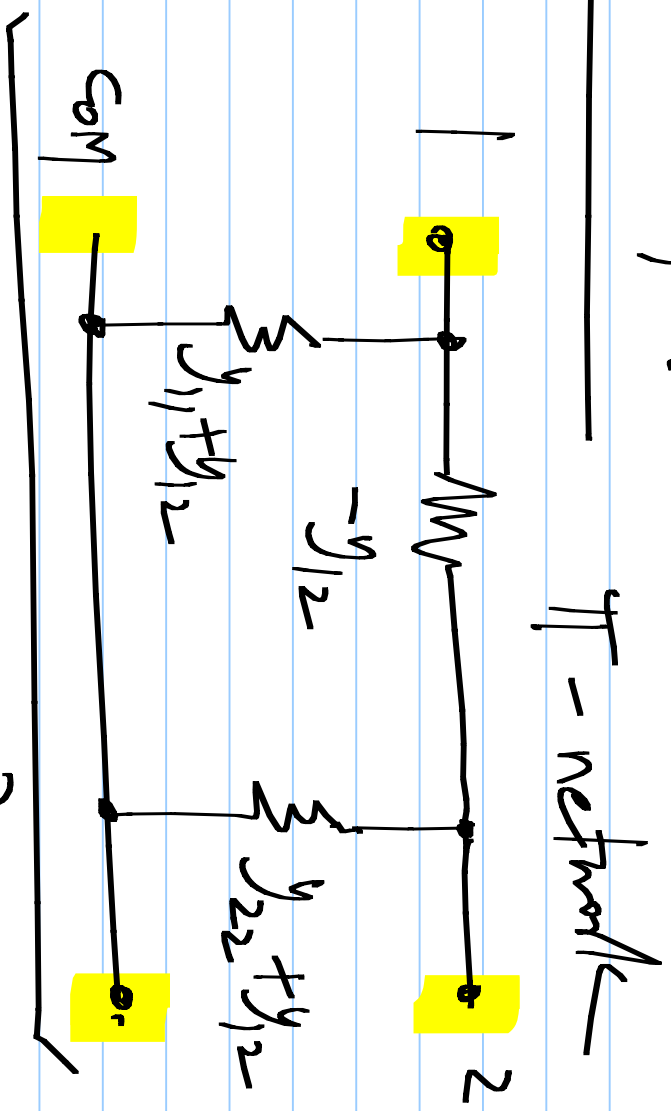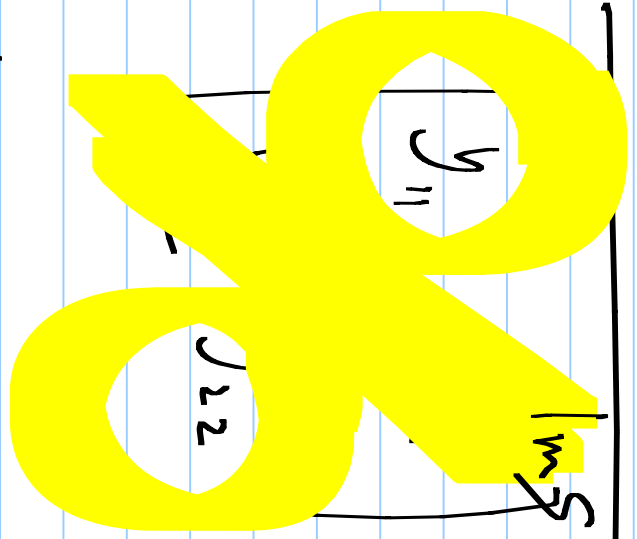

$$y_{12}, \cancel{0}$$


$$|y_{12}| \leq y_{11}, y_{22}$$


$$y = \begin{bmatrix} -y_{12} & y_{12} \\ y_{12} & -y_{12} \end{bmatrix}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{12} & y_{22} \end{bmatrix}^{-1} = \frac{1}{y_{11}y_{22} - y_{12}^2} \begin{bmatrix} y_{22} & -y_{12} \\ -y_{12} & y_{11} \end{bmatrix}$$




$$Z_{12} \neq 0 \qquad Z_{22}, Z_{11} \neq Z_{12}$$


Resistive 3-terminal
2-port

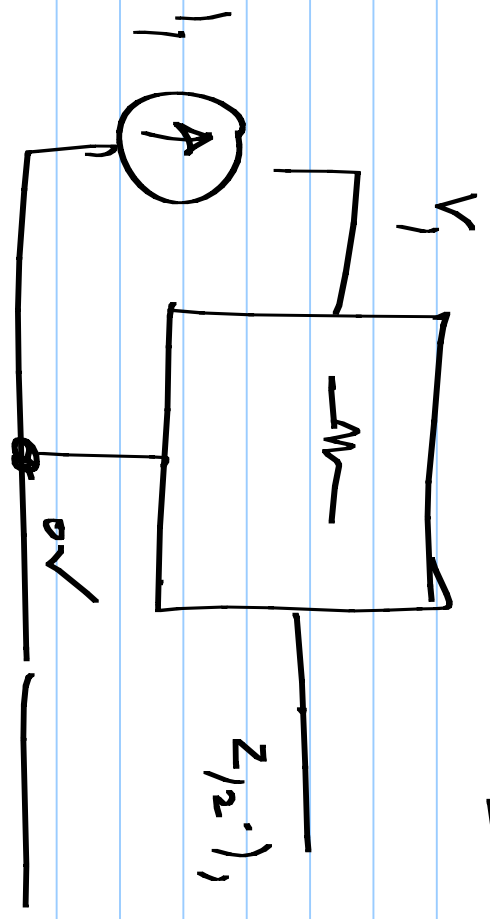


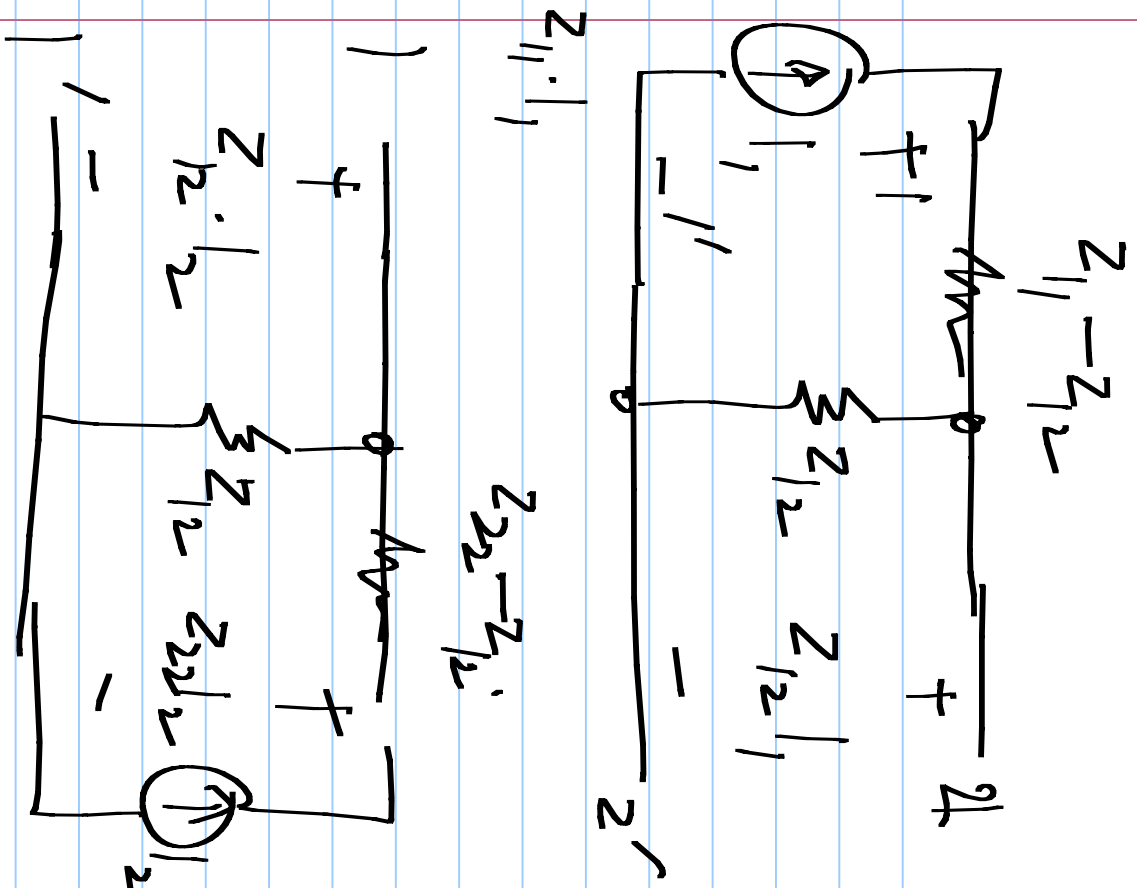

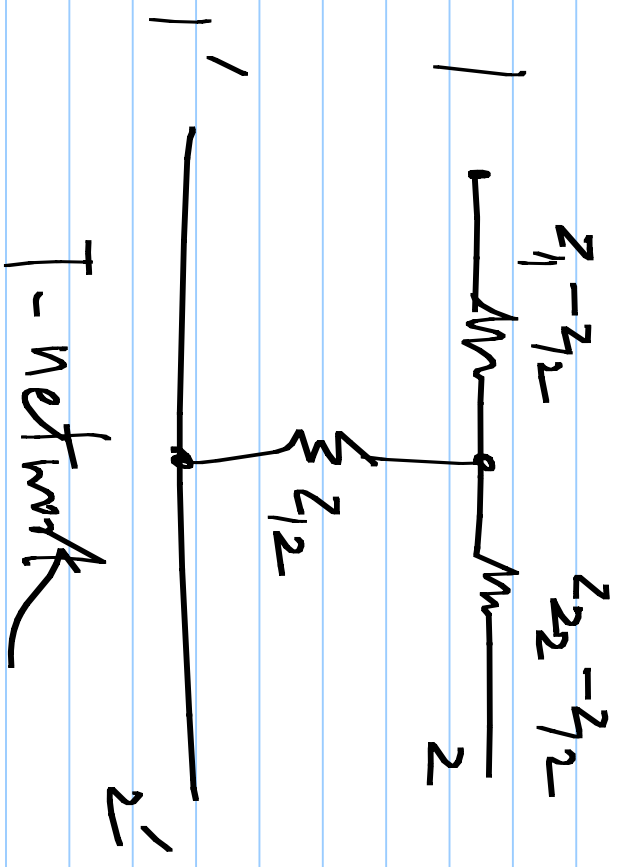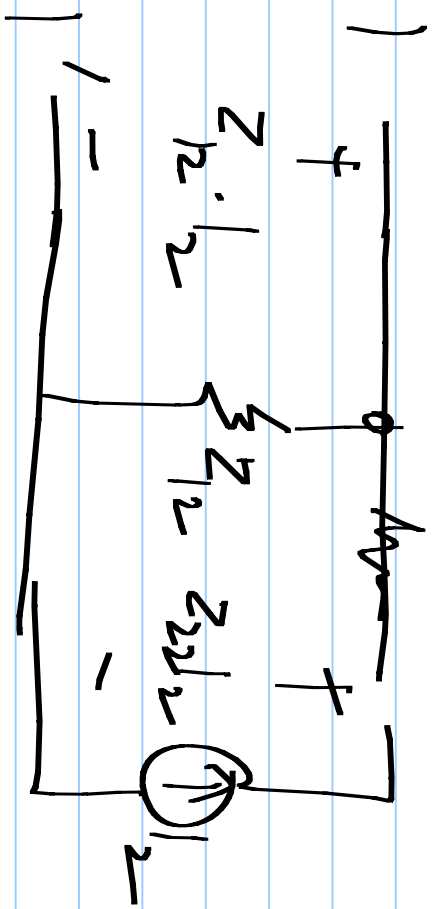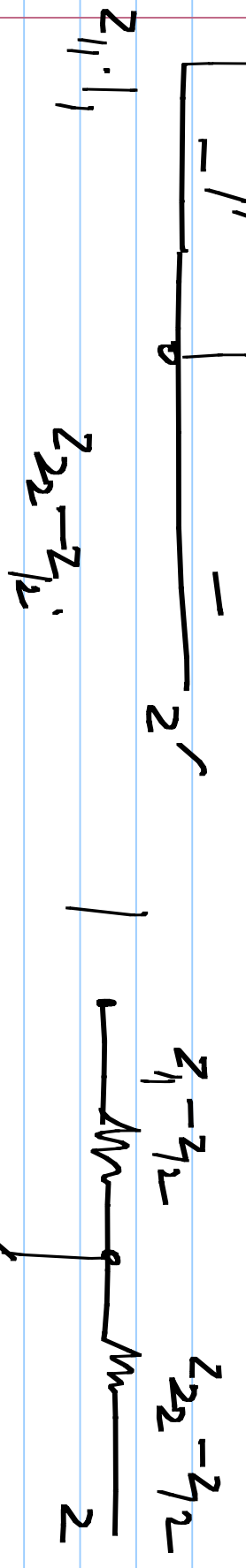
$$\begin{bmatrix} \text{[redacted]} & Z_{12} \\ Z_{12} & \text{[redacted]} \end{bmatrix}$$



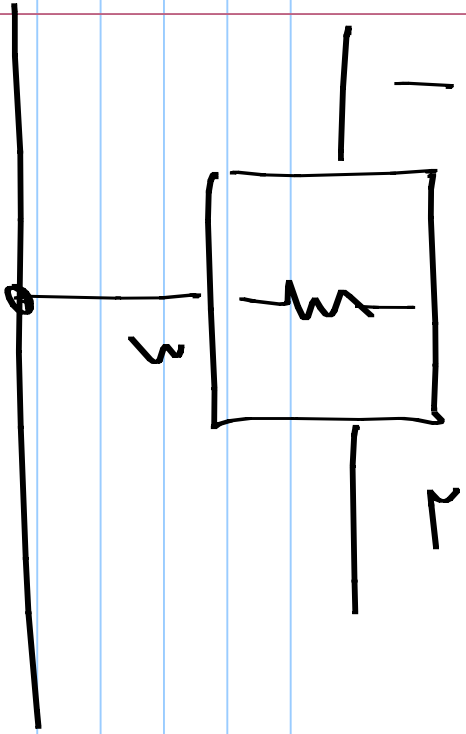

\equiv

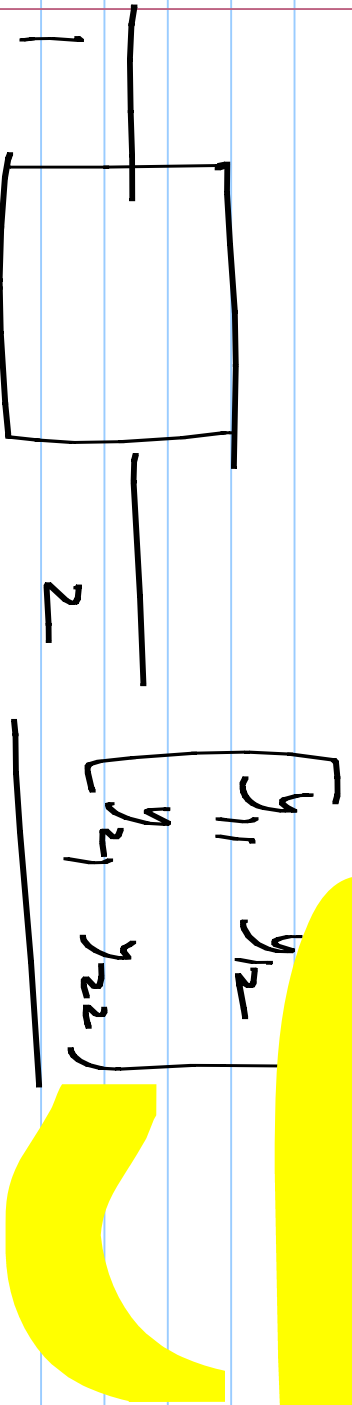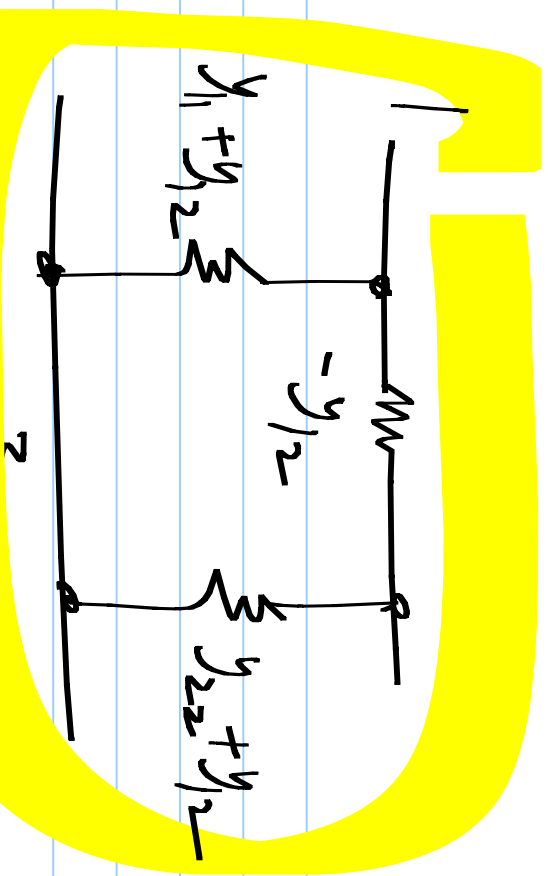

Not purely resistive

$$y_{12} \neq y_{21}$$