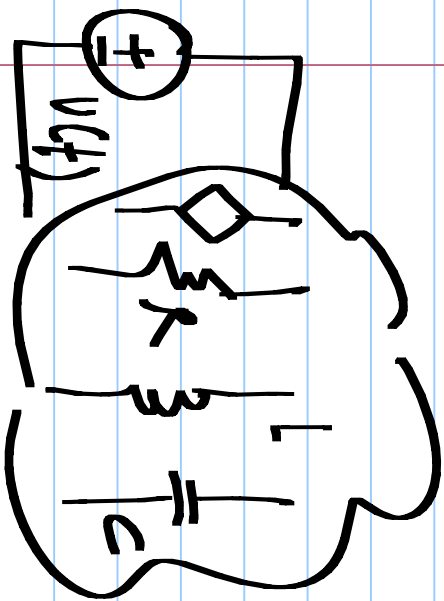


ECE 2015

R, L, C, Controlled sources

28/9/2017



Linear diff. equation with  
constant coefficients

Order  $N = \#$  states

(cap. voltages,  
inductor currents)

Natural response  
( $N$ . natural modes)

Forced response

Forced response


- Constant input  $\rightarrow$  constant (setting derivatives to zero)
- Exponential input  $\rightarrow$   $H(s) \cdot \exp(st)$

$\exp(j\omega t) \rightarrow H(j\omega) \exp(j\omega t)$

Real valued components

$\cos(\omega t) \rightarrow \text{Re} [ H(j\omega) \exp(j\omega t) ]$

$\cos(\omega t + \angle H(j\omega))$

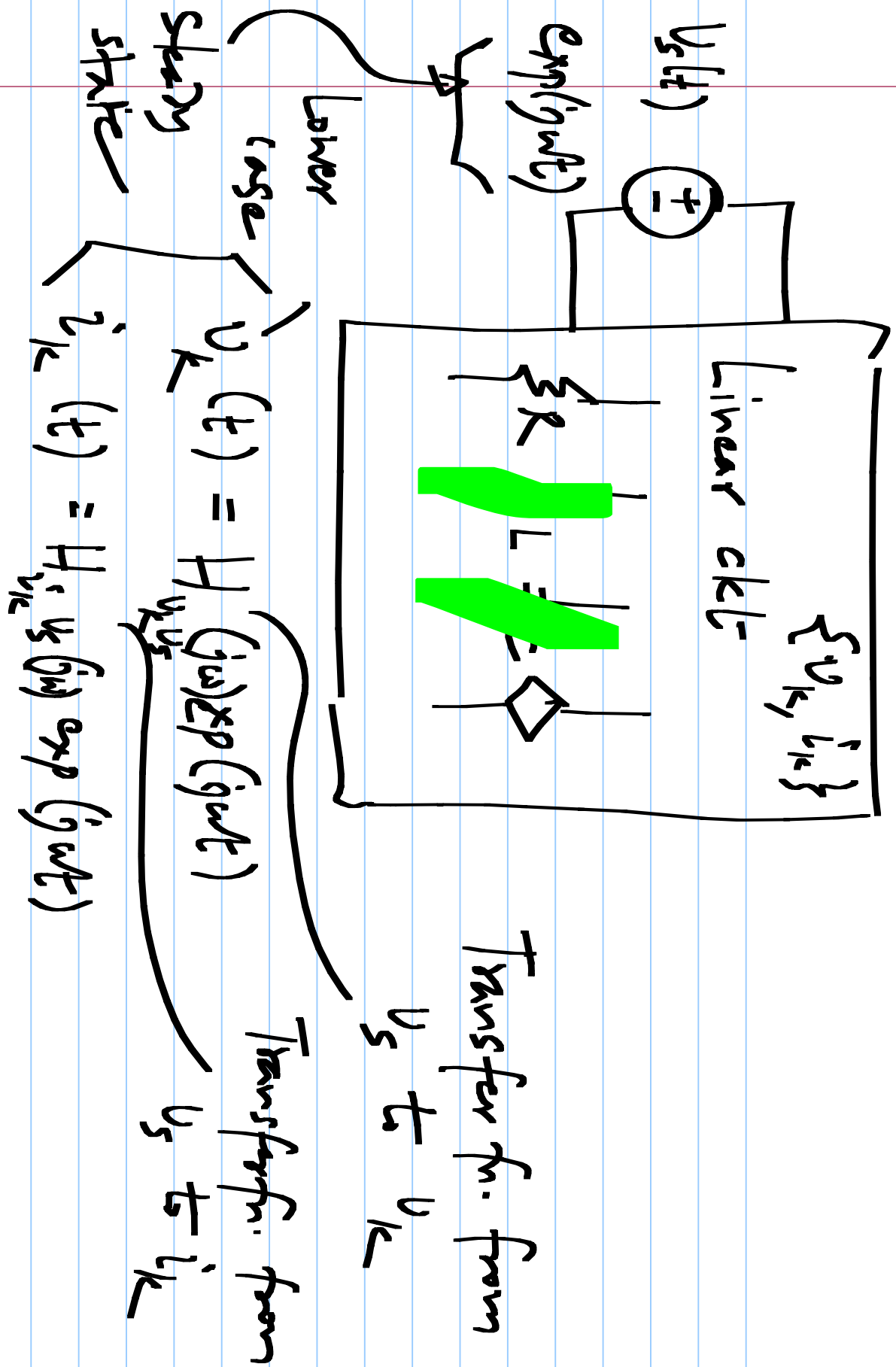


$$V_L(t) = H_{V_L, V_S}(\omega) \exp(j\omega t)$$

$$V_L = \underbrace{+ \dots +}_{\text{Ohm's law}} \underbrace{+ \dots +}_{\text{Ohm's law}} = H_{V_L, V_S}(\omega) \cdot \exp(j\omega t)$$


$$V_L = L \cdot \frac{di_L}{dt} = H_{V_L, V_S}(\omega) \cdot j\omega L \cdot \exp(j\omega t)$$
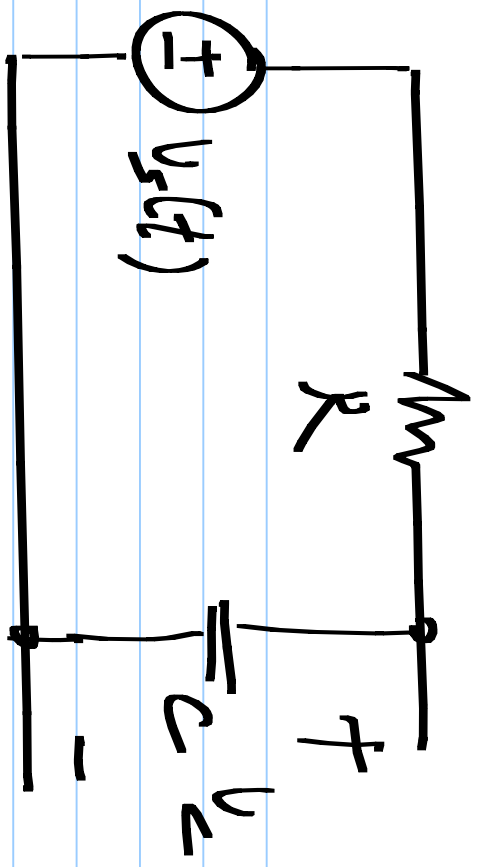
$$\frac{V_L(t)}{i_L(t)} = j\omega L = \frac{V_L(t)}{i_L(t)} = \underbrace{j\omega L}_{\text{constant}}$$



$$RC \cdot \frac{dv_c}{dt} + v_c = v_s$$
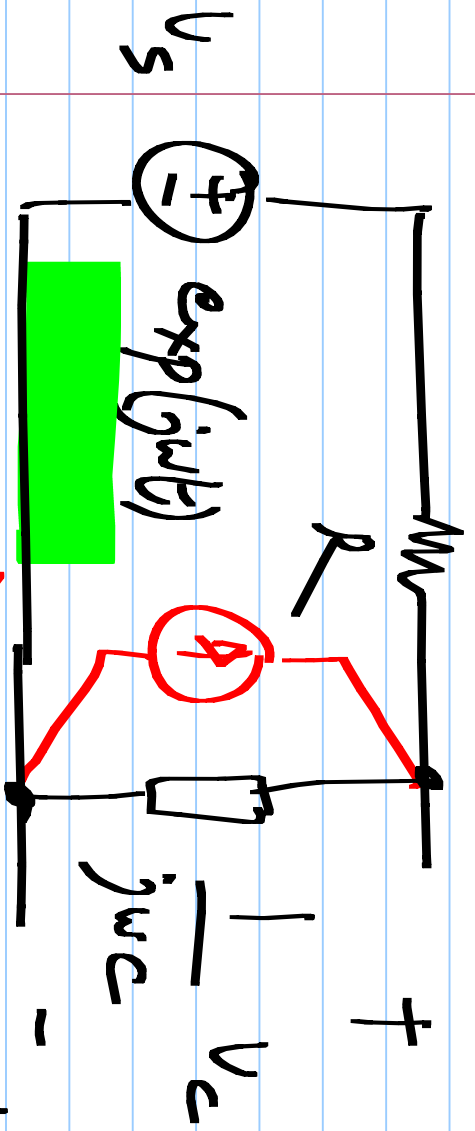
$$+ v_s(t) \cdot \frac{R \cdot 1/j\omega C}{R + 1/j\omega C} \cdot 1/j\omega C$$



$\sim \exp(j\omega t) \cdot v_s(t)$


only when  $v_s = \exp(j\omega t)$

$$v_c(t) = v_s(t) \cdot \frac{R \cdot 1/j\omega C}{R + 1/j\omega C}$$

$\Omega$

$$\frac{V(t)}{i(t)}$$

Impedance  $\sim$  Resistance

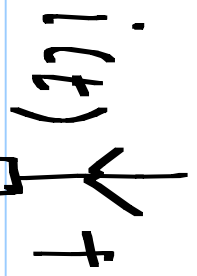


$$V(t)$$

Complex

Real  $\rightarrow$

(Steady-state  
w/ explicit  
input)

input

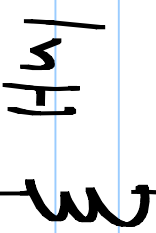

$$j2\pi \Omega$$

$$-j \frac{2}{2\pi} k\Omega$$


$$\frac{-j157\Omega}{1\mu F}$$

@ 1kH<sup>2</sup>


@

1kH<sup>2</sup>

$$v_s(t) = V_s \exp(j\omega t + \phi)$$

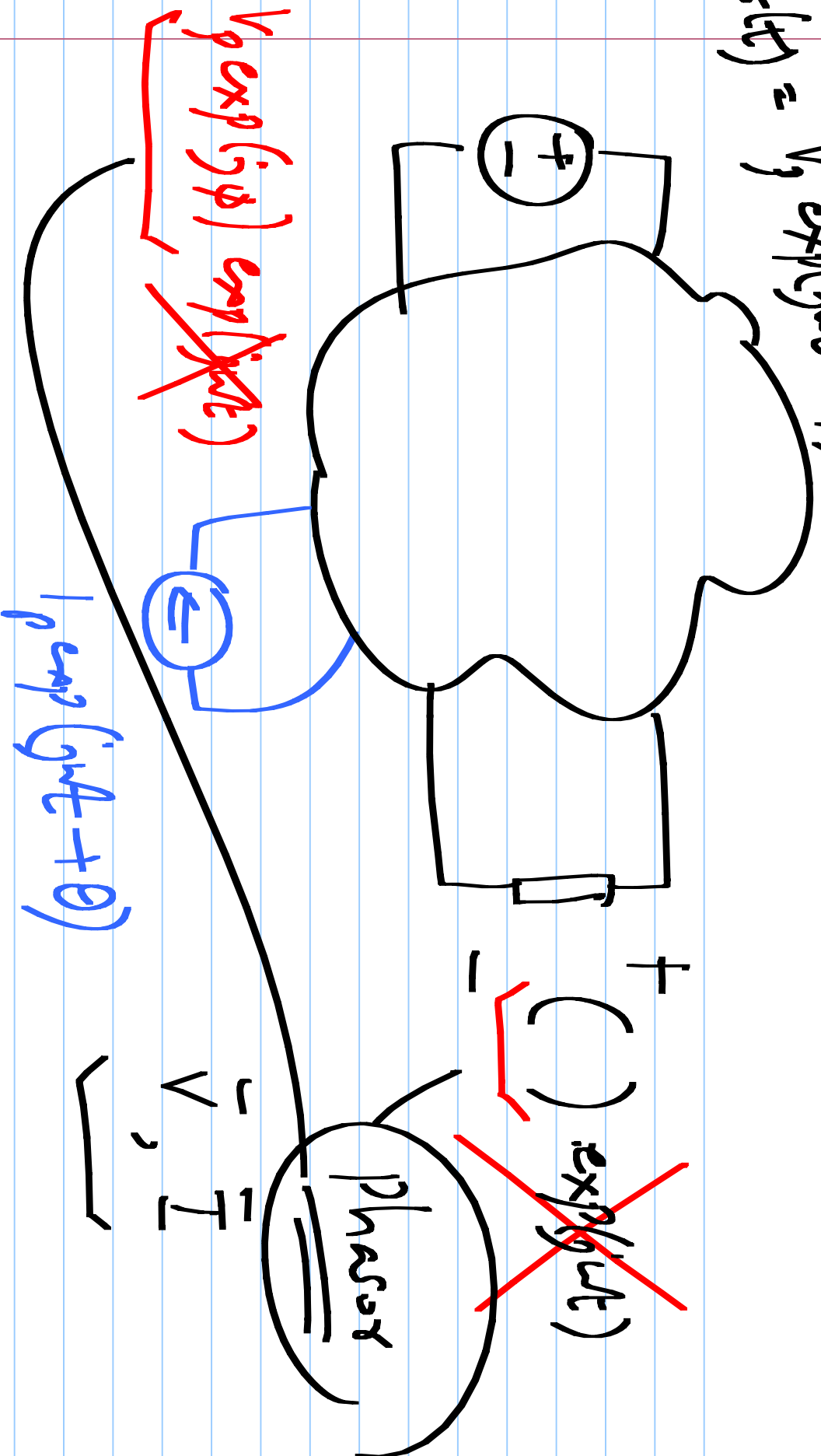

③

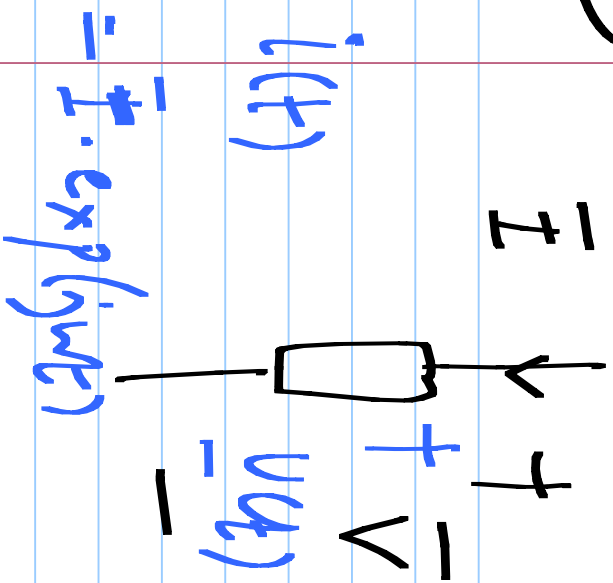

$= I \cdot \exp(j\omega t)$

phasor  $\rightarrow$


In steady-state


w/  $\exp(j\omega t)$  as

input

$V(t) = V \cdot \exp(j\omega t)$



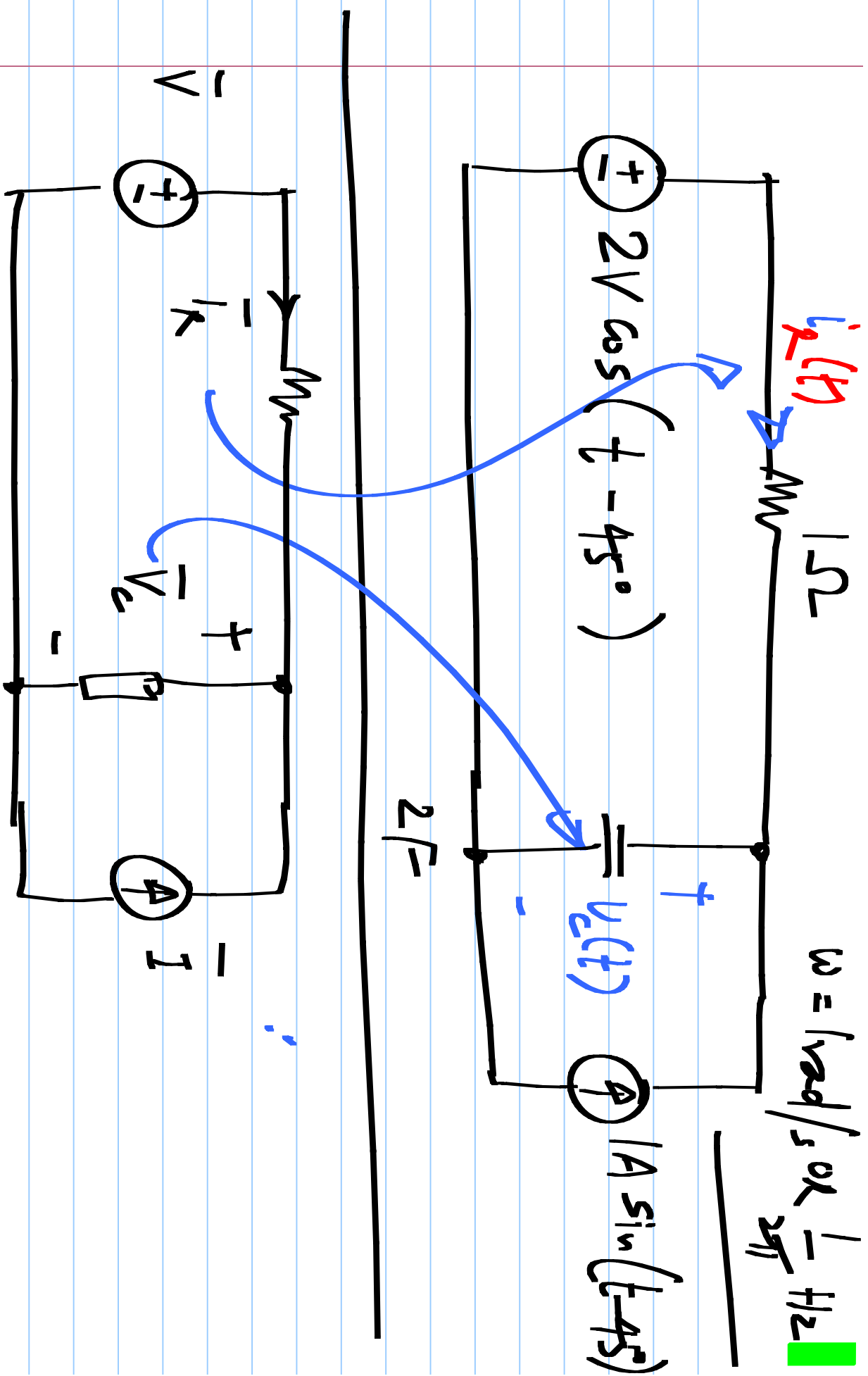

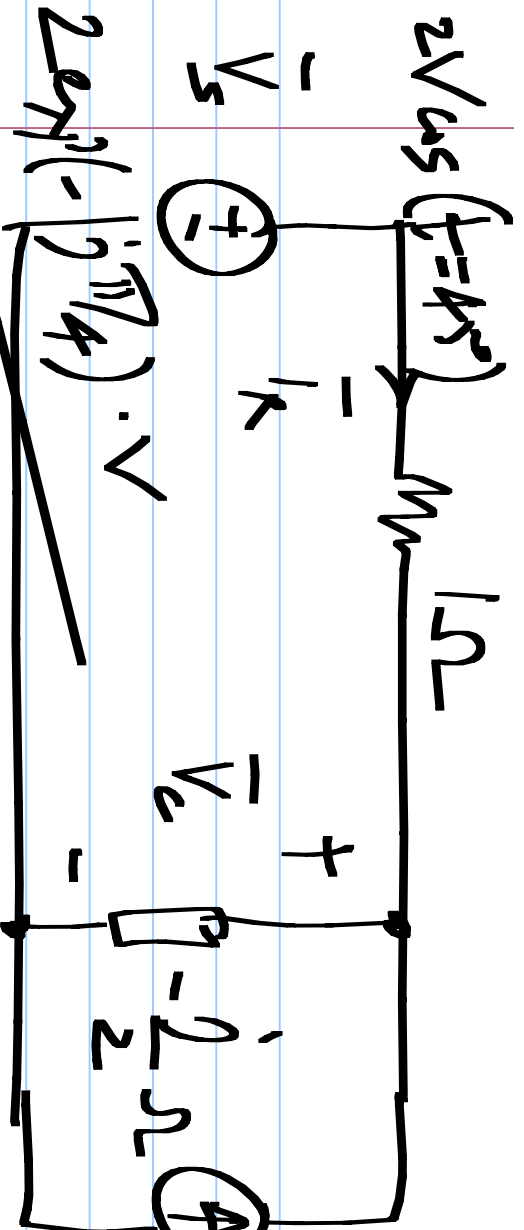

$$i_s(t) = 1A \sin(t - 45^\circ)$$

$$1A \cos(t - 135^\circ)$$

$$1A \angle -135^\circ$$

$$1A \exp(-j \frac{3\pi}{4})$$

$$V_c = V_s \frac{(-j/2)}{1 - j/2} + I_s \left[ \frac{1 \cdot (-j/2)}{1 - j/2} \right]$$

$$V_c = \left[ \underbrace{2 \exp(-j \frac{\pi}{4})}_{1A \angle -45^\circ} \cdot \frac{(-j/2)}{(1 - j/2)} + \underbrace{1 \cdot \exp(-j \frac{3\pi}{4})}_{1A \angle -135^\circ} \cdot \frac{1}{(1 - j/2)} \right]$$

$$V_c = 1 \exp(-j \frac{3\pi}{4}) \rightarrow v_c(t) = A \cdot \cos(t - \theta) \cdot V$$

$$(\sqrt{2} - j\sqrt{2}) \left(-j\frac{1}{2}\right) - \left(\frac{-1}{\sqrt{2}} - j\frac{1}{\sqrt{2}}\right) \cdot \left(-j\frac{1}{2}\right)$$

$A \exp(j\theta)$

$$1 - j\frac{1}{2}$$

$$\frac{1 \exp(-j\frac{3\pi}{4}) (\sqrt{2} + j\sqrt{2}) - j \left(\sqrt{2} - \frac{1}{\sqrt{2}}\right)}{1 - j\frac{1}{2}}$$

$$1 - j\frac{1}{2}$$

$$\cdot \left(-j\frac{1}{2}\right)$$