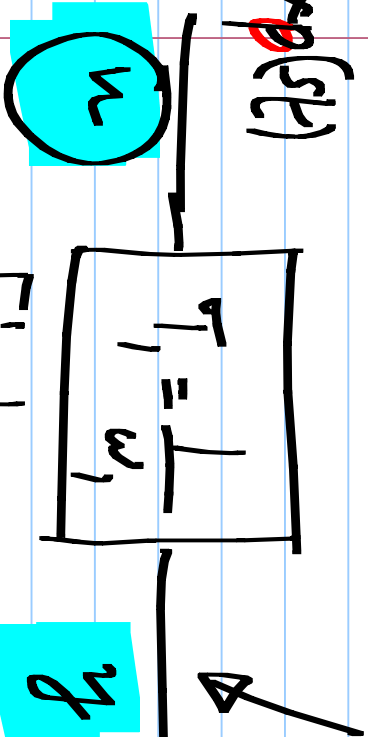


EE 2015



Second order systems

9/10/2017


exp(st)




First order system

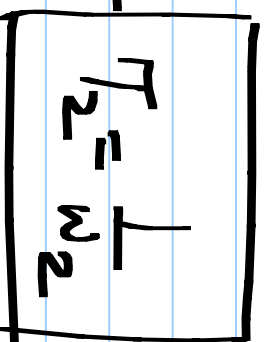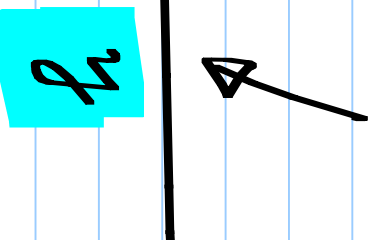

First order system

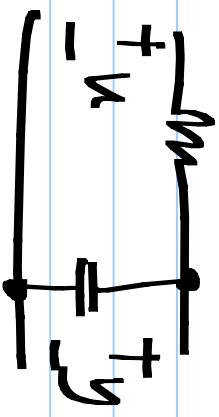

$T_1 = T_2 = T$

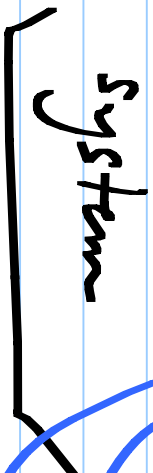

exp(-t/T)

$T_1 \cdot \frac{dy}{dt} + y = w$

$\frac{1}{s_1} \frac{dy}{dt} + y = w$

$T_2 \cdot \frac{dv}{dt} + v = y$

$\frac{1}{s_2} \frac{dv}{dt} + v = y$



exp(-t/T)

Eliminating y , we get:

$$\frac{d^2 v}{dt^2} + (s_1 + s_2) \frac{dv}{dt} + (s_1 s_2) \cdot v = (s_1 s_2) u$$

$$\tau_1 \tau_2 \frac{d^2 v}{dt^2} + (\tau_1 + \tau_2) \frac{dv}{dt} + v = u$$

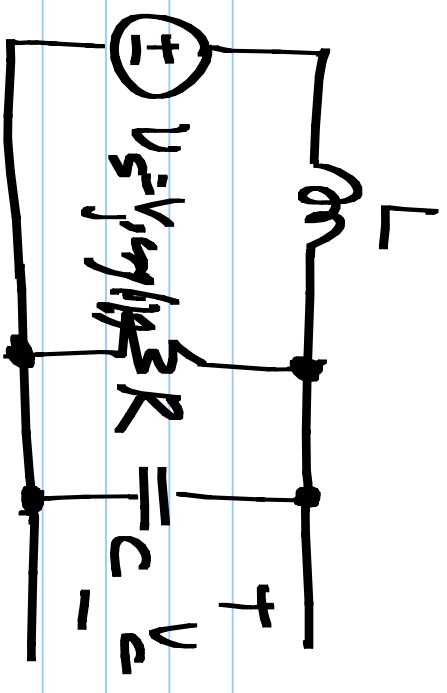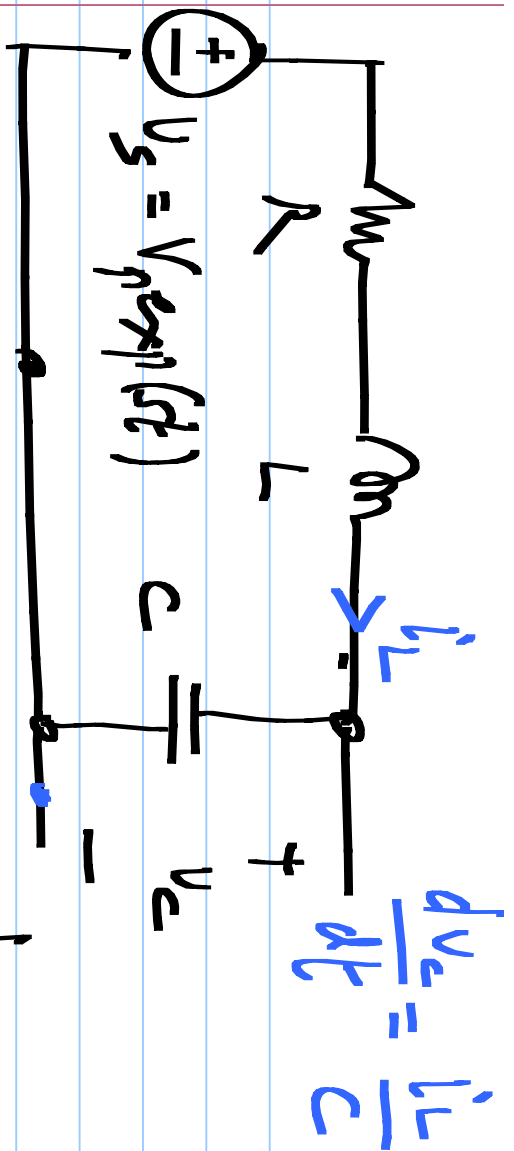$\tau_1 \tau_2$ order differential equation



$$LC \frac{d^2 v_c}{dt^2} + RC \frac{dv_c}{dt} + v_c = v_s$$

$$\tau_1 \tau_2 \frac{d^2 v_c}{dt^2} + (\tau_1 + \tau_2) \frac{dv_c}{dt} + v_c = v_s$$

$$LC \frac{d^2 v_c}{dt^2} + L \frac{dv_c}{dt} + v_c = v_s$$

Natural response of a second-order system $\tau_1 = \tau_2^* \Rightarrow A_1 = A_2^*$

$$\sim A_1 \cdot \exp(-t/\tau_1) + A_2 \cdot \exp(-t/\tau_2)$$

$$\sim A_1 \exp(-t/\tau) + A_2 t \exp(-t/\tau) \quad \left. \begin{array}{l} \tau_1 = \tau_2 \\ \tau_1 = \tau_2 \end{array} \right\}$$

$$\tau_1 \cdot \tau_2 = LC$$

$$\tau_1 \cdot \tau_2 = LC$$

$$\tau_1 + \tau_2 = C \cdot R$$

$$\tau_1 + \tau_2 = \frac{L}{R}$$

$$A_1 \exp(-s_1 t) + A_2 \exp(-s_2 t)$$

$H(s)$

$V_i \exp(st)$ input:

$$\frac{1}{s^2 L C + C R s + 1} V_i \exp(st)$$

ckt # 1

$$+ A_1 \exp(-s_1 t)$$

$$+ A_2 \exp(-s_2 t)$$

forced response

$H(s)$

$$\frac{1}{s^2 L C + s \frac{L}{R} + 1}$$

$$V_o \exp(st)$$

Input : $\underbrace{\exp(st)}$

Natural : $\exp(-s_1 t), \exp(-s_2 t)$ s_1, s_2 : real,
modos distinct

$s_1 = s_2$: real