


ECE 2019

VCVS


Integrator: $V_o = \omega_n \int V_e \cdot dt$

Amplifier: $V_o = A_o \cdot V_e$

24/1/2017

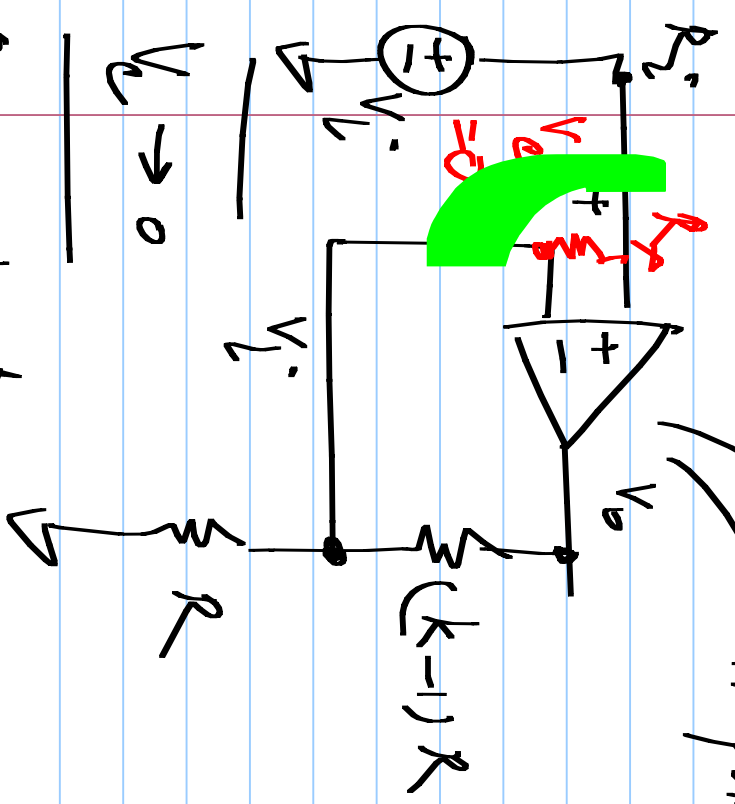

Opamp inputs are virtually shorted

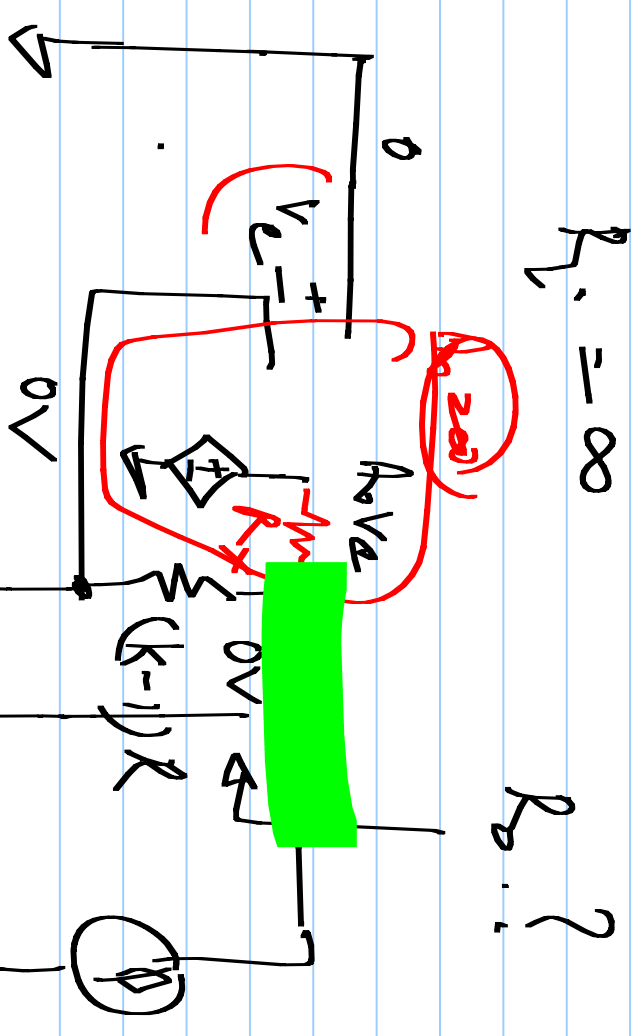


$R_i = \infty$

$R_o = ?$

$A_o = \infty$; $R_i = \infty$, $R_o = 0$ for the amplifier

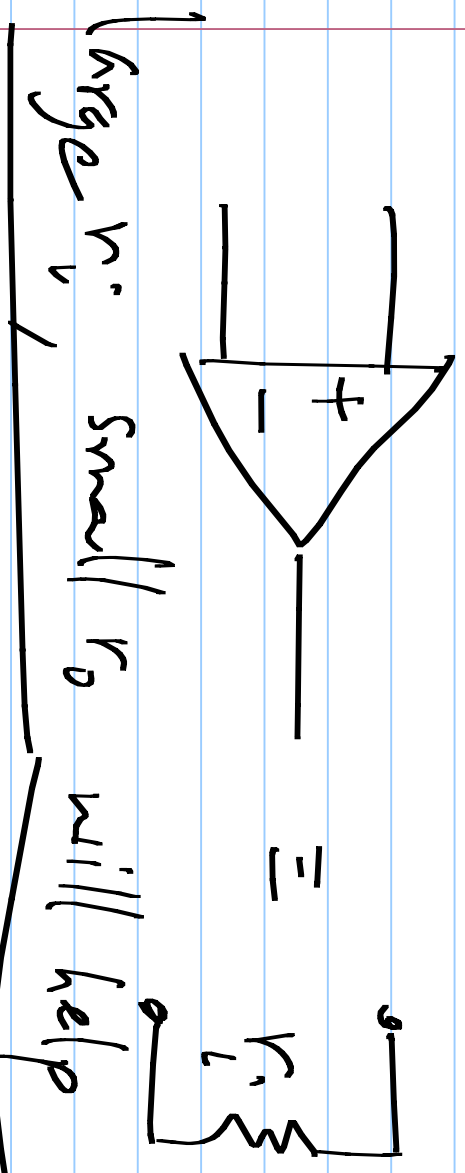regardless of the i/p & o/p resistances of the opamp.




large v_i , small v_o will help

R_o finite
&
 A_o non-zero v_o

$A_0 \gg k$

finite A_0

$9.99 < k < 10.01$

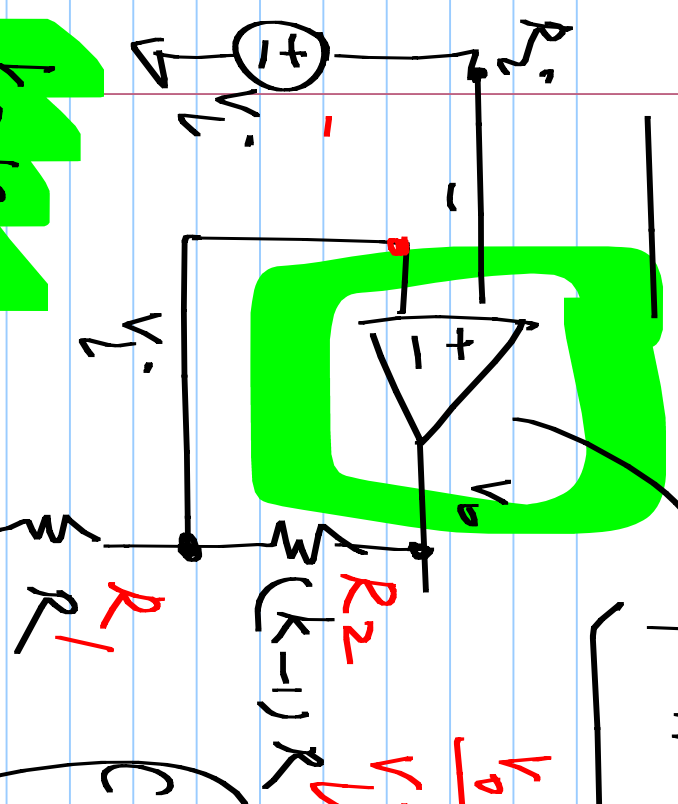


$$V_o = \left(1 + \frac{R_2}{R_1}\right) \frac{V_i}{k} = \frac{A_0 k}{k + A_0} V_i$$

Closed loop system

$k = 10$
 9.9990
 9.9999

A_0
 $\frac{1}{1 + \frac{1}{A_0}}$

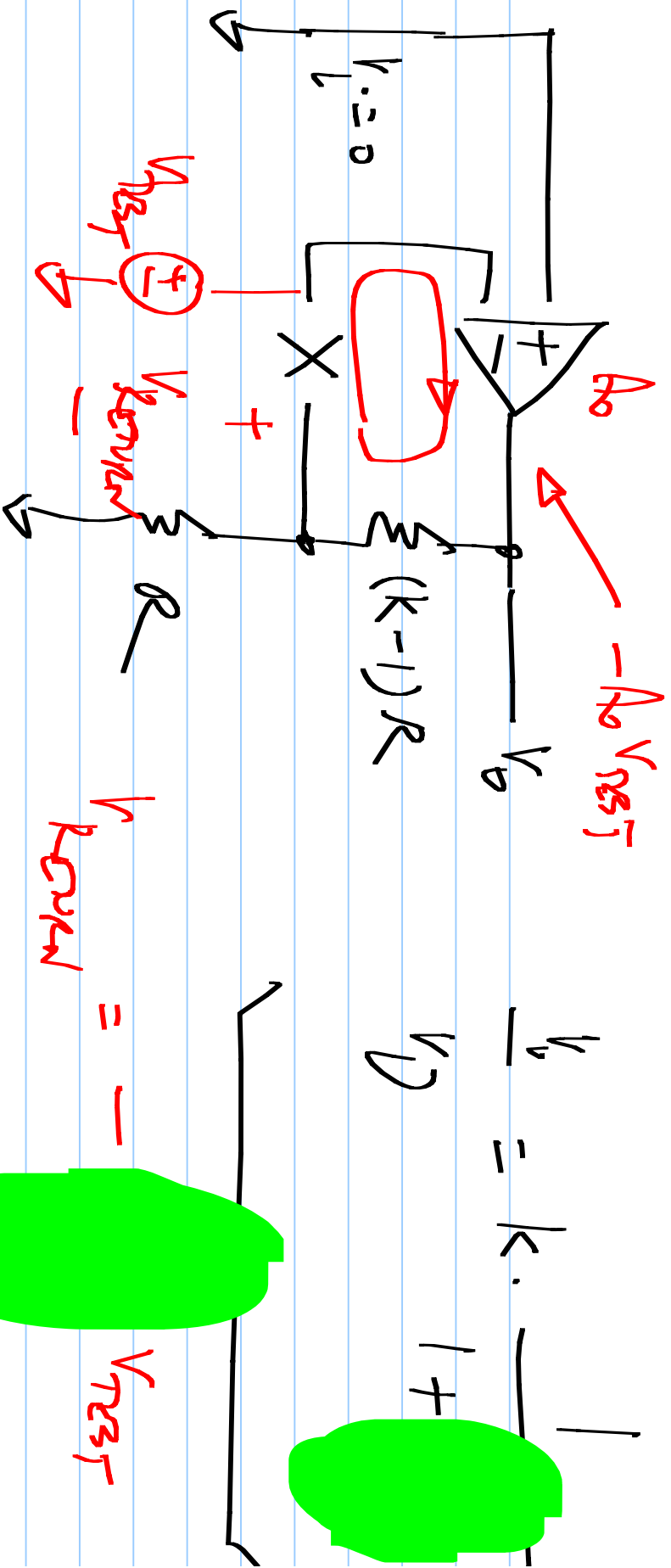

Loop gain:



$$= -L \cdot V_{res}$$

Loop gain L

$$V_o = K' \cdot \frac{1}{1 + \frac{K}{A_2}}$$

1 pool

↳ reciprocal of loop gain

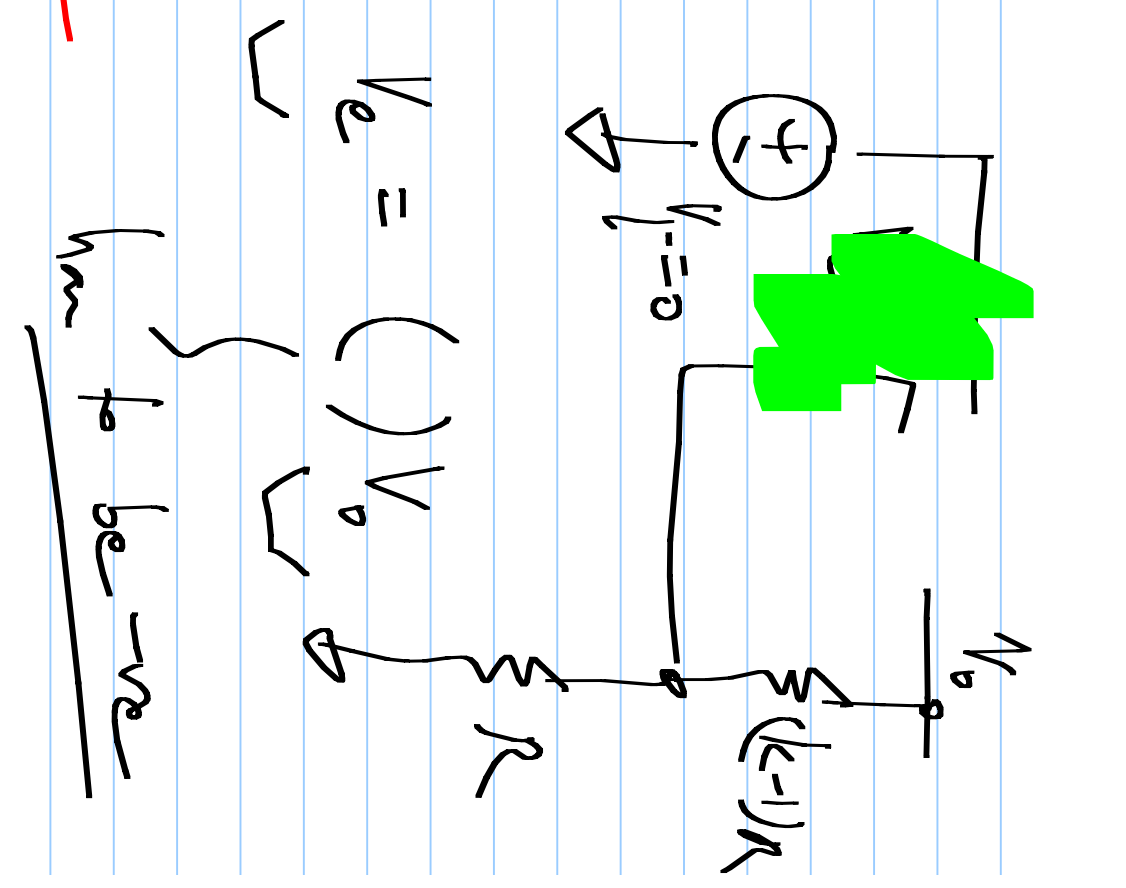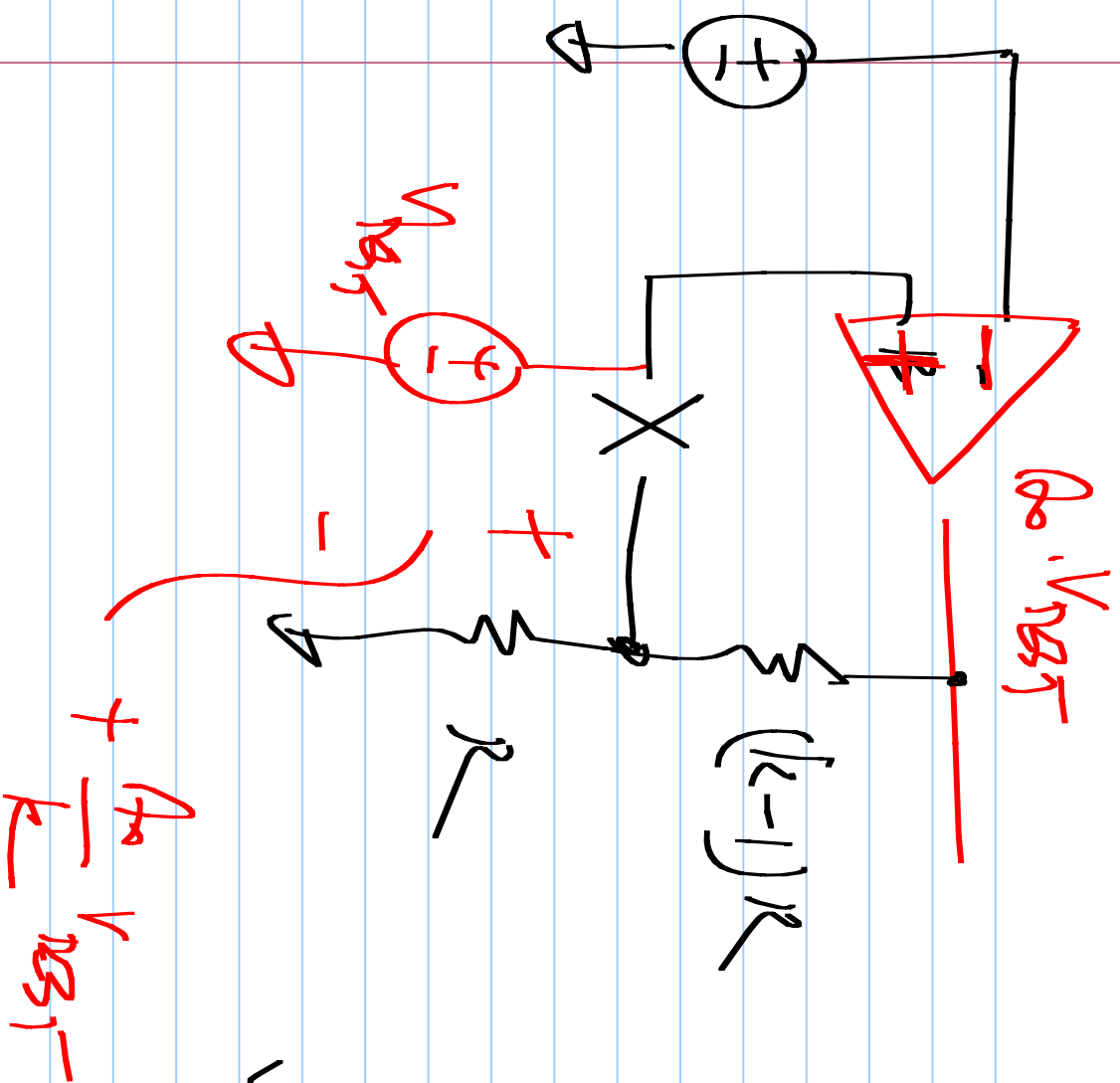


$$V_{th} = () V_0$$

how to be ve



Assume A : +ve
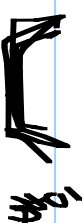
$$V_e = \cancel{(A)} \cancel{V_i} + (C) \cdot V_o$$





Current controlled voltage source


$$V_b = R_m I$$

Trans resistance

$$V_b - I_b R_m = 0$$

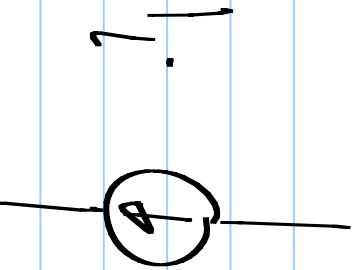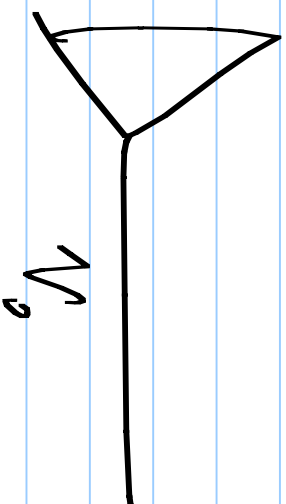

Implement this
using -ve Pb

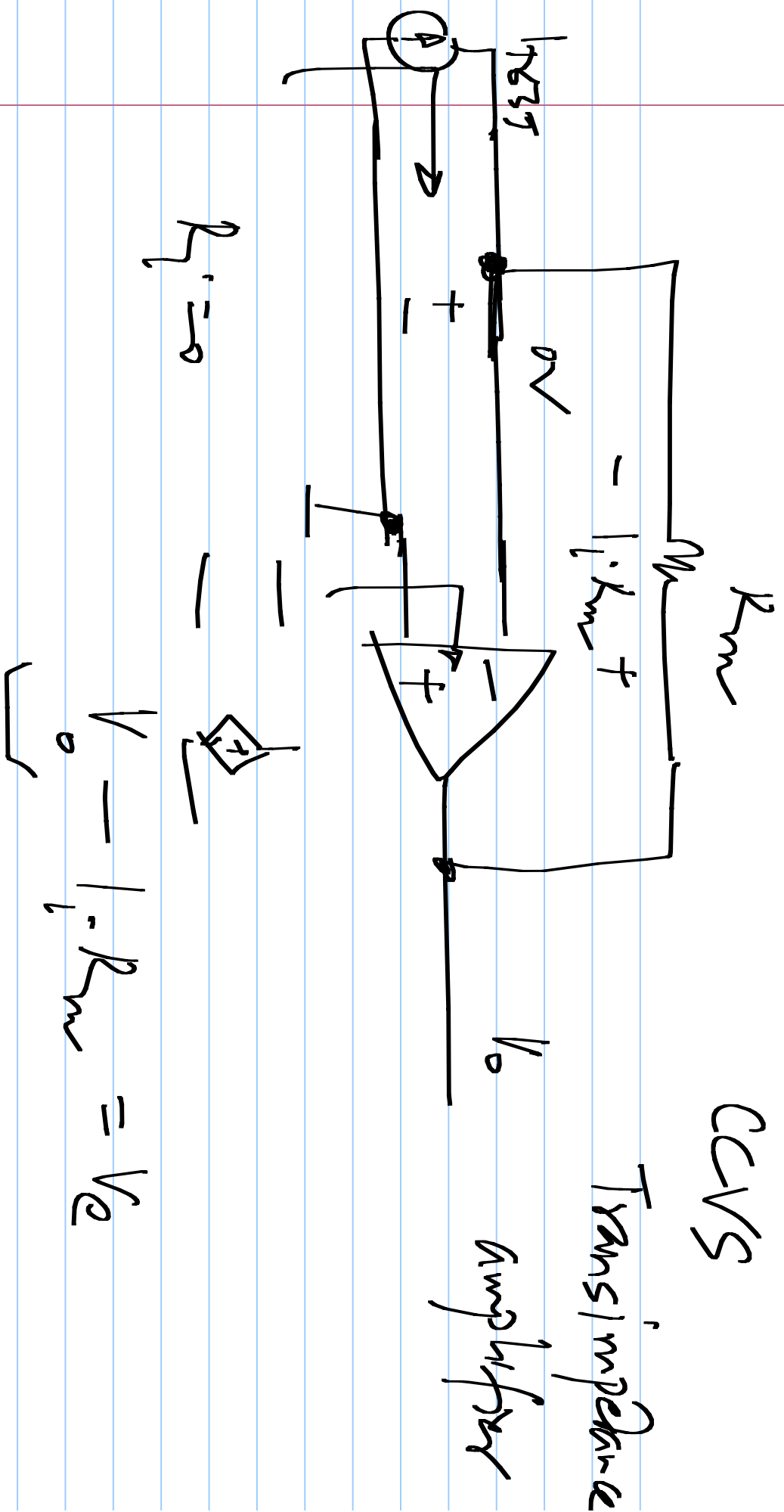

$$V_o = I_0 \cdot R_m = V_e$$