

EE 2019


25/1/2017



$$V_D = \frac{1}{2} R_m \Rightarrow V_D - \frac{1}{2} R_m = 0$$

[Redacted]



$$R_{in} = 0$$

$$R_{out} = 0$$


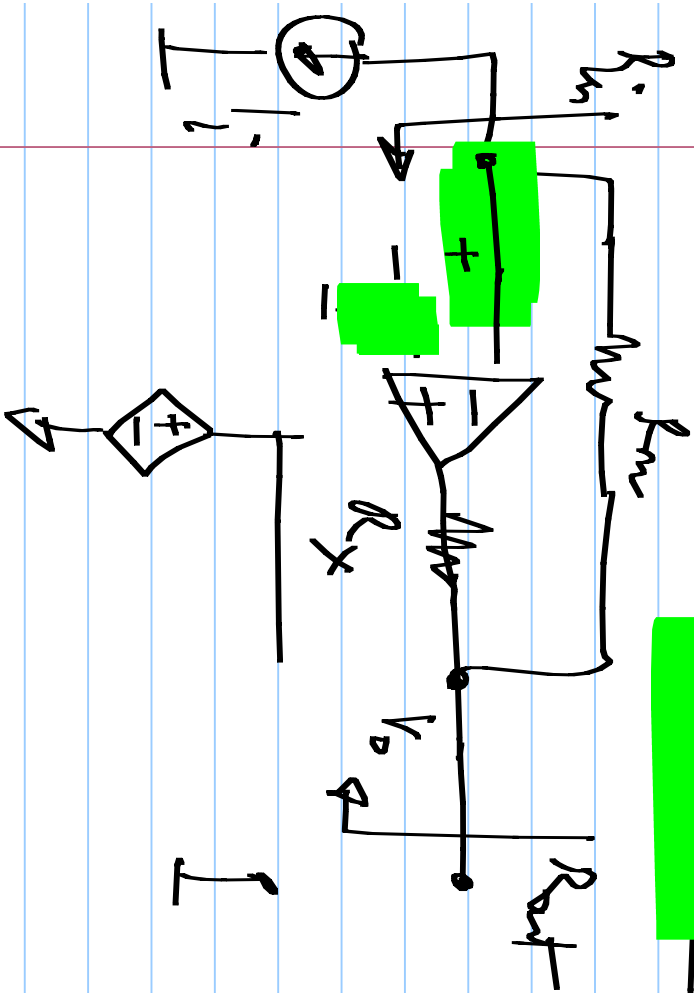


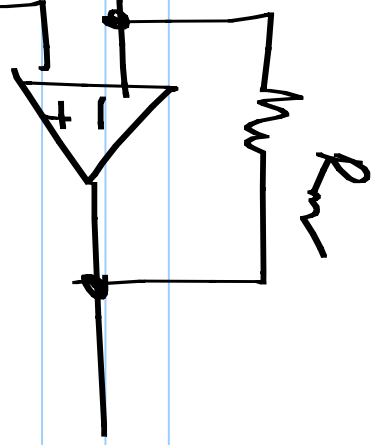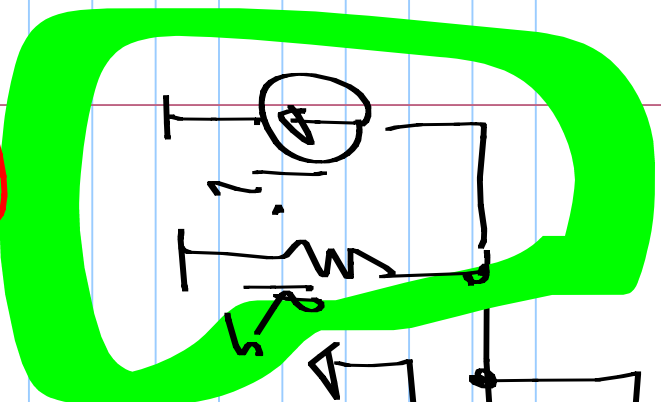



R_2

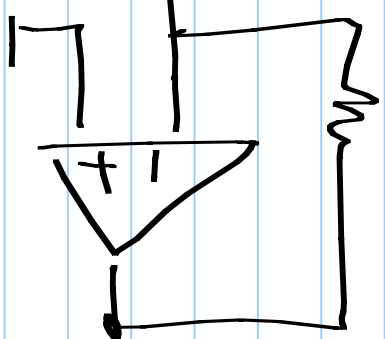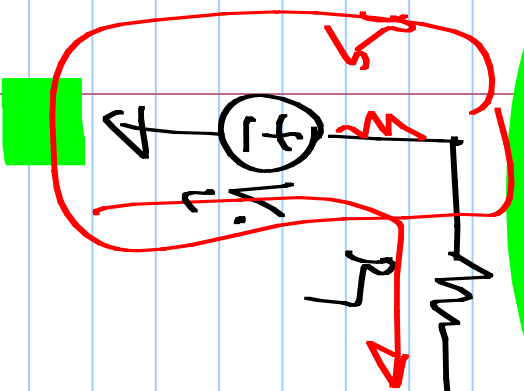


$$V_o = -\frac{R_2}{R_1} \cdot V_i$$

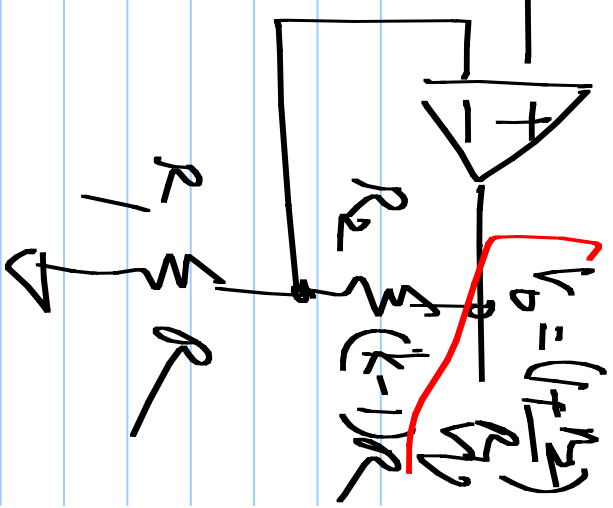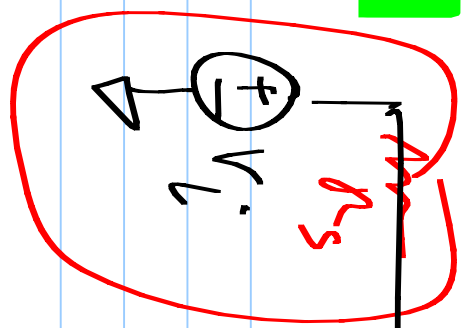
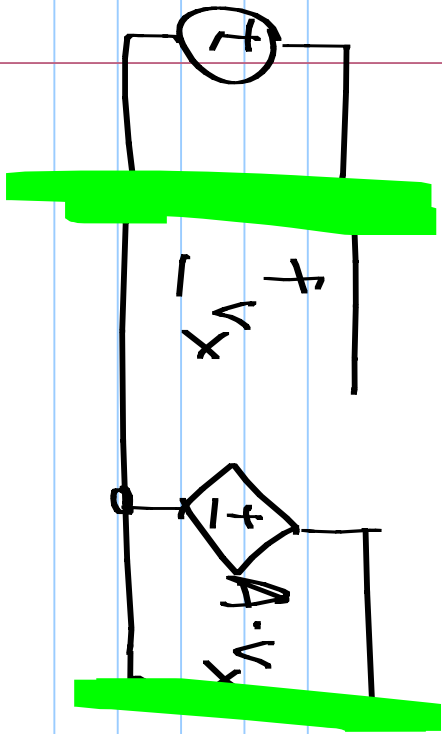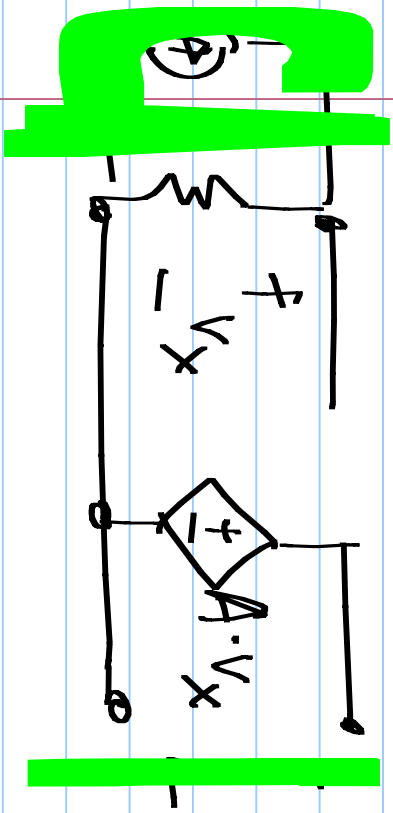
$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i$$




Non-inverting amplifier

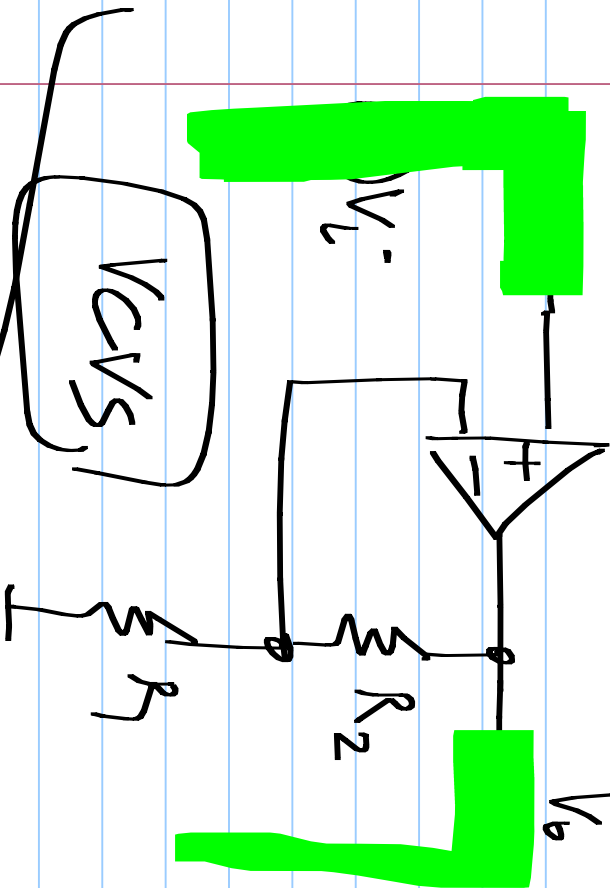

VCVS
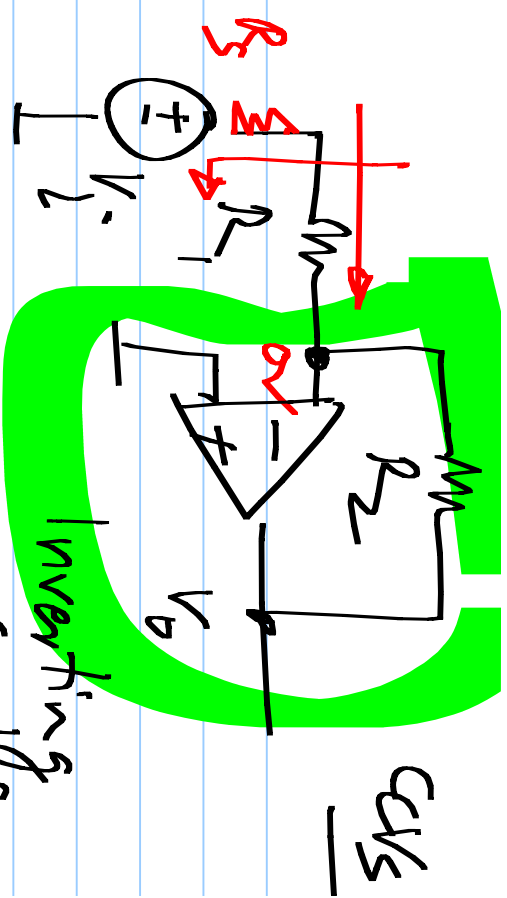
$$\underline{V_o} = \left(1 + \frac{R_2}{R_1}\right) \underline{V_L}$$





$R_3 \ll R_1$

CVS


Inverting amplifier

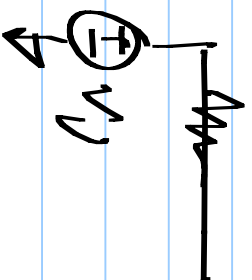
$$\underline{V_o} = -\frac{R_2}{R_1} \underline{V_L}$$



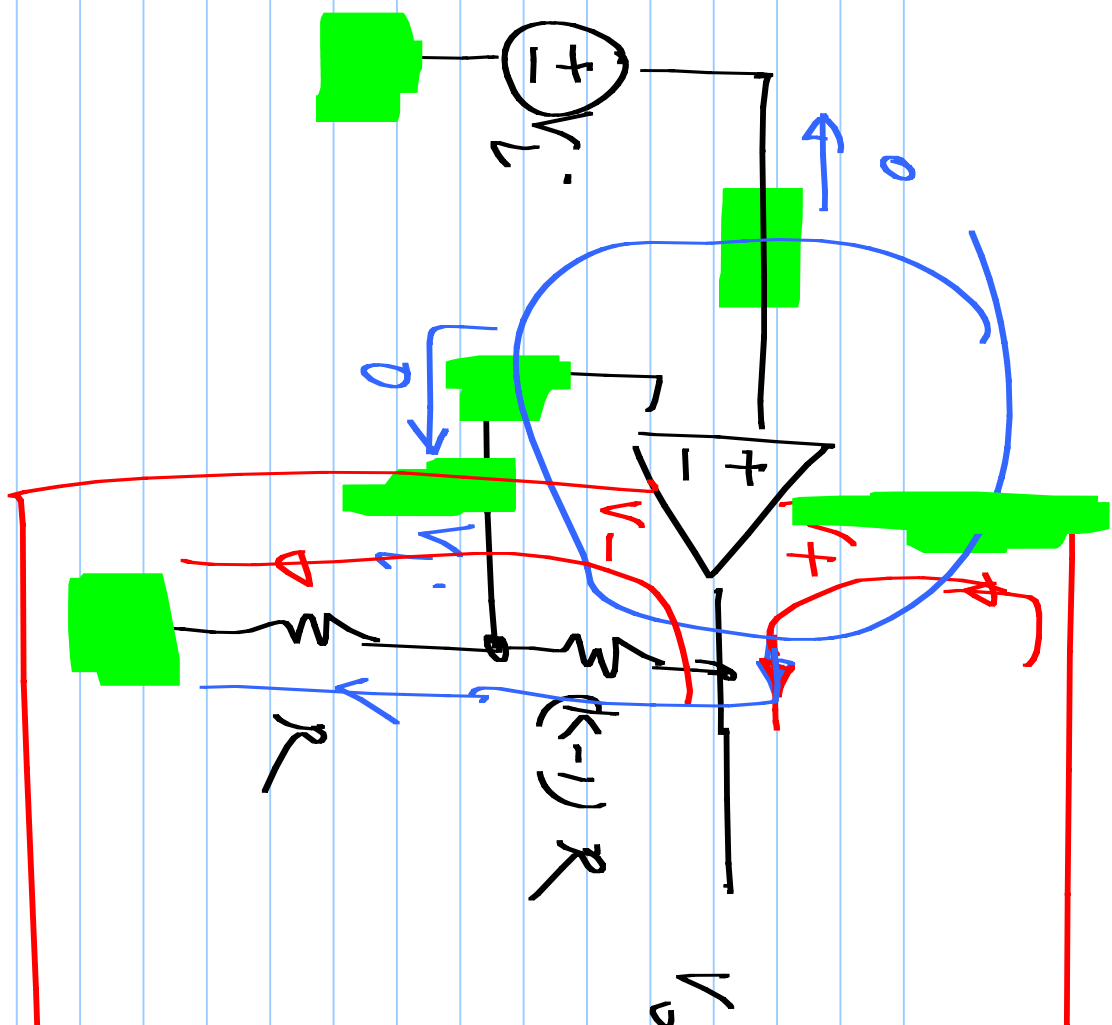



$$V_o = kV_i$$

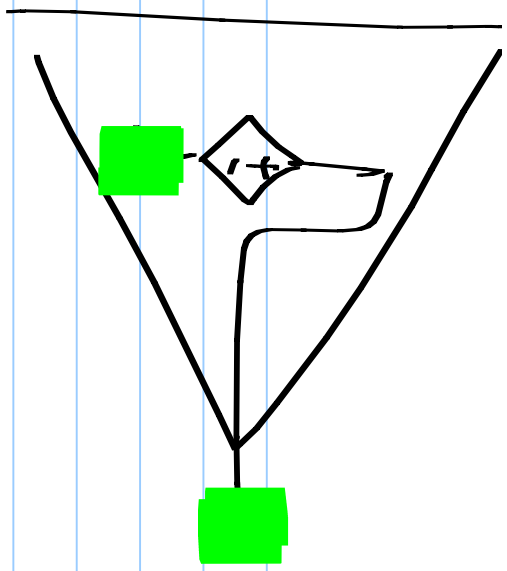

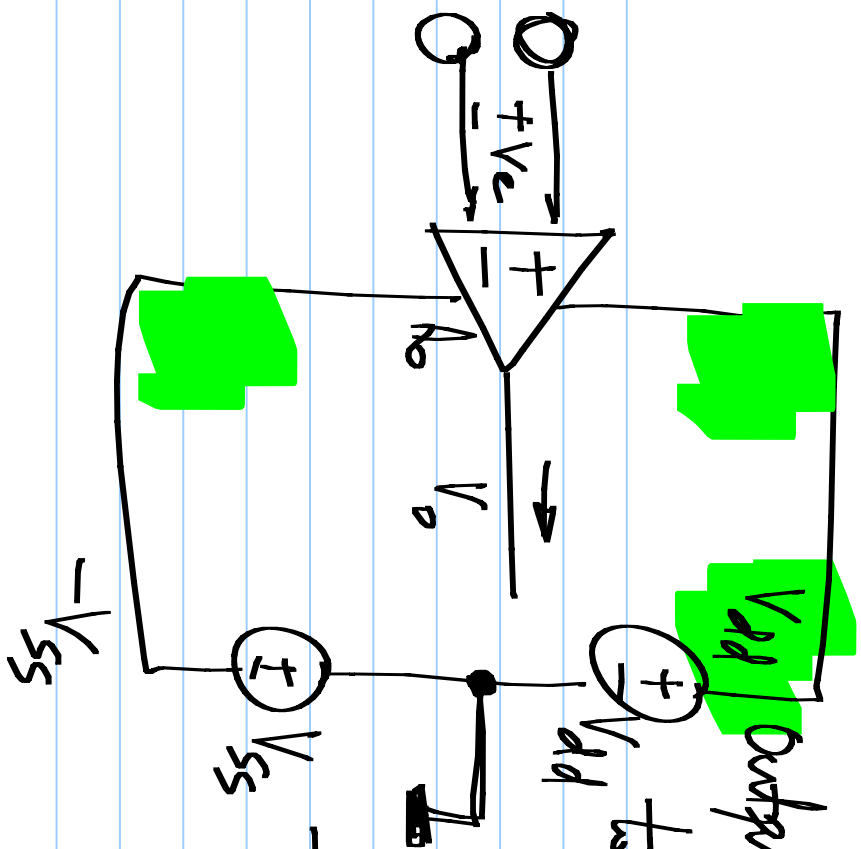

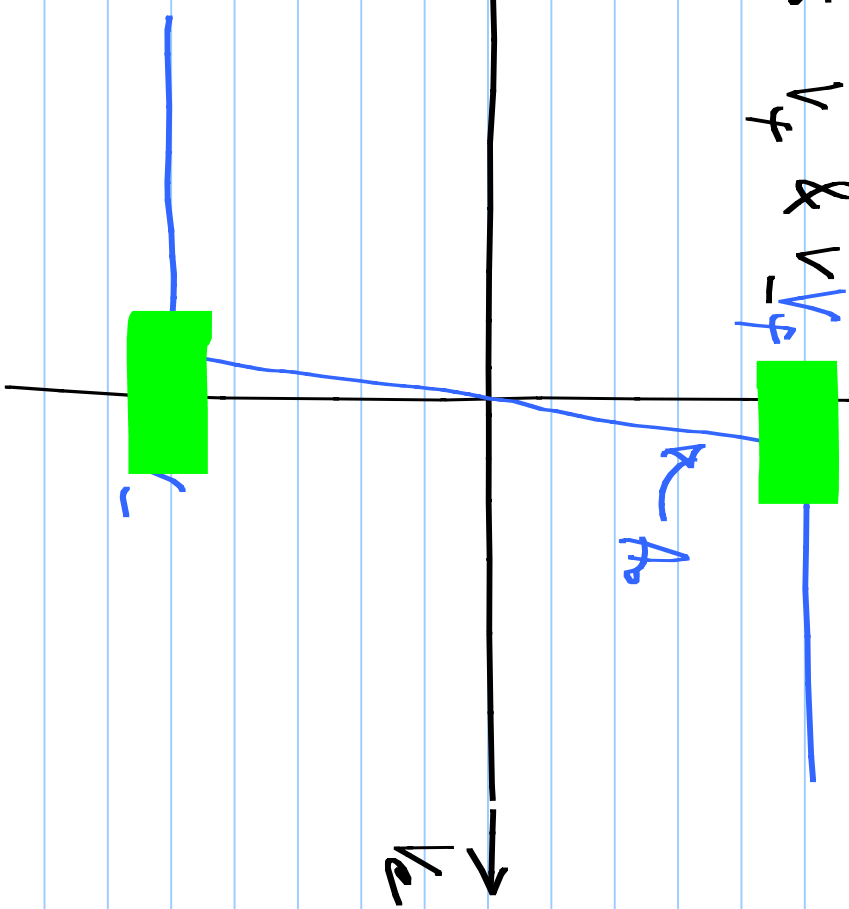V_{DD} Output saturates V_o
 Add to V_f & V_{Vf}



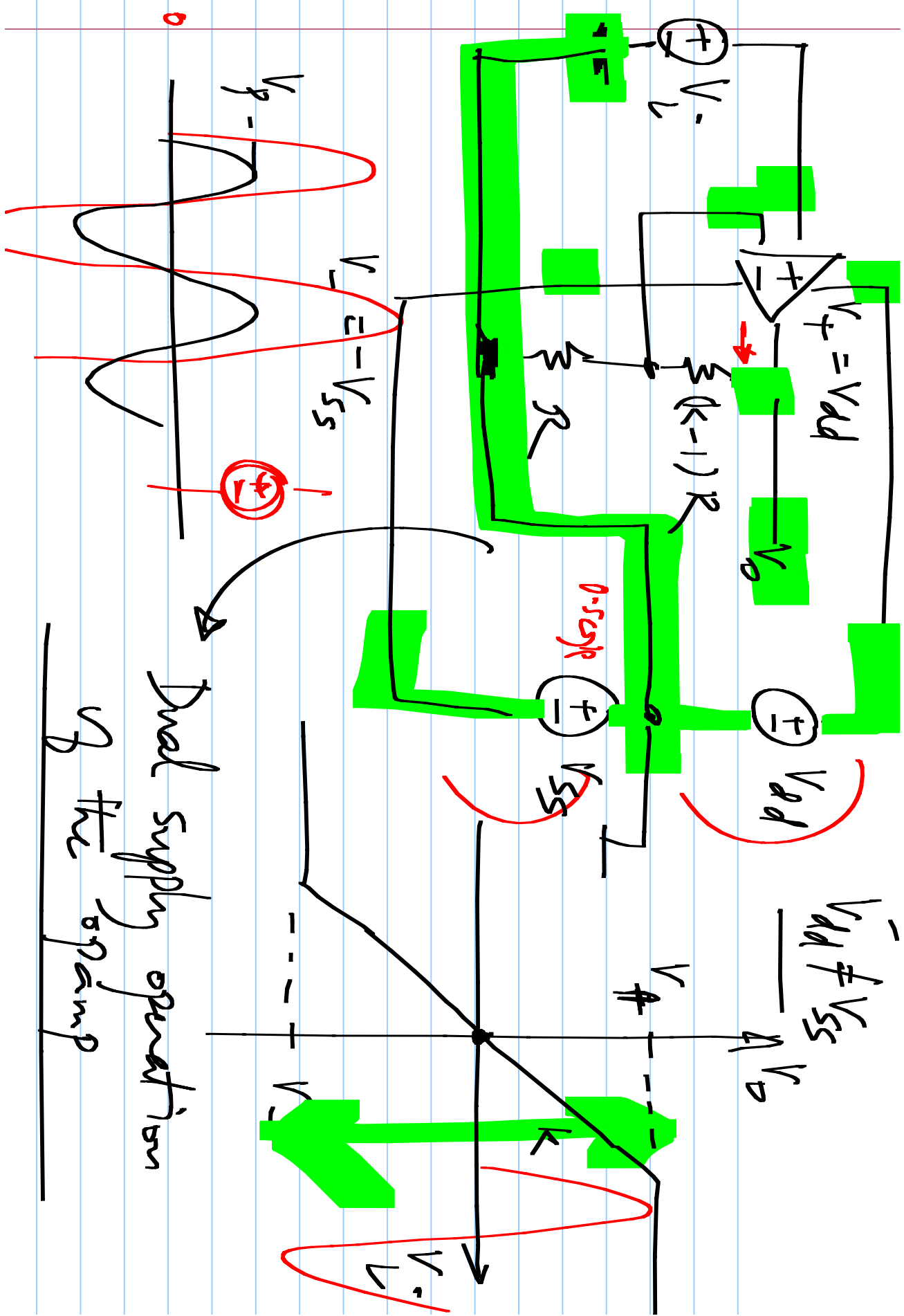

Dual supply operation
of the opamp

$$\frac{V_{DD} \neq V_{SS}}{V_o}$$

