

EE2019

Inverting Schmitt trigger


14/2/2017

$V_i < 0 \quad V_o = +V_{sat}$

$V_i > 0 \quad V_o = -V_{sat}$

$V_i < 0 :$

Set a +ve

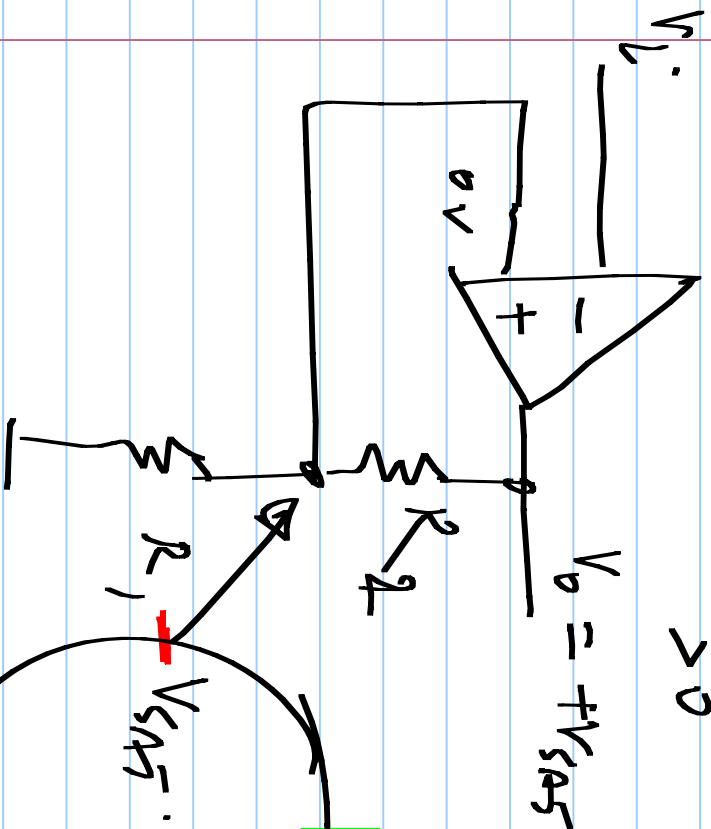



$V_{sat} \cdot \frac{R_1}{R_1 + R_2}$

$V_o \nearrow$ threshold



$V_i = \frac{V_{sat} \cdot R_1}{R_1 + R_2}$







Schmitt trigger

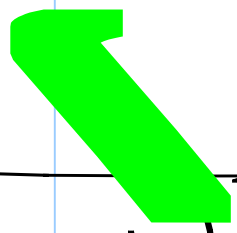
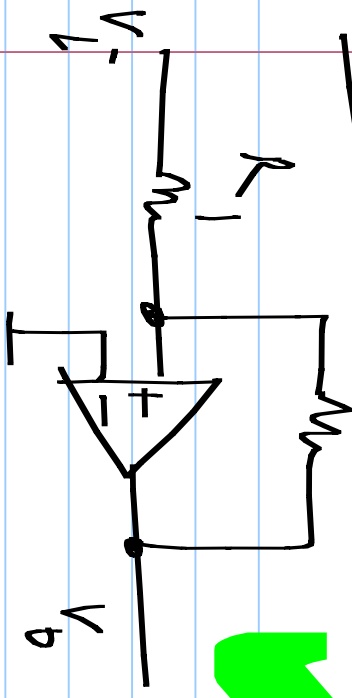


Amplifier

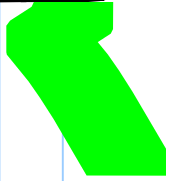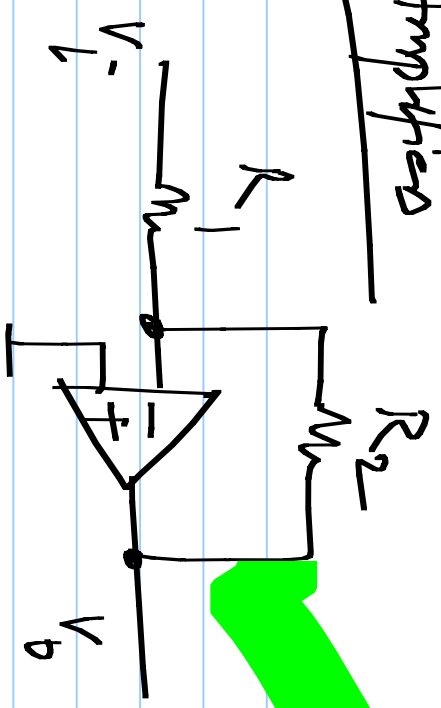


$$V_o \approx V_i$$

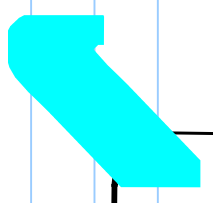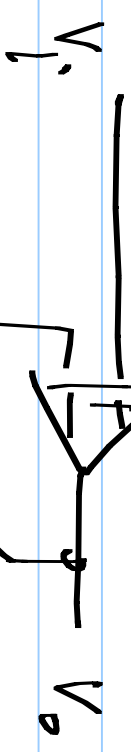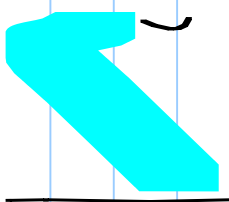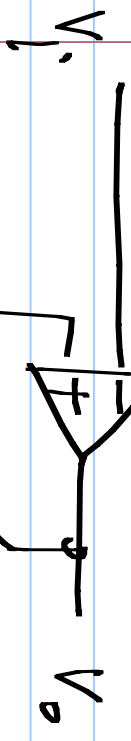


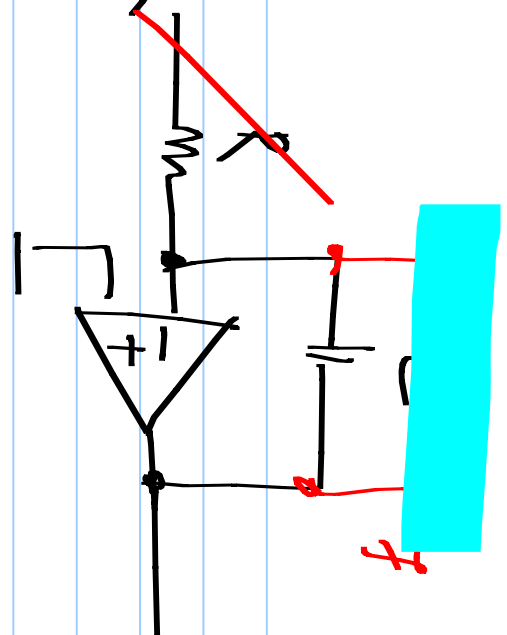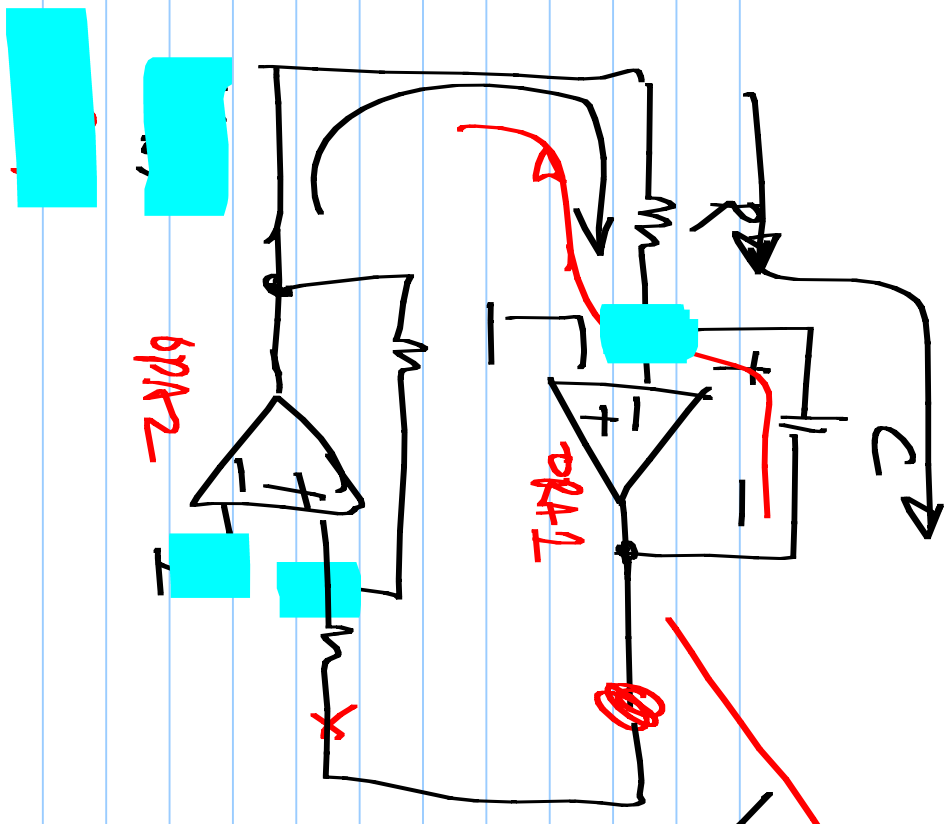

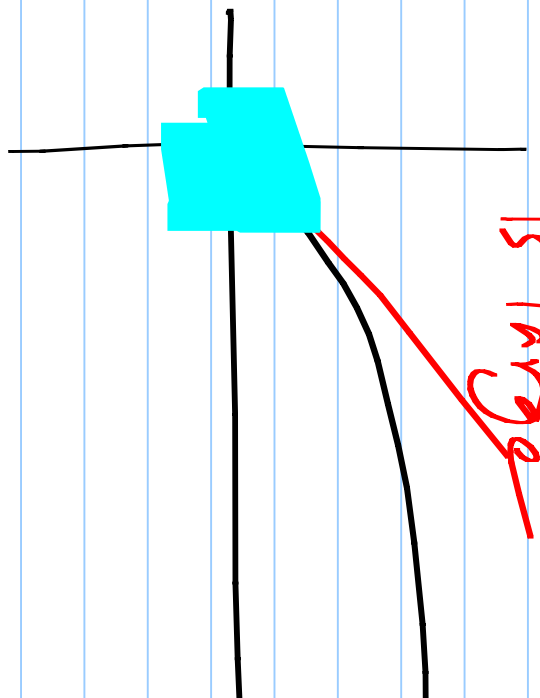\approx integrator if $\frac{R}{A} R$ is large



Pump - made using transistors


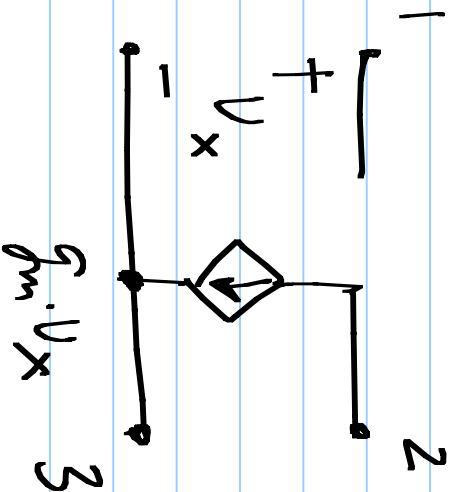


V_{CCS}

$A_2 = 10^6$


$$\frac{g_m}{g_n} = 100$$


$$V_o = \frac{g_m}{g_o}$$

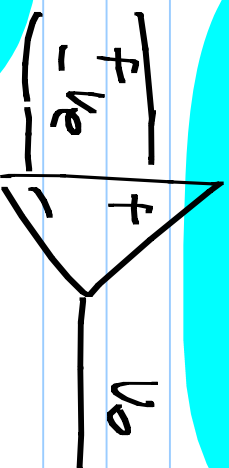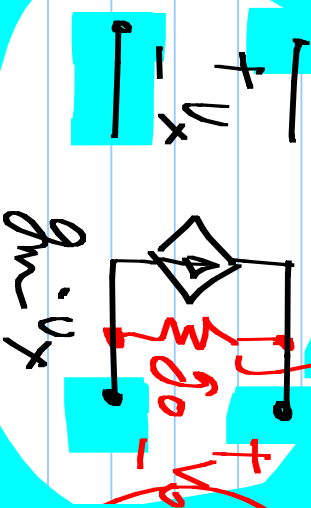

$$V_o = \frac{g_m}{g_n} = 2/100$$


$$g_o + g_L$$

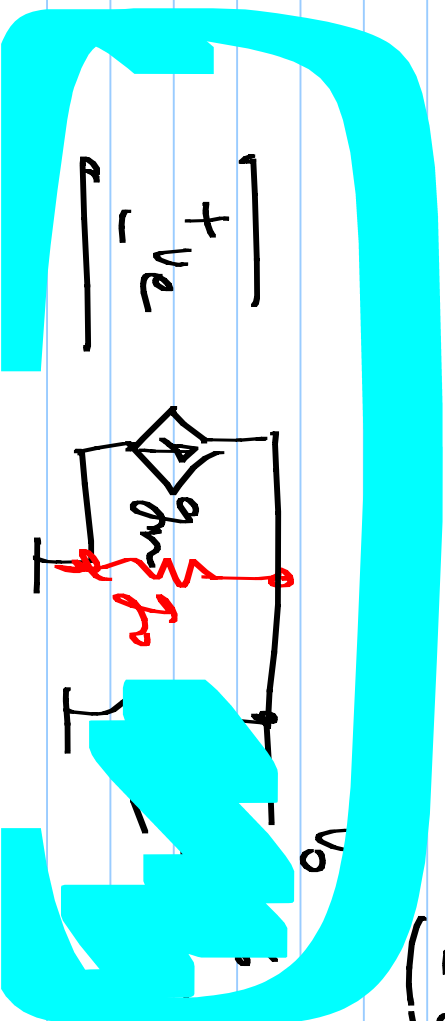

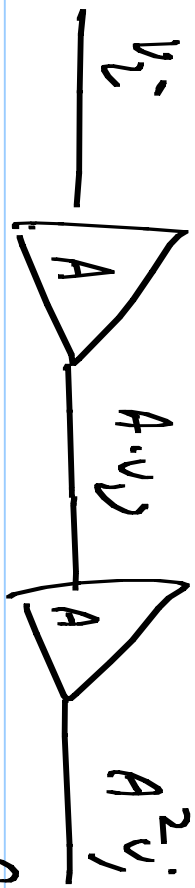


Cascade
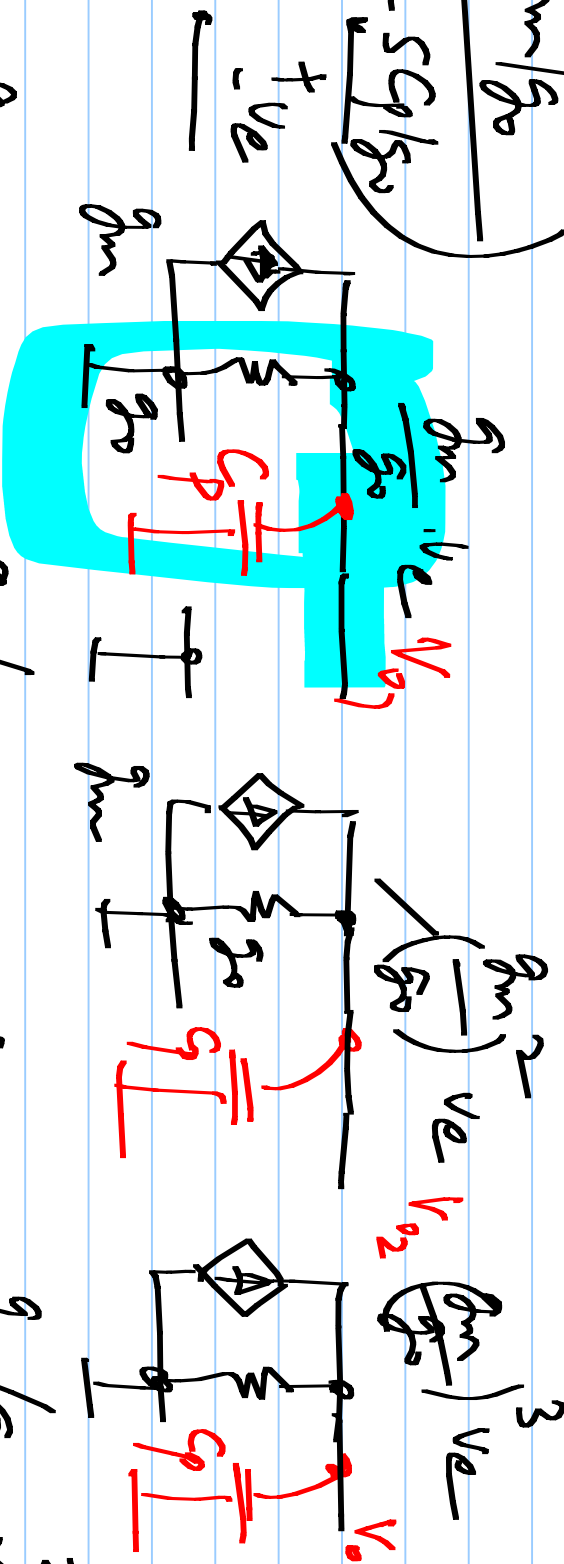
$$V_{o2} = \frac{g_m/g_o}{1 + sC_p/g_o} V_e$$



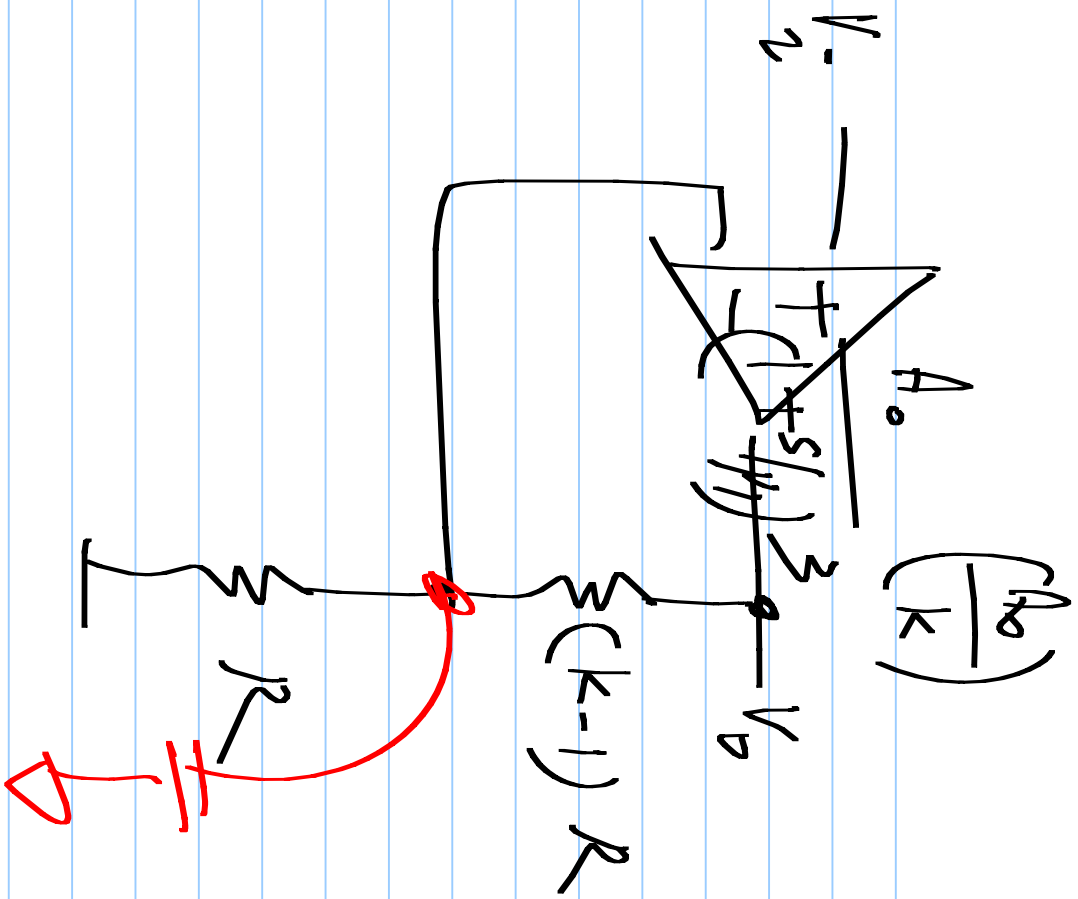
$$\frac{V_o}{V_e} = \frac{g_m}{g_o + sC_p} = \frac{g_m/g_o}{1 + sC_p/g_o}$$



$$V_0 = \frac{k}{1 + \frac{k}{A_0}} V_2$$

$$\left(\frac{A_0}{k}\right) =$$

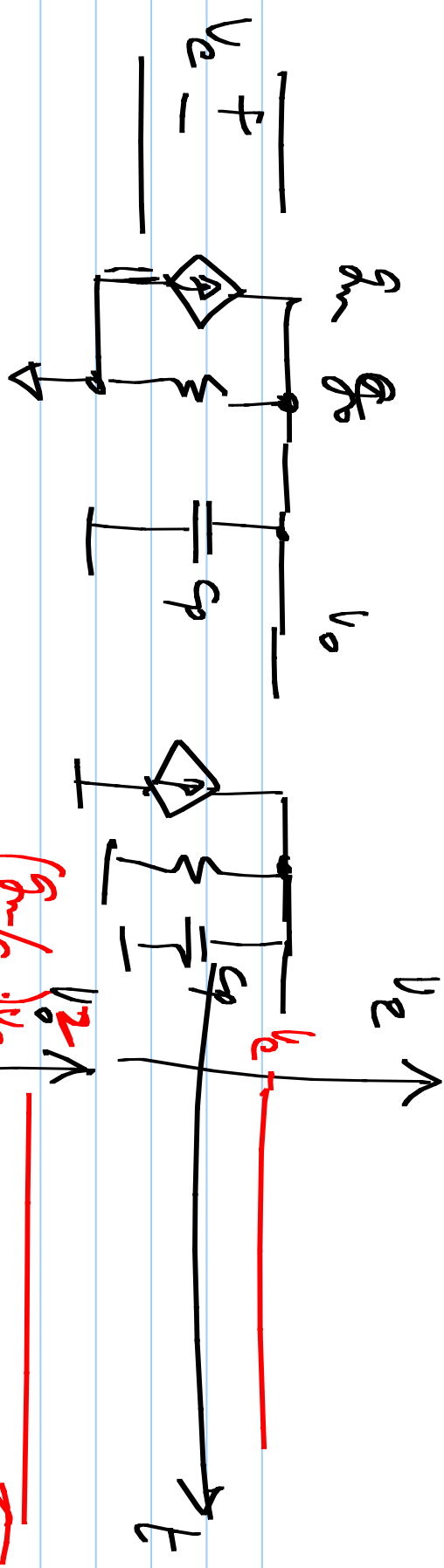

$$\frac{g_m/g_o}{1 + s C_P/g_o}$$

