
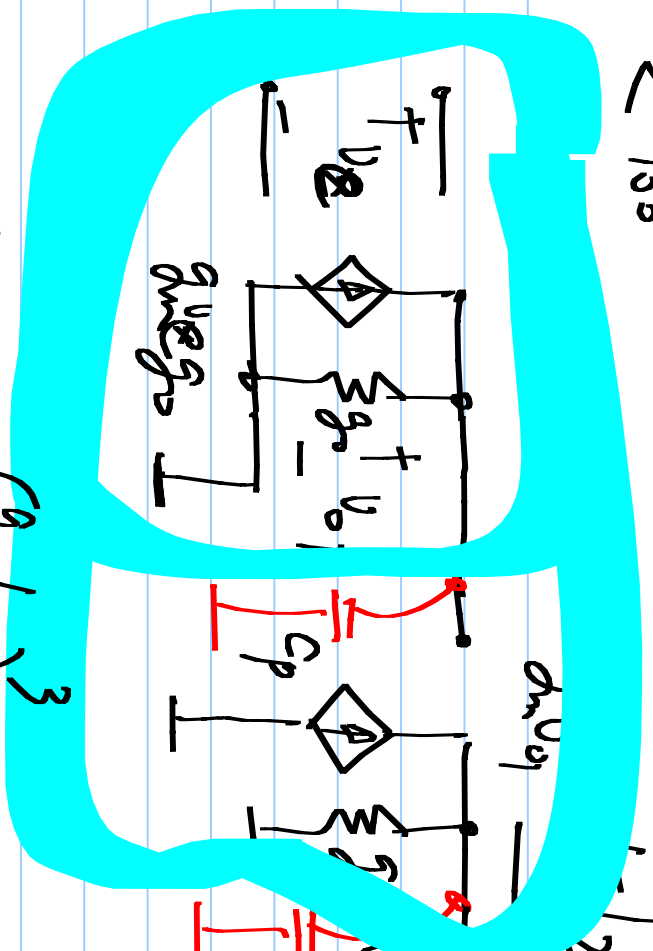


EE 2019

$$\frac{g_m}{g_o} < 100$$

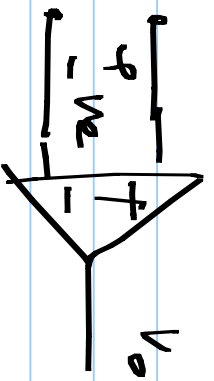



11/2/2017

$$\frac{V_{o1}}{V_e} = \frac{g_m/g_o}{1 + s \cdot C_p/g_o} \quad A_o$$

$$\frac{V_{o3}}{V_e} = \frac{(g_m/g_o)^3}{(1 + s C_p/g_o)^3}$$

$$\frac{V_{o2}}{V_e} = \frac{(g_m/g_o)^2}{(1 + s C_p/g_o)^2}$$

Single-stage opamp.

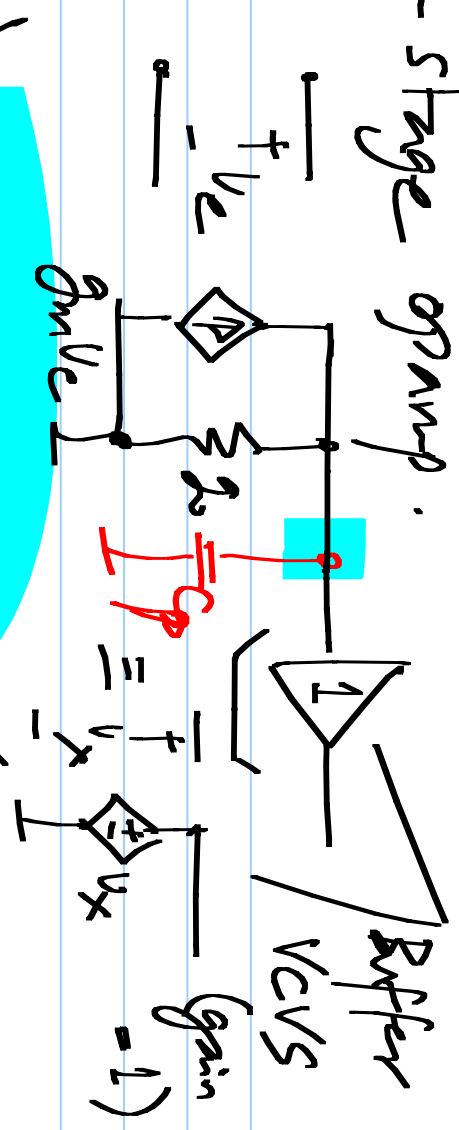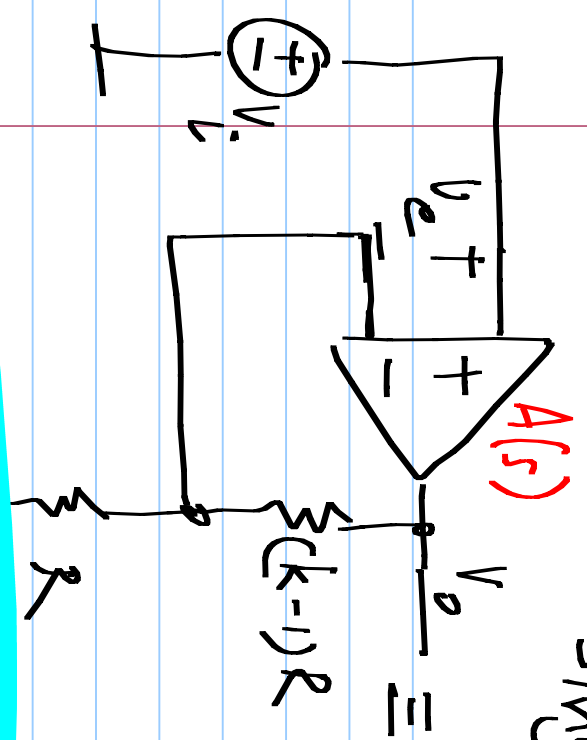

$$A(s) = \frac{A_0}{1 + sI}$$

$$A_0 = \left(\frac{g_m}{g_o} \right)$$

Closed-loop TF

$$\frac{V_o}{V_e} = \frac{k}{1 + \frac{k(1 + \frac{s}{\rho_1})}{A_0}} = \frac{k}{1 + \frac{k}{A_0} + \frac{k \cdot s}{A_0 \rho_1}}$$

$$V_o = \frac{k}{1 + \frac{k}{A_o} + \frac{k}{A_o} \cdot \frac{s}{p_1}}$$


dc gain:

$$\frac{k}{1 + k/A_o}$$

Pole: $-p_1 \left(1 + \frac{A_o}{k}\right) \approx -p_1 \frac{A_o}{k}$

Unconditionally stable



$$A_o \gg k$$

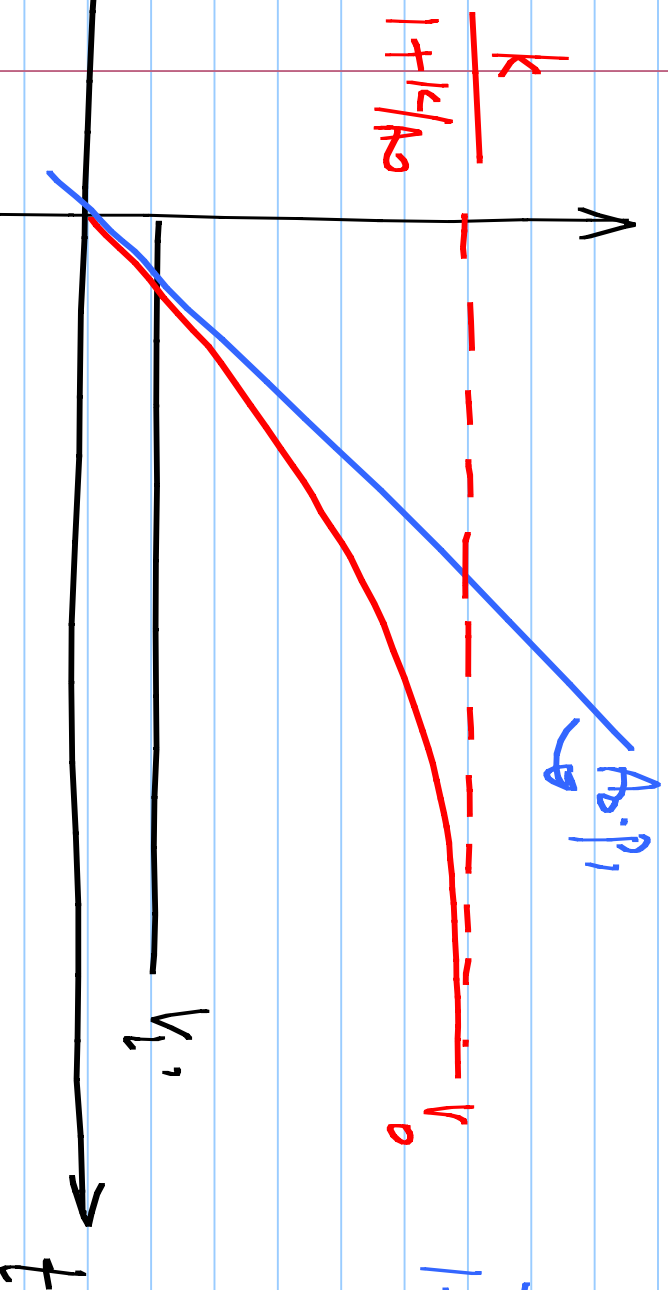

$$\frac{k}{1 + k/A_o} \left(1 - \exp\left(-\frac{p_1 t}{C}\right)\right)$$

Gain: Bandwidth product $\approx A_0 \cdot \rho_1$
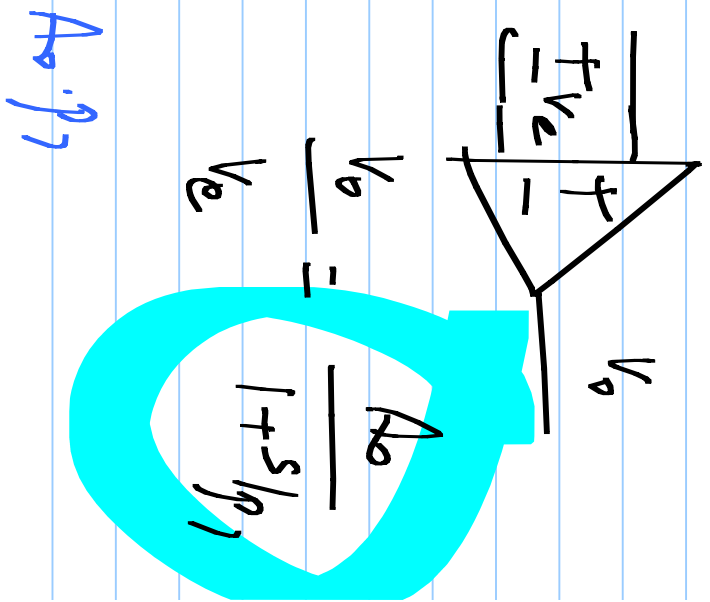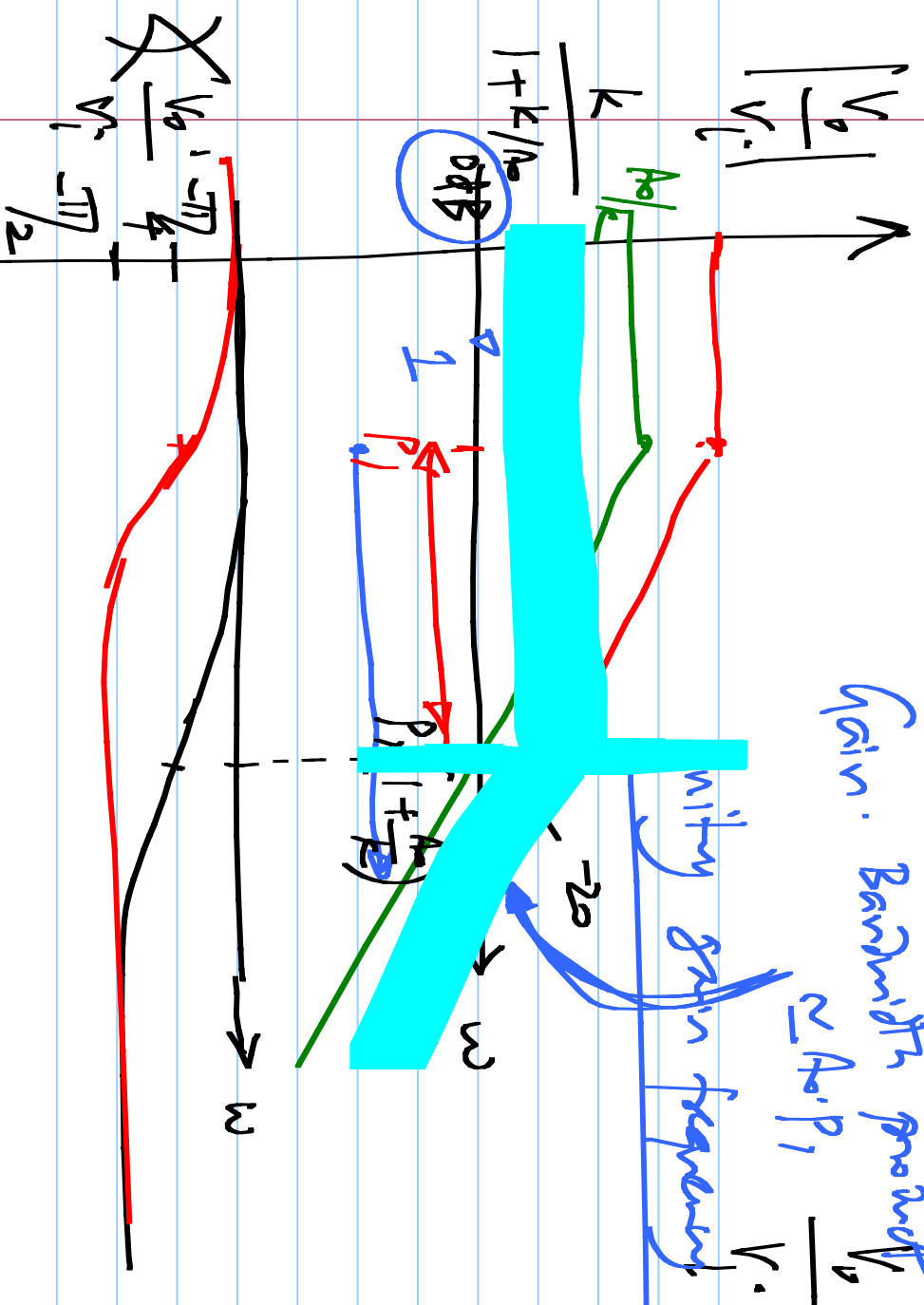
$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{k}{A_0} + \frac{k \cdot s}{A_0 \rho_1}}$$



$$\frac{k}{1 + \frac{k}{R}} \left(1 - \exp \left(- \underbrace{r_1 \left(1 + \frac{R}{k} \right)}_t \right) \right)$$