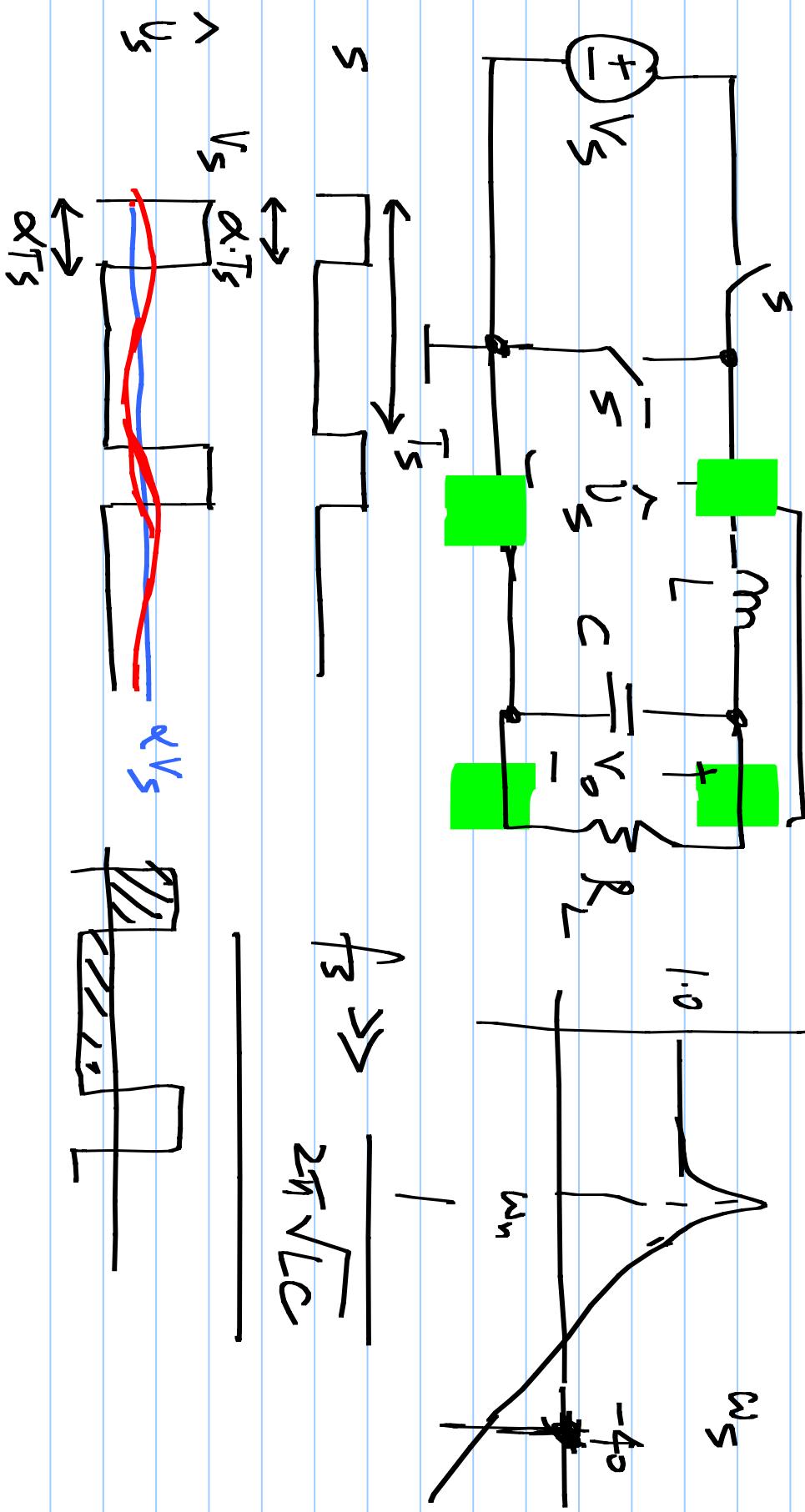



EE 2019


dc-dc converters


$$R_L \sqrt{\frac{C}{L}}$$


10/3/2017




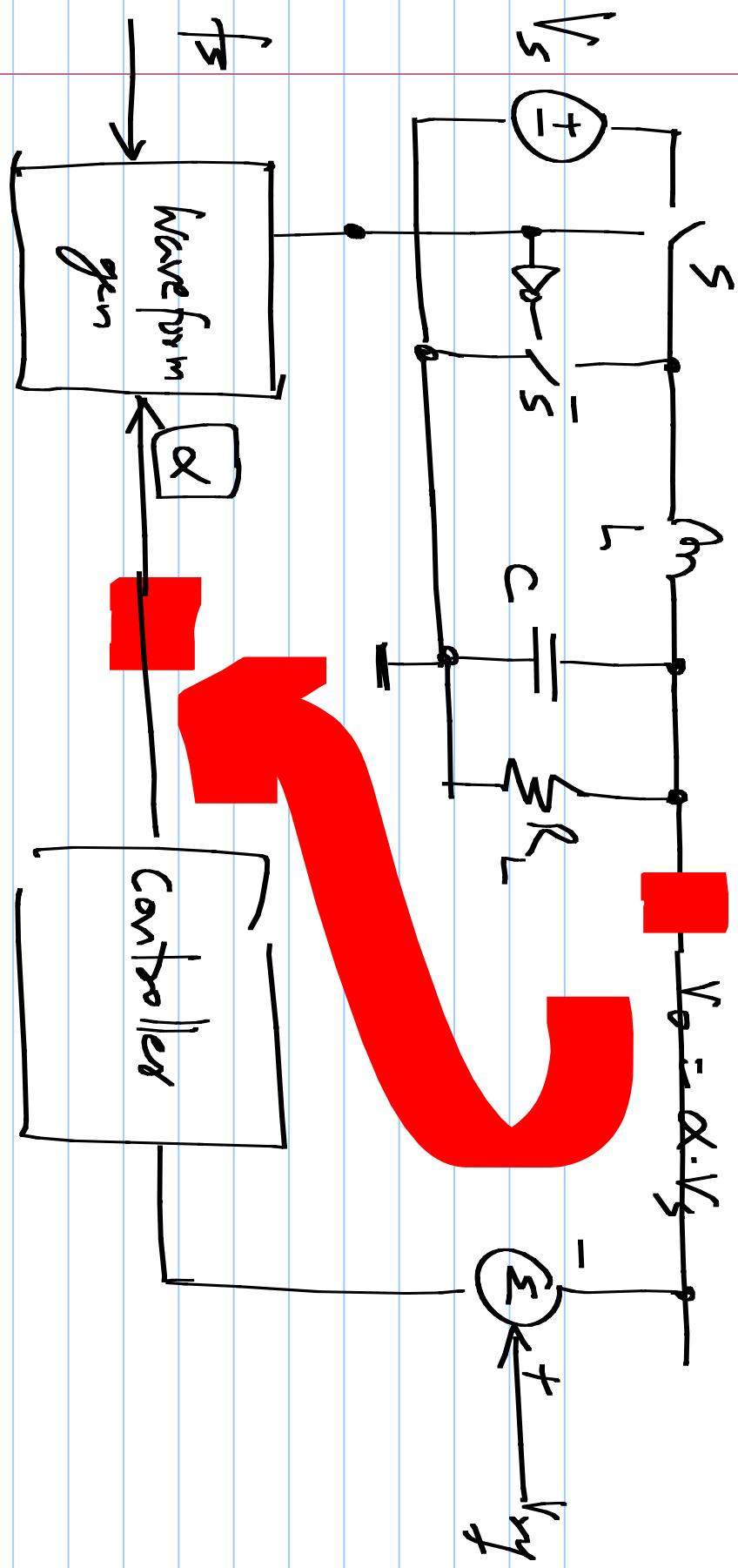

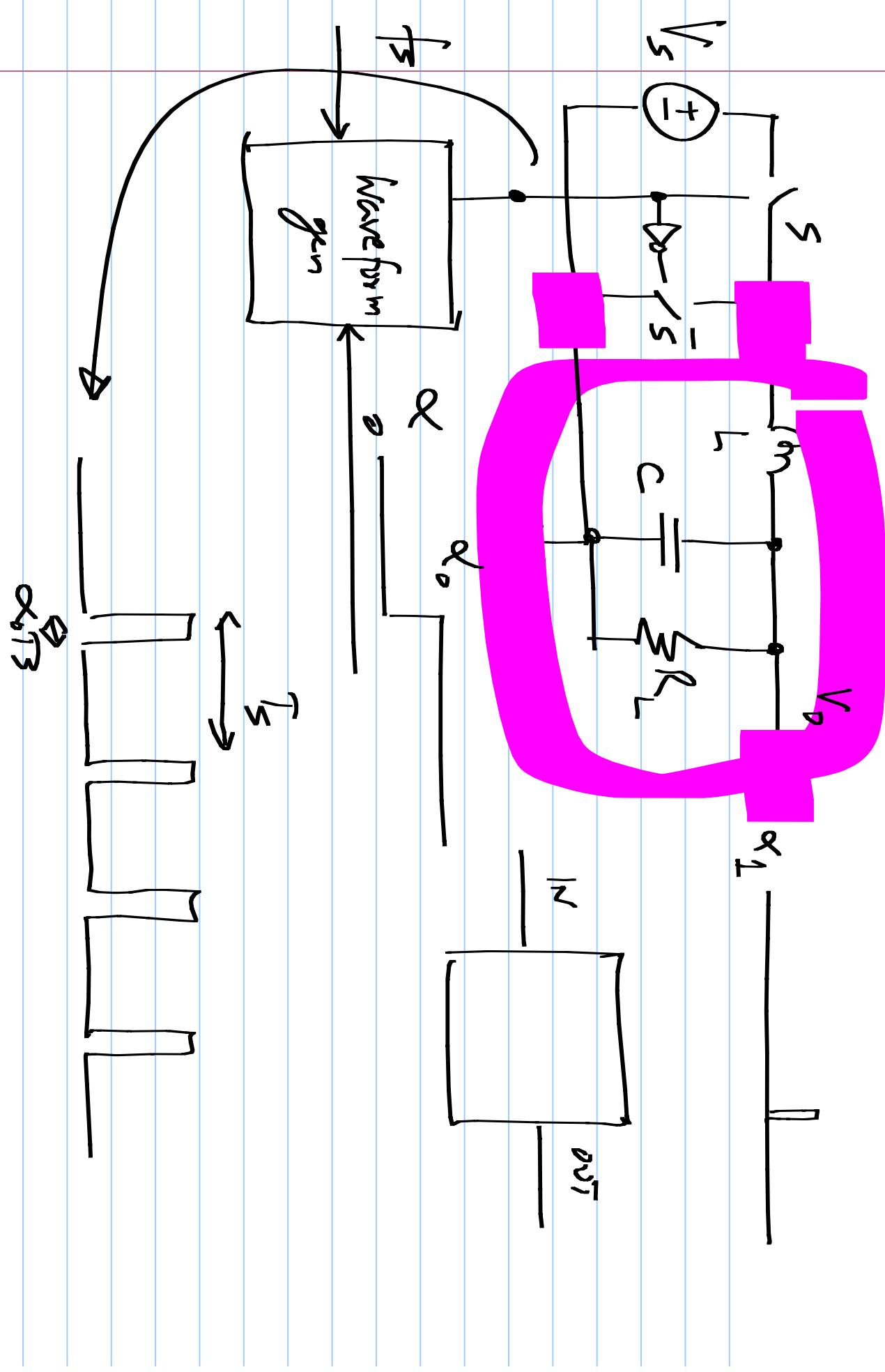


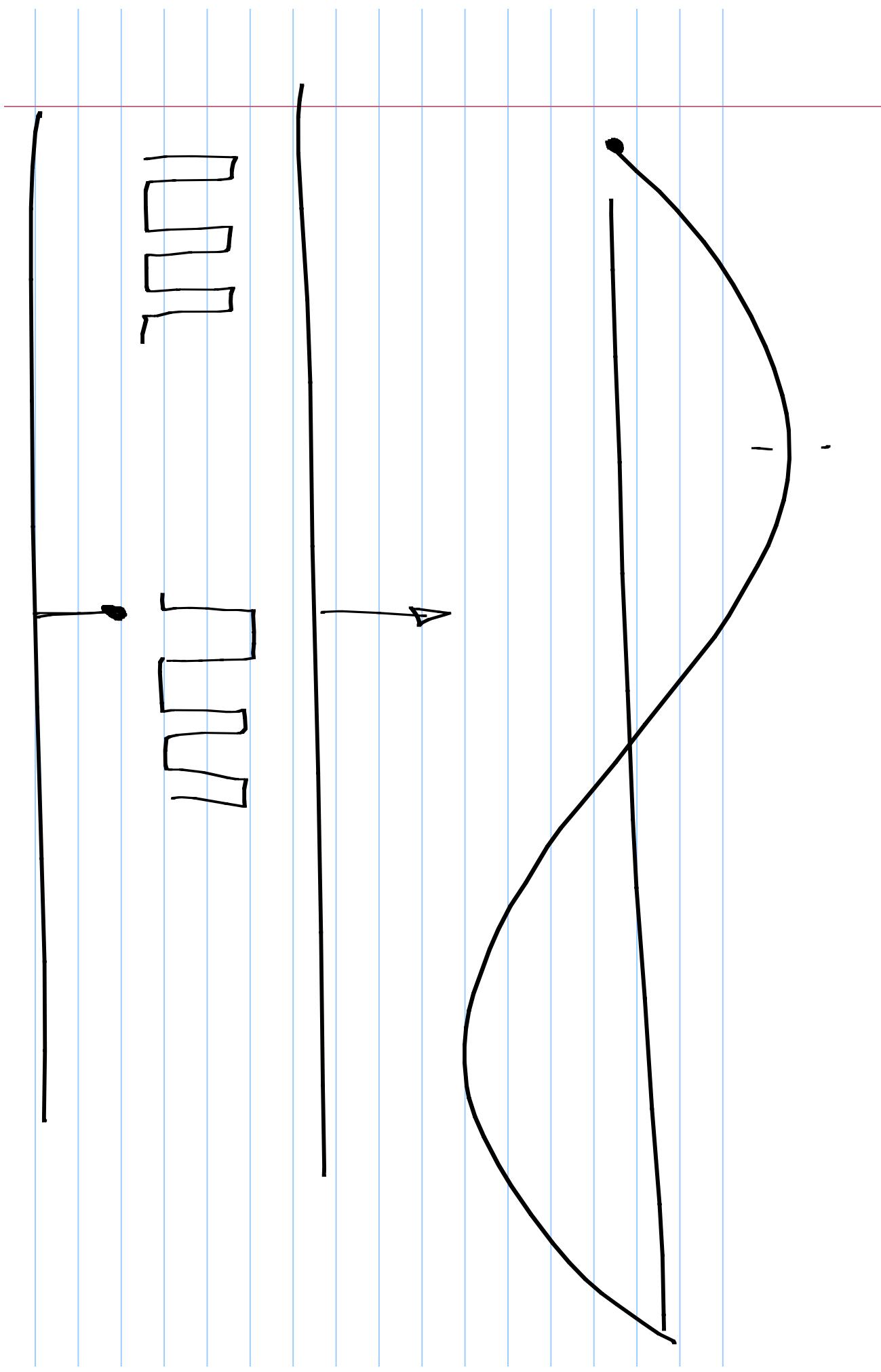

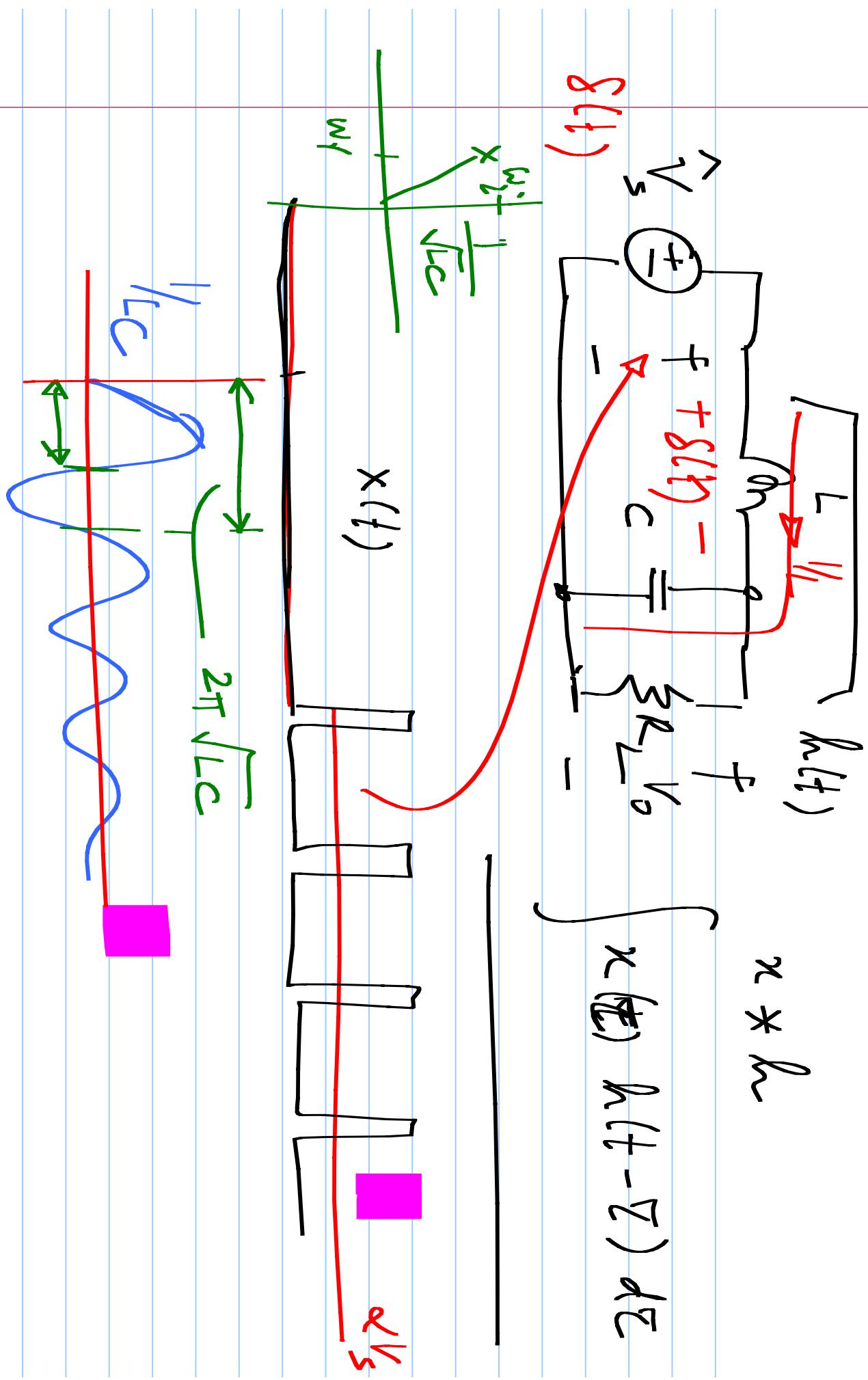

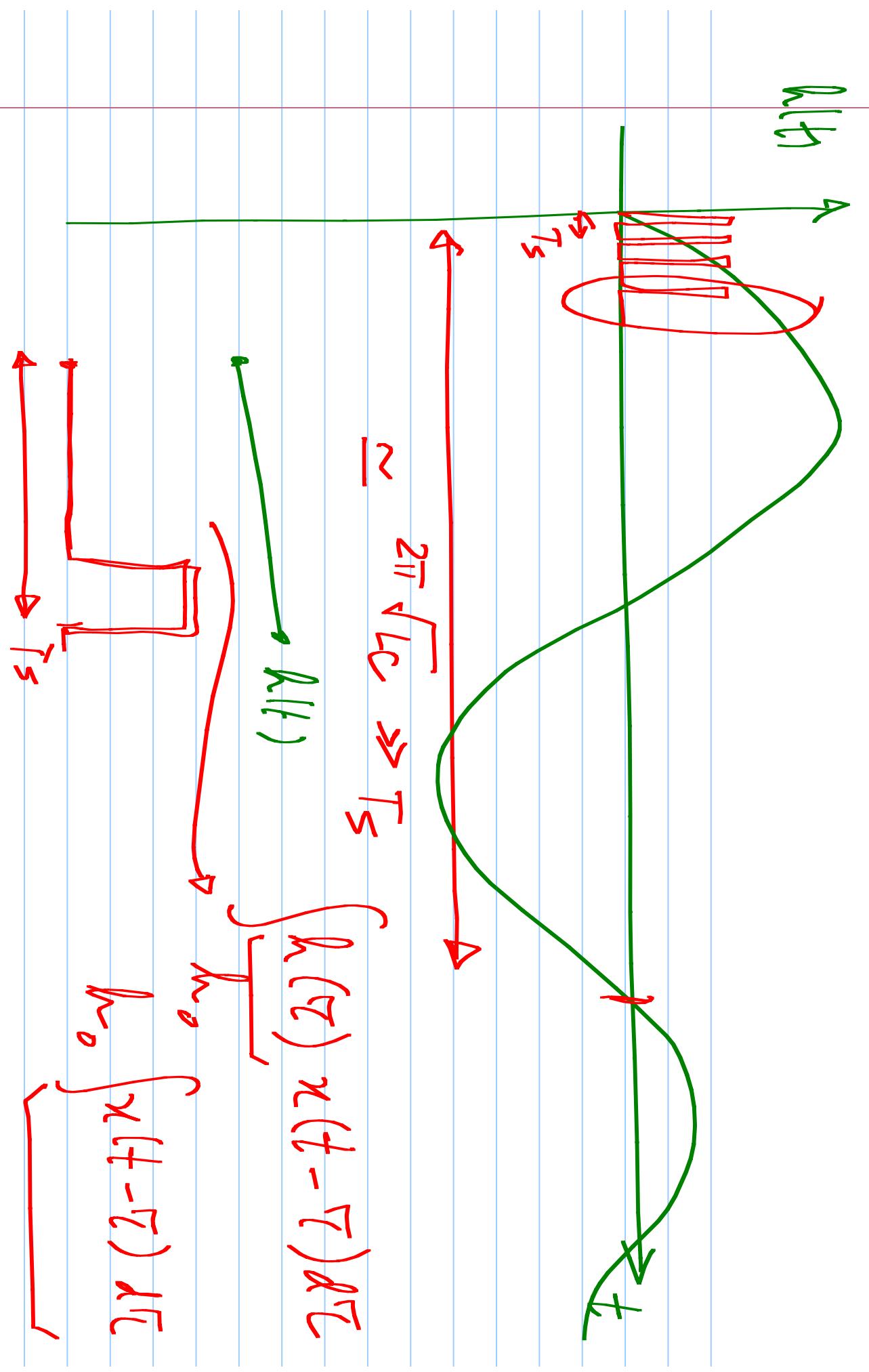

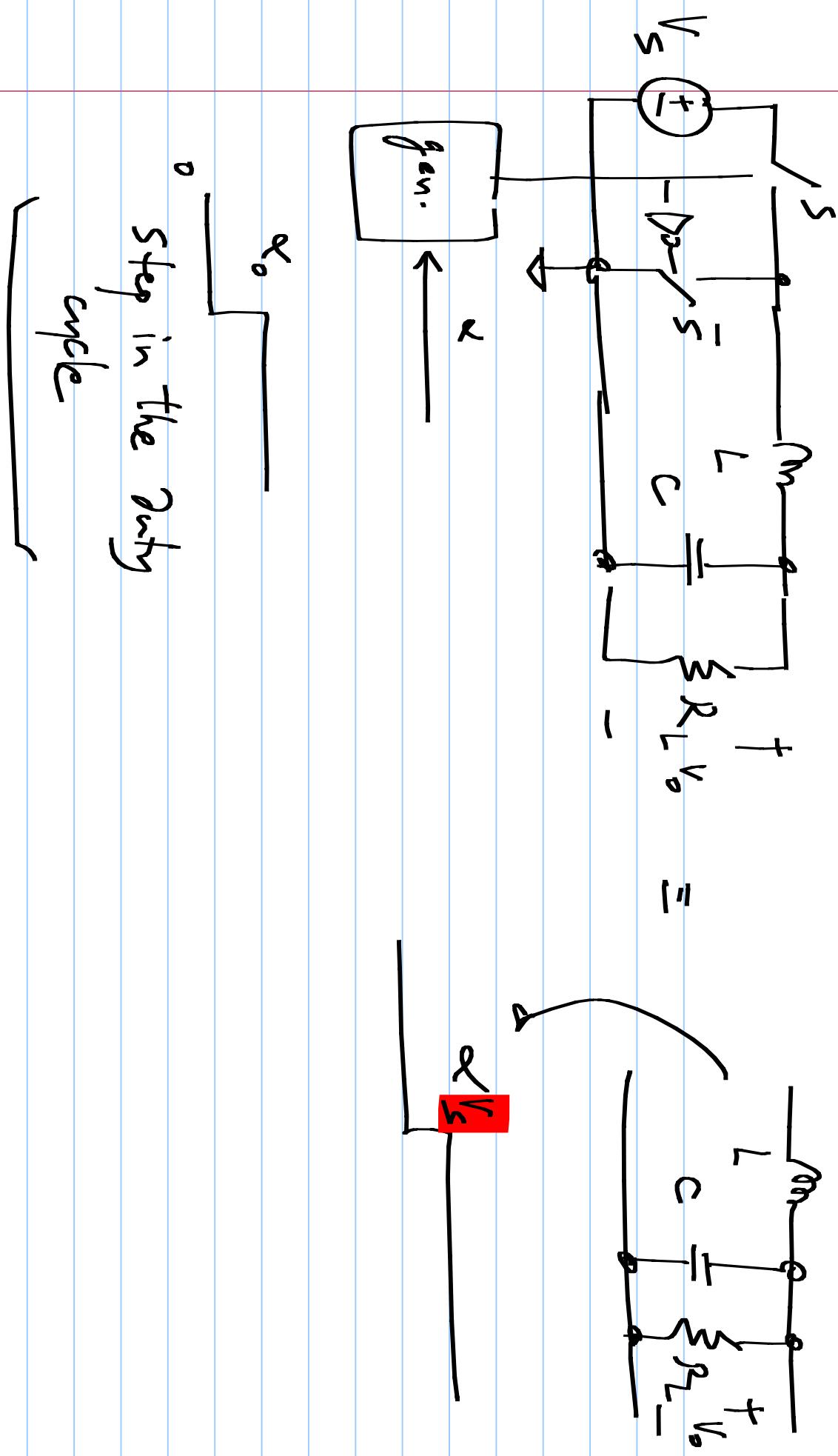- * Impulse response of the LC filter hardly changes within a switching period.
- * The input can be approximately represented by its average in each period.




Response of the circuit to a step α_0 in the

Duty cycle \approx

Response of the (LT) LC lowpass filter to

a step input $\alpha_0 V_s$
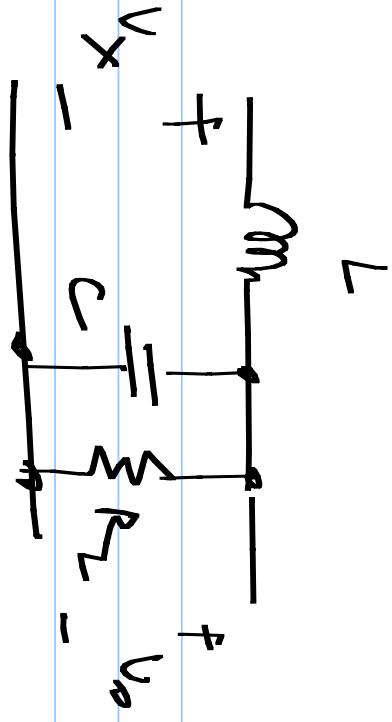
$$\frac{V_o(s)}{\alpha(s)} = \frac{1}{s^2 + \omega_0^2}$$



$$\frac{V(s)}{\alpha(s)} = \frac{s^2 L C + s \frac{1}{R_L} + 1}{s^2 L C + s \frac{1}{R_L} + 1}$$

