
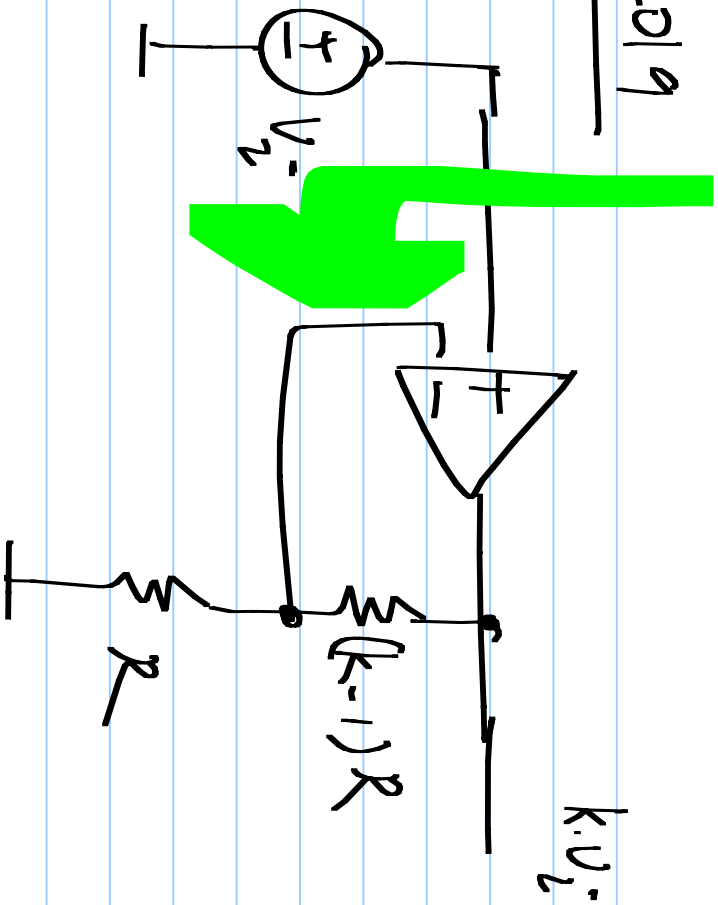



EE 2019

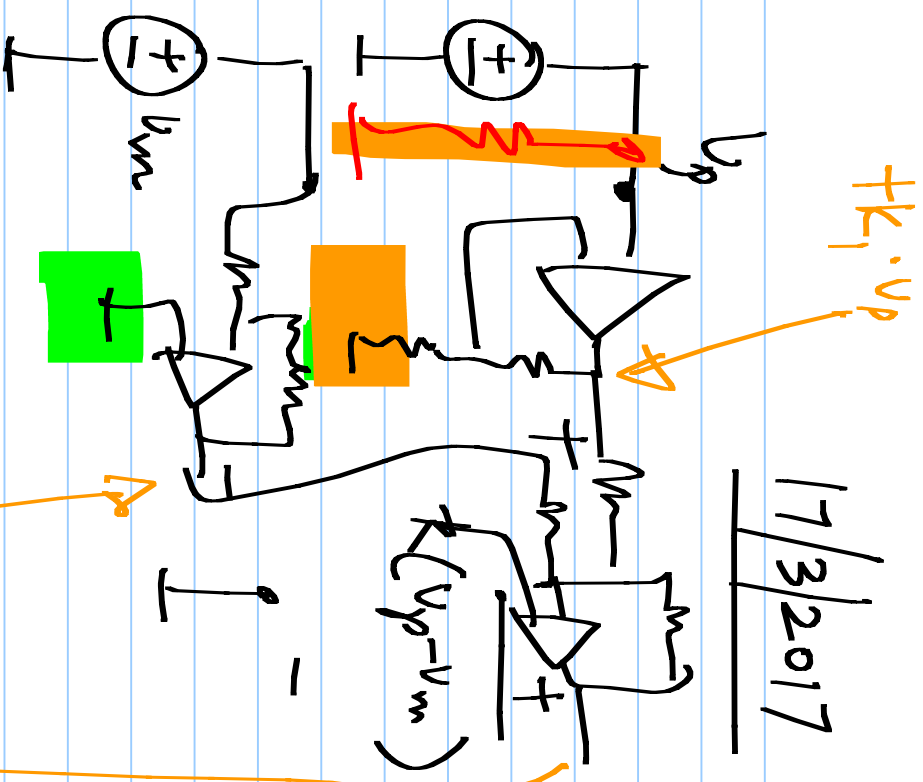



$$(k_1 \cdot v_p - k_2 \cdot v_m) k_3$$





1/7/3/2017

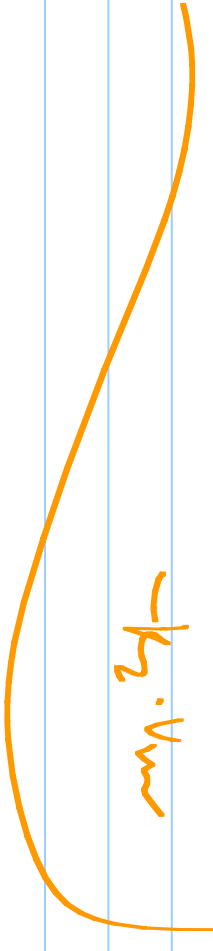

1

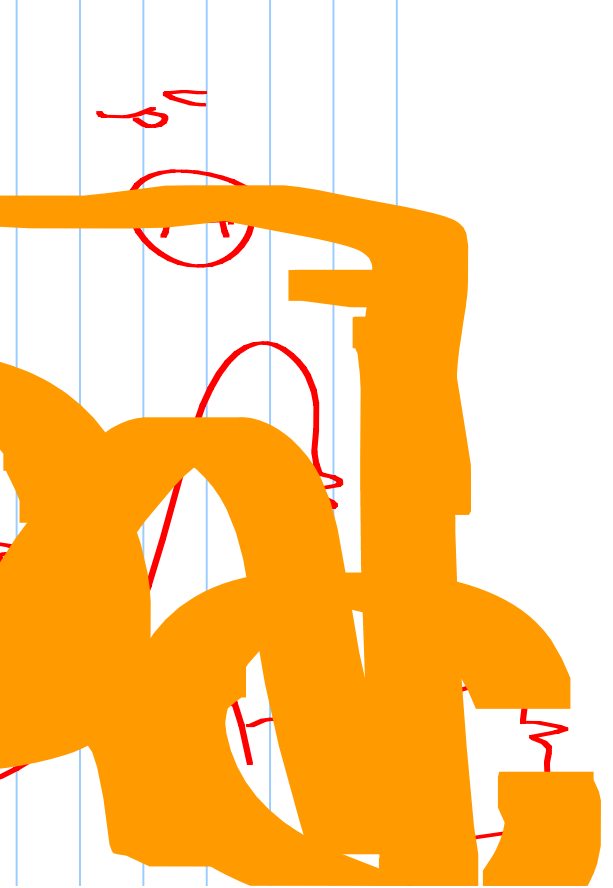
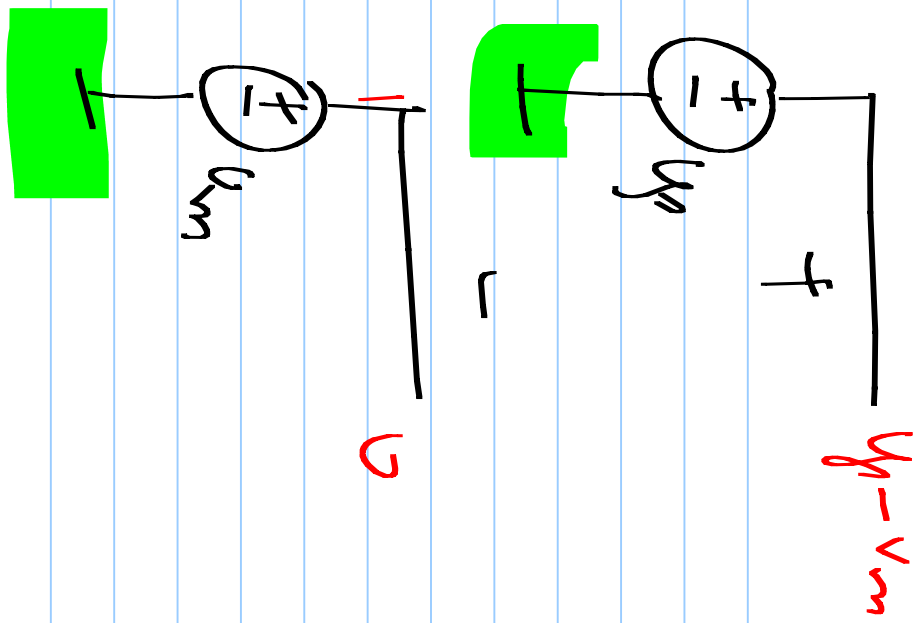


$$V_D (1 + R_2/k_1)$$

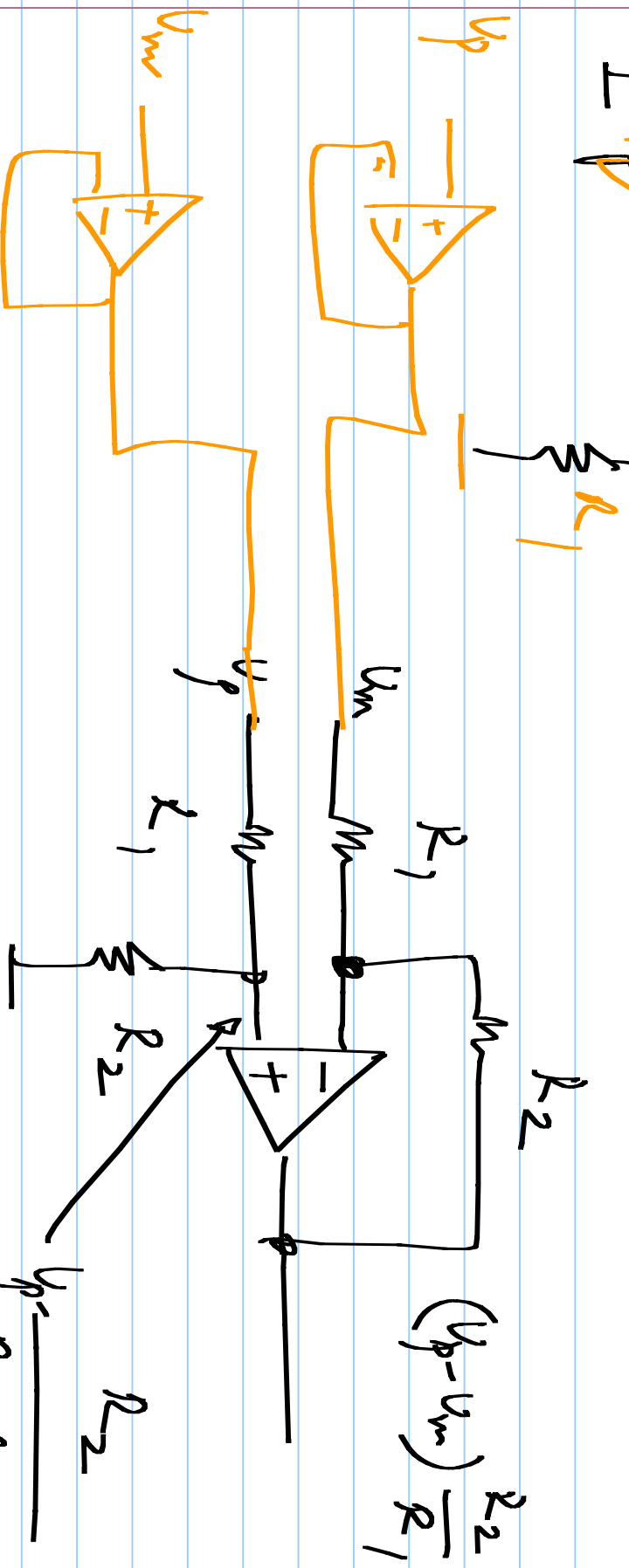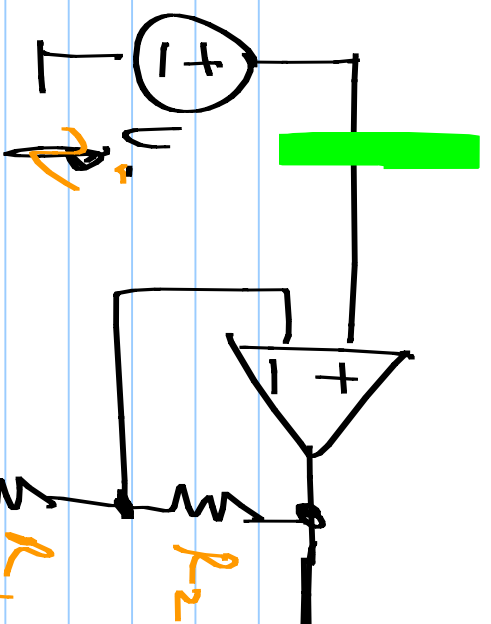

$$V_p^- \frac{R_2}{R_1 + R_2}$$

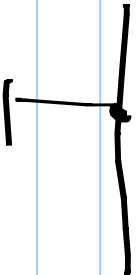
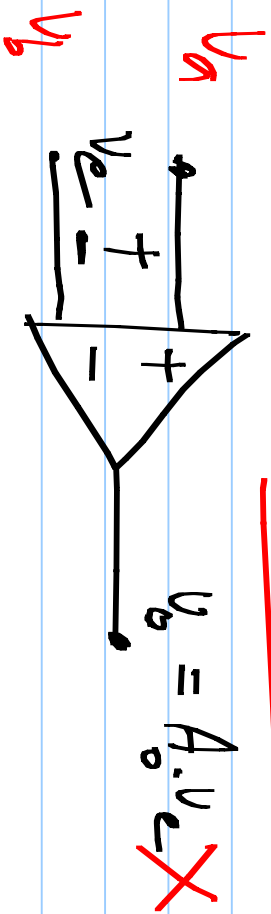
$$\underline{V_o = \alpha \cdot V_a + \beta V_b}$$



$$V_d = (V_a - V_b)$$

differential
component

$$V_{cm} = \frac{V_a + V_b}{2}$$

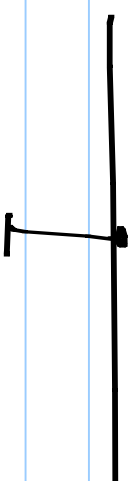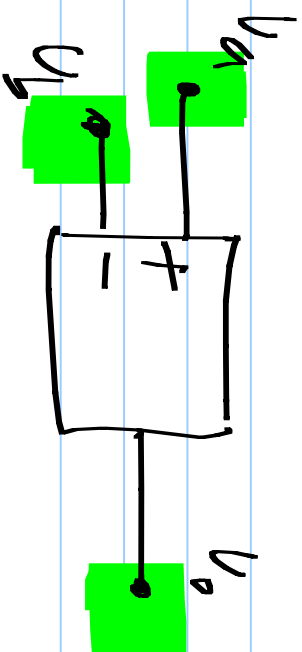

$$\underline{V_o = \alpha \cdot V_a + \beta \cdot V_b}$$

V_a, V_b

$$V_o = \frac{\alpha V_a + \beta \cdot V_b}{1} = (\frac{\alpha - \beta}{2}) V_d + (\frac{\alpha + \beta}{2}) V_{cm}$$

Differential voltage $V_d = V_a - V_b$

Common-mode voltage $V_{cm} = \frac{V_a + V_b}{2}$

(Average)


$$V_a = \text{[redacted]} = A_d \cdot V_d + A_{cm} \cdot V_{cm}$$

$$V_b = \text{[redacted]} = \text{[redacted]} \cdot V_d + \text{[redacted]} \cdot V_{cm}$$

Differential gain

Common mode gain

Difference amplifier

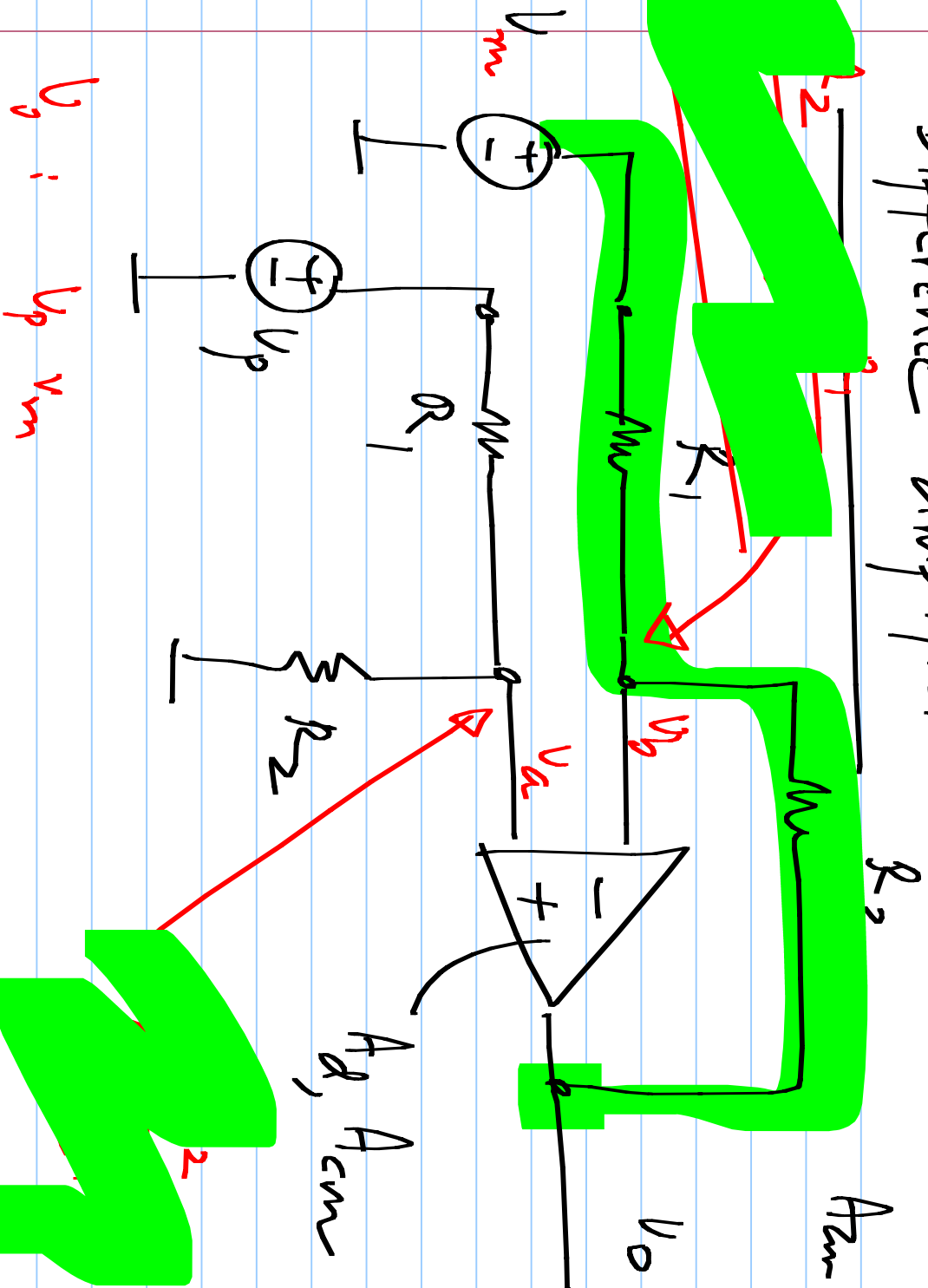


v_p, v_m

$A_1 \rightarrow \infty$
 $A_{cm} \rightarrow 0$

$$v_o = \frac{R_2}{R_1} (v_p - v_m)$$

v_a, v_b

v_1, v_m

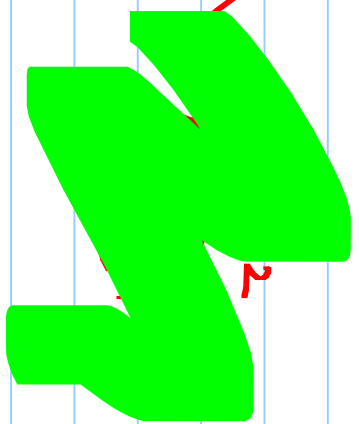

$$V_D = A_d \cdot V_d + A_{cm} \cdot V_{cm}$$

$$V_d = (V_p - V_m) \cdot \frac{R_2}{R_1 + R_2} - V_D \cdot \frac{R_1}{R_1 + R_2}$$

$$= A_d \cdot (V_p - V_m) \cdot \frac{R_2}{R_1 + R_2} - A_d \cdot V_D \cdot \frac{R_1}{R_1 + R_2}$$

$$V_{cm} = \frac{V_p + V_m}{2} \cdot \frac{R_2}{R_1 + R_2}$$

$$+ A_{cm} \left(\frac{V_p + V_m}{2} \right) \cdot \frac{R_2}{R_1 + R_2} + \frac{A_{cm} \cdot V_D \cdot \frac{R_1}{R_1 + R_2}}{2}$$

$$+ \frac{V_D}{2} \cdot \frac{R_1}{R_1 + R_2}$$

$$A_d \cdot (V_p - V_m) \cdot \frac{R_2}{R_1 + R_2} + A_{cm} \left(\frac{V_p + V_m}{2} \right) \cdot \frac{R_2}{R_1 + R_2}$$

$$V_D = \frac{1 + (A_d - A_{cm}) \cdot \frac{R_1}{R_1 + R_2}}{1 + (A_d - A_{cm}) \cdot \frac{R_1}{R_1 + R_2}}$$


$$V_D = \frac{A_{d1} \cdot (V_p - V_m) \frac{R_2}{R_1 + R_2} + A_{2m} \left(\frac{V_p + V_m}{2} \right) \cdot \frac{R_2}{R_1 + R_2}}{1 + (A_{d1} - \frac{A_{2m}}{2}) \cdot \frac{R_2}{R_1 + R_2}}$$

$$\frac{A_{d1} \cdot (V_p - V_m) \frac{R_2}{R_1 + R_2} + A_{2m} \left(\frac{V_p + V_m}{2} \right) \cdot \frac{R_2}{R_1 + R_2}}{1 + (A_{d1} - \frac{A_{2m}}{2}) \cdot \frac{R_2}{R_1 + R_2}}$$

$$= \frac{(V_p - V_m) \cdot \frac{R_2}{R_1} \cdot \frac{1}{1 - \frac{A_{d1} R_2}{R_1 + R_2}} + \frac{A_{2m} (V_p + V_m)}{2} \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + \frac{A_{2m} R_2}{2(R_1 + R_2)}}}{1 + (A_{d1} - \frac{A_{2m}}{2}) \cdot \frac{R_2}{R_1 + R_2}}$$

$$+ \frac{(V_p + V_m) \cdot \frac{R_2}{R_1} \cdot \frac{1}{1 - \frac{A_{d1} R_2}{R_1 + R_2}}}{1 + (A_{d1} - \frac{A_{2m}}{2}) \cdot \frac{R_2}{R_1 + R_2}}$$

$\frac{A_{2m}}{A_{d1}} \ll 10^{-4}$

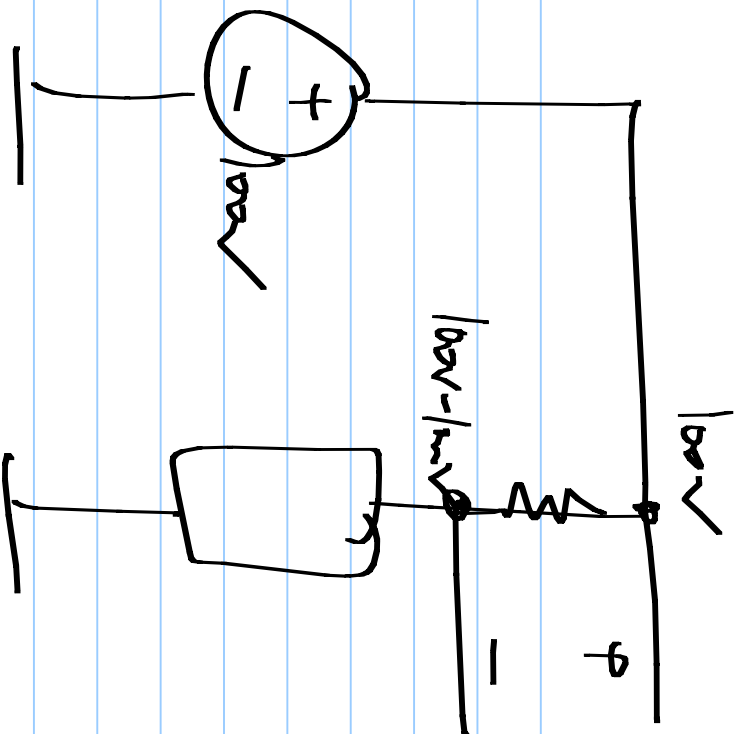

Common-mode rejection

ratio

A_1

A_{cm}