

EE 2019

- * Channel selection
- * Noise removal
- * Anti-aliasing
- * Reconstruction

''''

22/3/2017

Filter:



$$H(s) = \frac{N(s)}{D(s)} = \frac{V_0}{V_1}$$

Filter synthesis: obtain

N & D , from specifications

Zeros & poles

Match / Zener

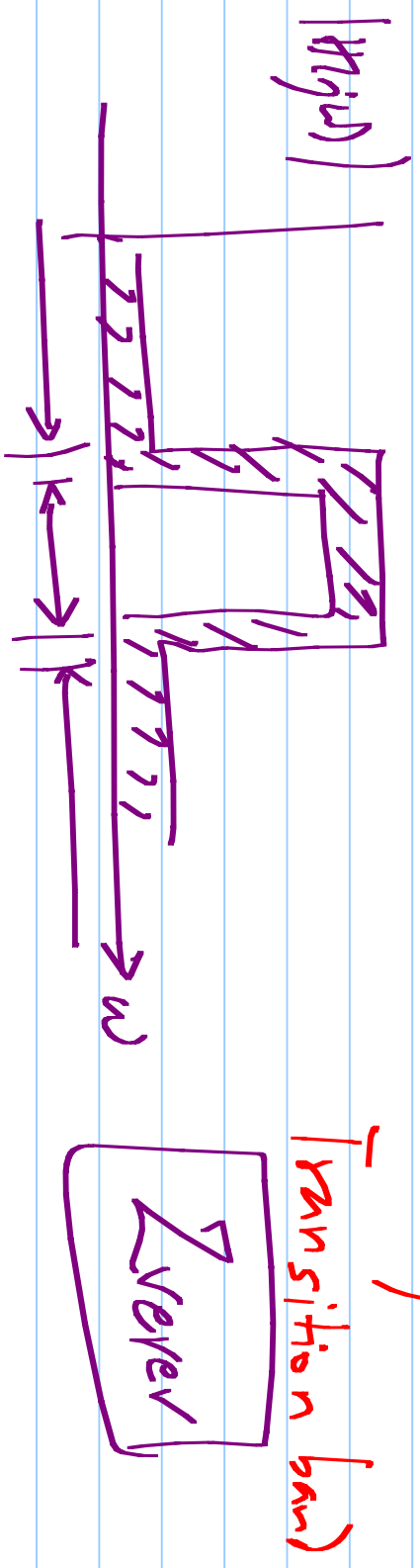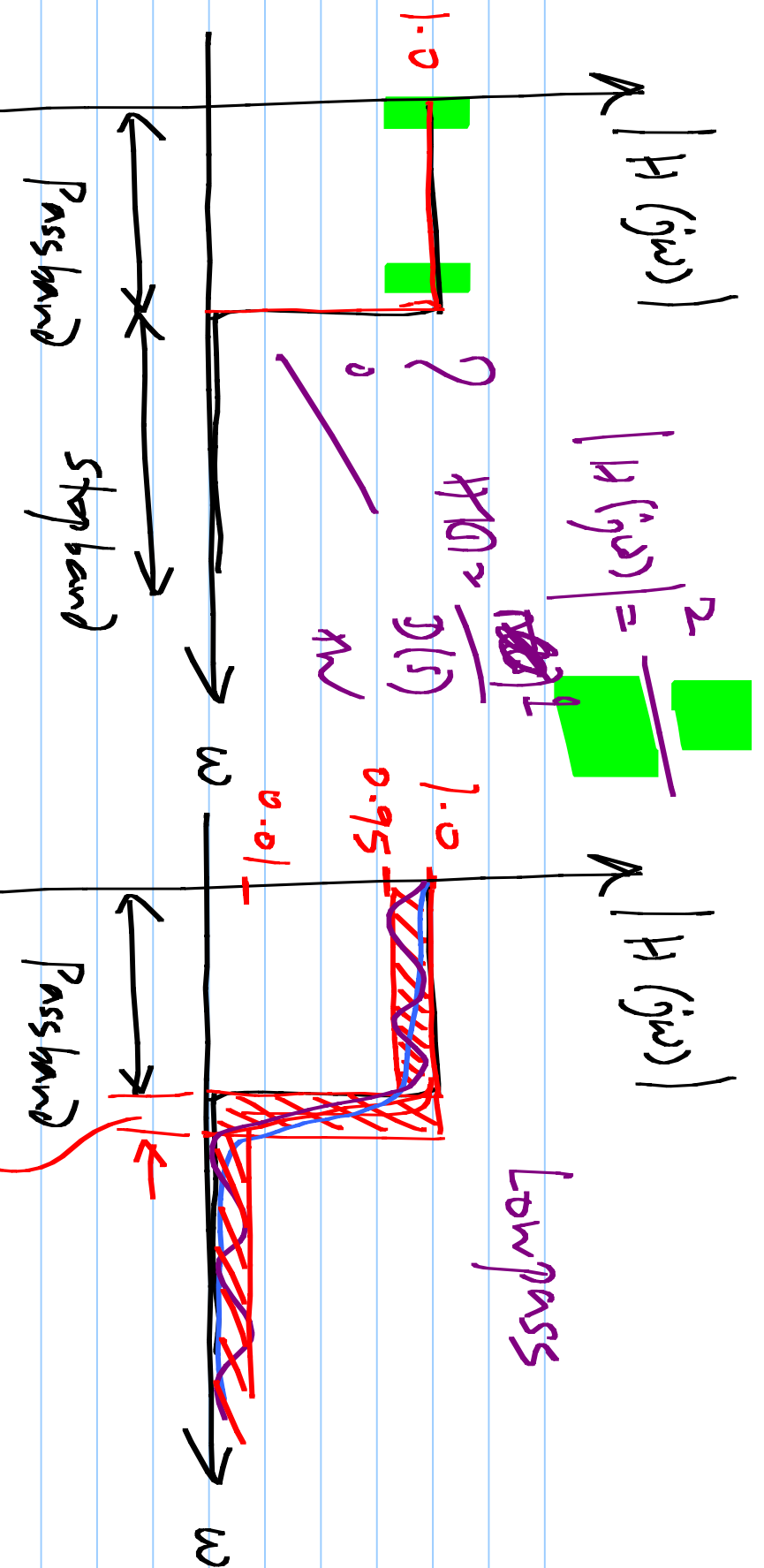

$$H(s) = \frac{N(s)}{D(s)} \quad \# \text{ zeros} \leq \# \text{ poles}$$

N^{th} order polynomial with real coefficients

Even N $\frac{N}{2}$ 2^{nd} order polynomials w/ real coeff.

odd N



$\left(\frac{N-1}{2}\right)$ — " —

+ 1 1^{st} order polynomial w/ real coeff

$$H(s) = \frac{1}{D(s)} = \frac{1}{D_1(s) \cdot D_2(s) \cdots D_k(s)} \cdot \frac{1}{D(s)}$$



Product of first & second order terms
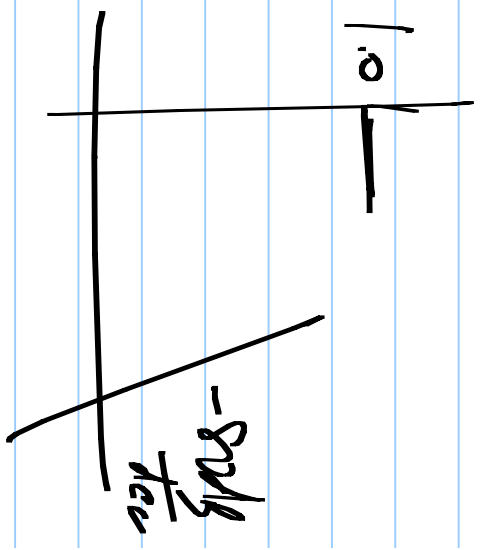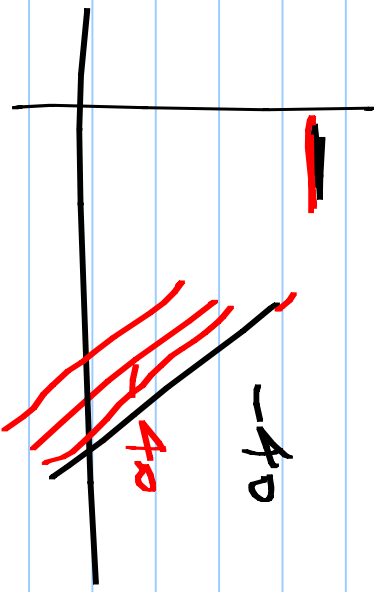
$$= \frac{1}{D_1(s)} \cdot \frac{1}{D_2(s)} \cdots \frac{1}{D_k(s)}$$




$$\frac{N_1}{D_1(s)} + \frac{N_2}{D_2(s)} + \dots$$

$$\frac{N_k}{D_k(s)}$$

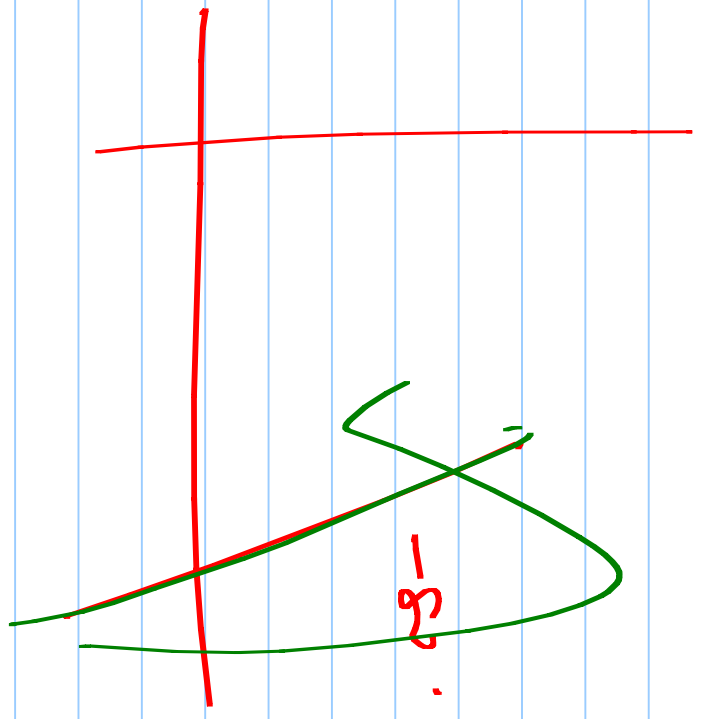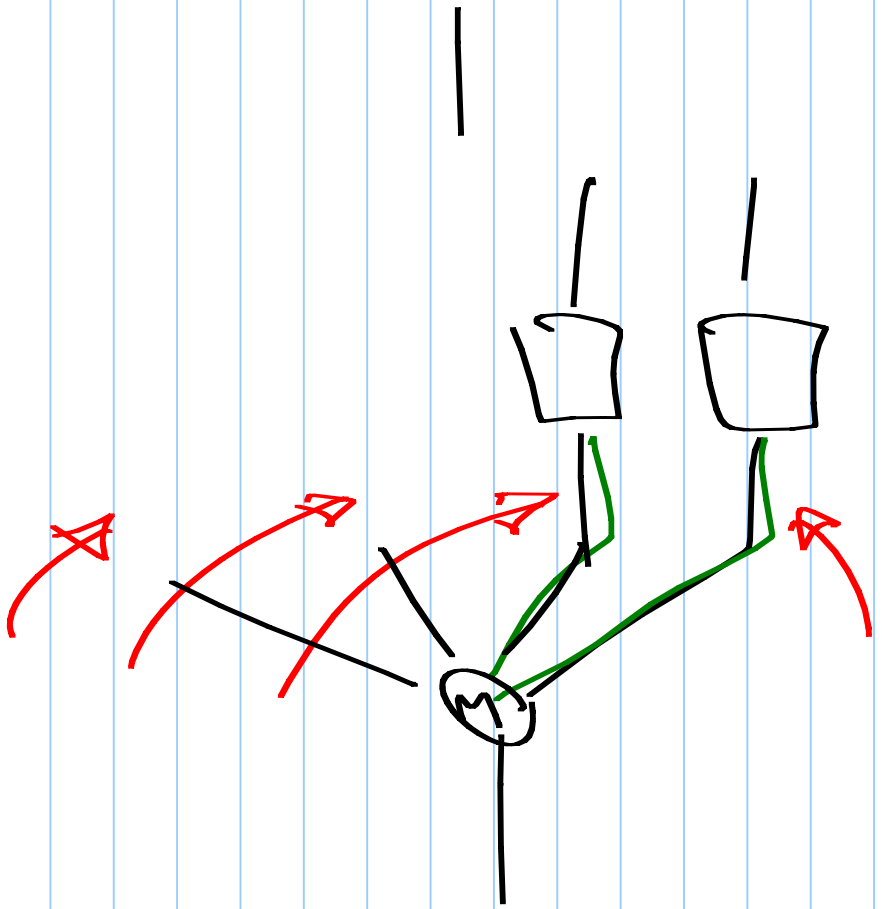

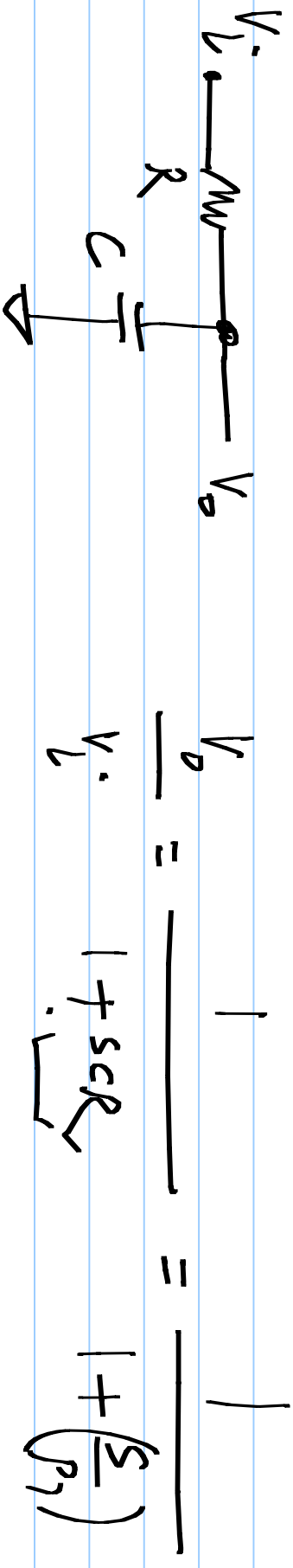
First & second order active filters (lowpass)



$$\frac{V_o}{V_i} = \frac{1}{1 + sCR} = \frac{1}{1 + \left(\frac{s}{f_p}\right)}$$

$$V_o \left(1 + \frac{s}{f_p}\right) = V_i \quad ; \quad (V_o - V_i) = -V_o \cdot \frac{s}{f_p}$$


$$-(V_o - V_i) = V_o$$

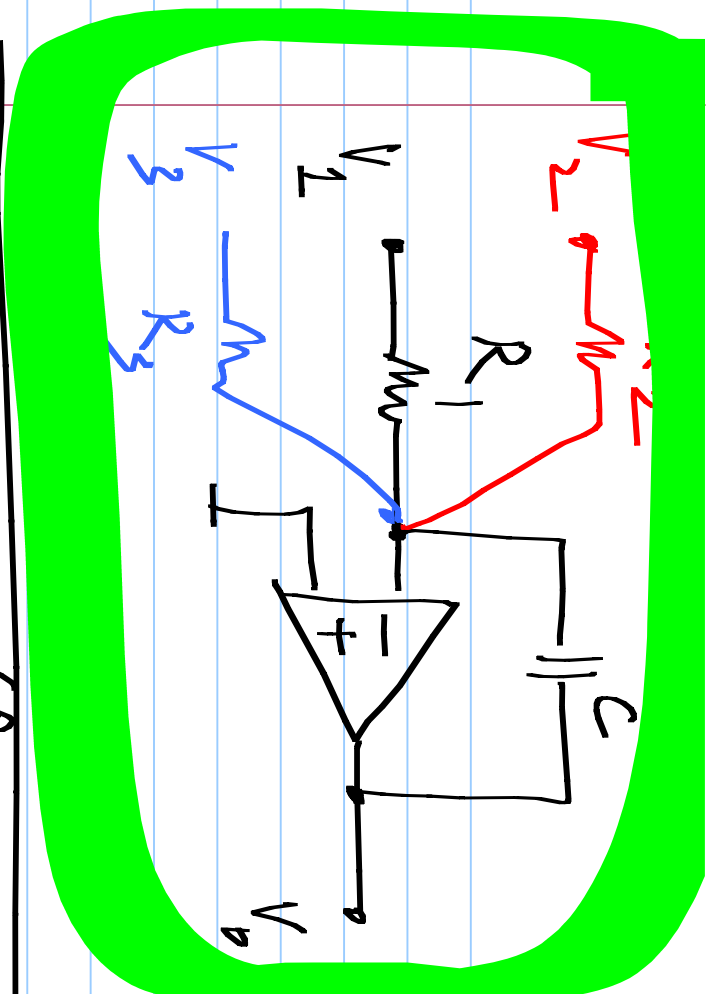


(Assuming dc -ve feedback around the integrator)


$$V_o = -\frac{1}{sCR_1} \cdot V_1 - \frac{1}{sCR_2} \cdot V_2 - \frac{1}{sCR_3} \cdot V_3$$
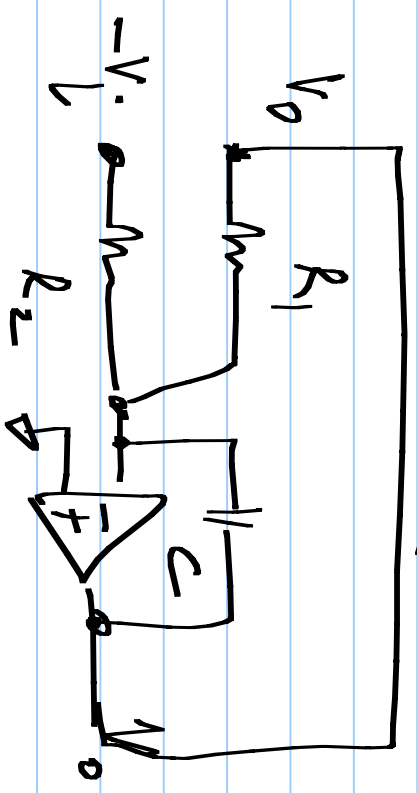
$$(V_o - V_L) \left(-\frac{R_1}{s} \right) = V_o$$



o/p of an integrator

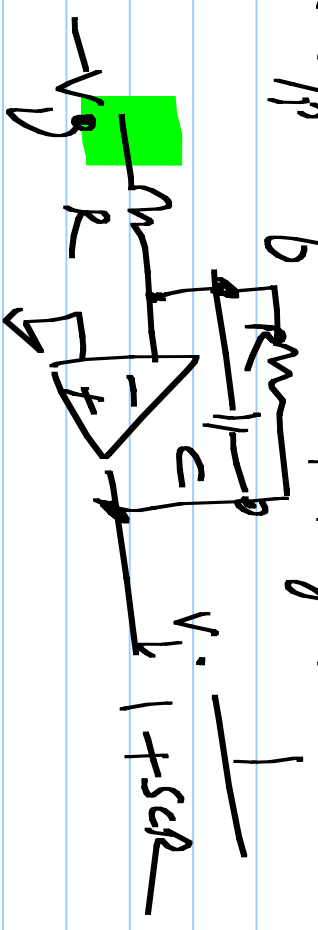

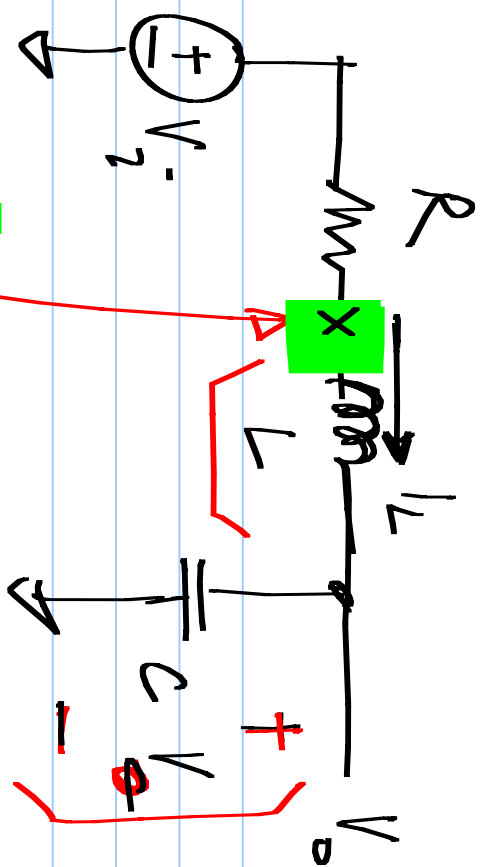

$$I_L = \frac{1}{sL}$$

$$V_0 = \frac{1}{sC}$$

$$V_L = I_L \cdot R$$

$$V_0 = V_C$$

$$(V_L - I_L \cdot R - V_0)$$

$$\cdot \frac{R}{sL} =$$

$$I_L \cdot R$$

$$R \cdot I_L$$

$$\frac{1}{sCR} =$$

$$V_0$$

$$(-V_2 + \hat{V}_L + V_0) \left(\frac{R}{sL} \right) = \hat{V}_L$$

$$(-\hat{V}_L) \left(\frac{1}{sCR} \right) = V_0$$

