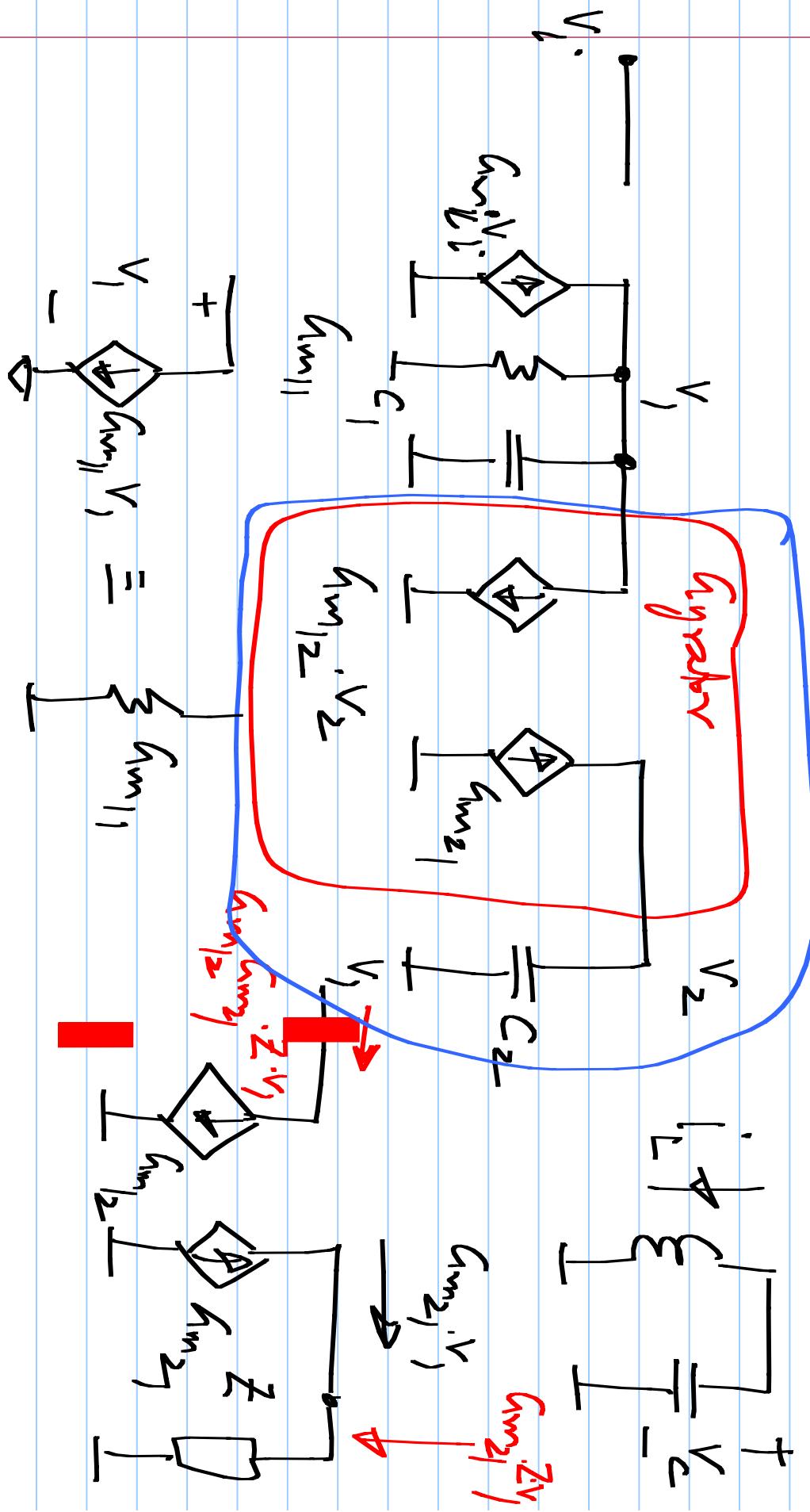



EE 2019

$G_m - C$ filter

4/4/2017



Sallen-Key filter

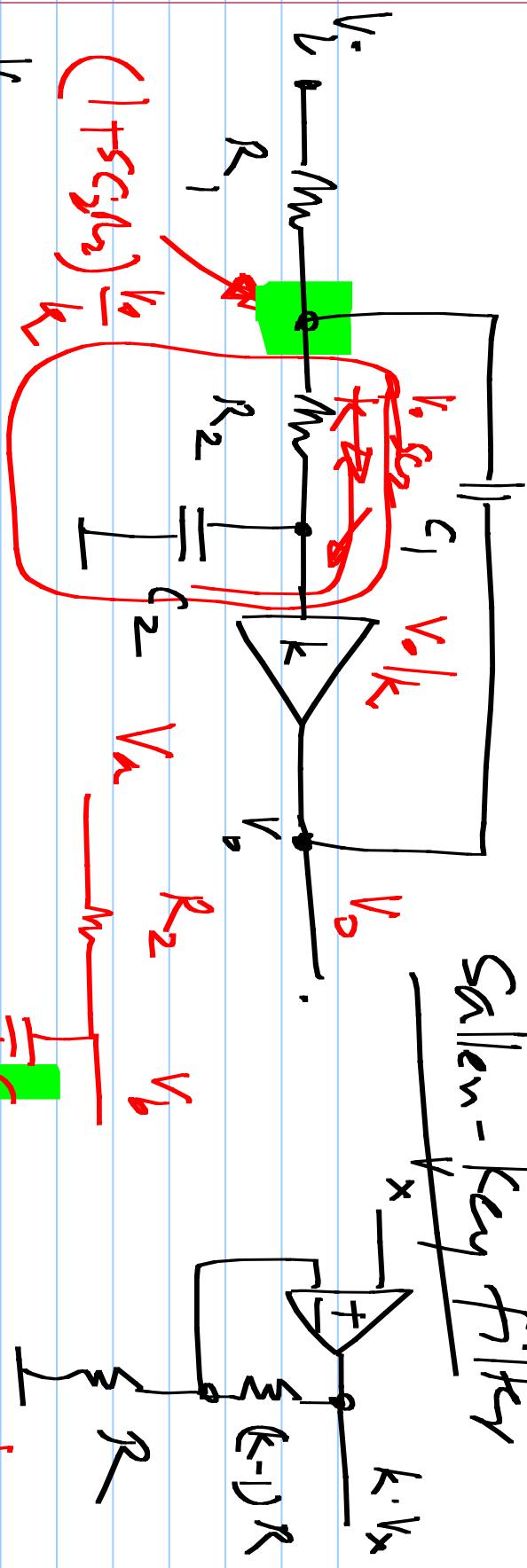

$$\frac{V_o}{V_1} = \frac{(1 + sC_1R_2) \frac{V_0}{k}}{1 + sC_2R}$$

$$\frac{V_o}{R_1} = \frac{V_1 - (1 + sC_2R_2) \frac{V_0}{k}}{(1 + sC_1R_2) \frac{V_0}{k}} = \frac{(1 + sC_2R_2) \frac{V_0}{k} - V_0}{(1 + sC_1R_2) \frac{V_0}{k}} = \frac{1 + sC_2R_2}{1 + sC_1R_2}$$

k

$$\frac{V_o}{V_i} = \frac{s^2 c_1 c_2 R_1 R_2 + s(R_1 c_2 + R_2 c_1(1-k))}{s^2 c_1 c_2 R_1 R_2 + 1}$$

$$R_1 c_1 = R_2 c_2$$


k

$$R_1 = R_2 = R$$

$$s^2 c^2 R^2 + s c R (3 - k) + 1$$

$$c_1 = c_2 = c$$
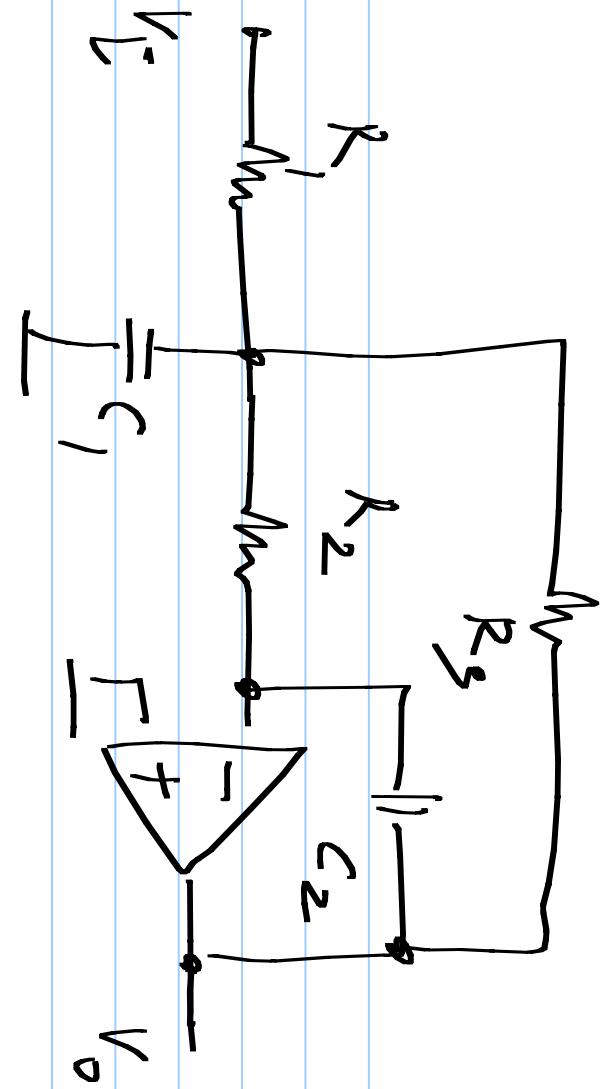
$$\frac{s^2 / \omega_n^2 + s}{\omega_n + 1}$$




Rance filter

$$\frac{V_o}{V_s} = \frac{1}{sC + \frac{1}{R}}$$

$$\omega_m \ll \frac{1}{CR}$$

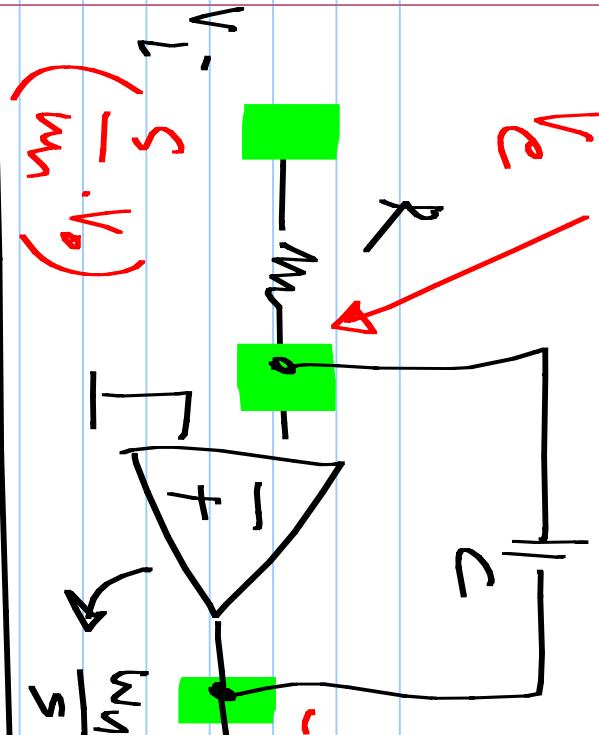
$$\frac{V_o}{V_s} = \frac{s}{sC + \frac{1}{R}} = \frac{1}{\frac{1}{R} + sC}$$





$$\frac{V_o}{V_s}$$

ideal opamp

$$\frac{V_o}{V_s} = \frac{1}{sCR}$$

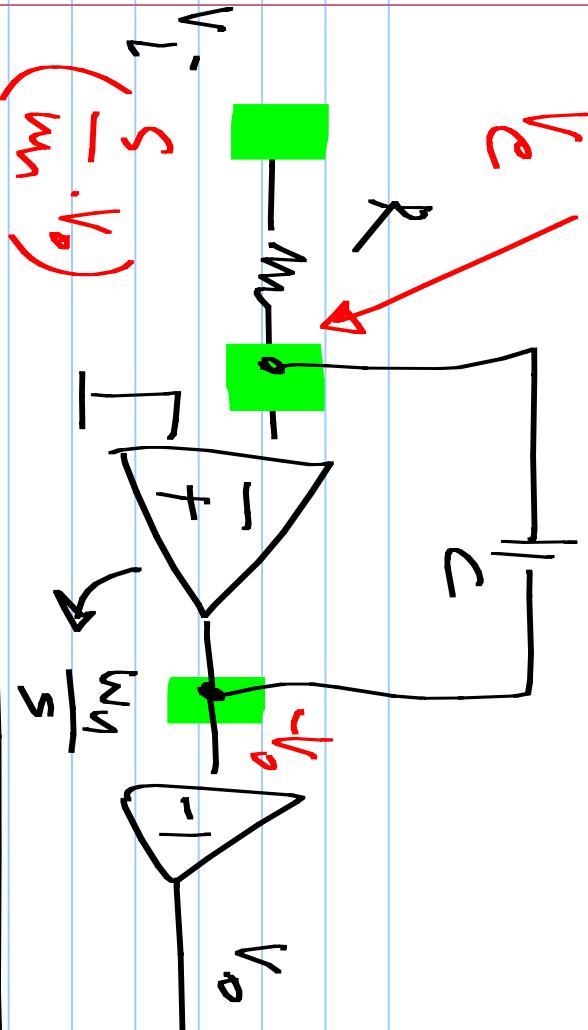

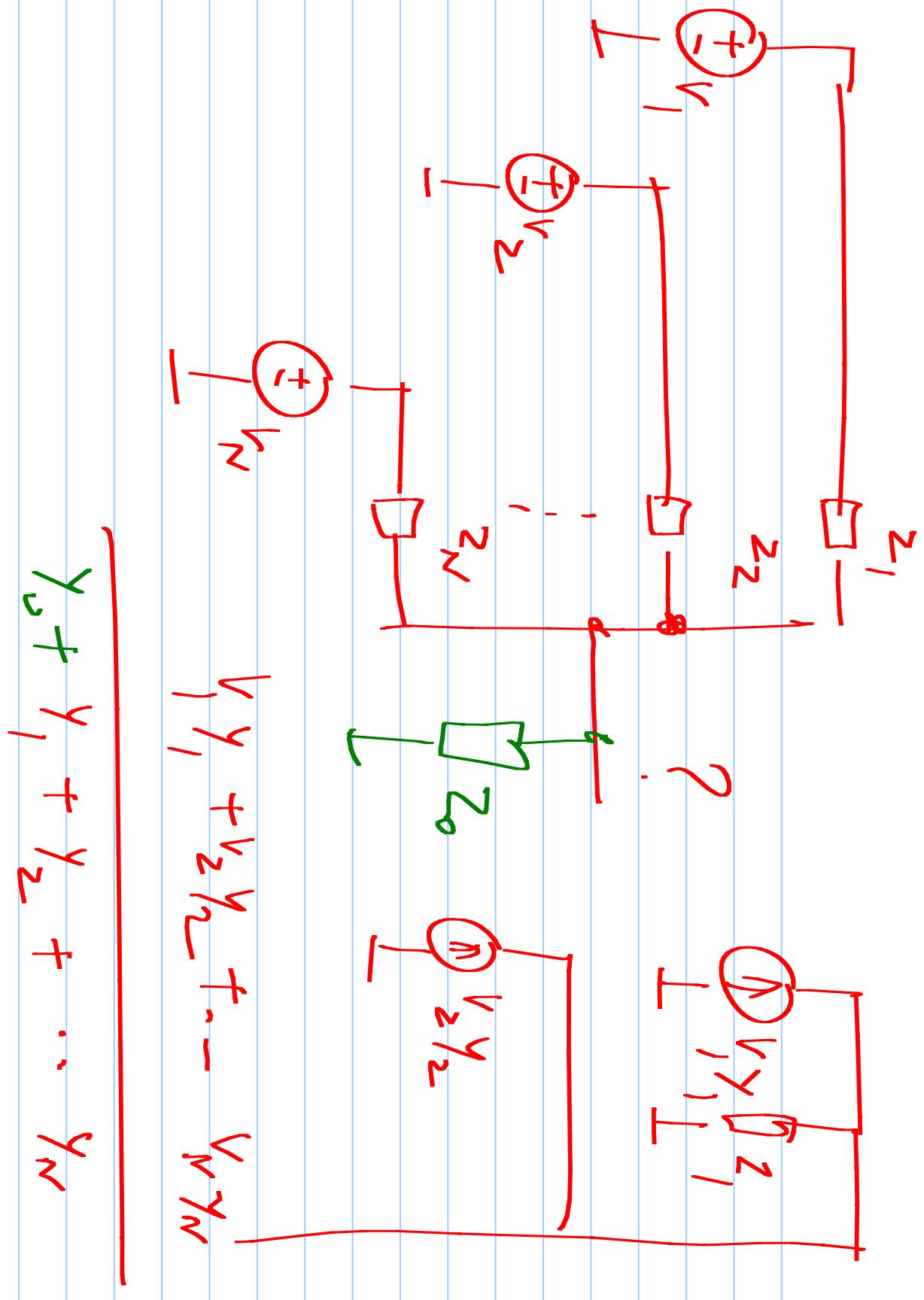

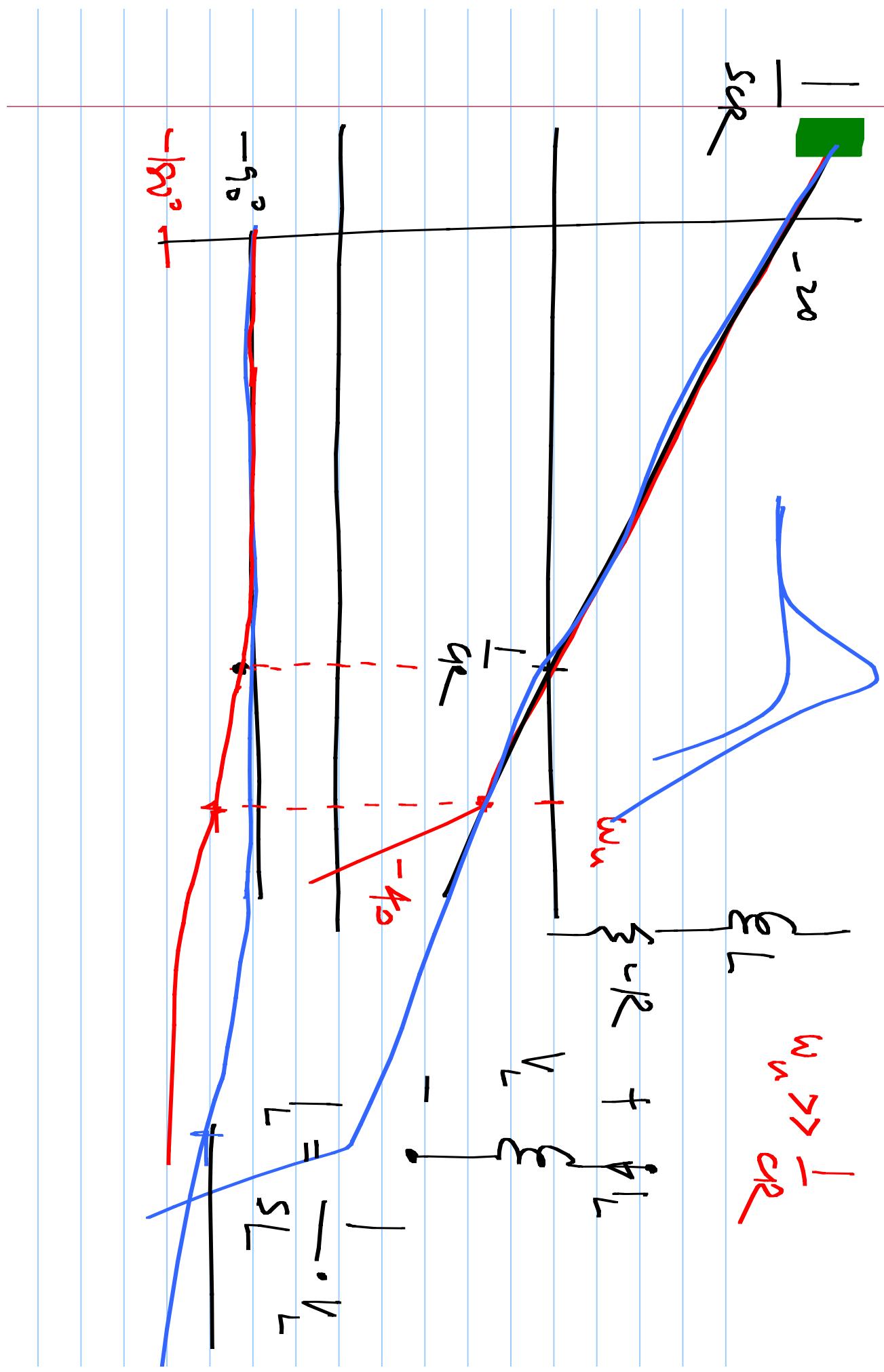

$$R_e(Z(s)) \leq 0$$

$$R_e(Z(s)) = \frac{1}{2} \rho_e (V \cdot A \cdot J \cdot V)^*$$

$$R_e(Z(s)) < 0$$

$$\pi^2 \leq \rho \leq \pi^2$$

$$Z(s)$$

$$J = V \cdot R'_{LC}$$