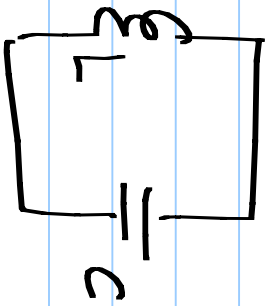



EE 2019

ideal, lossless LC



6/4/2017


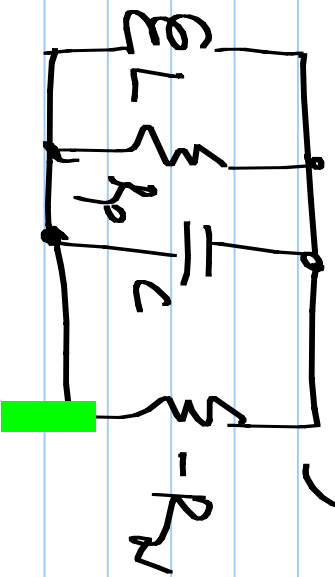
Lossy LC compensated by linear -ve resistance



Uncertain

constant amplitude oscillations

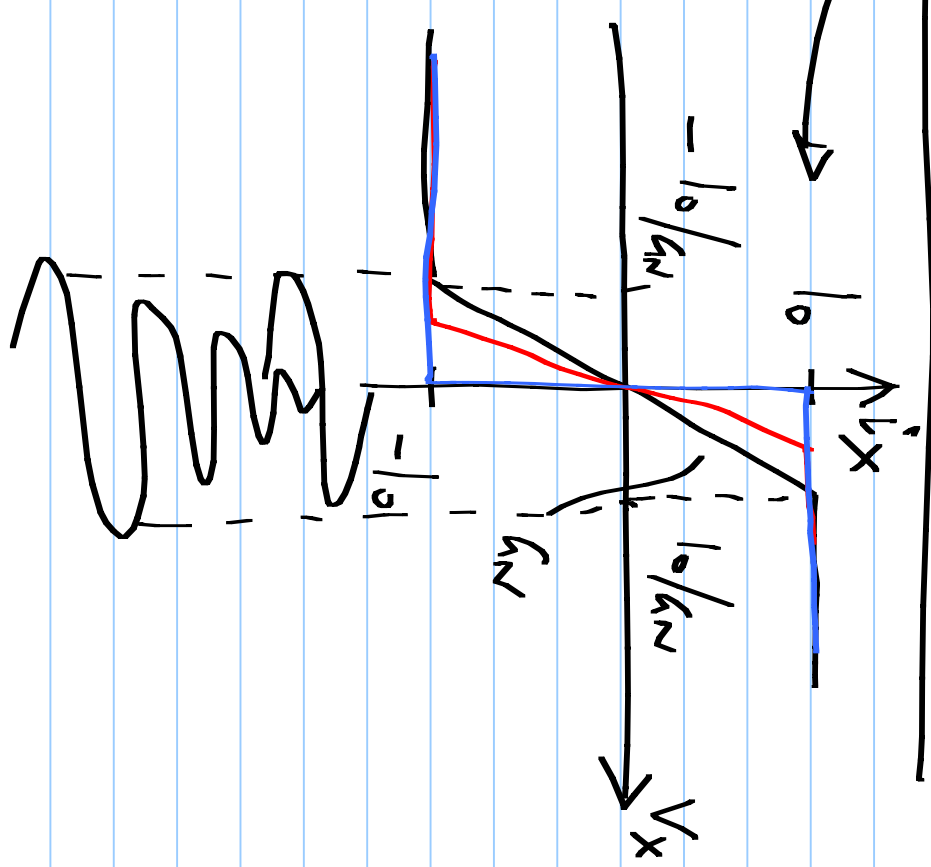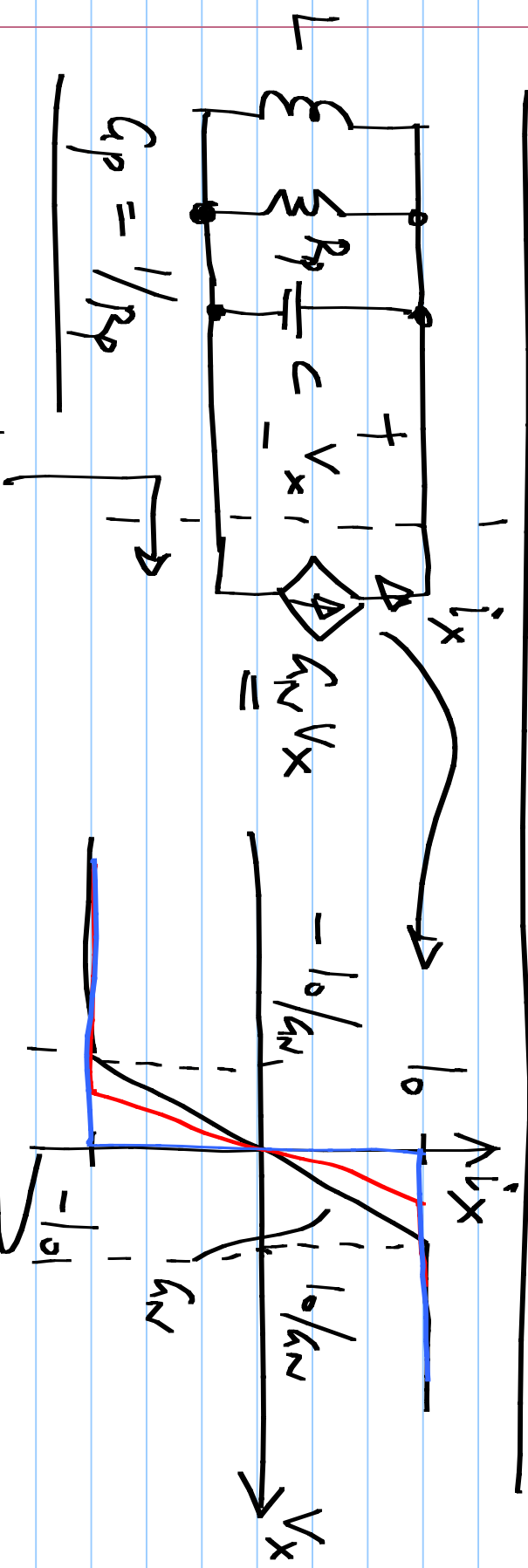
Lossy LC, compensated by -ve conductance w/
current saturation




$g_m > g_p$

$-g_m$

$g_m = 2g_p$

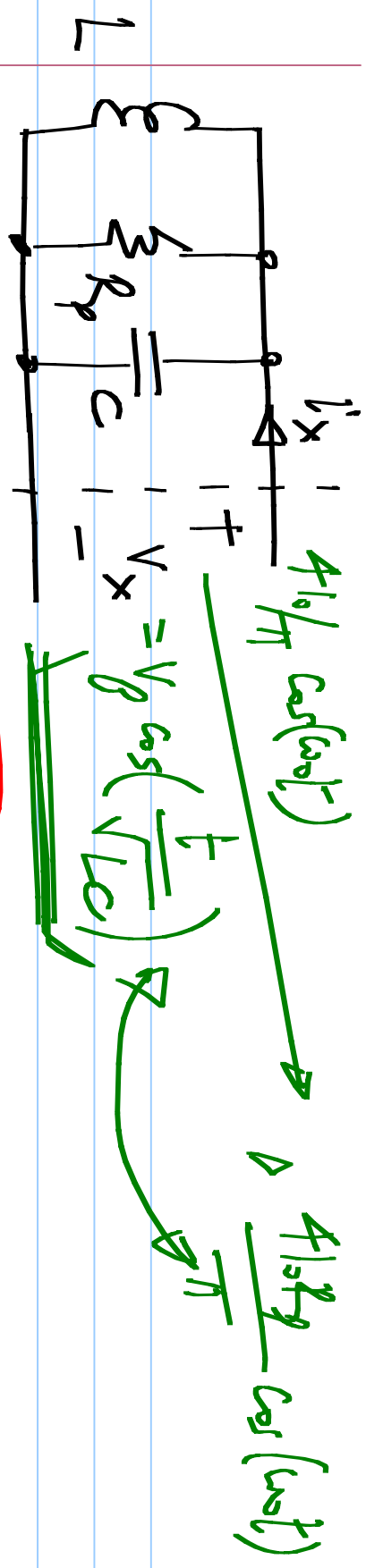


$$\left| \frac{V_x}{I_x} \right| = R_p$$

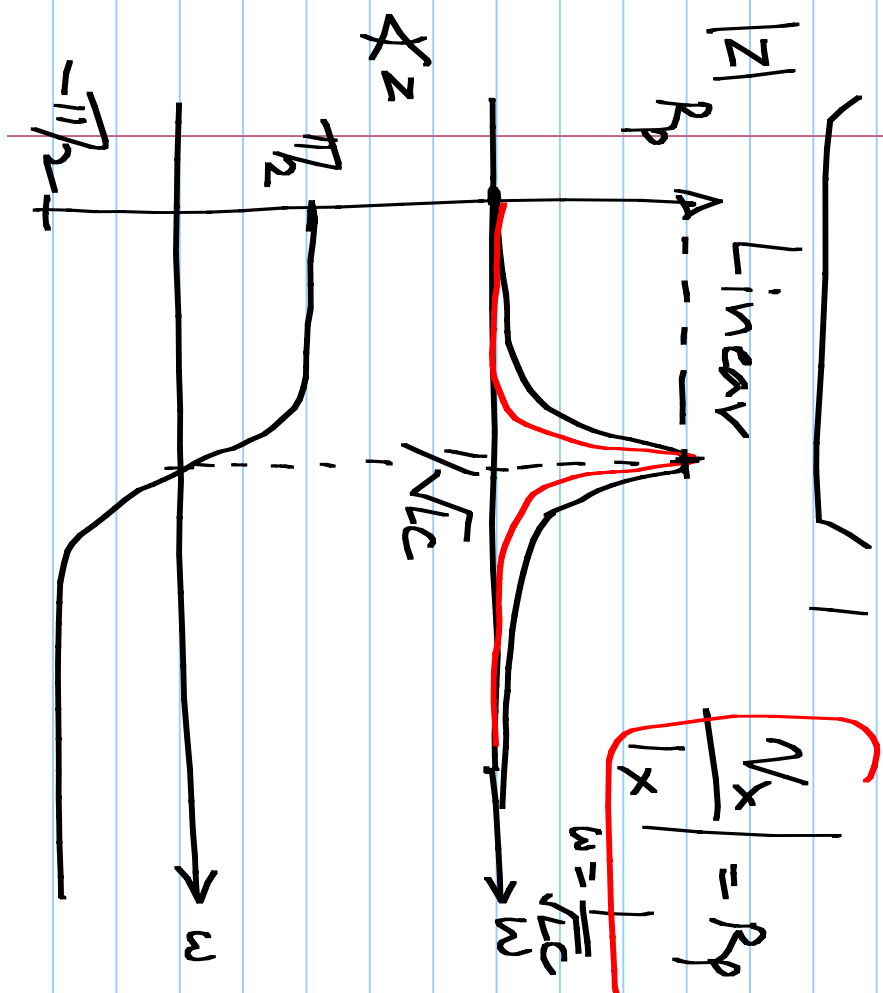


$$\frac{V_x}{I_x} = R_p \frac{sL/R_p}{sL/R_p + \frac{sL}{R_p} + s^2LC}$$

$$Q = R_p \sqrt{\frac{C}{L}}$$

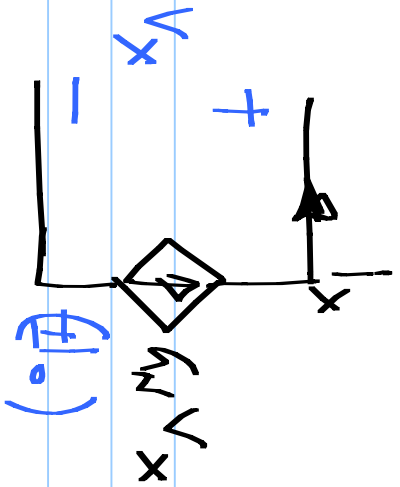



$$\frac{4V_0}{T} \cdot \cos(\omega t)$$

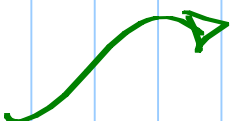

$$i(t) = \sum_{k=1}^{\infty} (-1)^k \left(\frac{4V_0}{kT} \right) \cos(k\omega t)$$
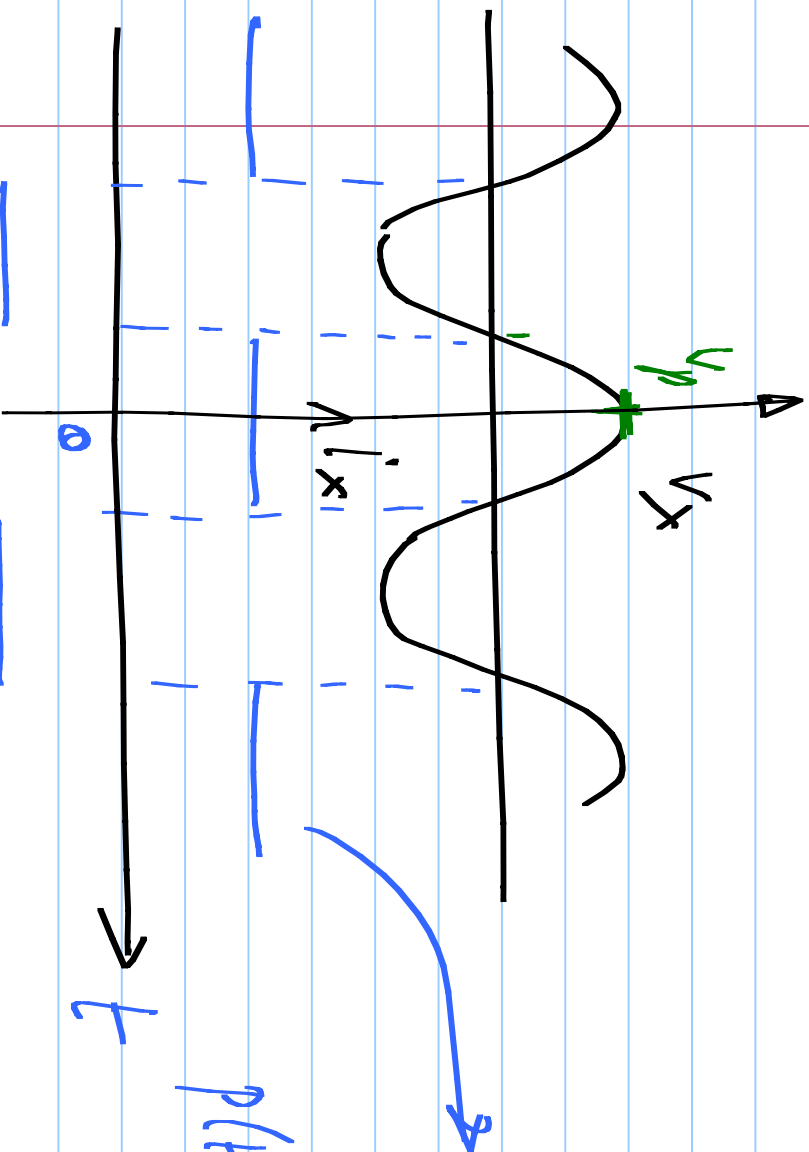
$$p(t) = \cancel{V_0} + \sum_{k=1}^{\infty} (-1)^k \left(\frac{4V_0}{kT} \right) \cos(k\omega t)$$



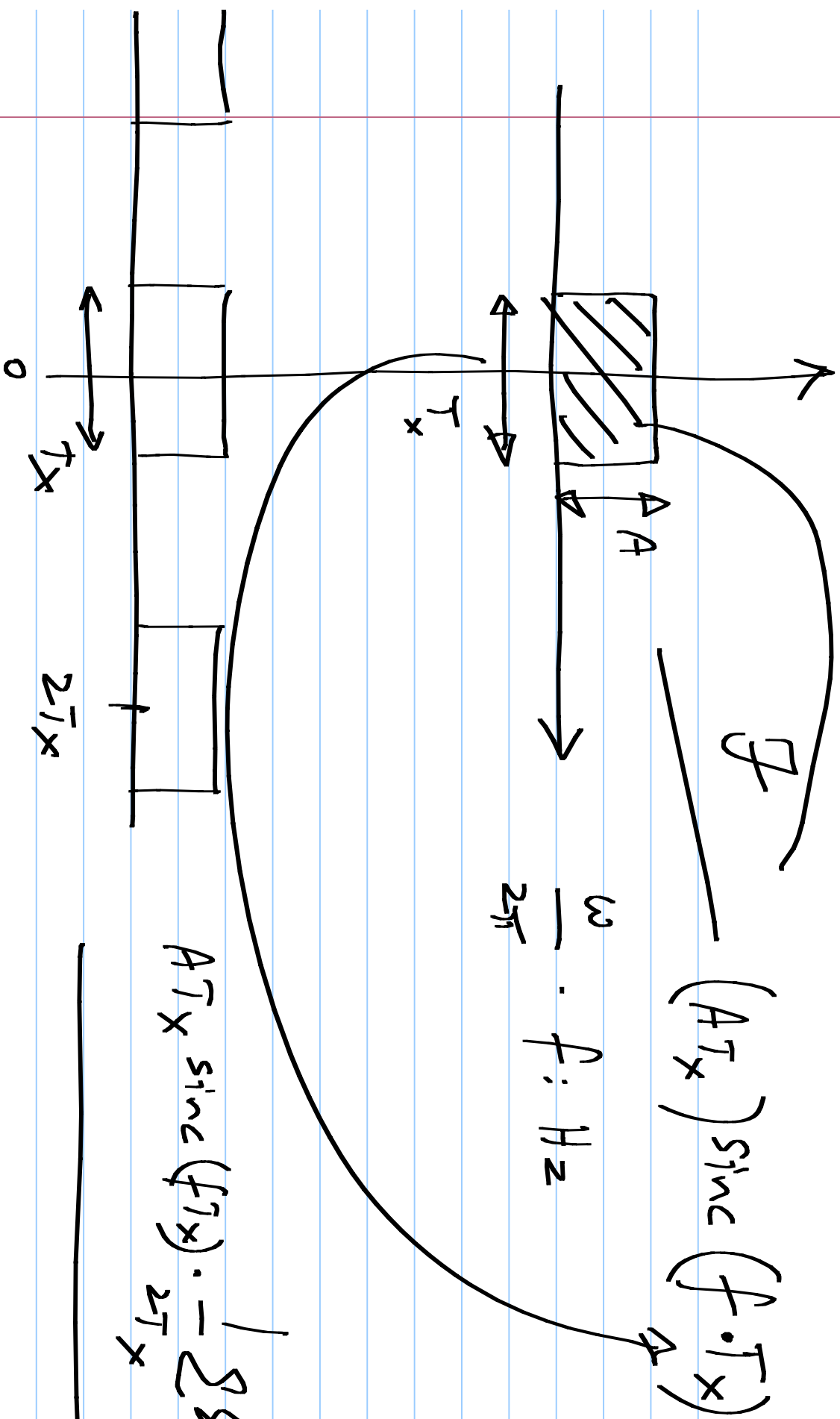


$$(A T_x) \text{sinc}(f \cdot T_x)$$

$$\omega = \frac{\omega}{2\pi} \cdot f; \text{ Hz}$$

$$A T_x \text{sinc}(f T_x) \cdot \frac{1}{2 T_x} \int_{-T_x}^{T_x} \text{rect}(f - \frac{\omega}{2\pi}) d\omega$$


$$f_c = 0$$

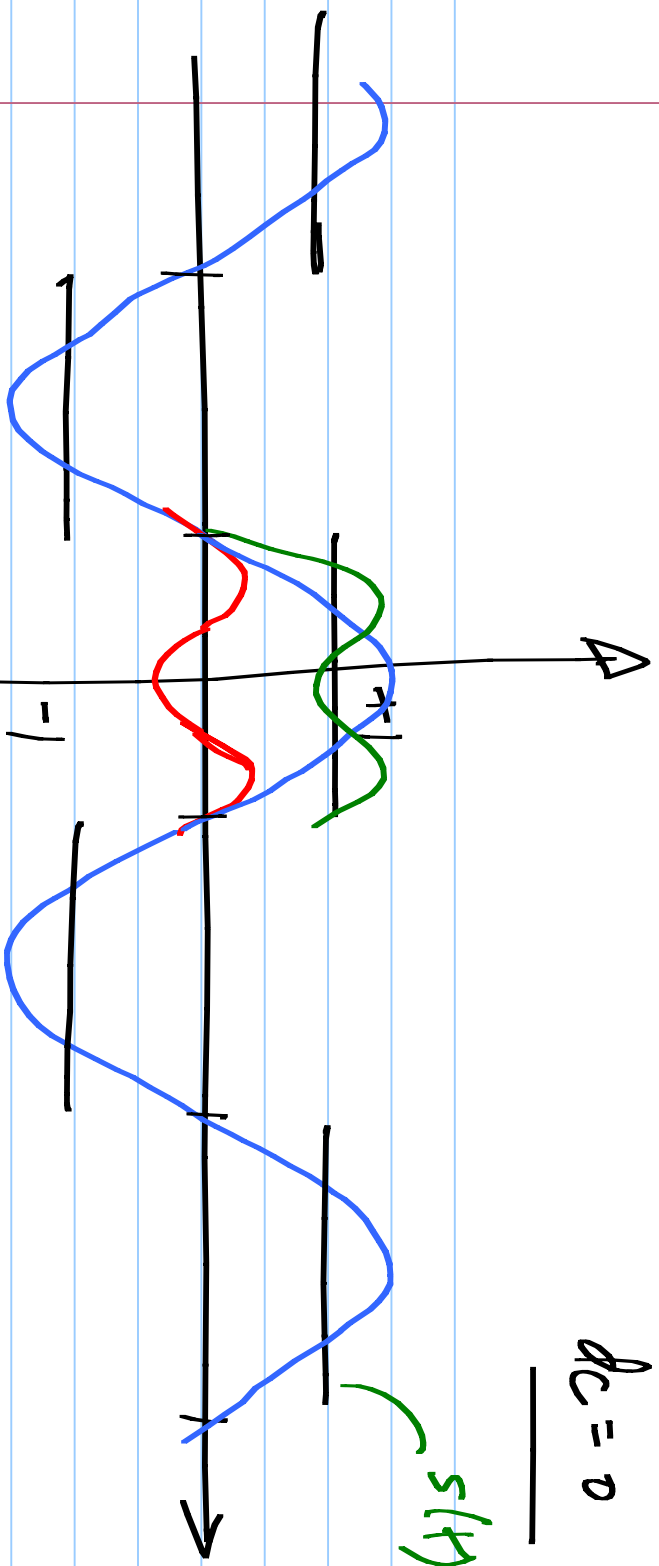

$$\frac{4}{\pi}, \frac{4}{3\pi}$$

$$s(t) = \sum_{k=0}^{\infty} (-1)^k \frac{4}{(2k+1)\pi} \cdot \cos((2k+1)\omega_0 t)$$
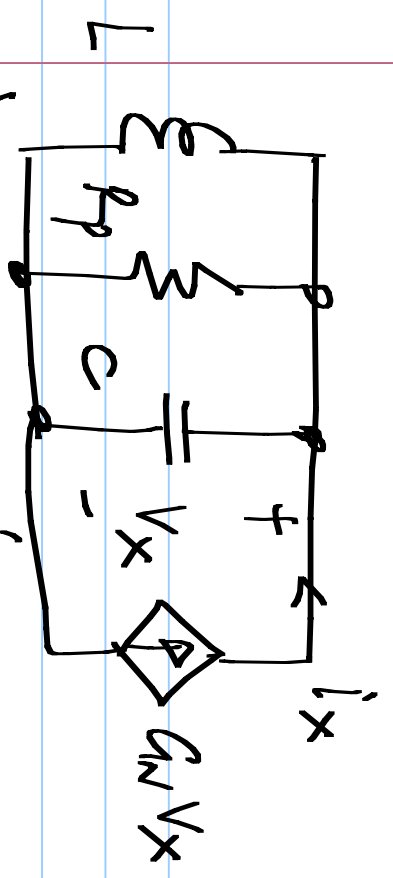
$$\sum_{k: \text{odd}} \frac{4}{k\pi} \cos(k\omega_0 t) \cdot (-1)^{\frac{k-1}{2}}$$




$$V_x = \left[\frac{4I_0 R_p}{\pi} \right] \cos(\omega t)$$

Amplitude :

$$\frac{4I_0 R_p}{\pi}$$

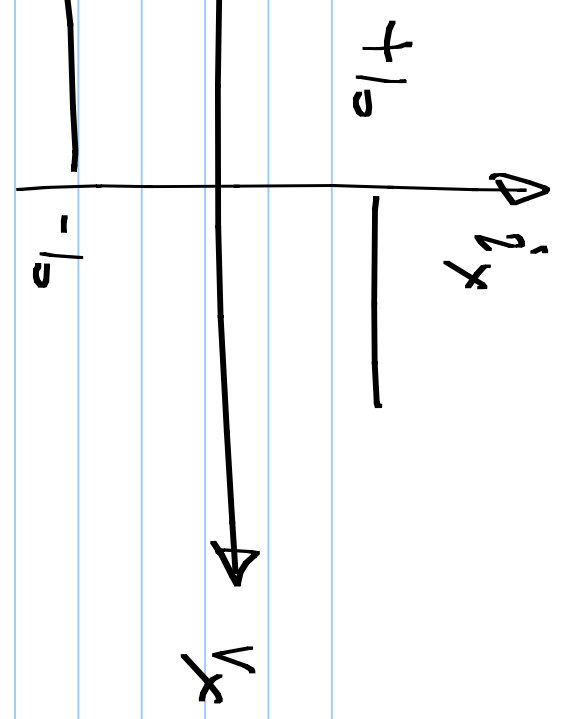High $Q \Rightarrow$ only fundamental voltage exists across the tank



$$G_N \gg G_p$$

High: Tank voltage is of the form

$$V_p \cos\left(\frac{t}{\sqrt{LC}}\right)$$

Current from I_{in} :

$$\sum_k \left(\frac{4I_0}{\pi} \right) (-1)^{k-1/2} \cos\left(\frac{kt}{\sqrt{LC}}\right)$$

fund. comp.

$$\frac{4I_0}{\pi} \cos\left(\frac{t}{\sqrt{LC}}\right)$$

③ $\frac{1}{\sqrt{LC}} \frac{V}{I} \Big|_{I_{tank}} = R_p$

$$\frac{4I_0}{\pi} \cdot R_p = V_p$$
