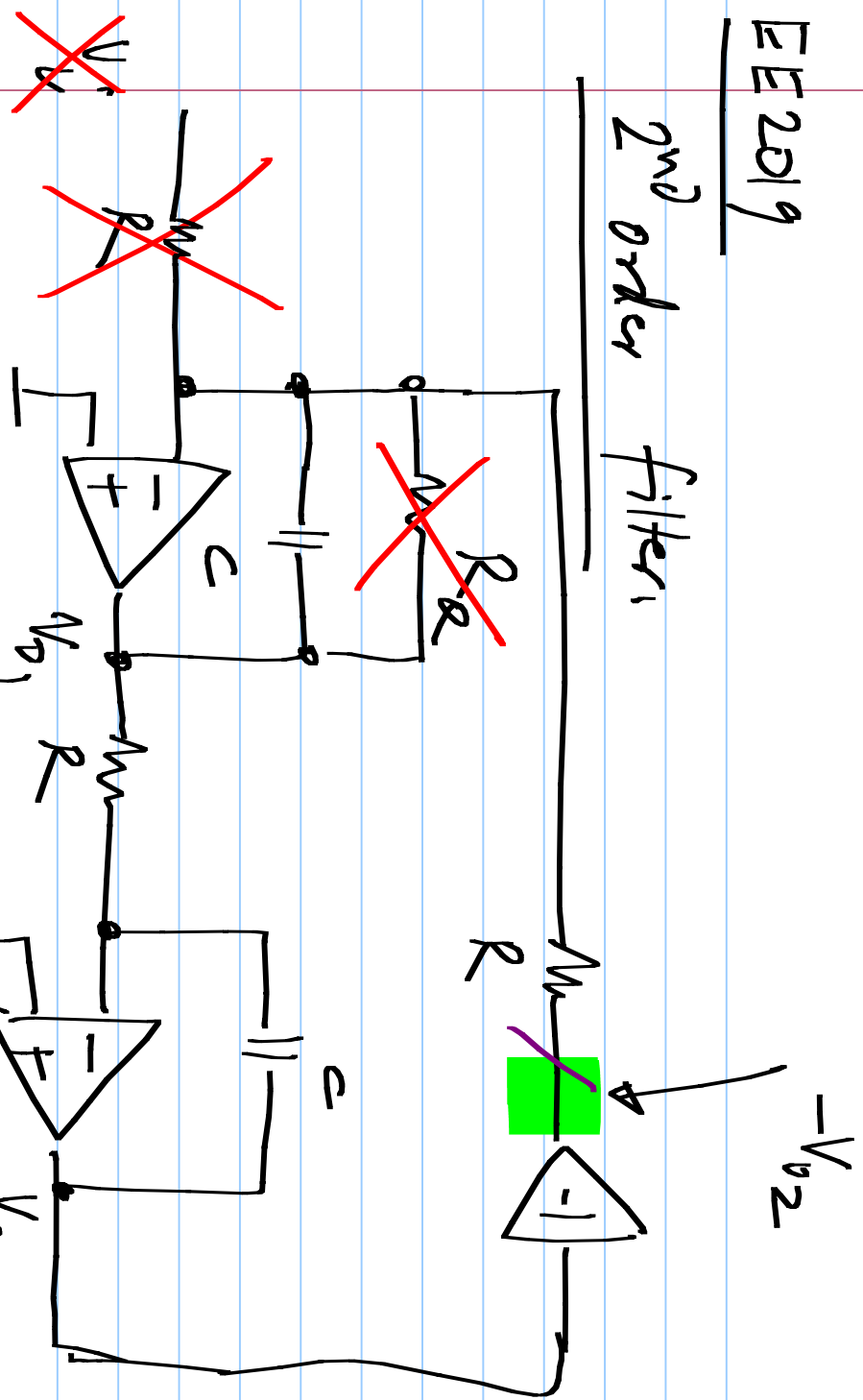


EE 2019

2nd order filter



7/4/2017

$$Q = \frac{K_R}{R}$$


Oscillator

$$R_R = \infty$$

No input


$$V_{o1} = \frac{1}{sCR} \cdot V_{o2}$$



$$V_{o2} = \frac{1}{sCR} \cdot V_{o1}$$

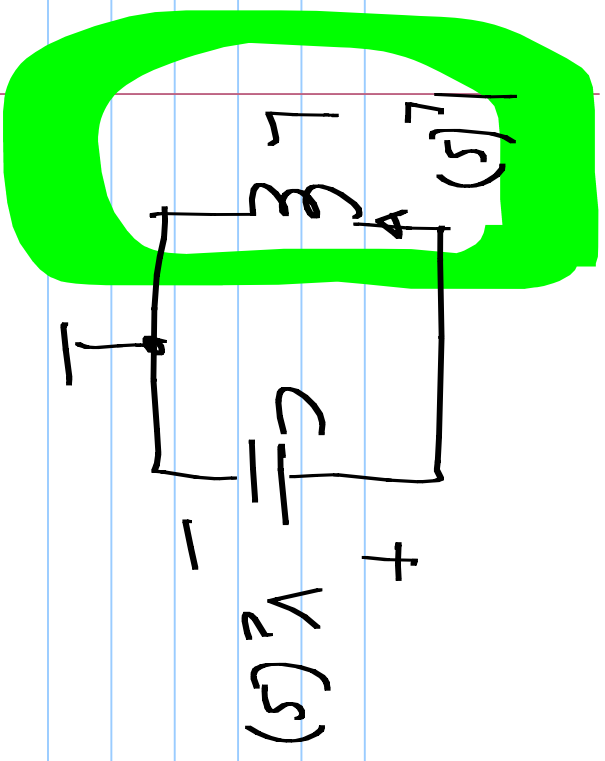

$$I_L(s) = \frac{1}{sL} \cdot V_c(s)$$






$$V_c(s) = -\frac{1}{sC} \cdot I_L(s)$$

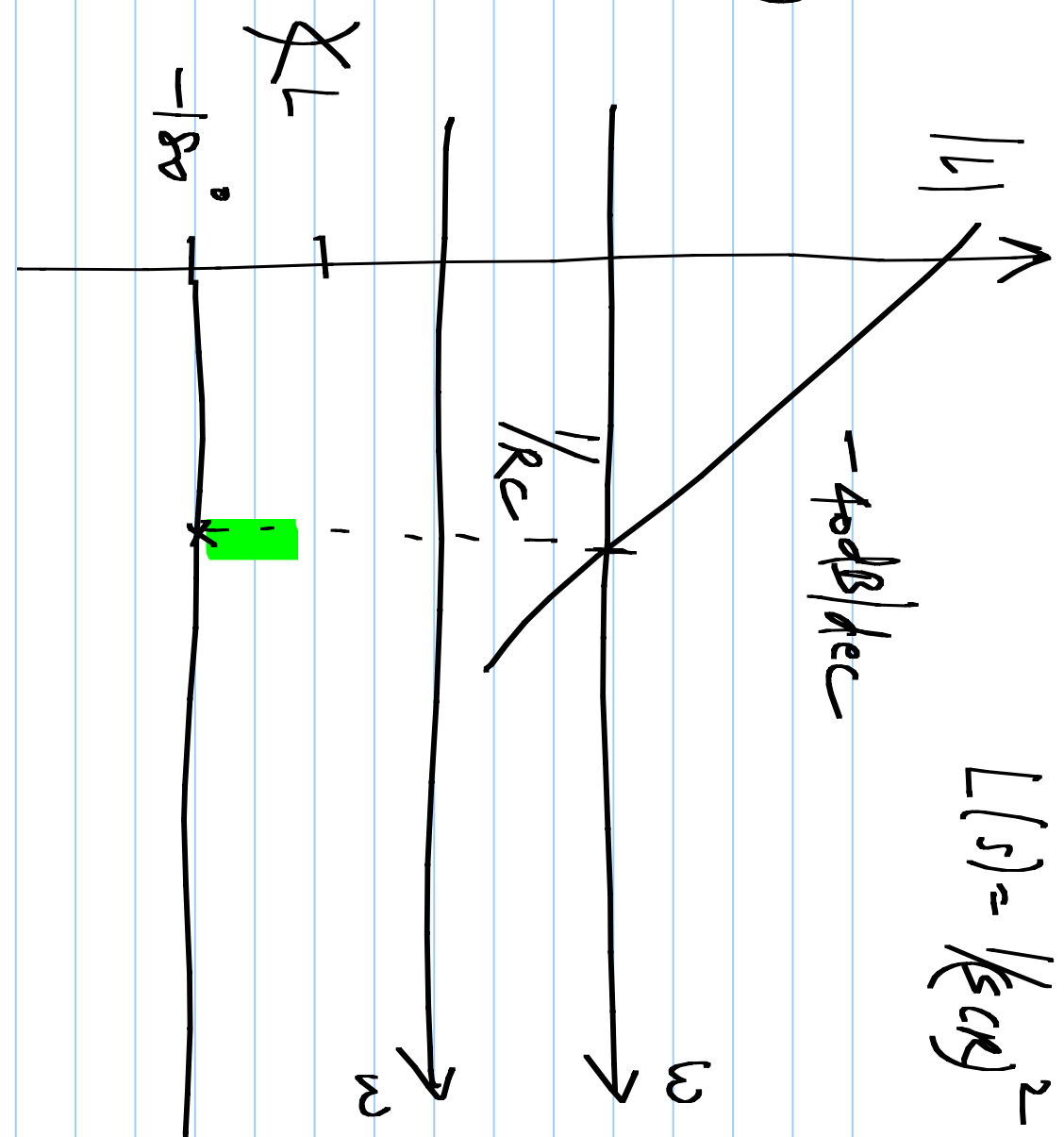


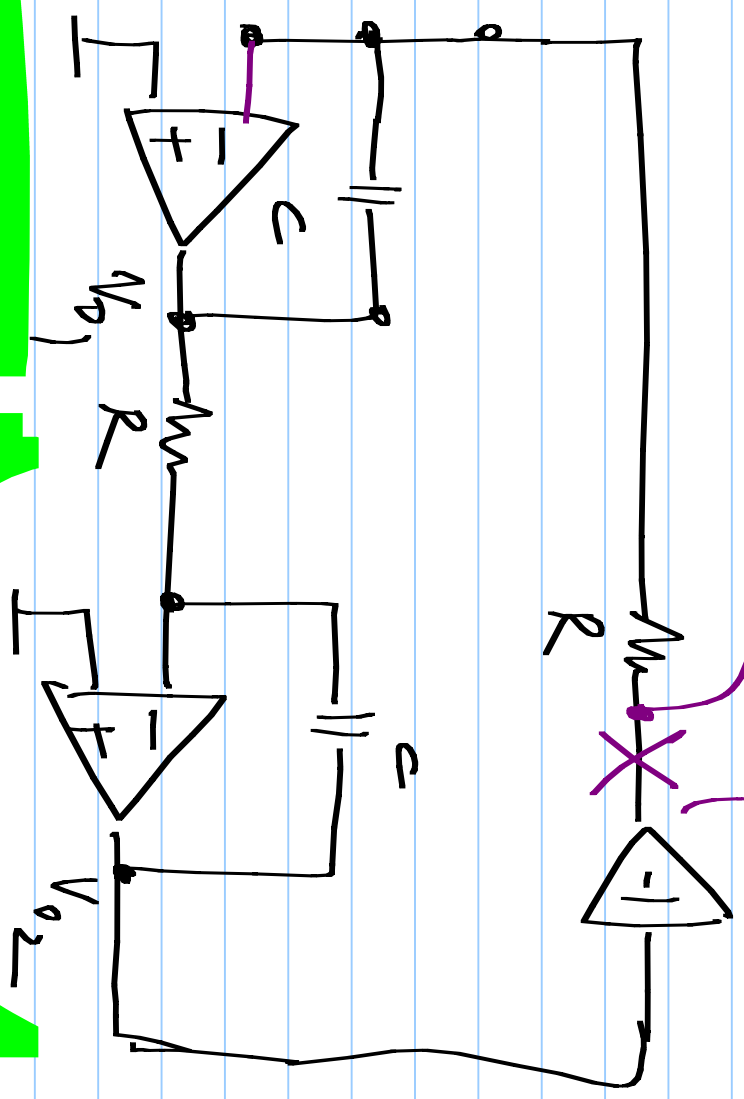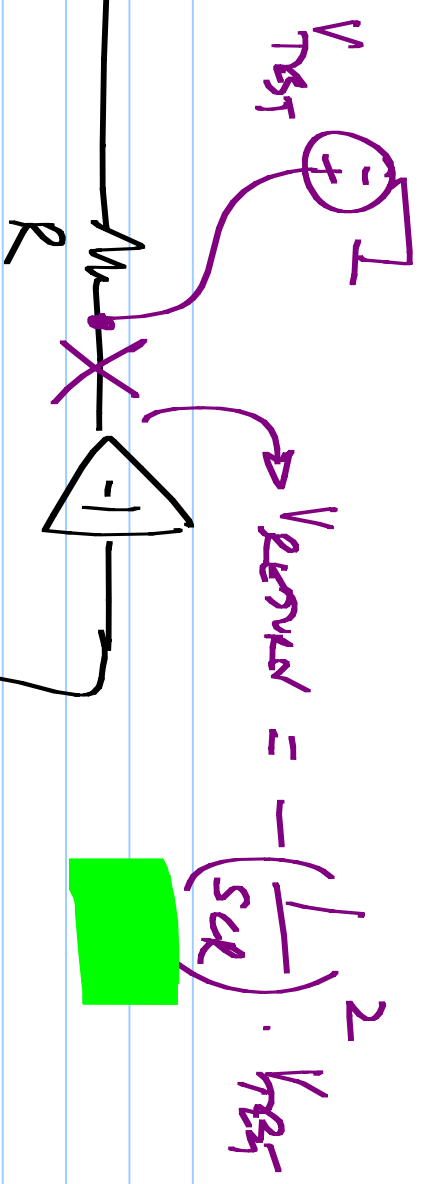


$$V_{01} = \frac{1}{sCR} \cdot V_{02}$$

$$V_{02} = \frac{1}{sCR} \cdot V_{01}$$

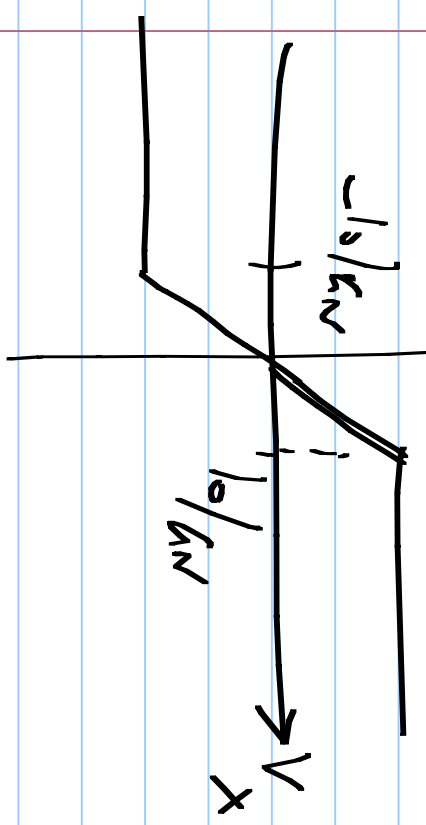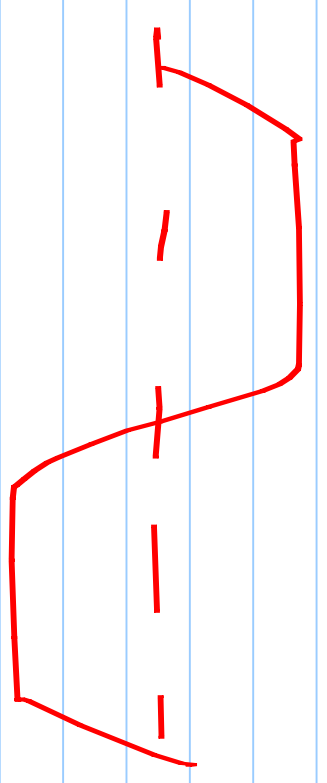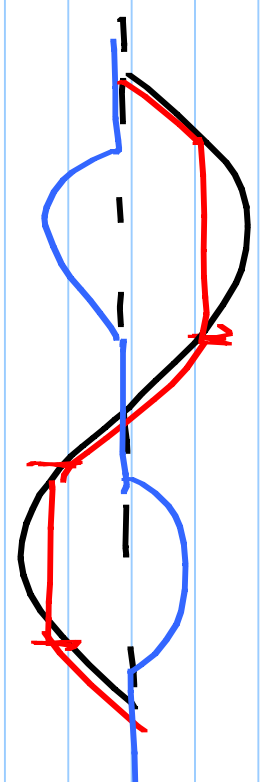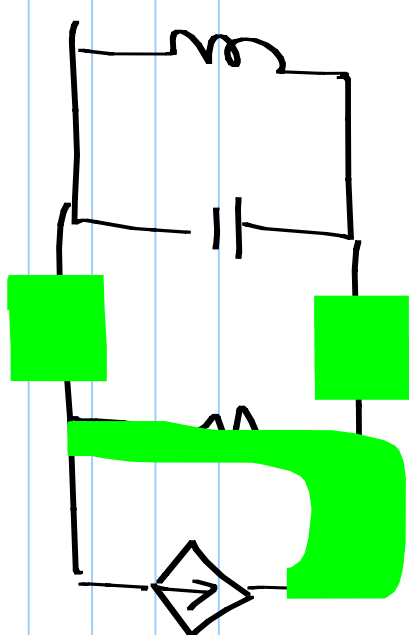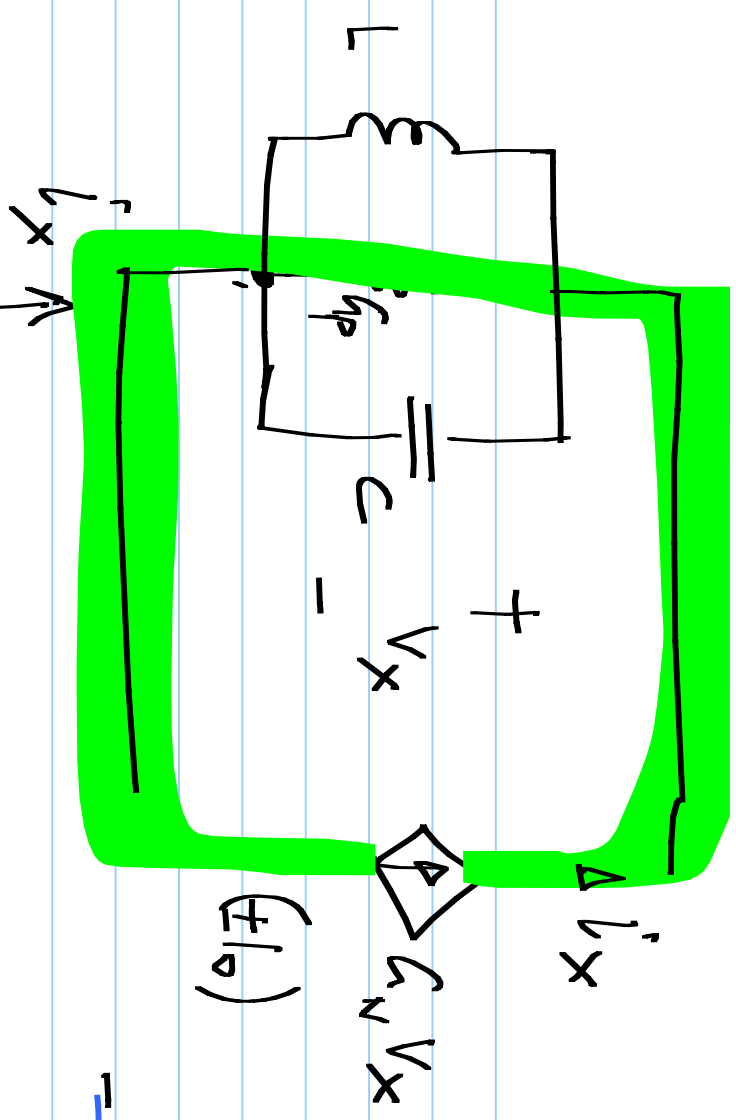

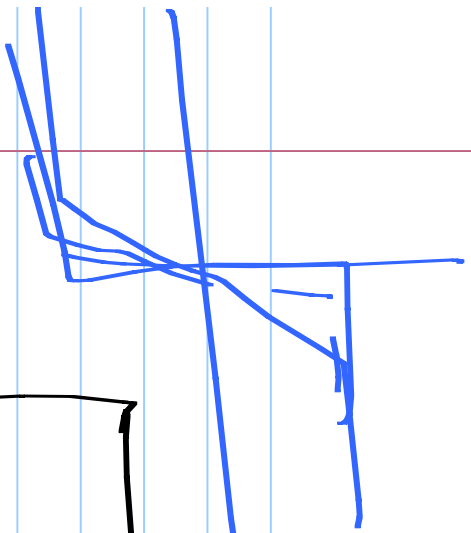

+ - +

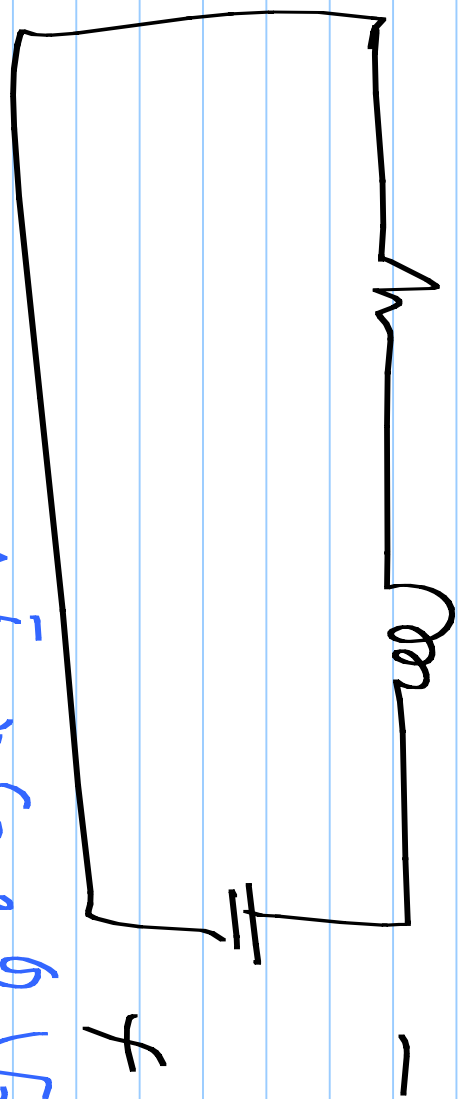



Force Comp of (F_x)


$4/11 l_0$

$(+/-)$

$u_N < u_P$

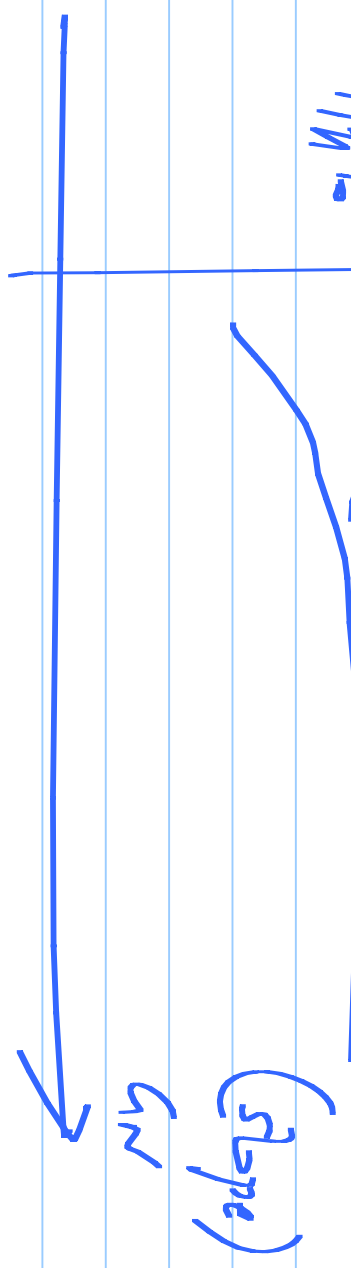

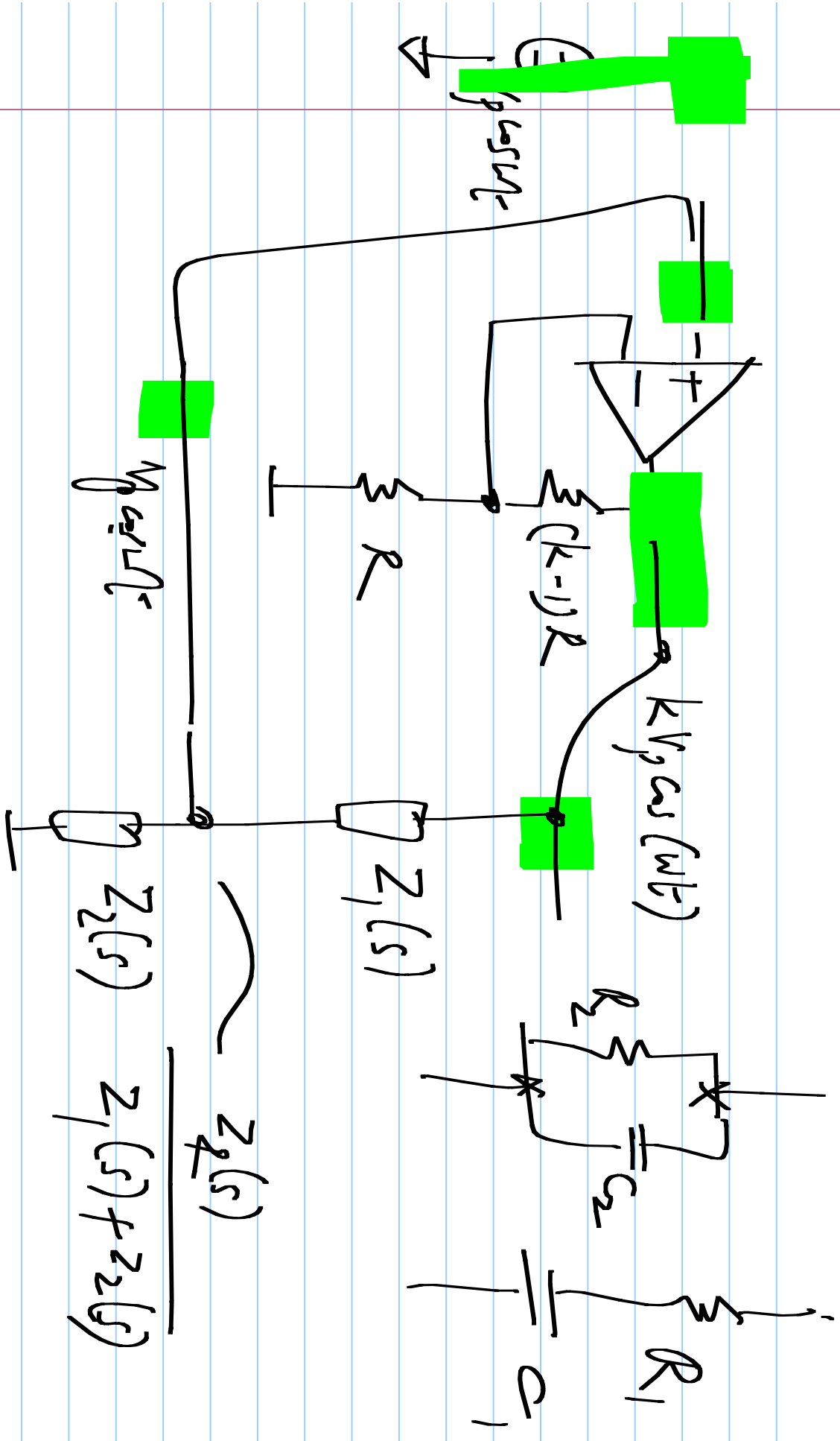


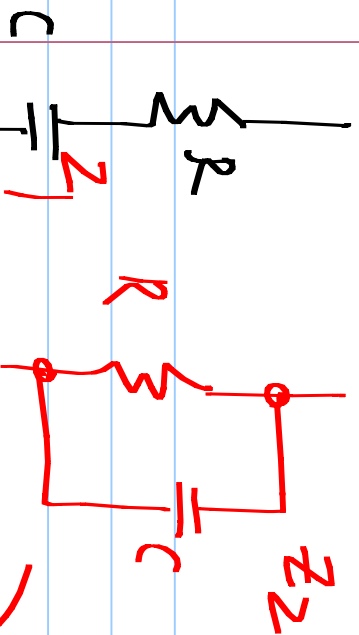

② $\omega = 1/Rc$



$\sqrt{2} R \exp(-j\pi/4)$

$\frac{R}{\sqrt{2}} \exp(-j\pi/4)$

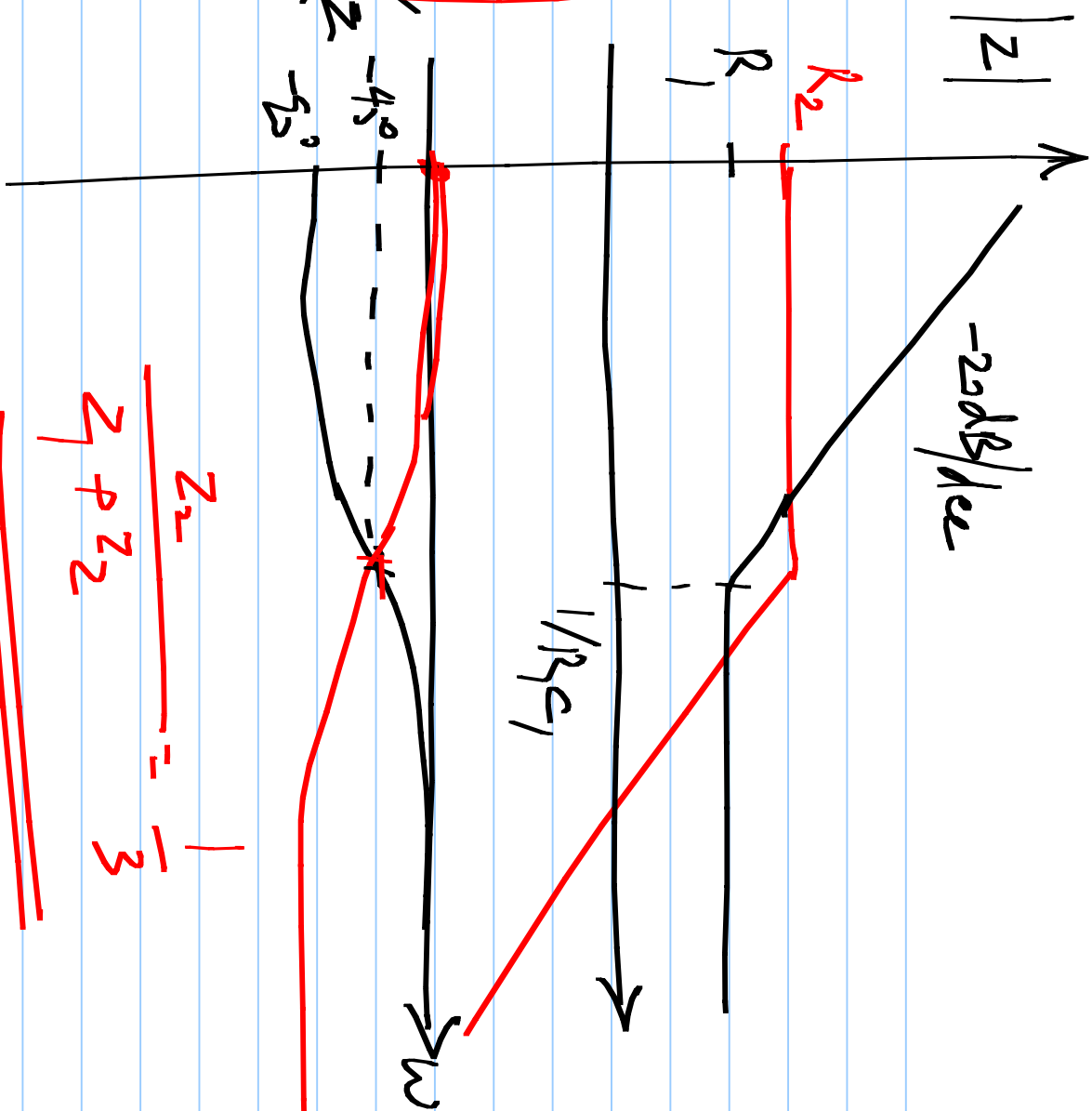


$\frac{Z_2}{Z_1 + Z_2} = \frac{1}{3}$

Wien-Bridge
Oscillator

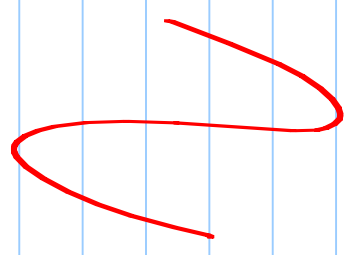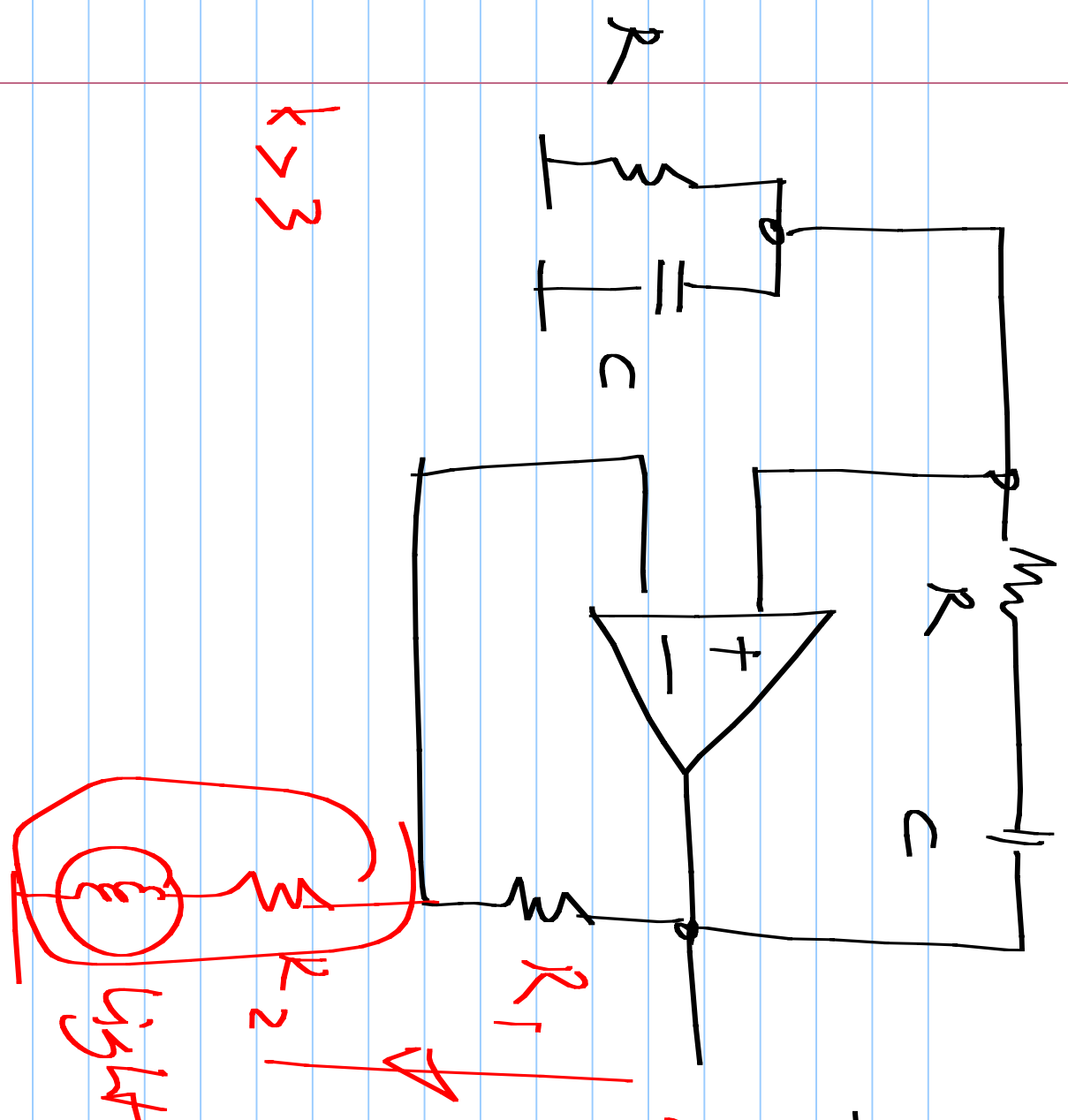

light bulbs

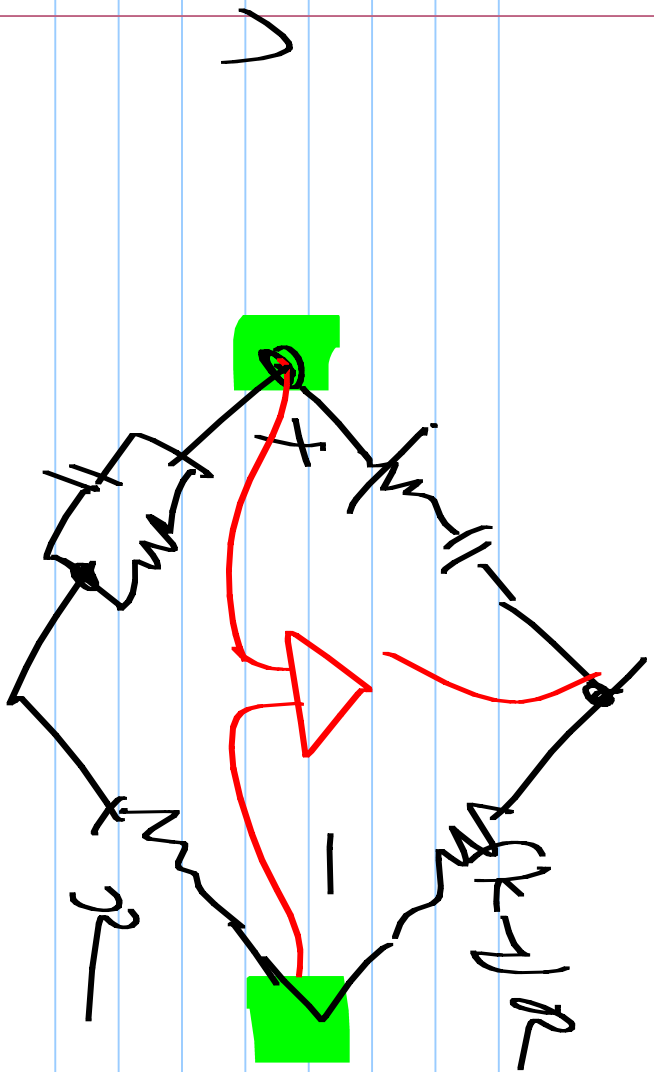

Archer's Circuit

Design

Archer Science

Personalities

Jim Williams