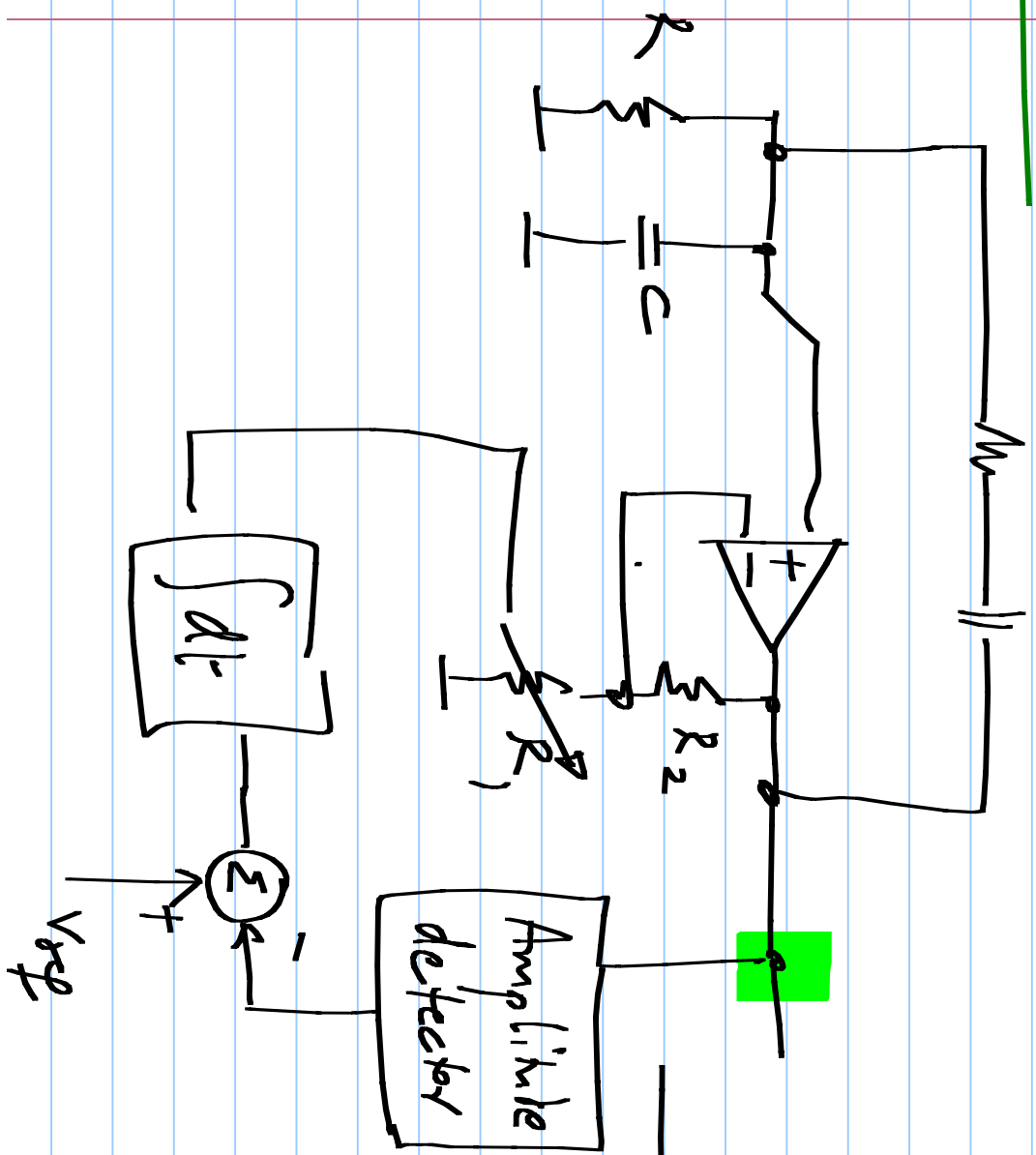


EE 2019

R C

11/4/2017




$\frac{R_2}{R_1} \geq 2$  for oscillation

Oscillate @


$\omega_0 = 1/RC$

amplitude  $V_{rf}$

$V_{ref}$

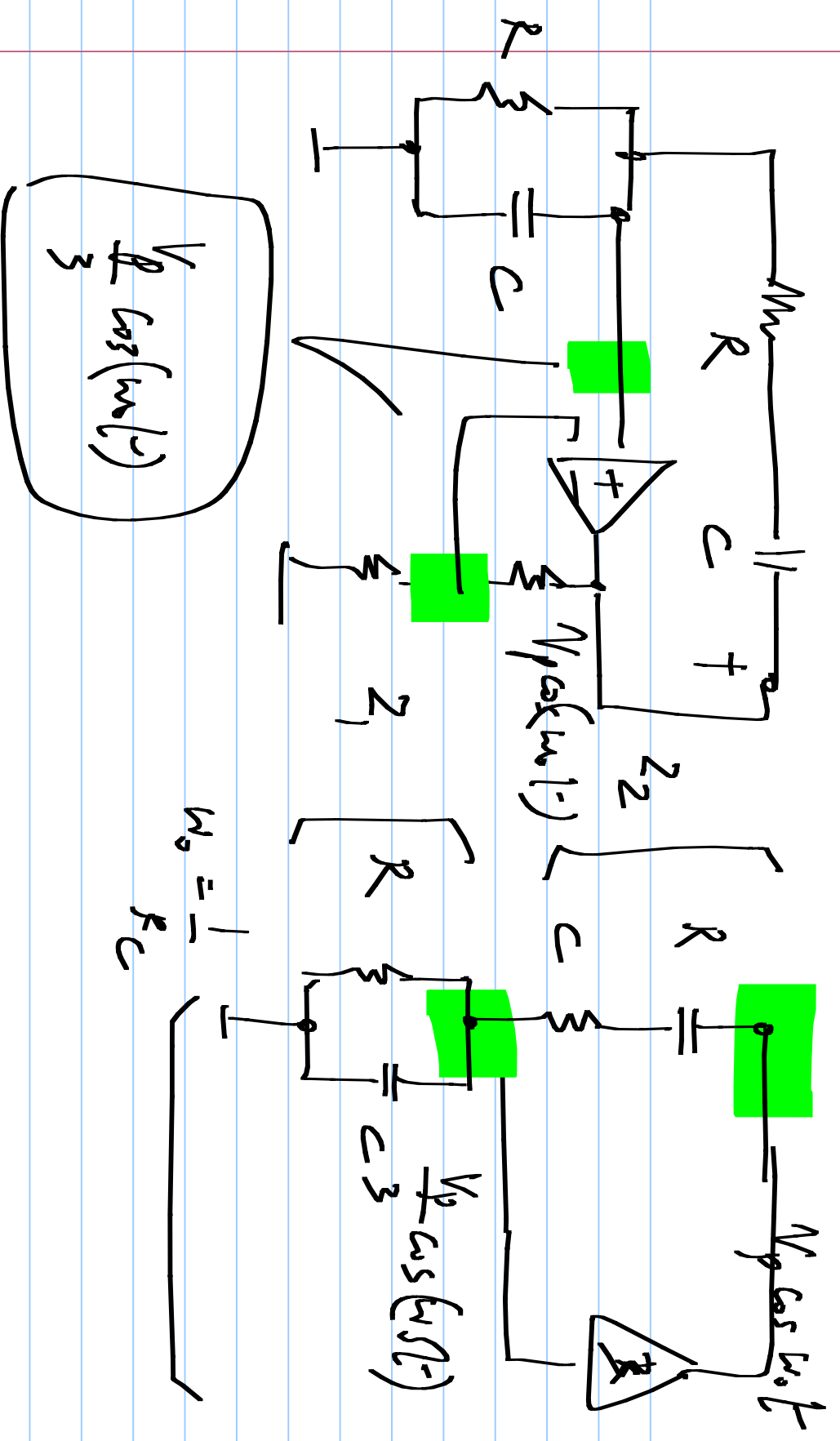


$$\omega_0 = \frac{1}{RC}$$

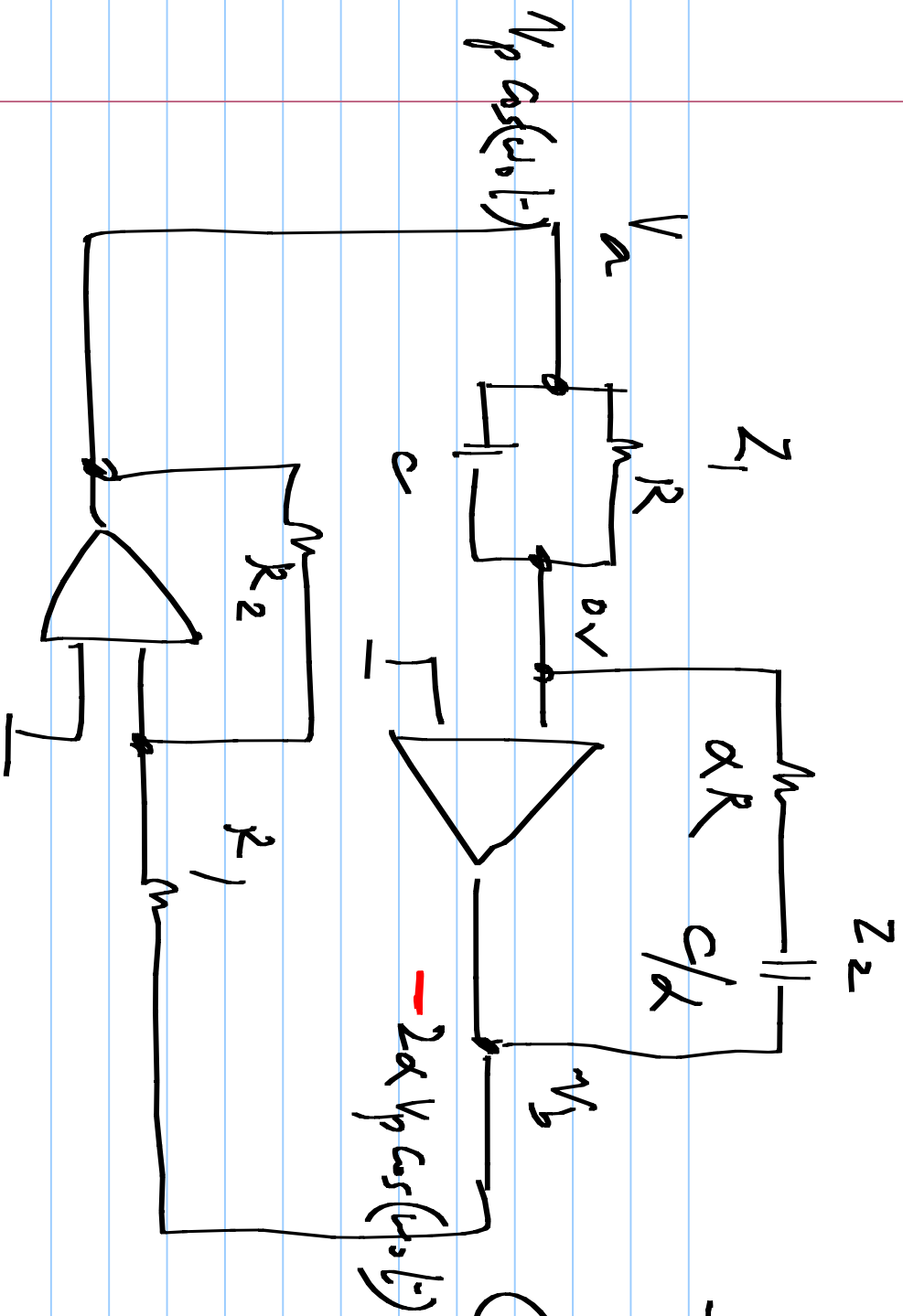


$$\frac{v_b}{v_a} = -\frac{Z_2}{Z_1}$$

$$\textcircled{a} \frac{1}{R_C} = -2\alpha$$

$$\frac{R_2}{R_1} = \frac{1}{2\alpha}$$

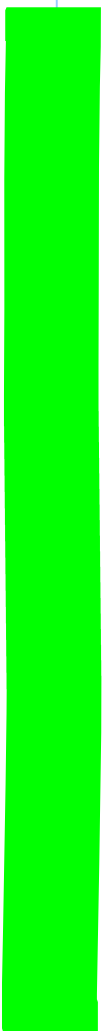


$V_p \cos(\omega t)$   $Z_2$

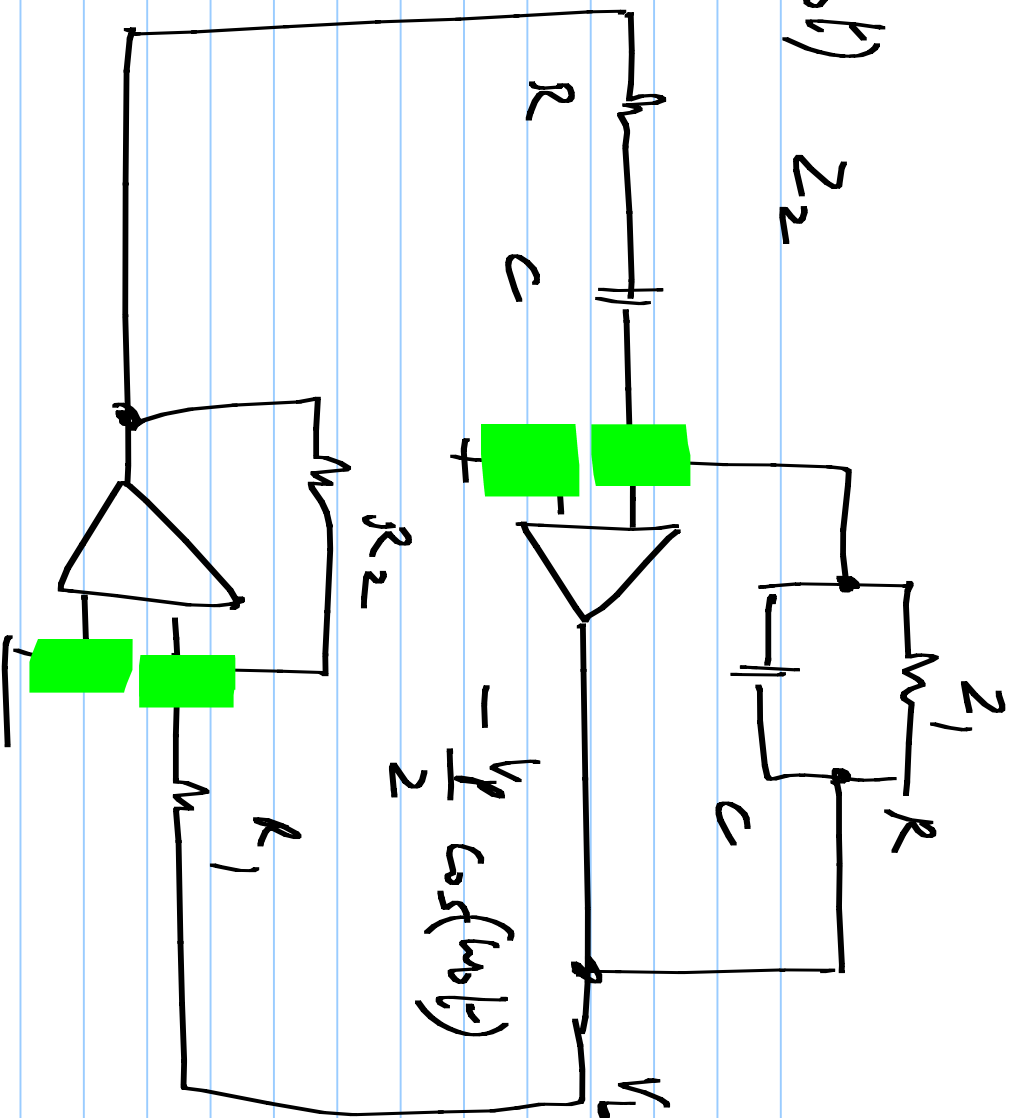

$$\frac{V_o}{V_i} = -\frac{1}{2}$$

$$\text{@ } \frac{1}{R_2}$$

$$\frac{R_2}{R_1} = 2$$

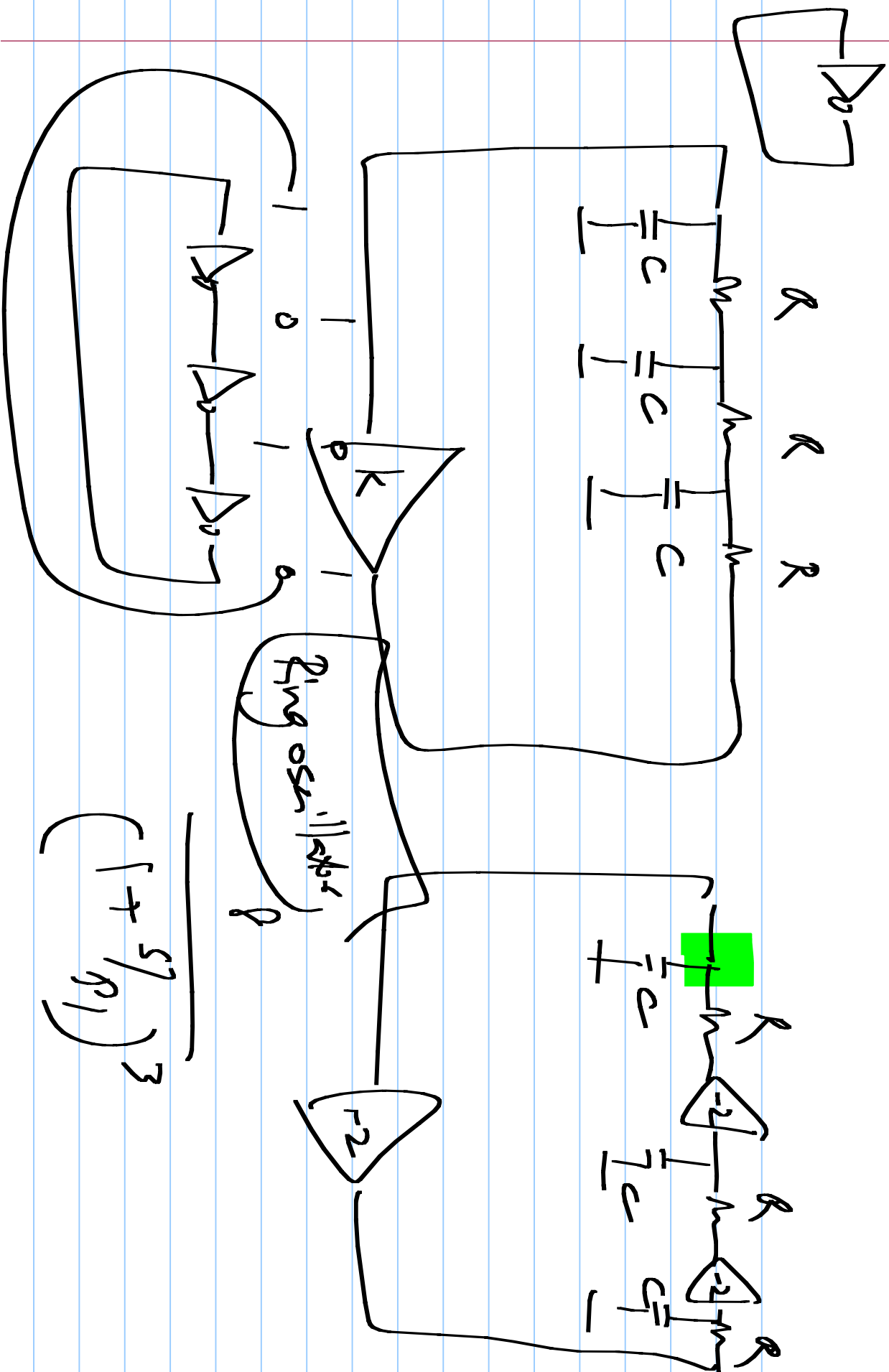

# Oscillators:


LC: Very "good" periodicity


Ping oscillators:

Harmonic oscillators:  $\left\{ \begin{array}{l} \text{Double integrator (opamp)} \\ \text{Wien bridge} \end{array} \right.$



Relaxation oscillators: Schmitt trigger osc.

Better periodicity  
Higher frequency

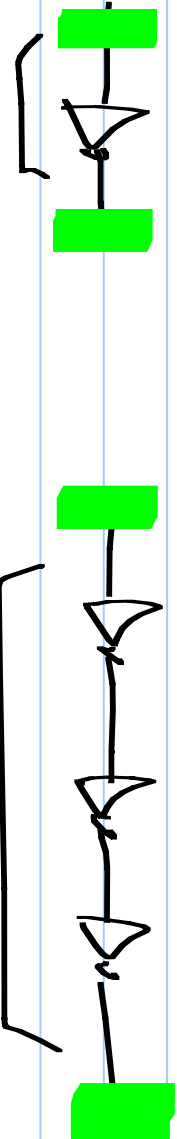

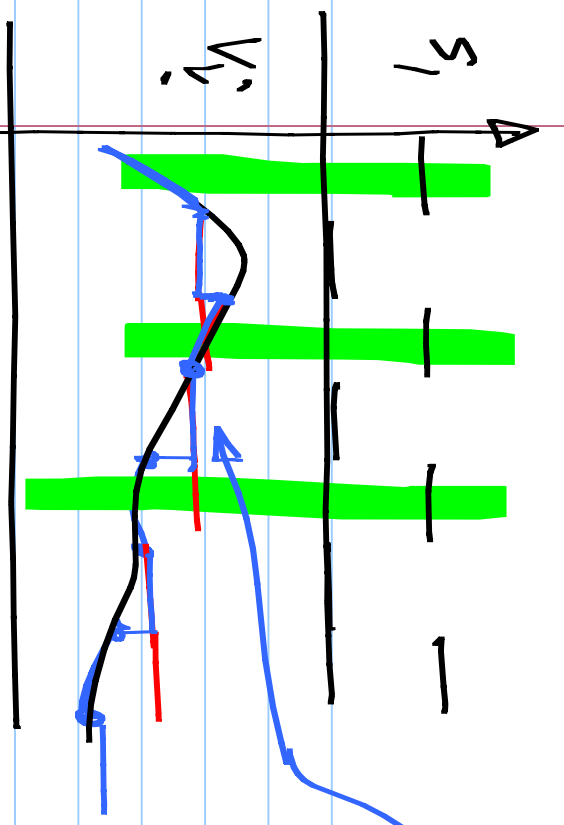

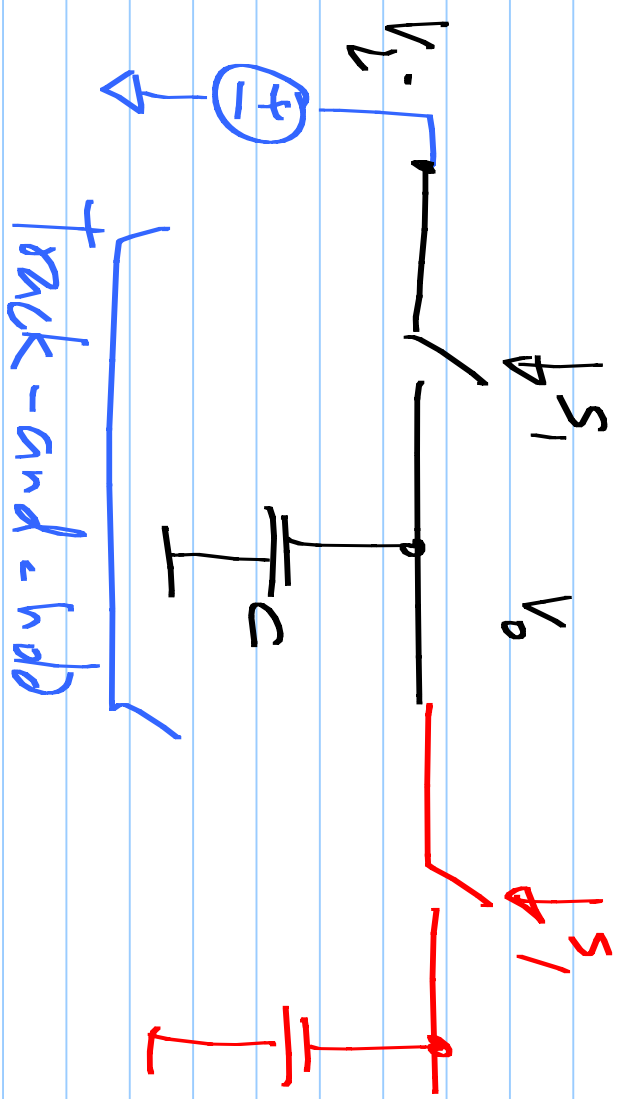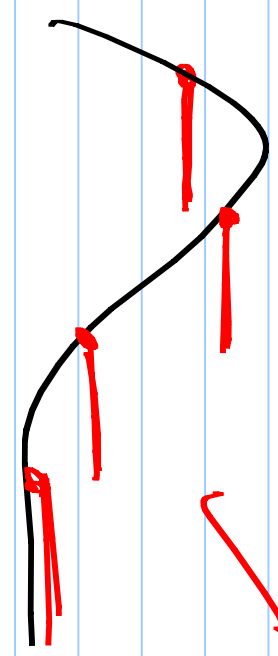Sampled just before  $s_1$  falls to zero.



Track-and-hold