


EE 2019

Analog circuits and lab

17/1/2018

1/17/2018


Controlled sources (unilateral)

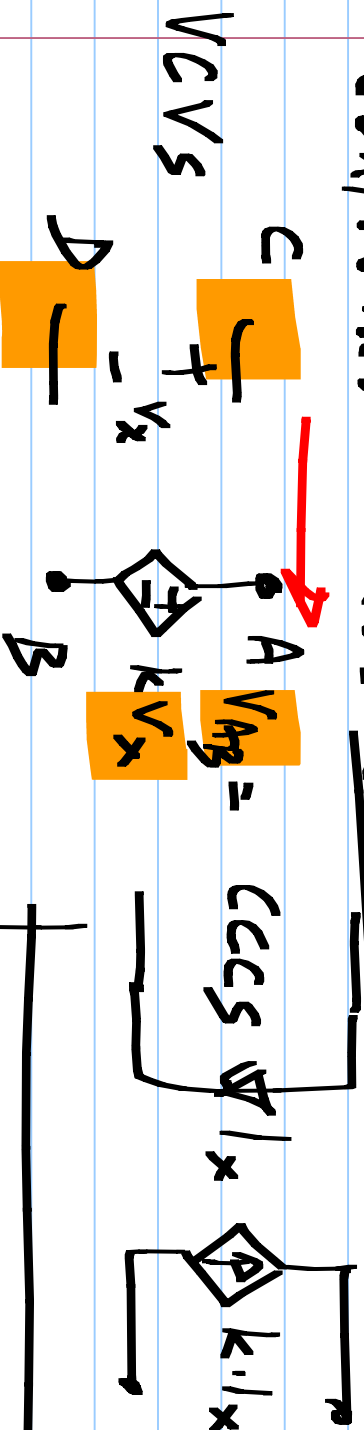

$$V_{AB} = V_x$$

$$V_x = V$$


$$V = V_x$$

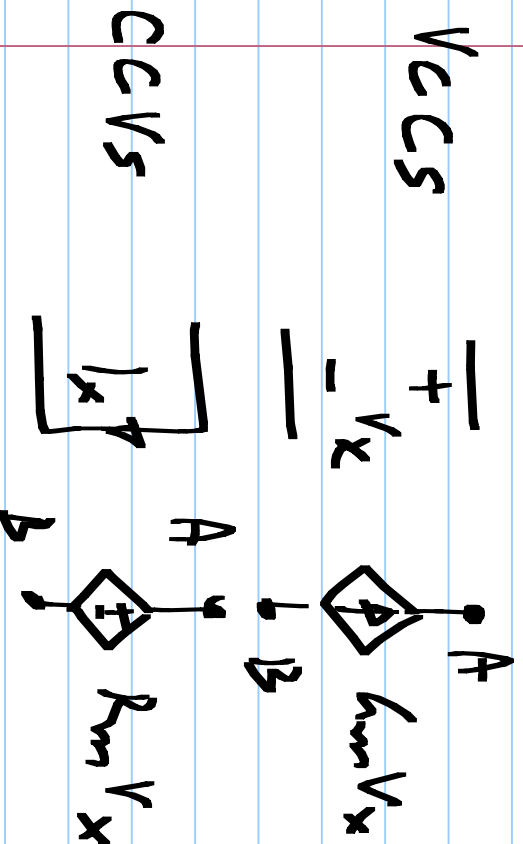

$$V_{AB} = V_x$$


$$V_x = V$$

$$V = V_x$$

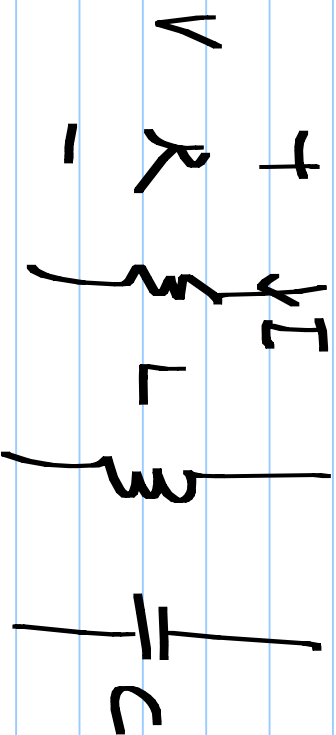

$$V = V_x$$

$\frac{1}{R}$

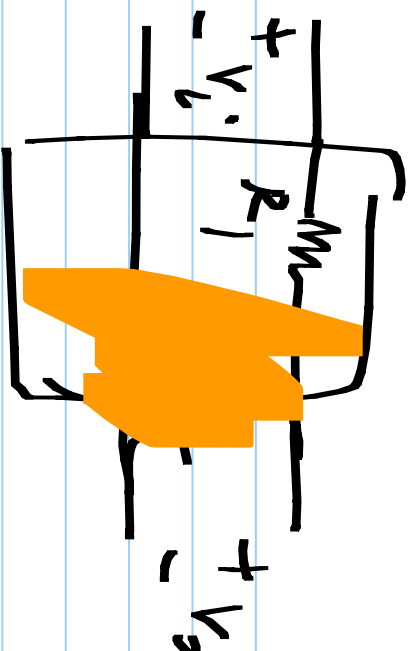



$$\frac{-R_2}{R_1 - R_2}$$

Controlled sources: Unilateral


Amplifiers


Physical devices

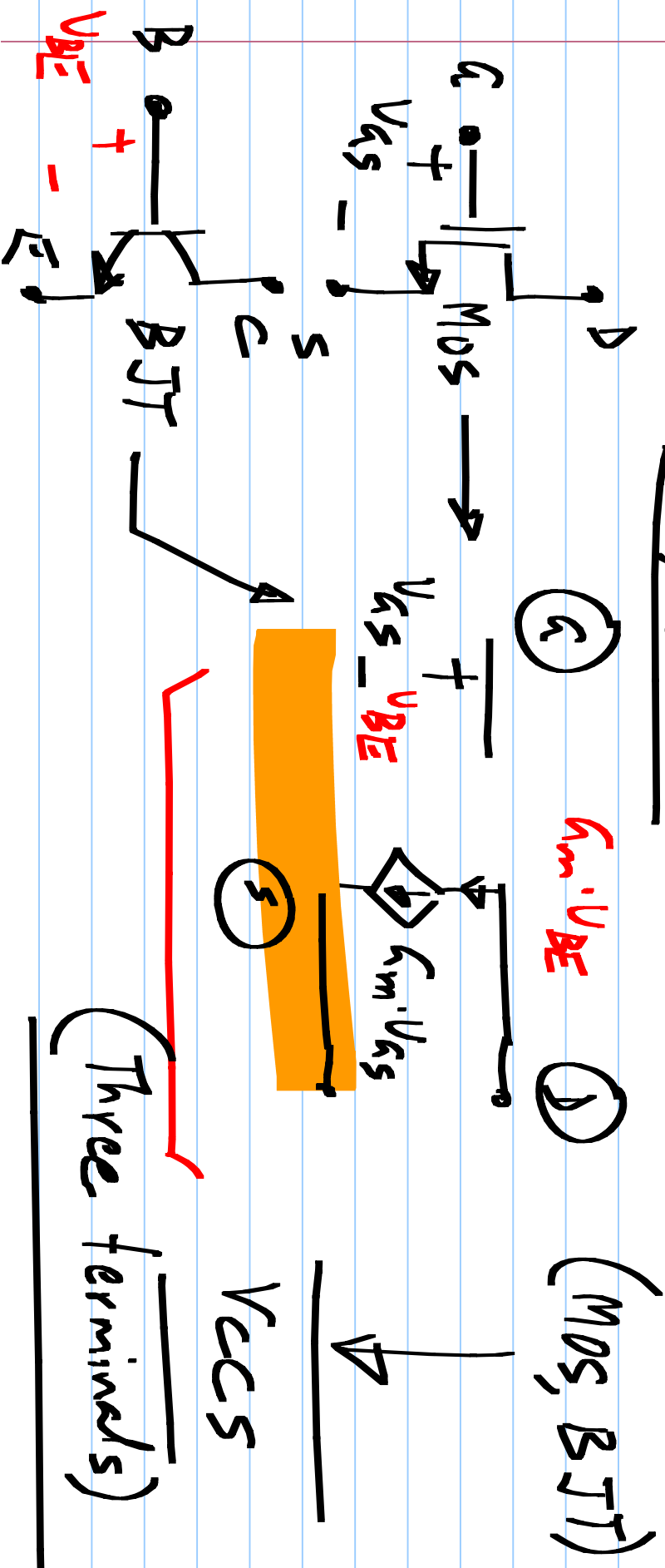


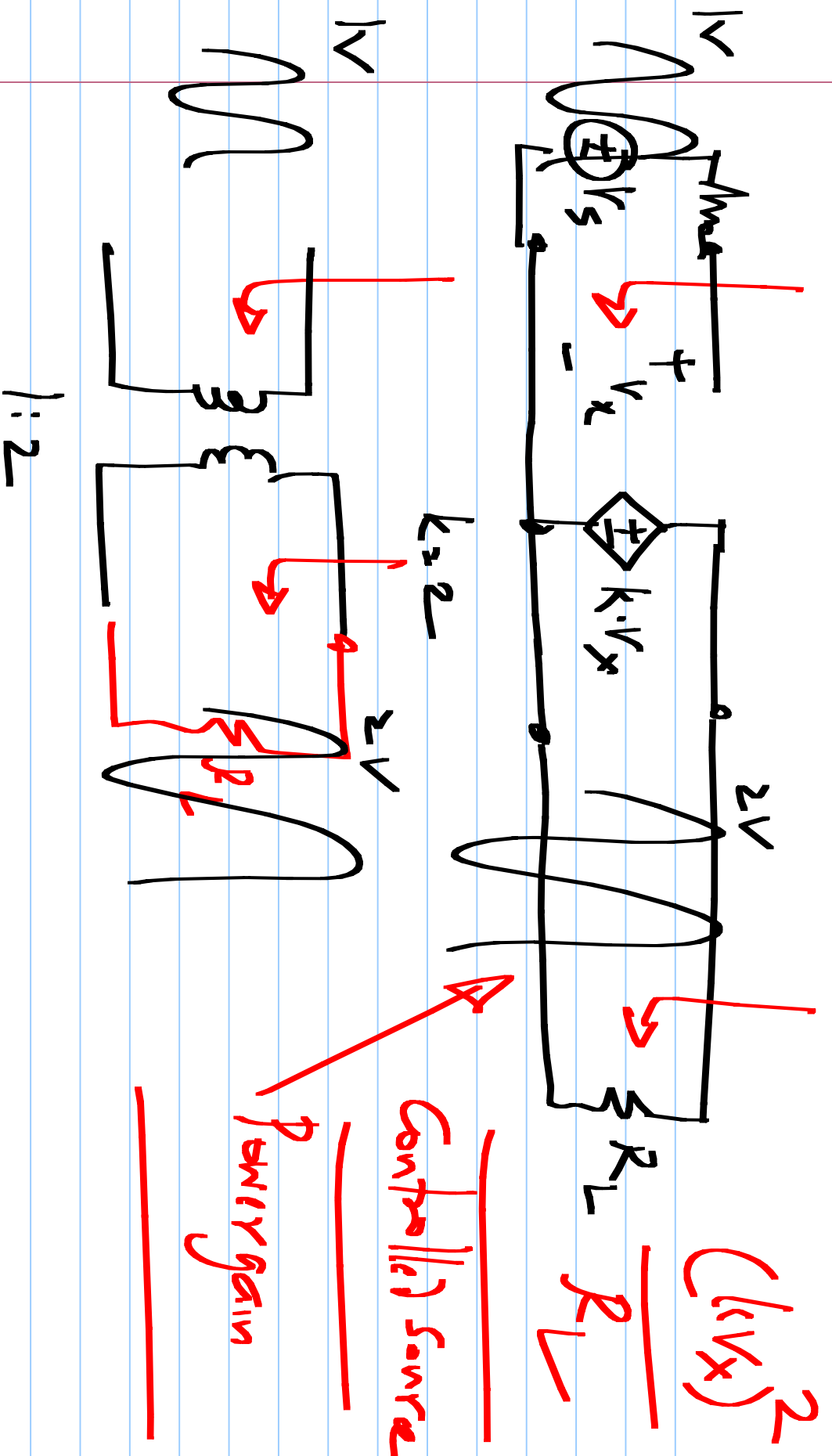


Power gain

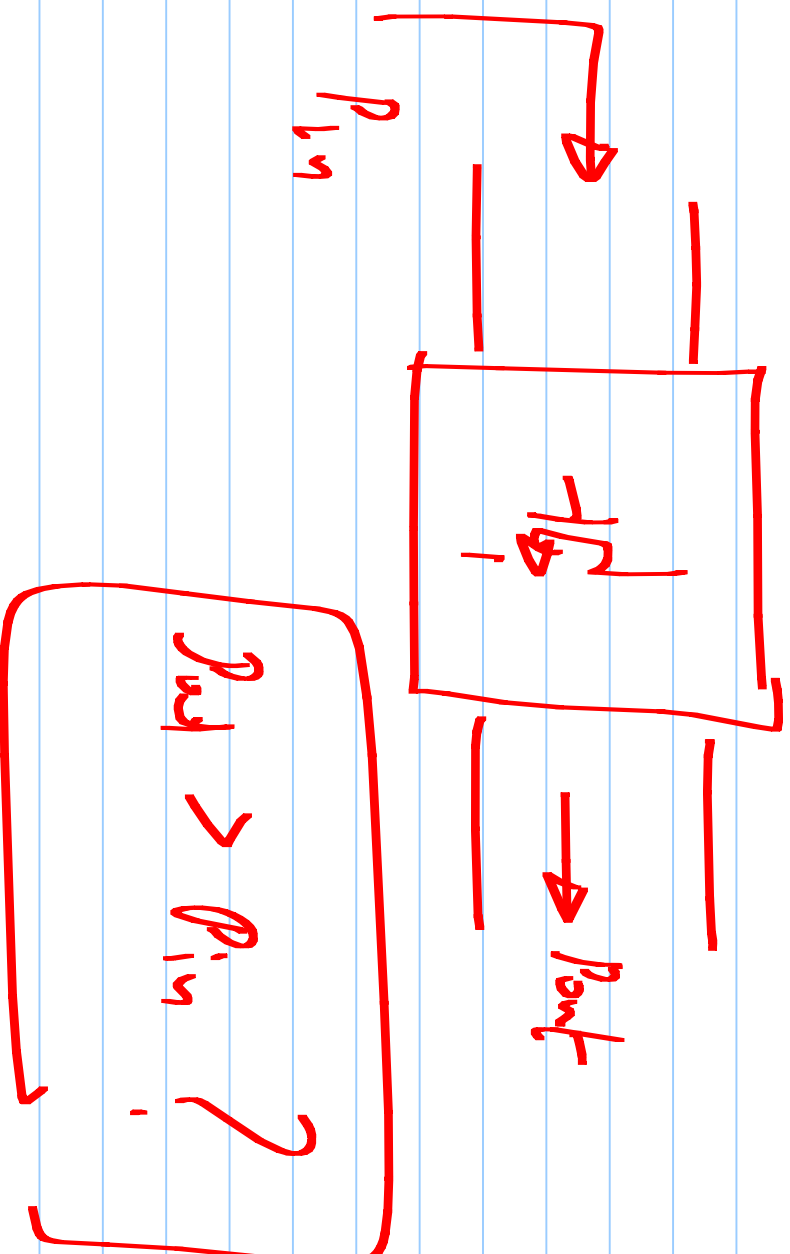

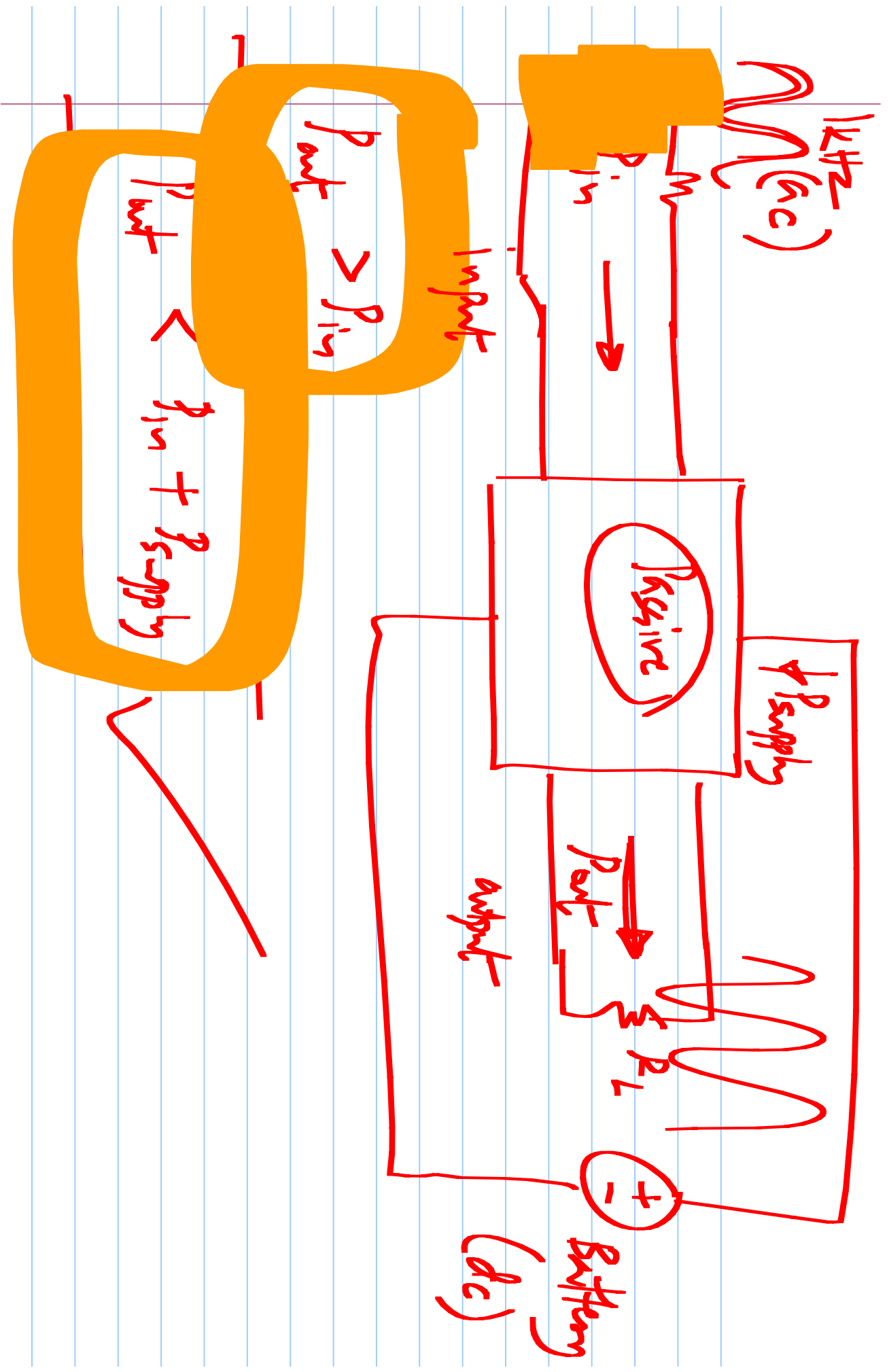


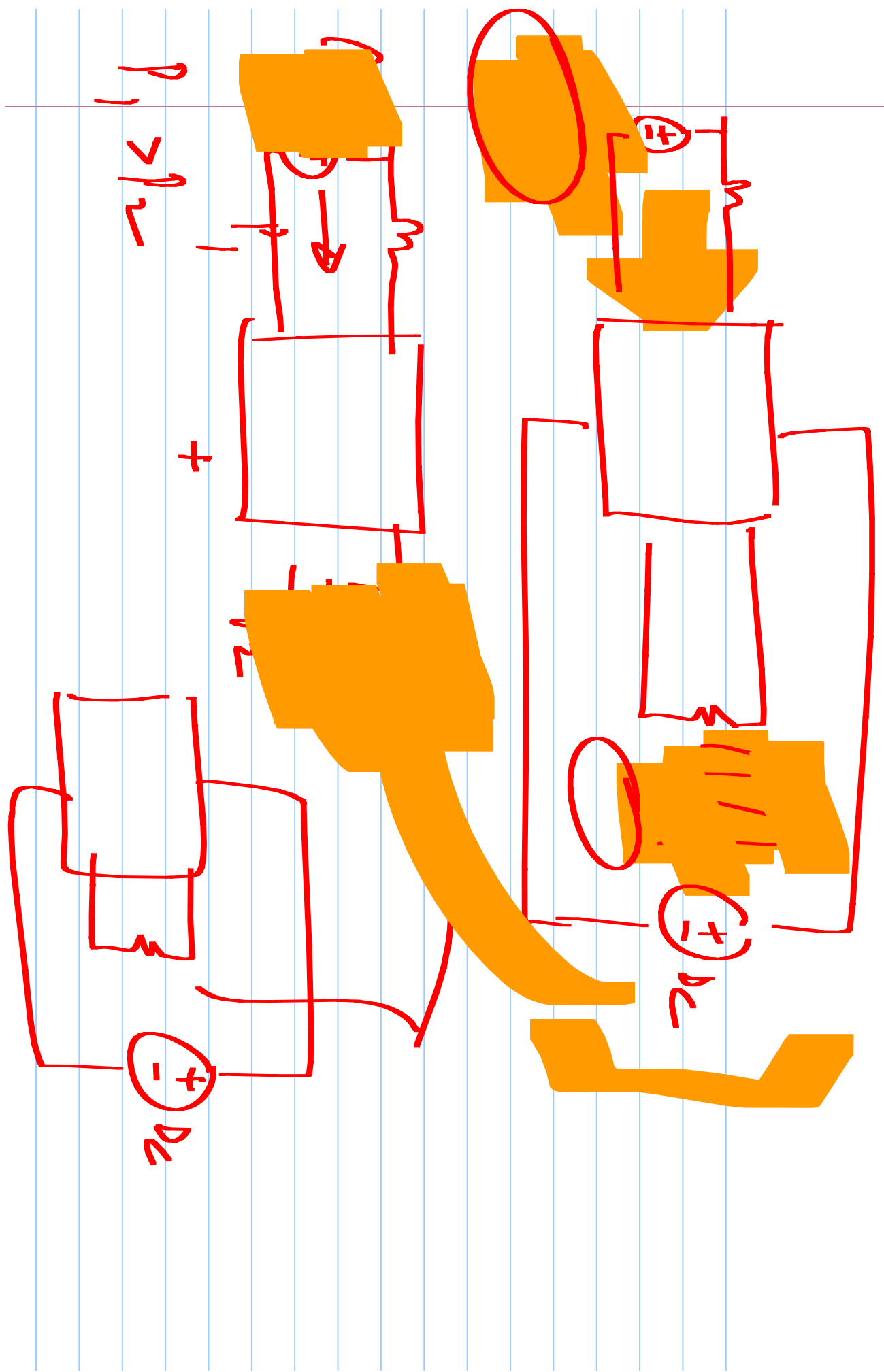




$V_C V_S$!

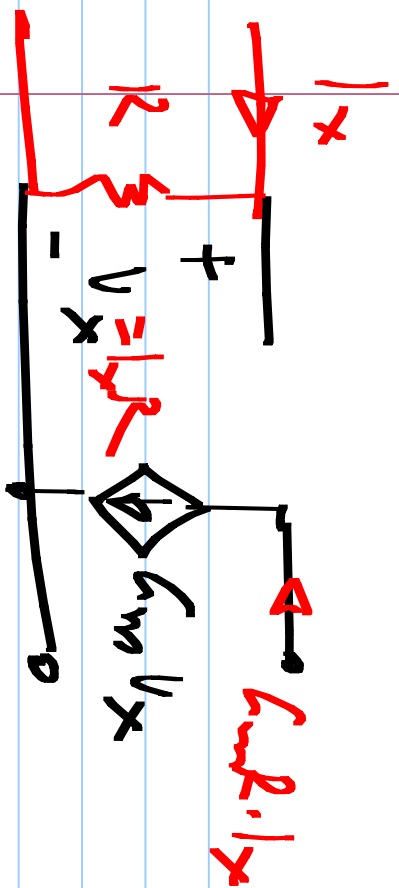

$V_C V_S$

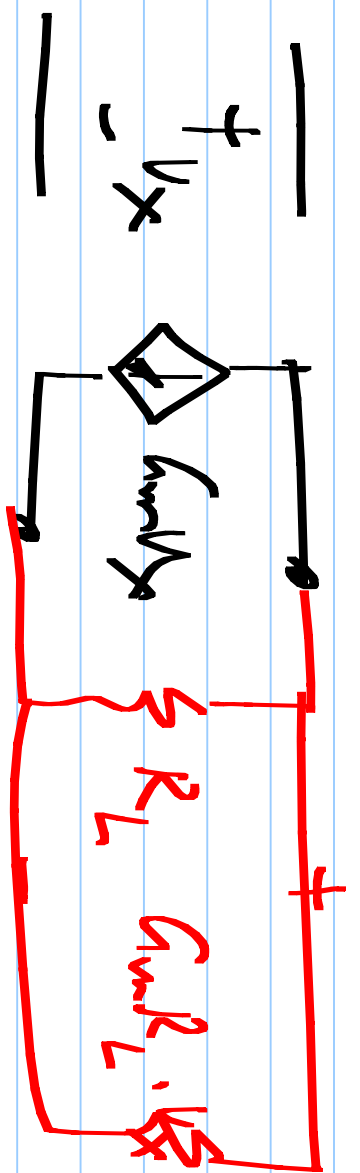

CCCS

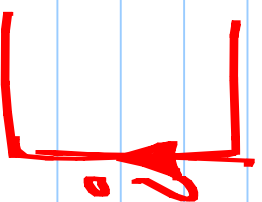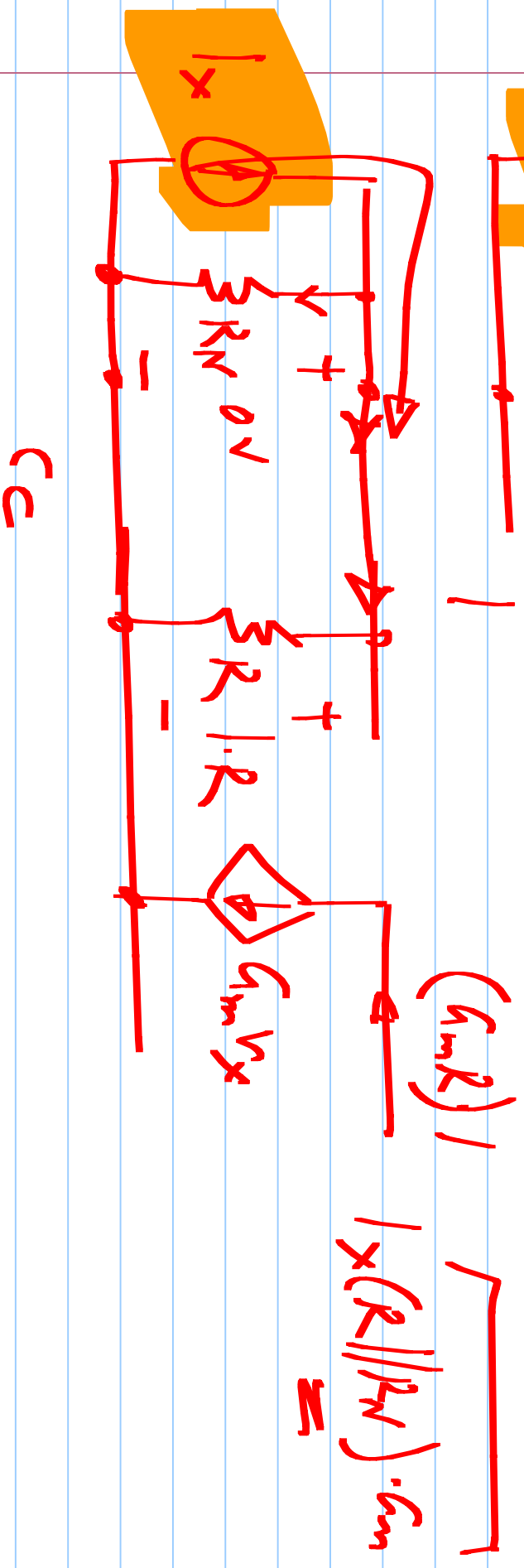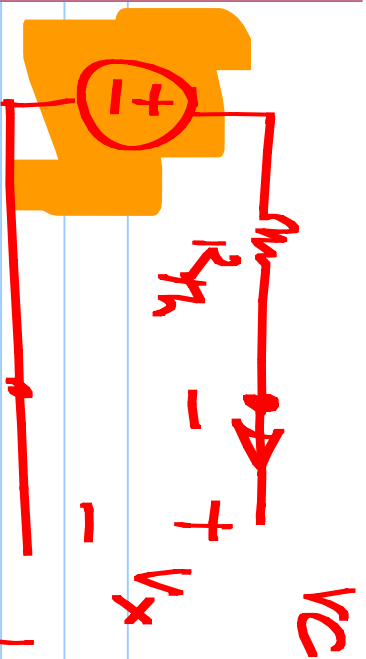

$$R_{th} = \frac{1}{I_x (R \parallel R_L)} \cdot g_m$$