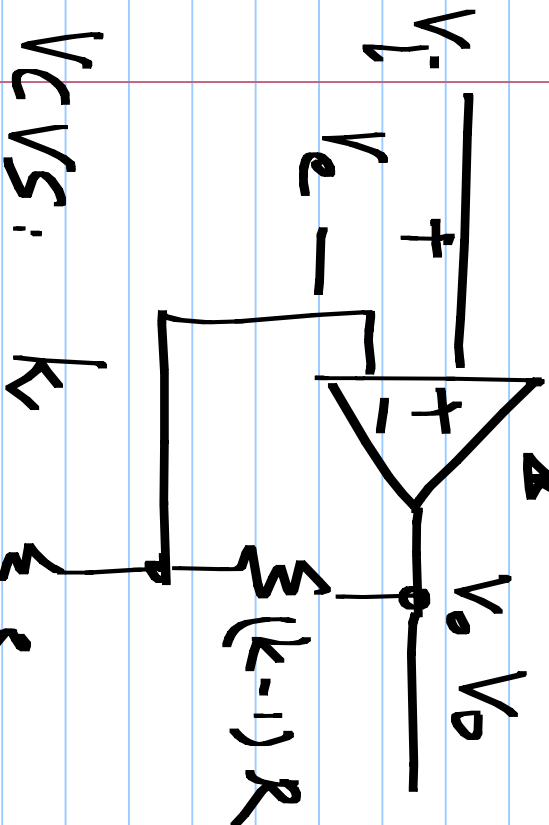


EE2019

$$\frac{V_o}{V_e} = \frac{A}{1 + s \cdot \frac{A}{\omega_u}}$$

$$\boxed{\frac{V_o}{V_e} = A}$$

24/1/2018



$$V_o = k \cdot V_i \cdot \frac{1}{1 + k/A_o}$$
$$V_e = \frac{k V_i}{k + A_o} \approx \frac{1}{A_o}$$


$$\frac{k}{1 + k/A_o}$$

$$\frac{V_o}{V_i} = \frac{k}{1 + k/A_o} \quad (\text{dc steady state})$$

$$\omega_n \rightarrow \infty$$

$$\frac{V_o}{V_e} = \frac{\omega_n}{s}$$

In sinusoidal steady state,

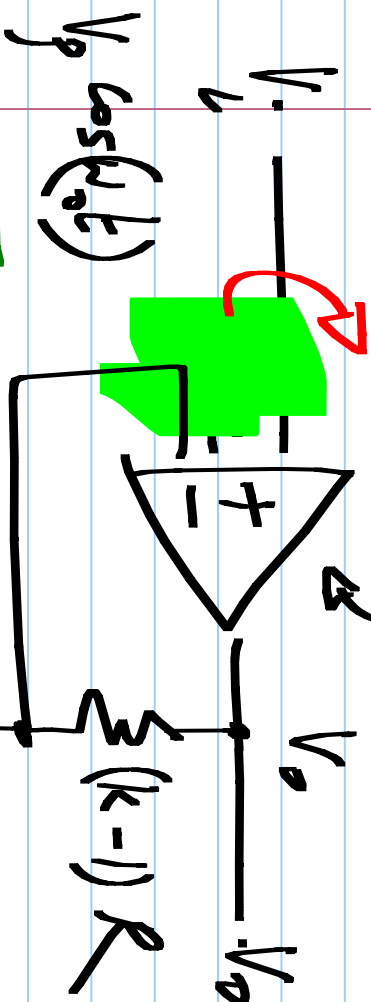

$$\frac{V_o}{V_i} = \frac{k}{1 + k \cdot \frac{s}{\omega_n}}$$

$$V_i \left(1 + k \cdot \frac{s}{\omega_n} \right)$$

$$V_i = V_p \cos(\omega_n t)$$

$$V_o = k V_p \frac{1}{(1 + k \frac{j\omega}{\omega_n})} \cdot \cos(\omega_n t - \tan^{-1} \frac{k \cdot \omega}{\omega_n})$$

(steady state) $\frac{k \omega}{\omega_n} \ll 1$

opamp: Integrator $\frac{w}{s}$

dc: ∞ gain: Ideal behavior

$[V_o \rightarrow 0 \text{ in dc steady state}]$


$w \rightarrow \infty$: Ideal opamp

∞ gain everywhere

$[V_o \rightarrow 0 \text{ @ all frequency}]$

Real opamp: finite dc gain

opamp = High gain amplifier

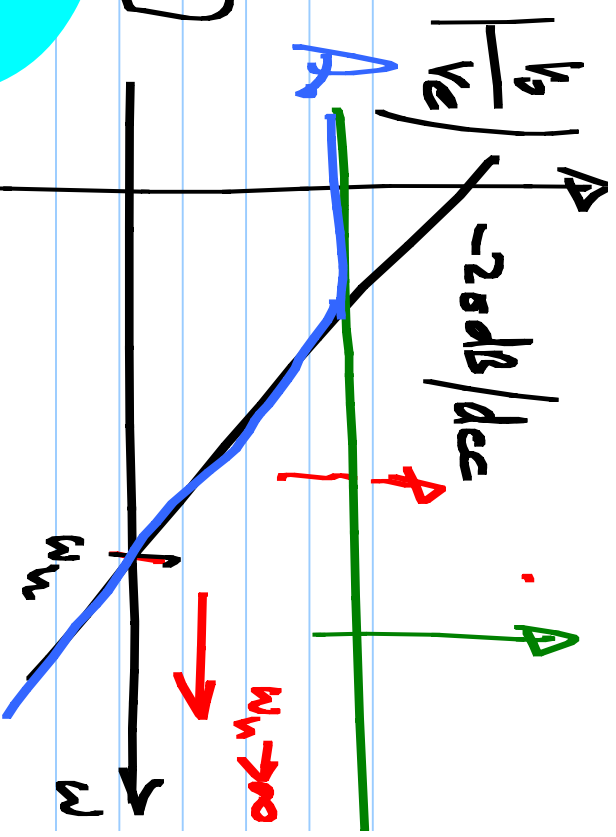


$$\frac{V_o}{V_e} = A_o$$

$A_o \rightarrow \infty$

supply terminal

V_- : negative supply terminal

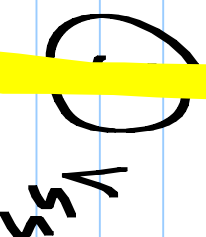

if $l_{out} > 0$
 $l_p = l_{out}, l_m = 0$

$\ln$	$\ln$
$\ln$	$\ln$

$$14 \frac{1}{2} \times 10$$

Yes

Supply currents in an opamp

Most efficient case:

$$\text{if } I_{out} \geq 0, \quad I_p = I_{out}, \quad I_n = 0$$

$$\text{if } I_{out} < 0, \quad I_p = 0, \quad I_n = -I_{out}$$

Slightly more realistic $I_L > 0$

$$\text{if } I_{out} \geq 0, \quad I_p = I_{out} + I_L, \quad I_n = I_L$$
$$I_{out} < 0, \quad I_p = I_L, \quad I_n = -I_{out} + I_L$$