
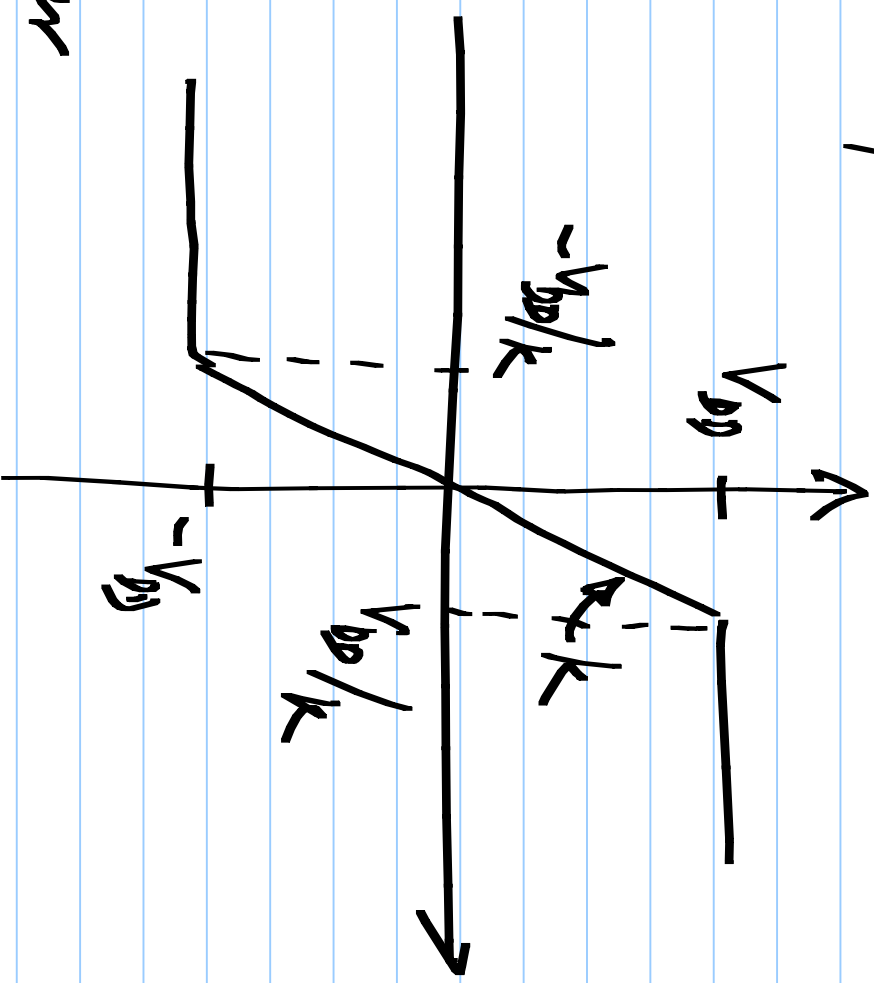




EE 2019

$$k = 1 + \frac{R_2}{R_1}$$

30/1/2019

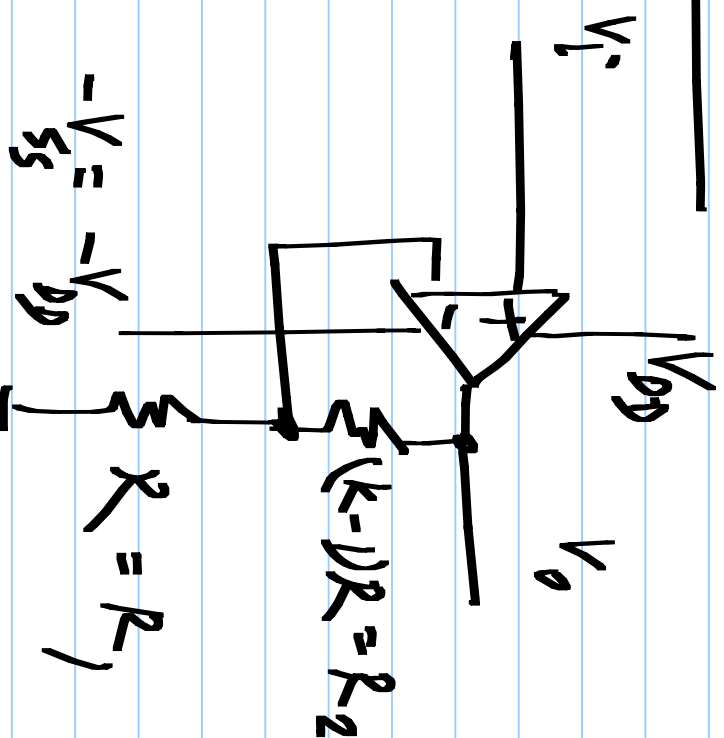


Non-inverting amplifier

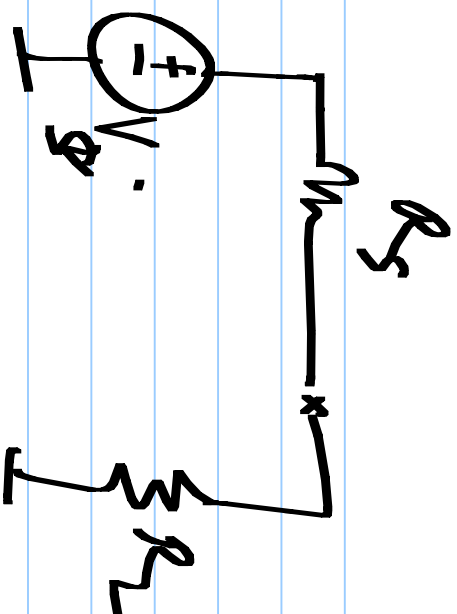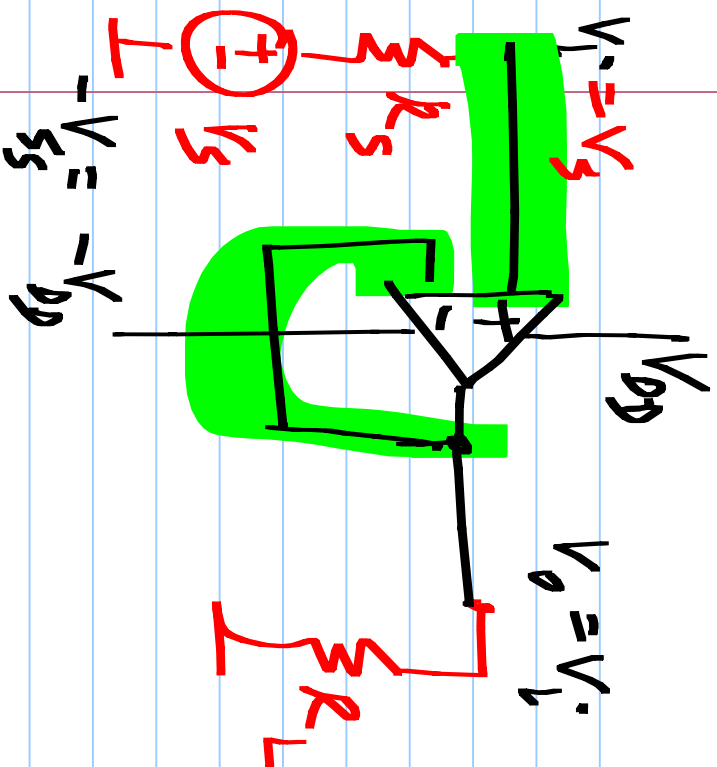

$$V_o = V_i$$

Voltage follower


Buffer

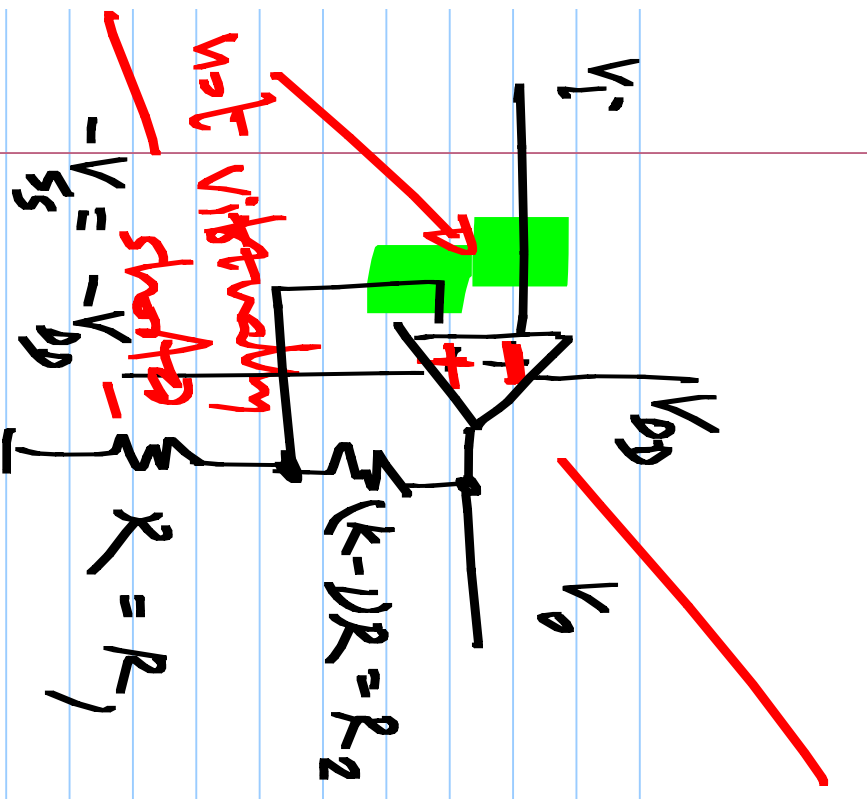

positive feedback

~~Non-inverting amplifier~~


~~Inverting Schmitt trigger~~

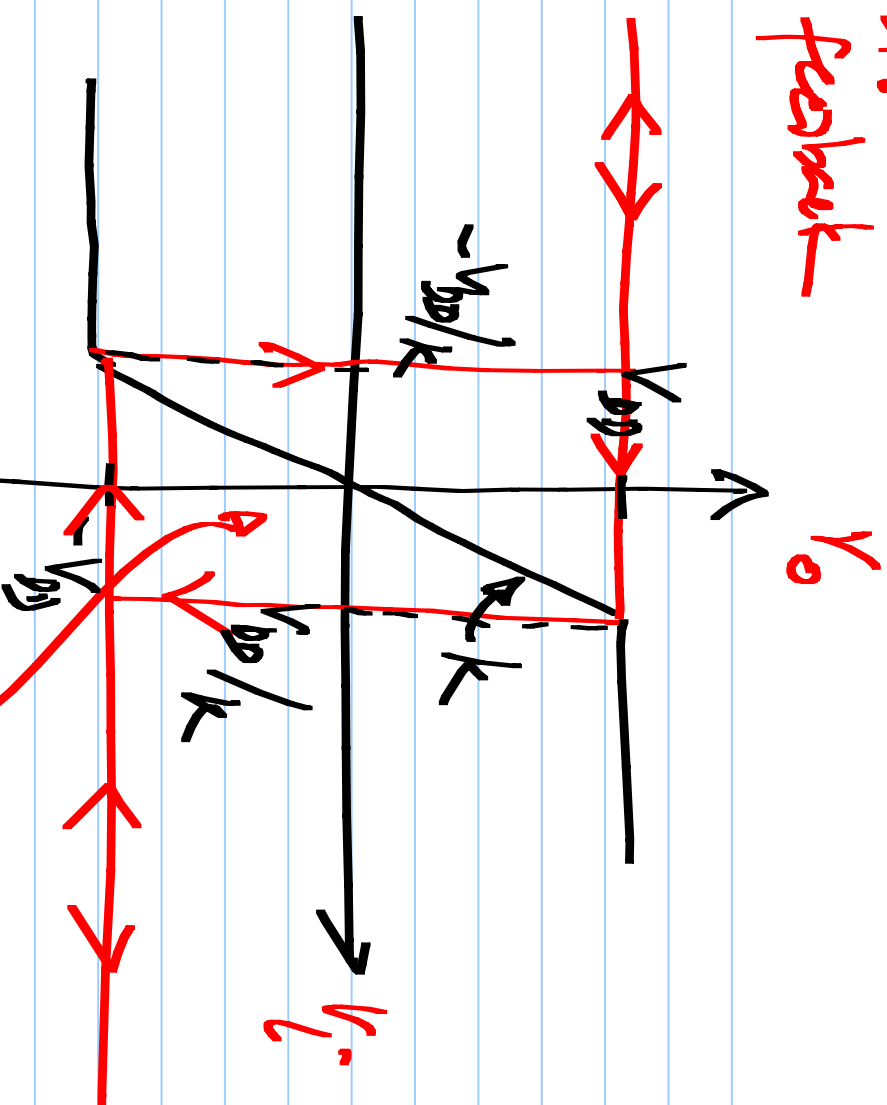


hysteresis loop


ideal opamp
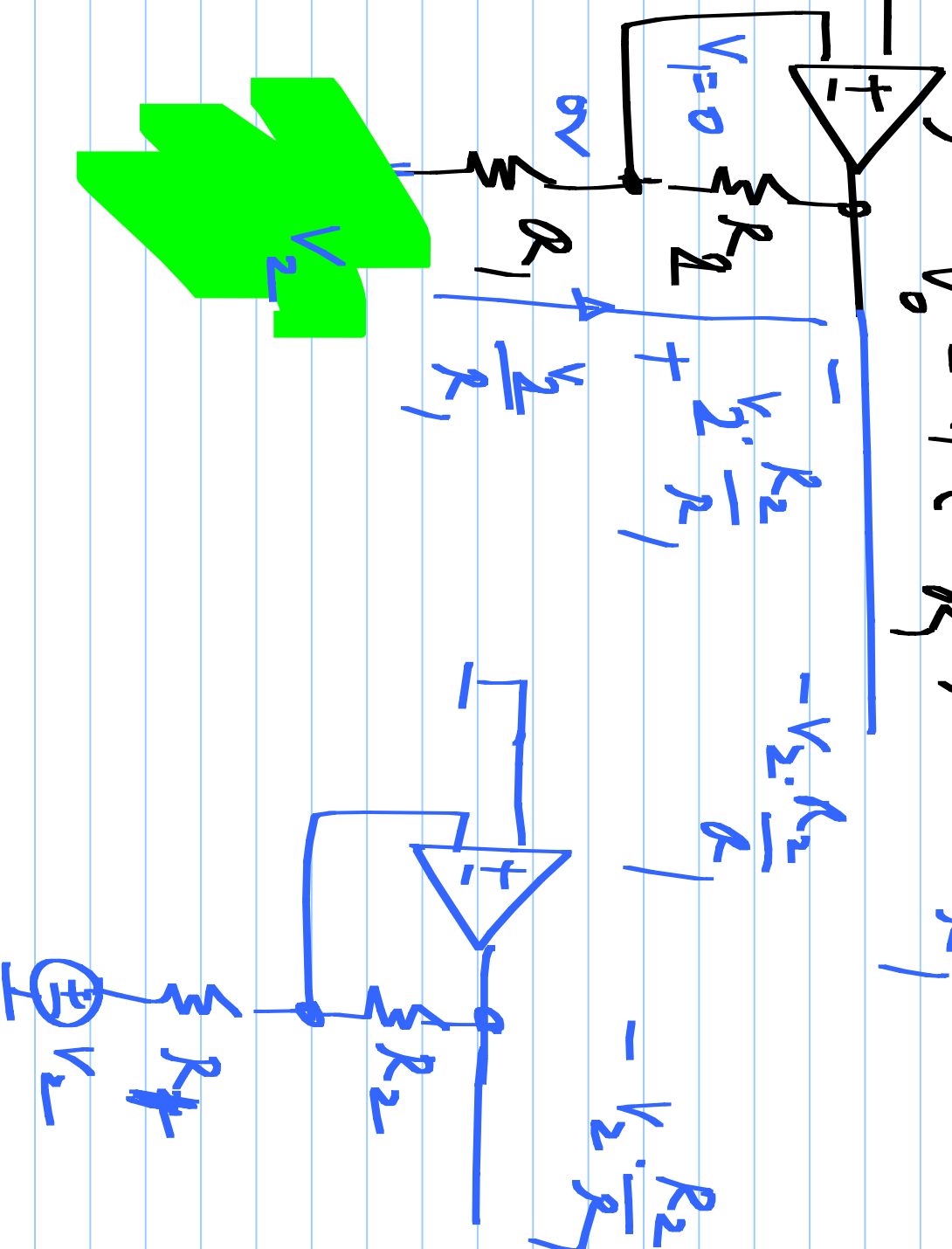
$$V_o = V_1 \cdot \left(1 + \frac{R_2}{R_1}\right) - V_2 \cdot \frac{R_2}{R_1}$$



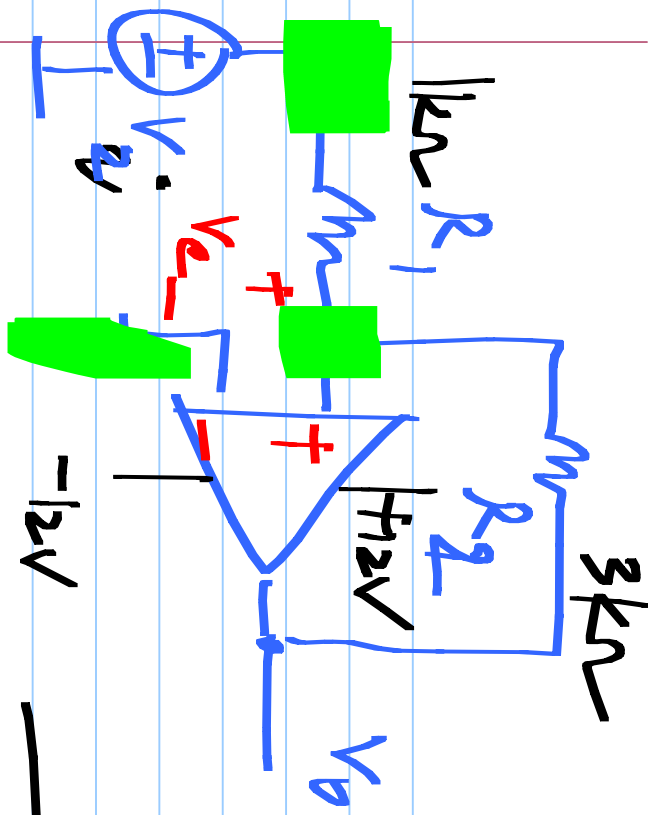


$$\frac{V_o}{V_2} = -\frac{R_2}{R_1}$$

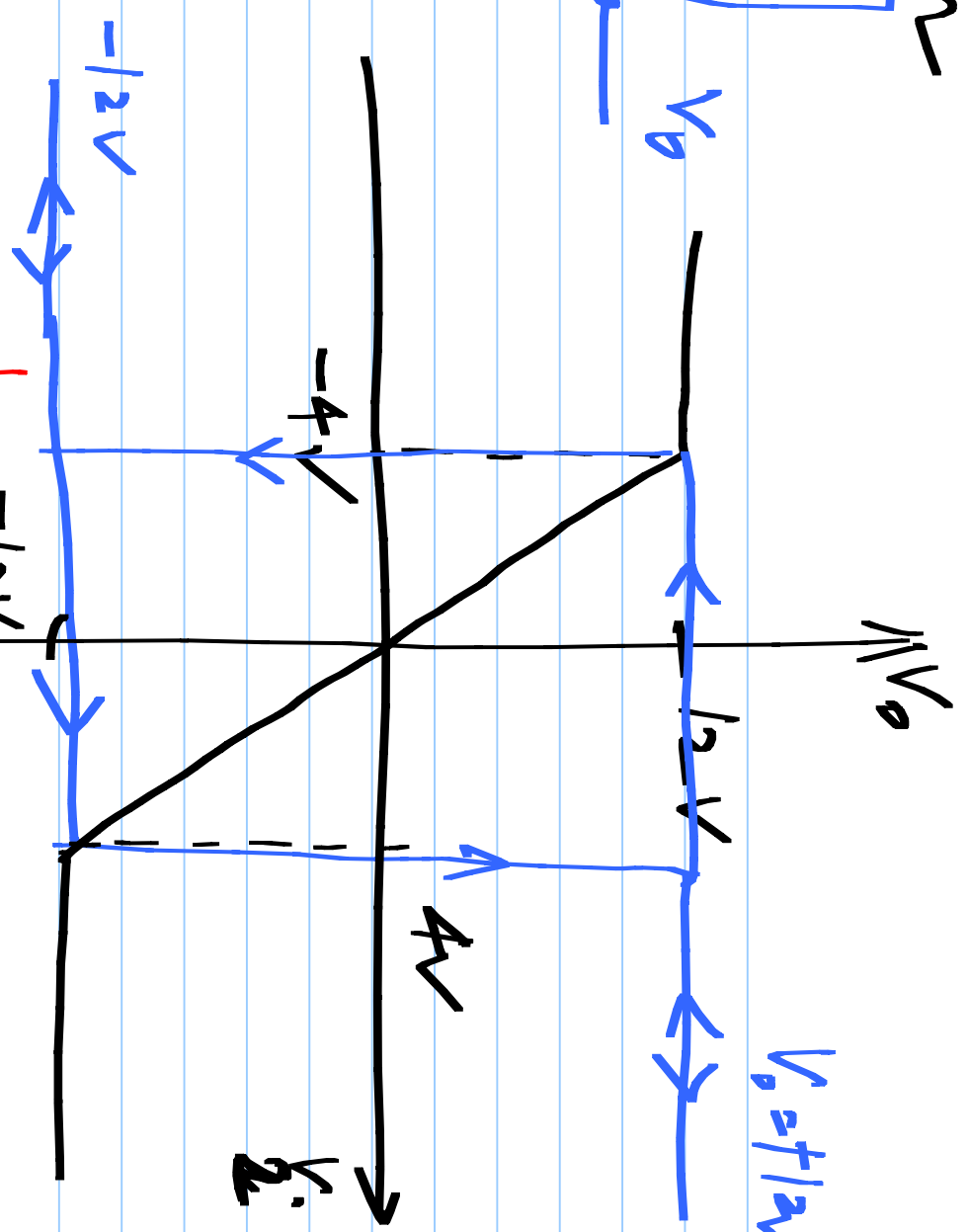

Inverting amplifier


Non-inverting Schmitt trigger

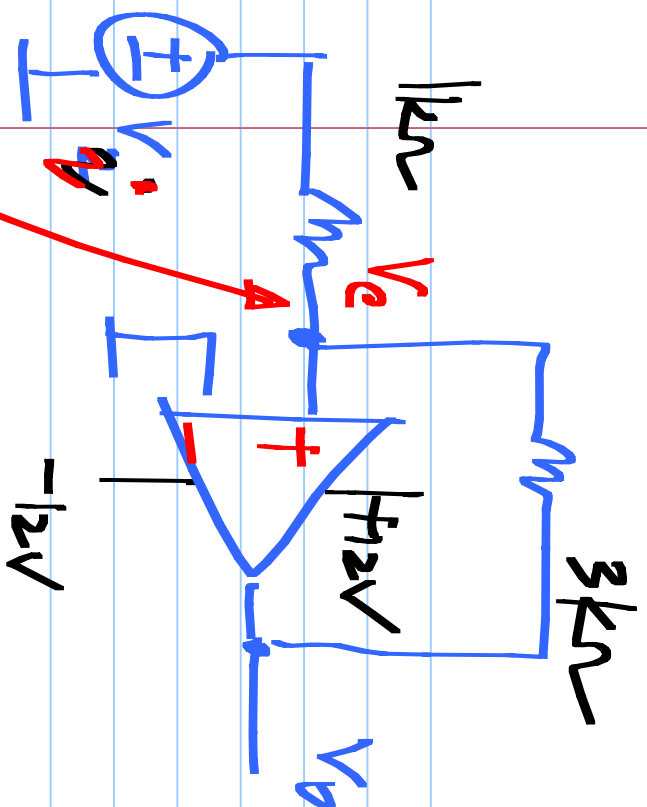


$\pm 12V$

$$V_e = \frac{3}{4}V_i + \frac{1}{4}V_o$$

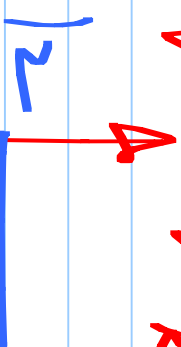
$$V_e = \frac{3}{4}V_i + \frac{1}{4}(-12V)$$


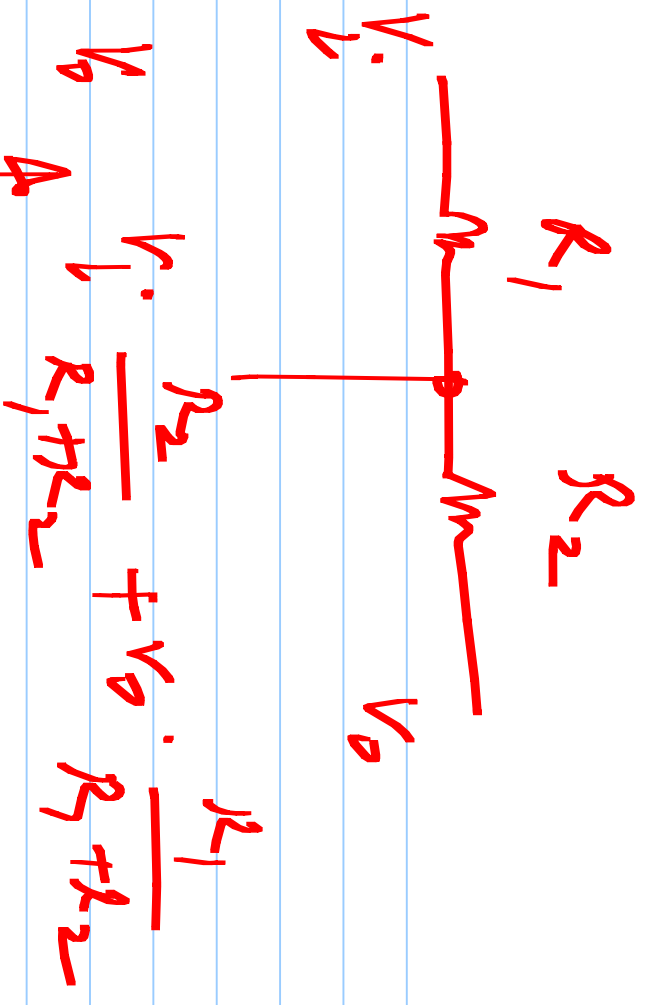
$$V_e = \frac{3}{4}V_i + \frac{1}{4}(-12V)$$


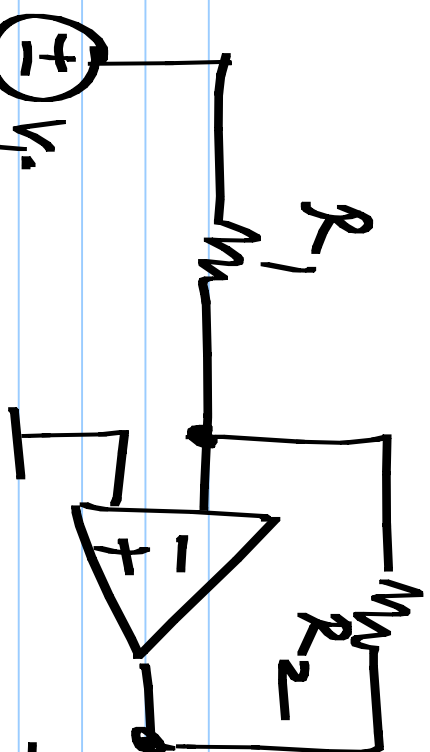
$$V_o = V_i \cdot \frac{R_2}{R_1 + R_2} + V_o \cdot \frac{R_1}{R_1 + R_2}$$




$$V_o = -\frac{R_2}{R_1} \cdot V_i$$




Integrator
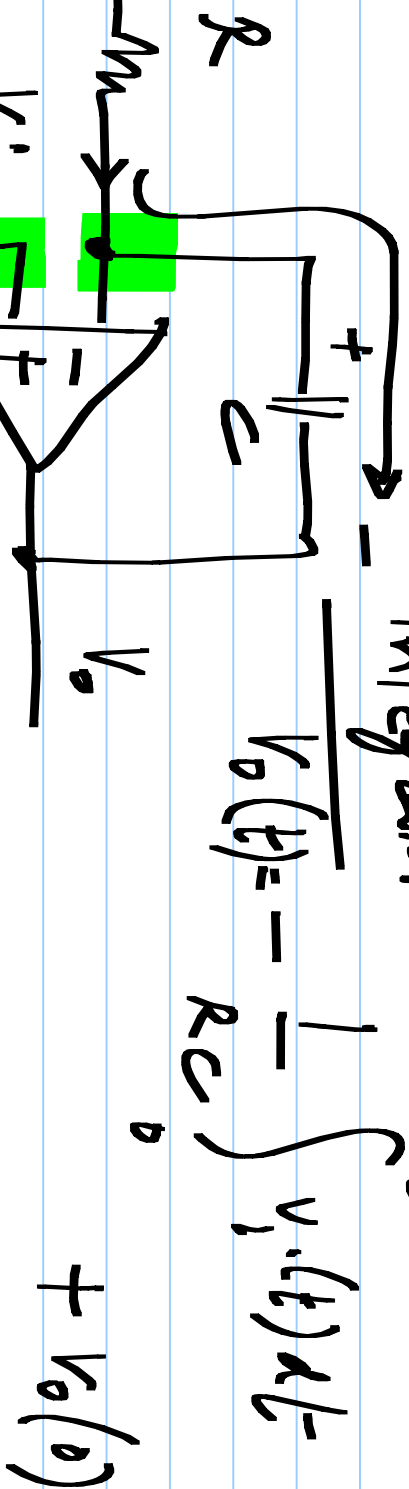
$$V_o(t) = -\frac{1}{R_C} \int V_i(t) dt + V_o(0)$$







+ $V_o(0)$

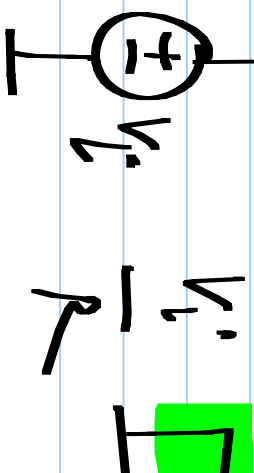

Constant V_i


$$\frac{dV_o}{dt} = -\frac{V_i}{R_C}$$

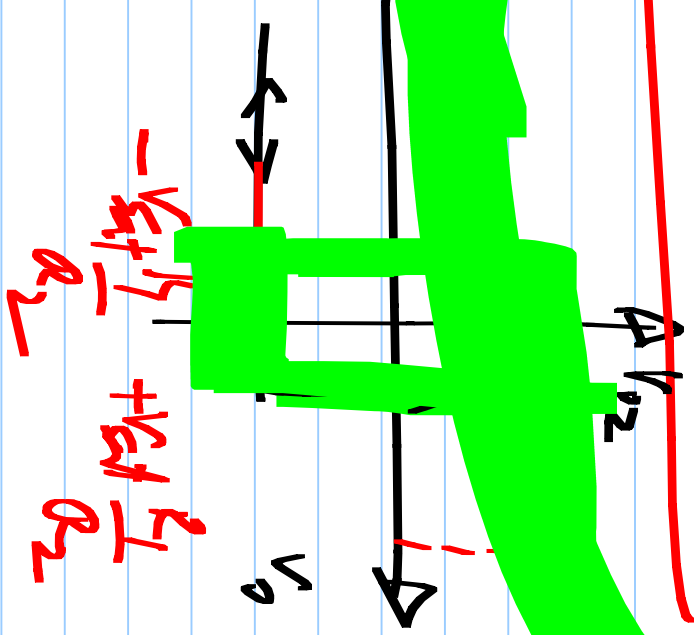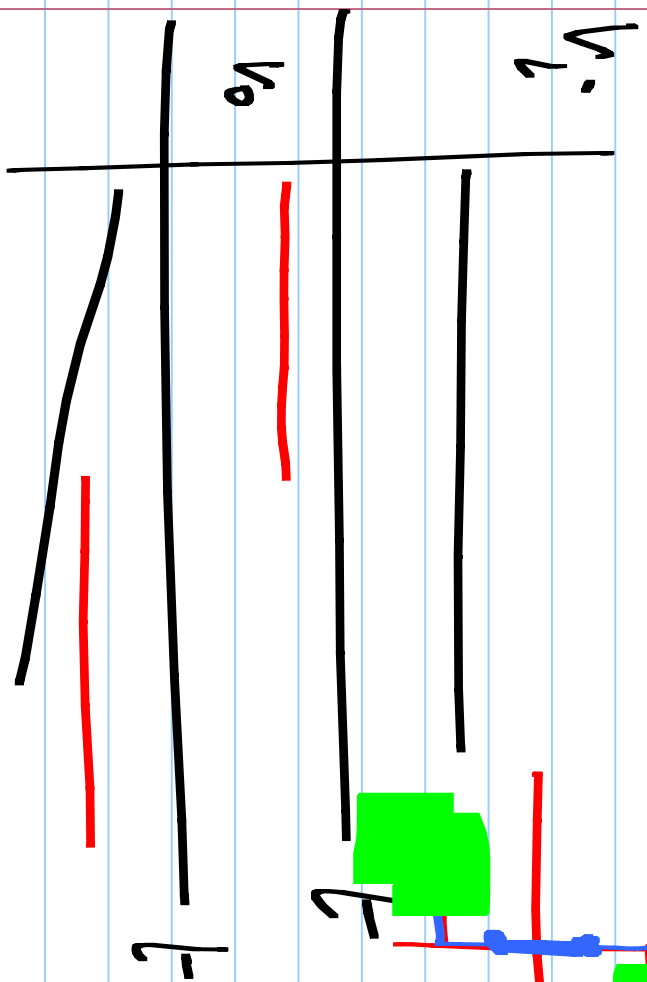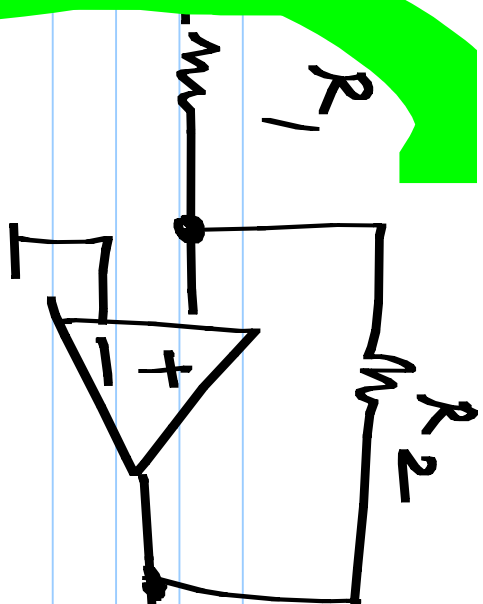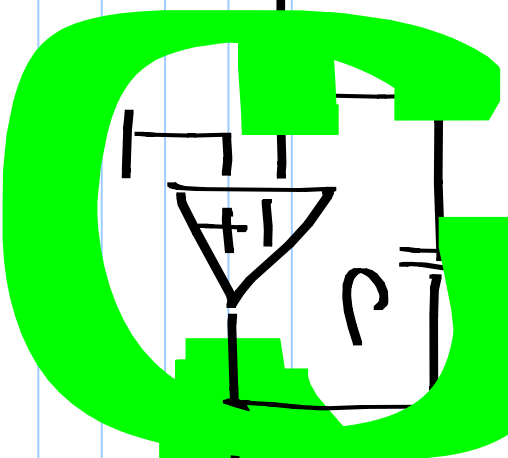

Initially V_o (o/p of the integrator) : large & the

$\rightarrow V_{o2}$ (o/p of the Schmitt trigger) = V_{sat}

Oscillator

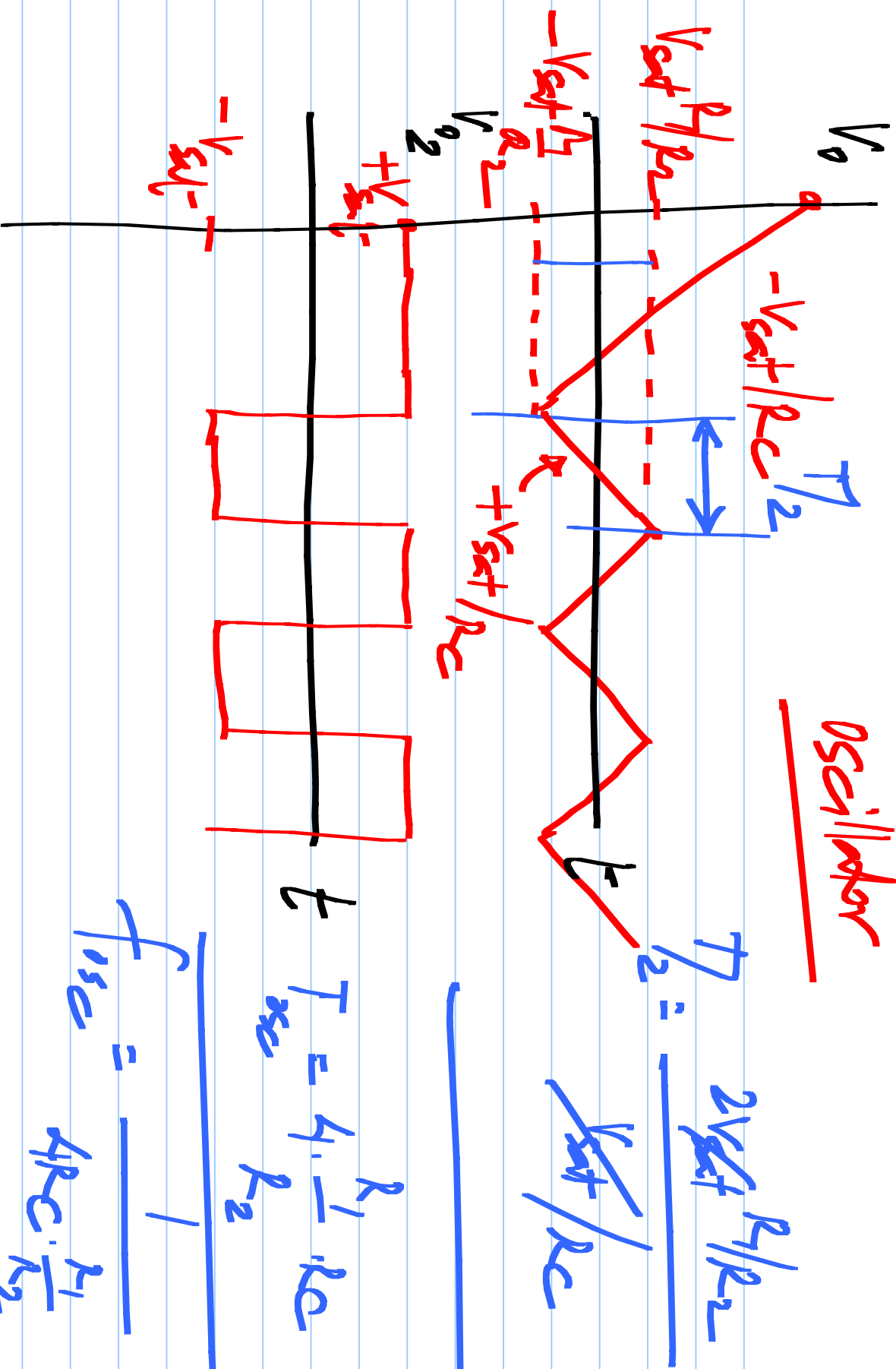

$$T = \frac{2V_{sat} R_1/R_2}{V_{sat}/R_C}$$

$$T_{osc} = 4 \cdot \frac{R_1}{R_2} \cdot R_C$$

$$f_{osc} = \frac{1}{4R_C \cdot \frac{R_1}{R_2}}$$