
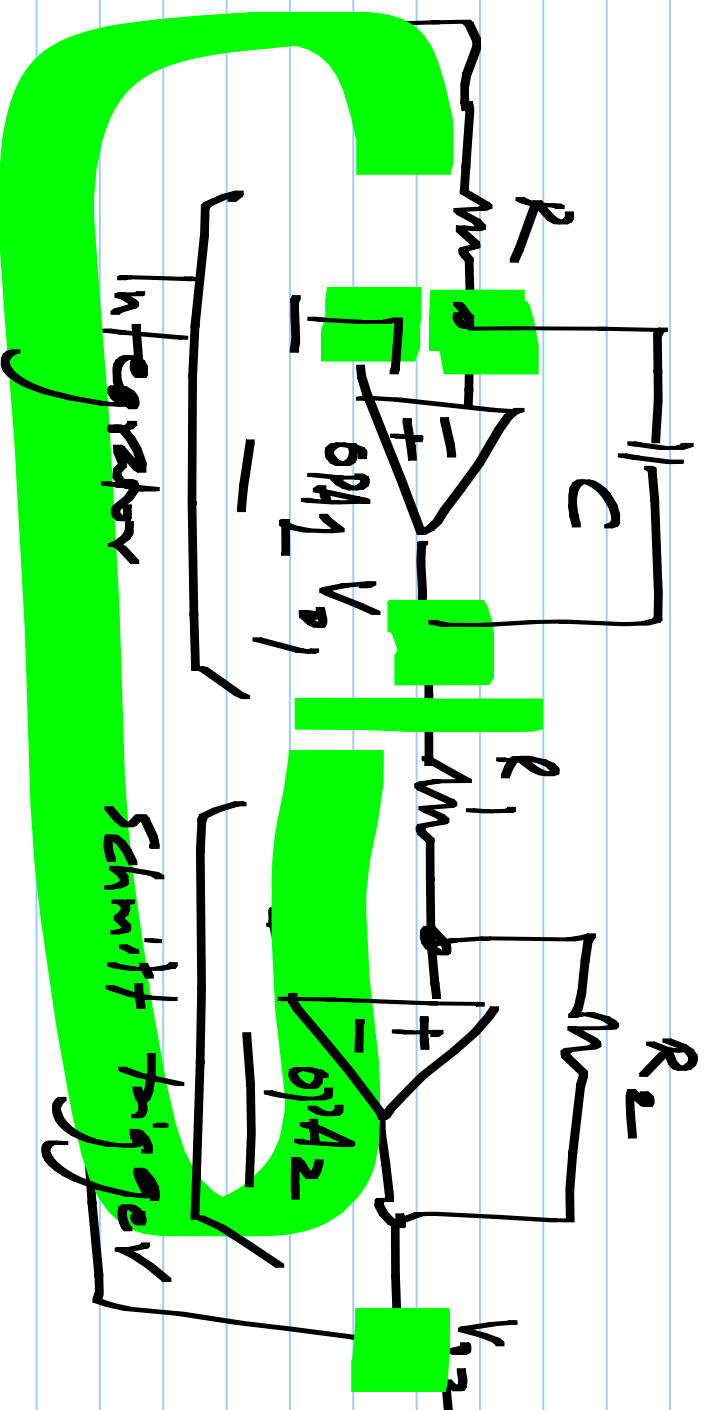


EE2019

Schmitt-trigger oscillator

2/2/2018

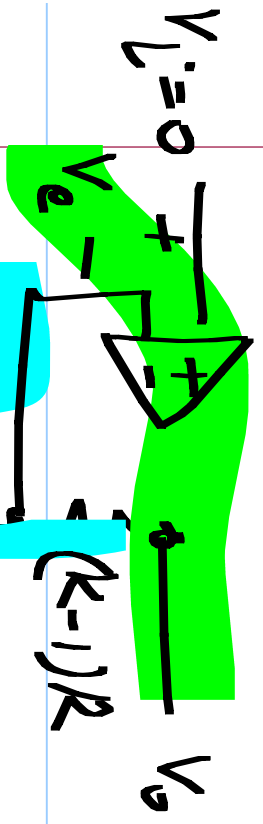






$$V_e = -\frac{V_o}{K}$$


$$V_o = -KV_e$$

offset voltage

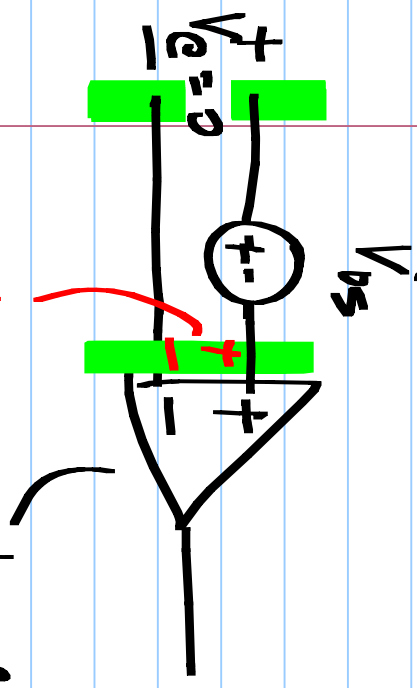

1 μV output
w/ no offset

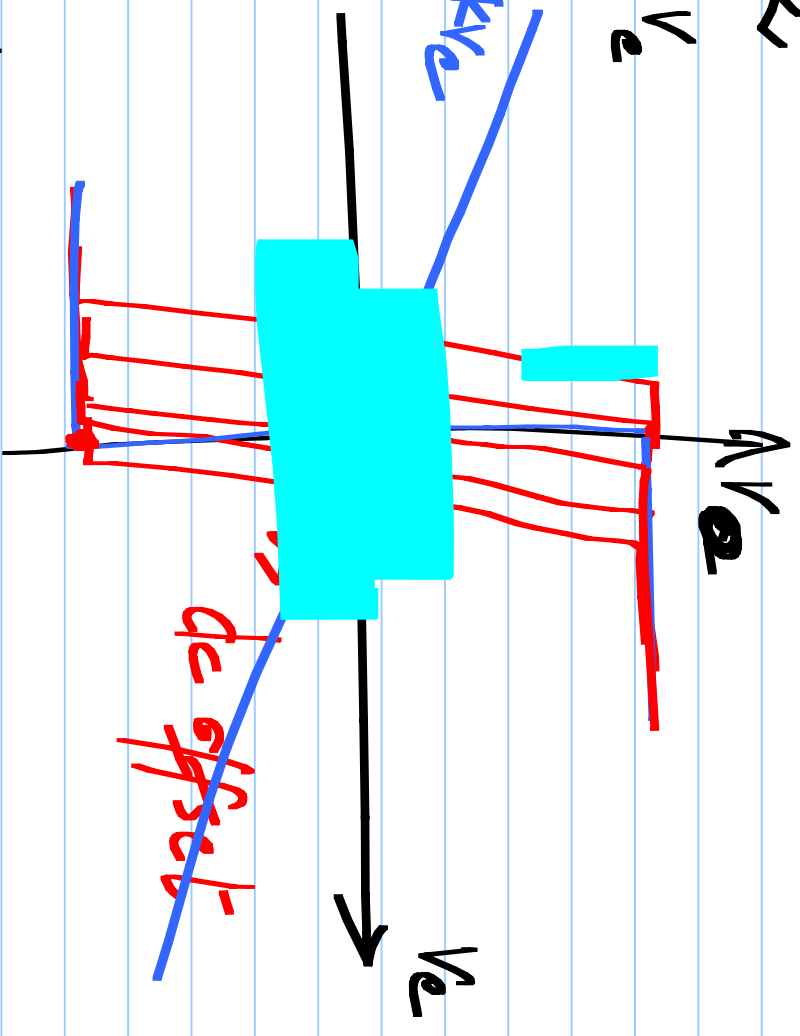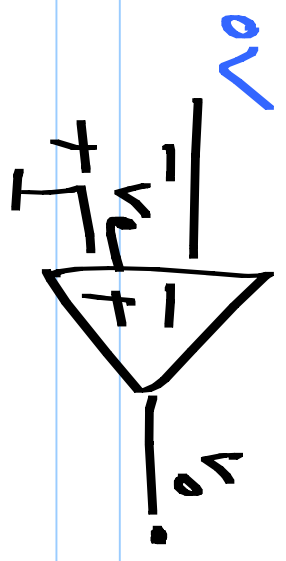

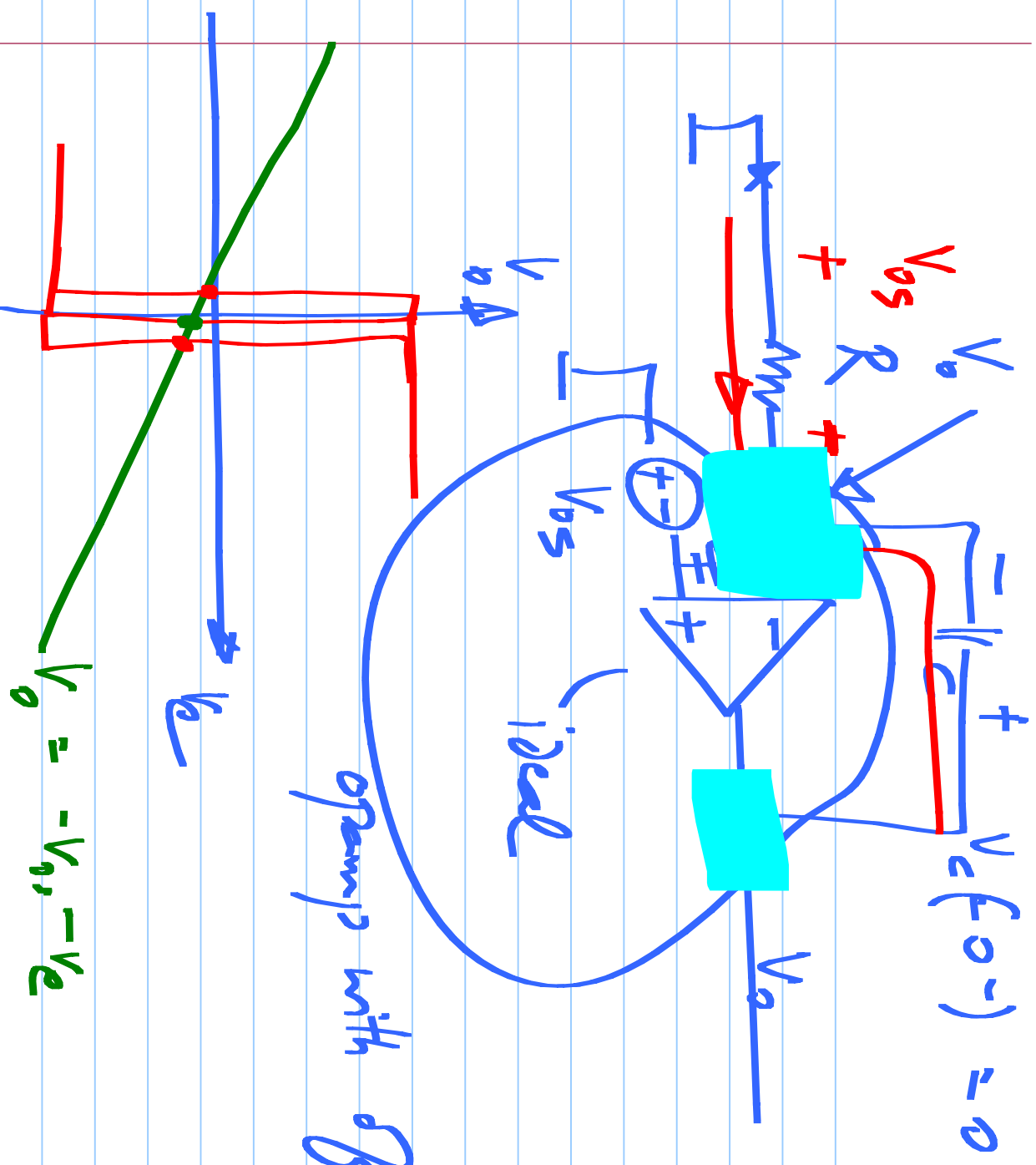

$$V_e(f=0^-) = 0$$

$$V_e = -V_o - V_{os}$$


$$V_o = -V_{os} - V_e$$


opamp with offset



$$V_o = -V_{os} - V_e$$

$$-V_{SS} < k V_{\text{caswl}} < V_{DD}$$

V_{caswl}

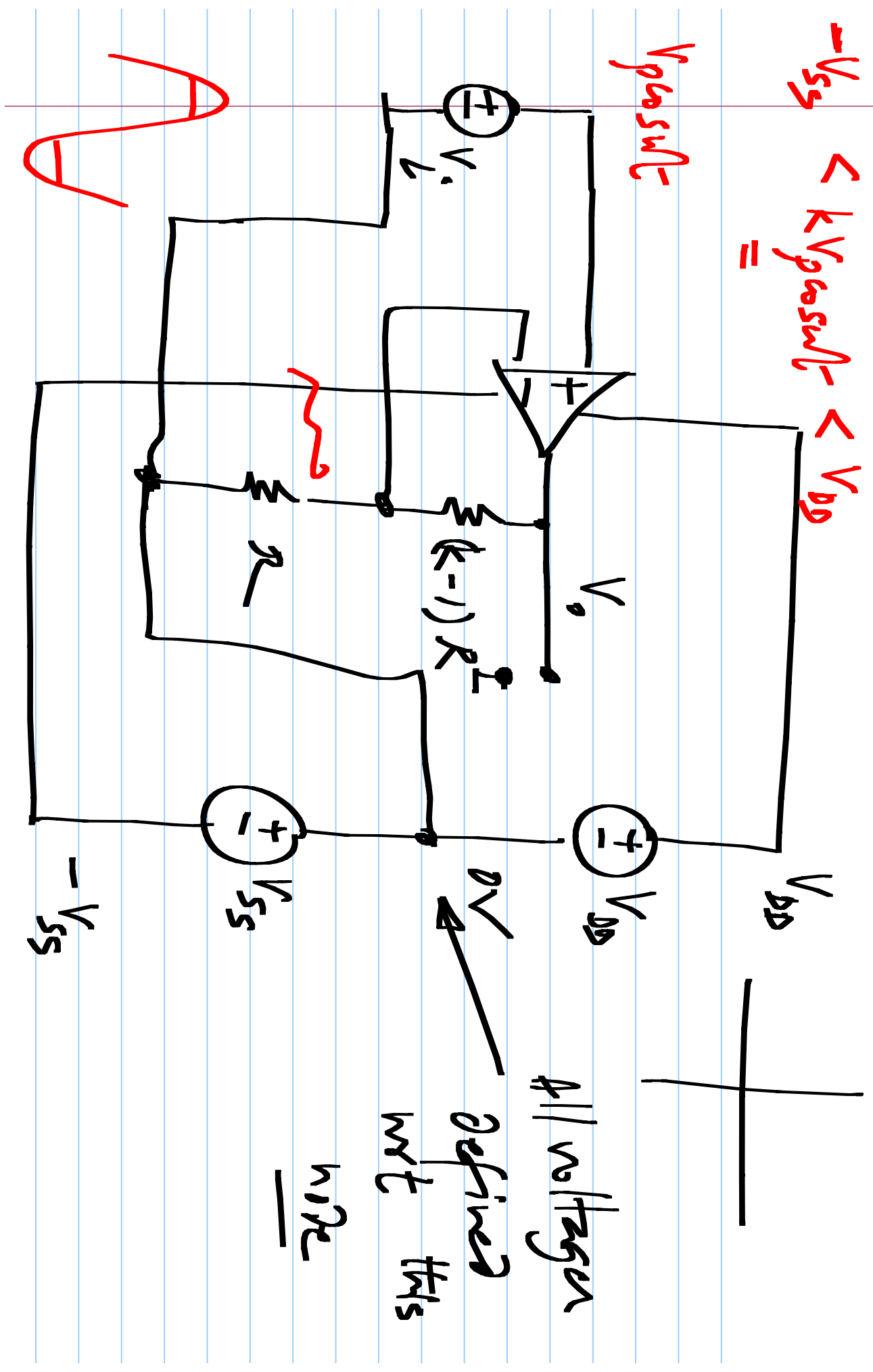


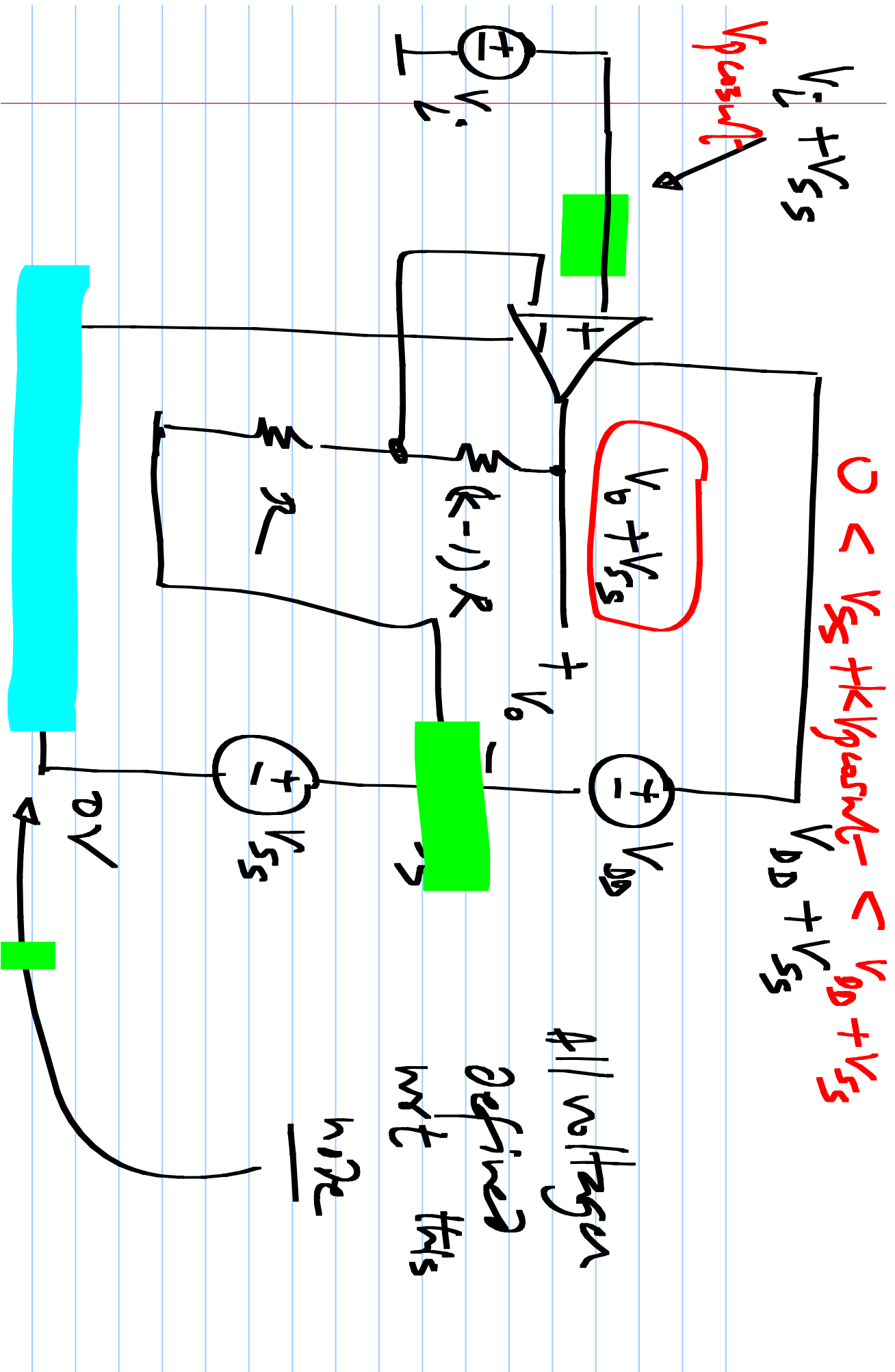

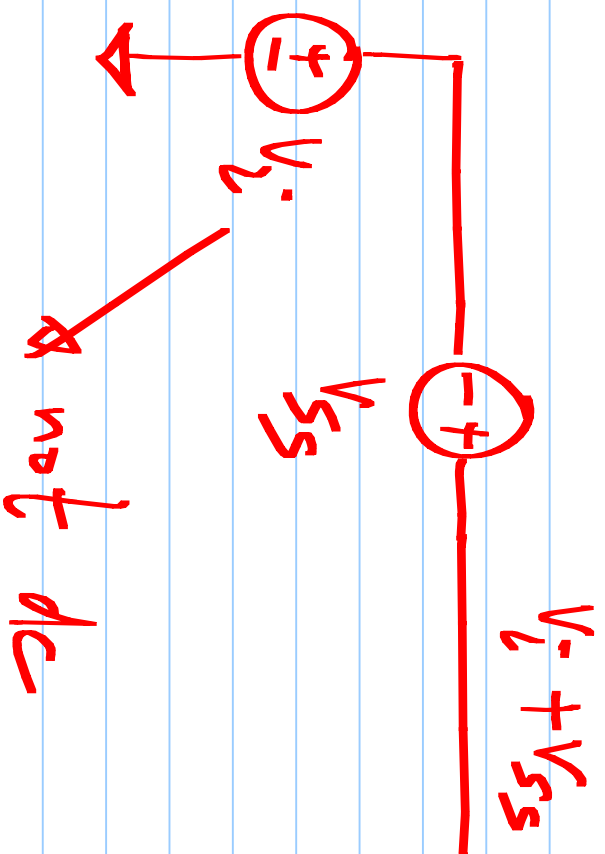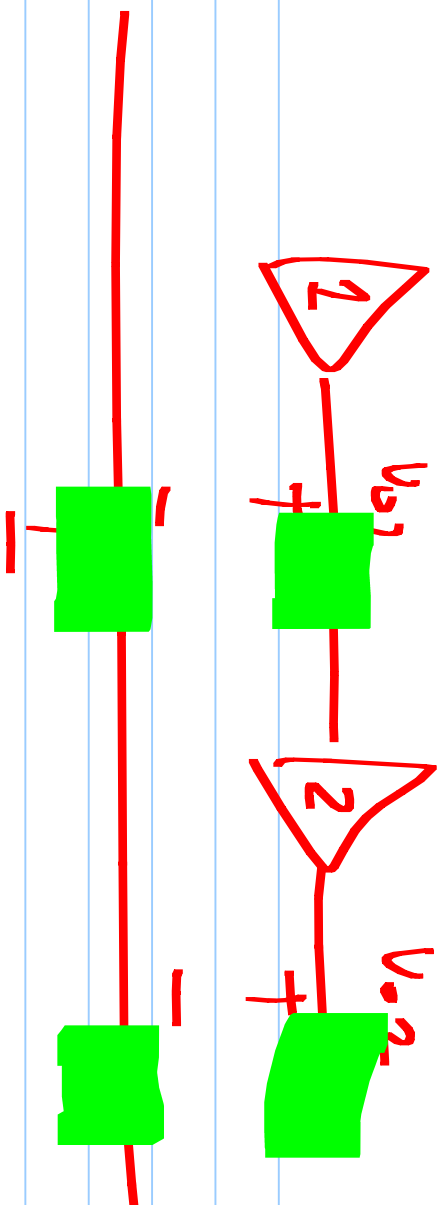

$V_{pcos \omega t}$

$\omega > 0$

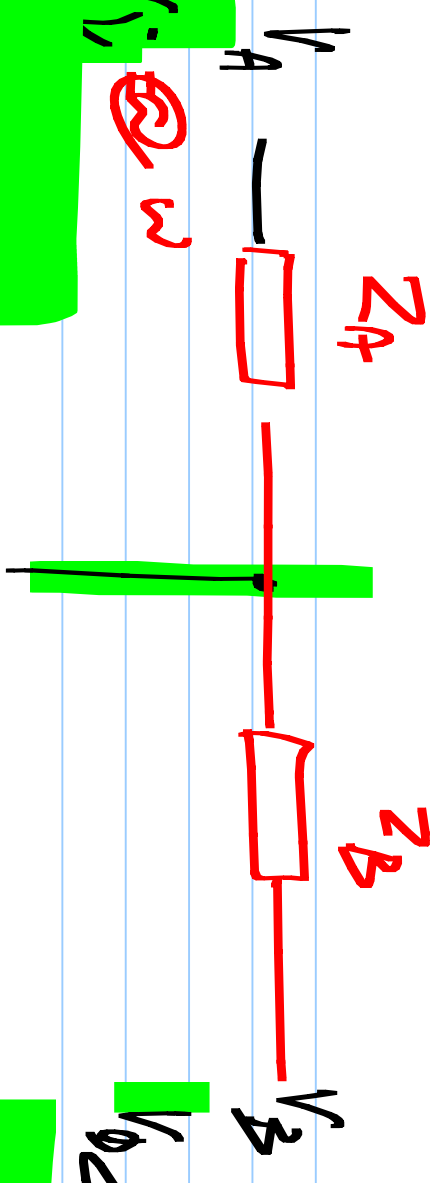


$$\begin{aligned}
 &|Z_A(j\omega)| < |Z_B(j\omega)| \\
 &|Z_A(0)| \gg |Z_B(0)|
 \end{aligned}$$

$$\alpha V_A + \beta V_B = \frac{Z_B(j\omega)}{Z_A(j\omega) + Z_B(j\omega)} V_A + \frac{Z_A(0)}{Z_A(0) + Z_B(0)} V_B$$

$$\frac{1}{\omega C} \ll R$$

$$\frac{Z_A}{C} \quad \frac{Z_B}{L}$$

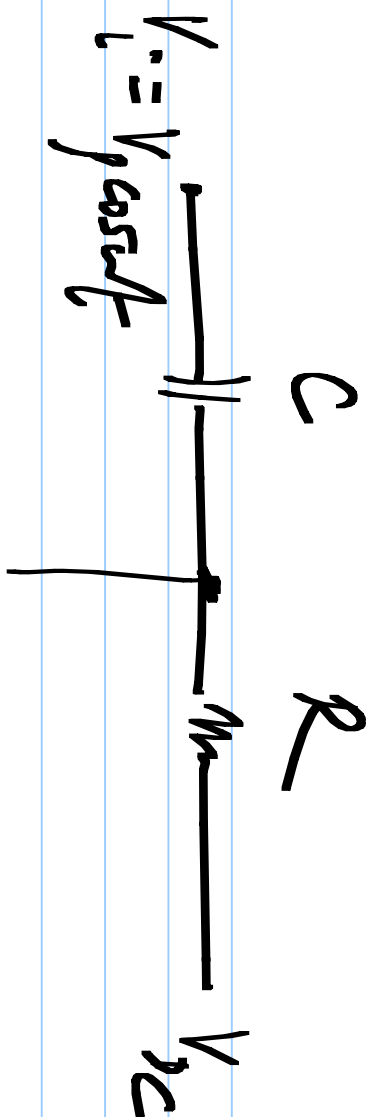

$$\approx V \cos \omega t + V_{DC} \quad \text{if} \quad \frac{1}{\omega C} \ll R$$

Add dc & ac : ac coupling network

