
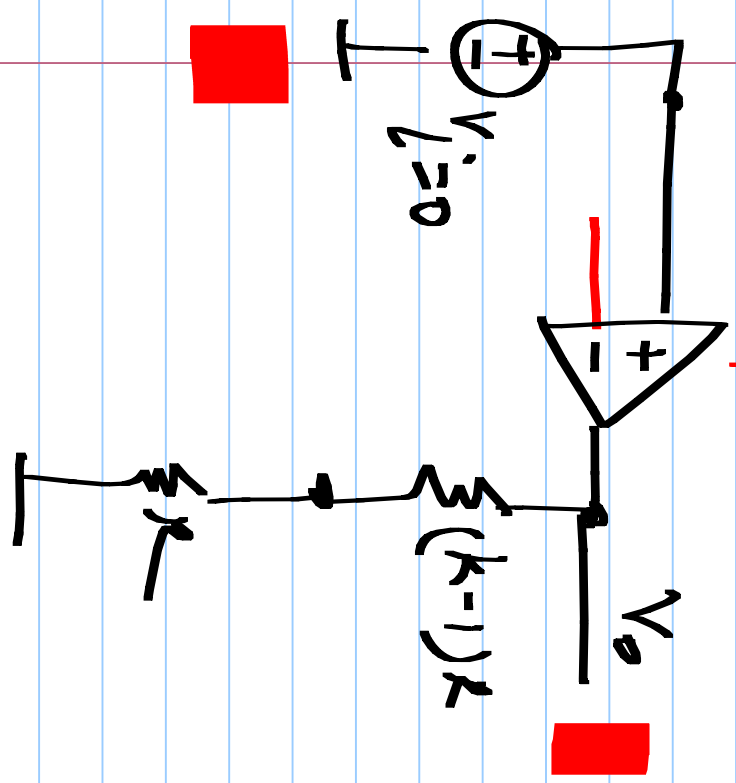


EE 2019

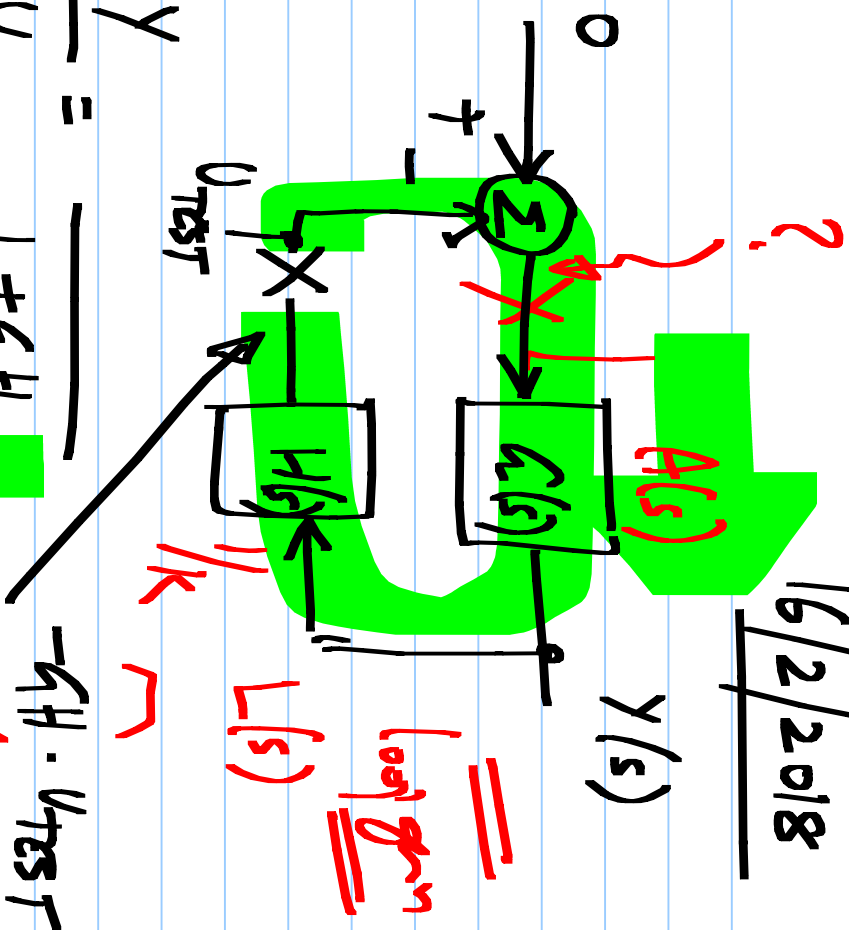Closed loop gain: $\frac{V_o}{V_i}$
Loop gain: $G = A(s)$



16/2/2018




$$\frac{Y}{V} = \frac{1}{1 + GH}$$

$$\frac{Y}{V} = \frac{1}{1 + GH}$$

Loop gain

$$\frac{Y}{V} = \frac{G}{1 + GH}$$

$$|GH| \gg 1 \quad \frac{Y}{V} \approx \frac{1}{H}$$

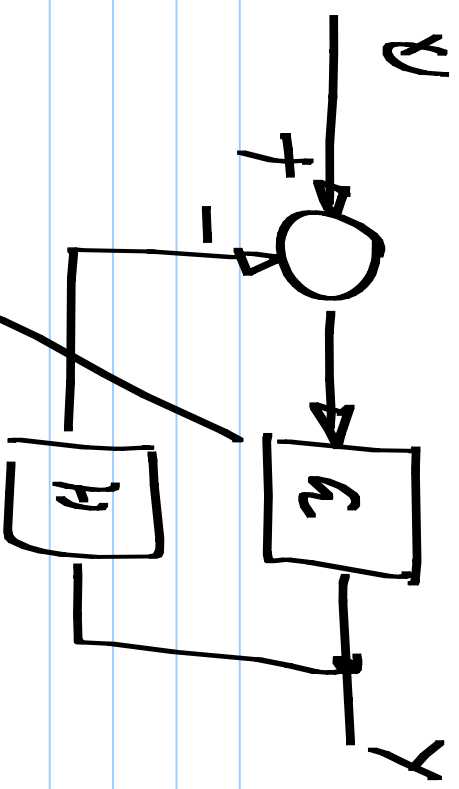


Forward path: Active devices



Feedback path

(Transistors)

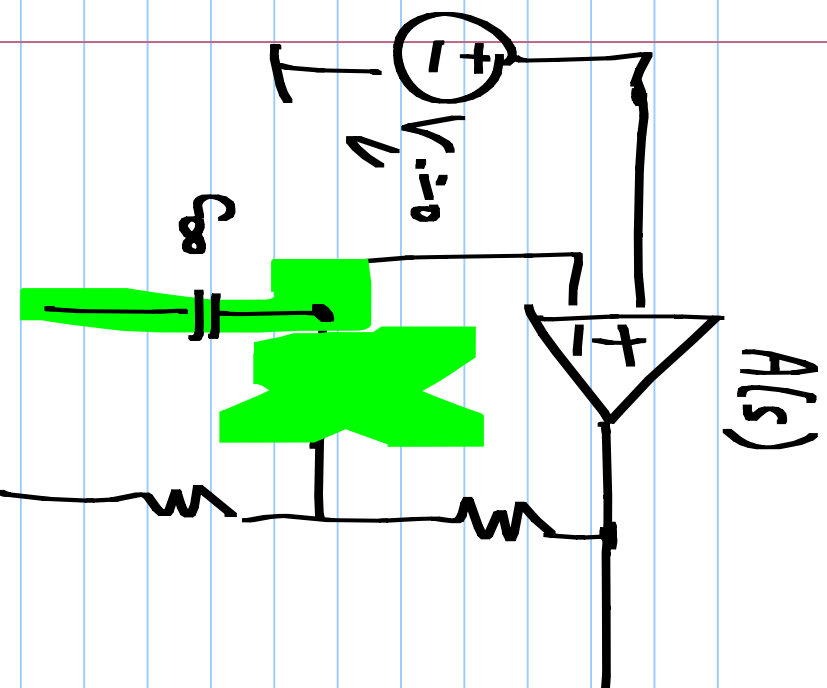
$$\frac{V_{\text{error}}}{V_{\text{TEST}}} = - \frac{A(s)}{1} \quad \text{loop gain}$$



break the loop for dc
not for ac

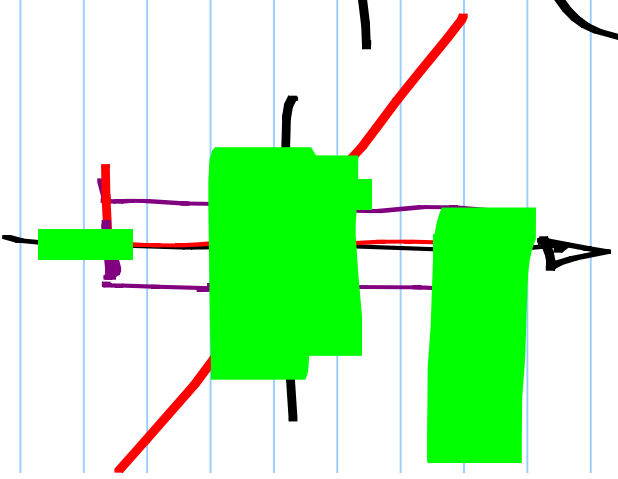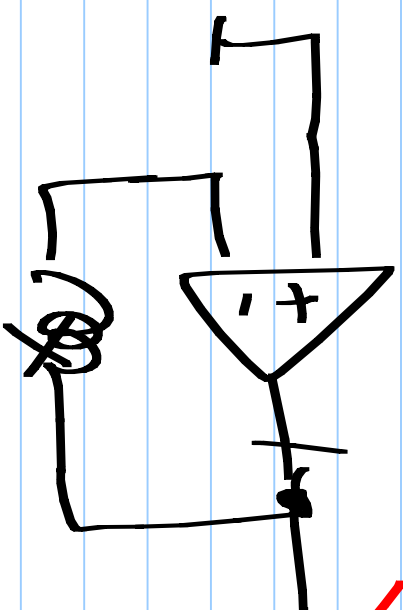


$$L(s) = \frac{A(s)}{k}$$

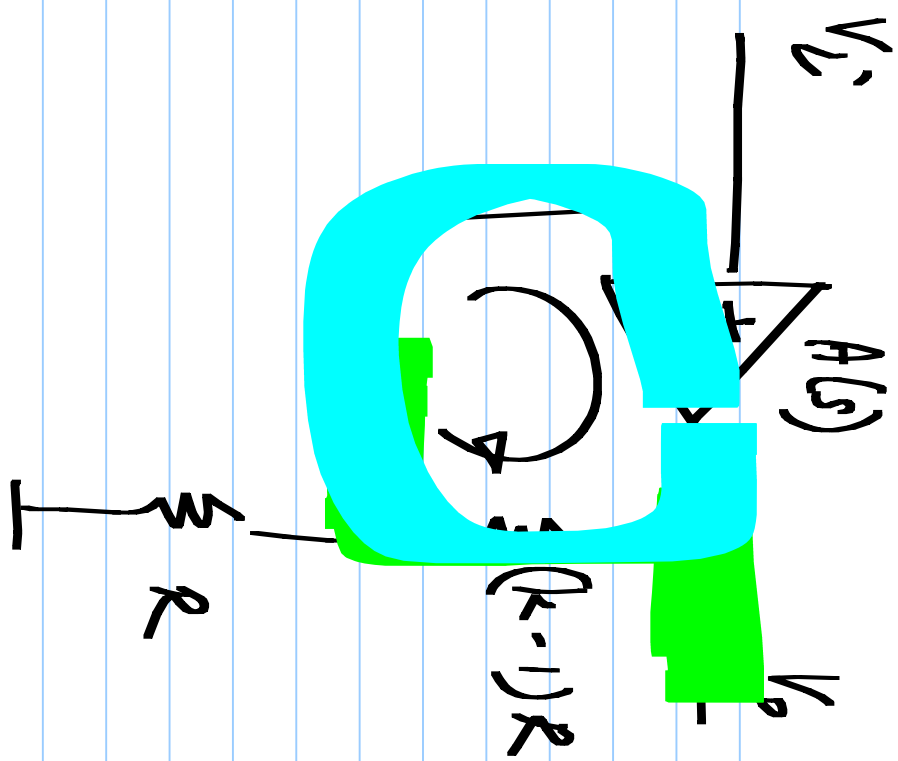

$$\frac{V_b}{V_c} = \frac{1}{1 + kH}$$
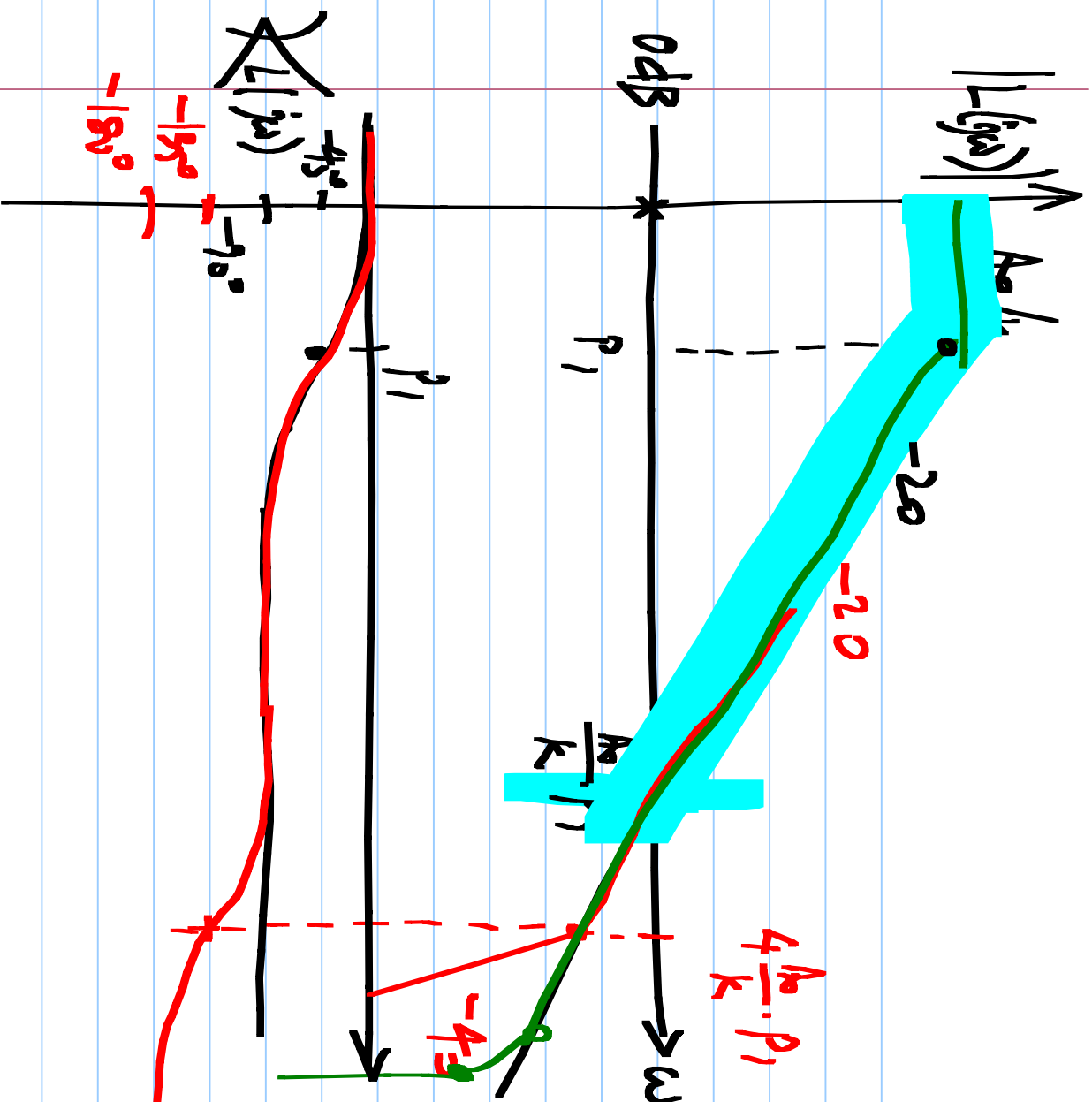
$$\frac{V}{V_c} = \frac{k}{1 + kH} = \frac{1}{\frac{1}{k} + H}$$



1st order

$$L(s) = \frac{A_0}{k} \cdot \frac{1}{1 + \frac{s}{p_1}}$$

2nd order

$$L(s) = \frac{A_0}{k} \cdot \frac{1}{(1 + \frac{s}{p_1})(1 + \frac{s}{p_2})}$$

$$Z = 1$$

$$\frac{p_2}{p_1} = 4 \left(\frac{A_0}{k} + 1 \right)$$

3rd order:

$$L(s) = \frac{K}{k \left(1 + \frac{s}{p_1}\right)^3}$$

of $\frac{v_i}{v_n}$ in axes

for $\frac{K}{k} = 8$
