

EE2019

Stabilizing opamps (feedback amplifier)

27/2/2018


Freq. compensation



Dominant pole compensation

Unity gain compensated opamp: $A(s)$


Noninv. amp

$$L(s) = \frac{A(s)}{K}$$


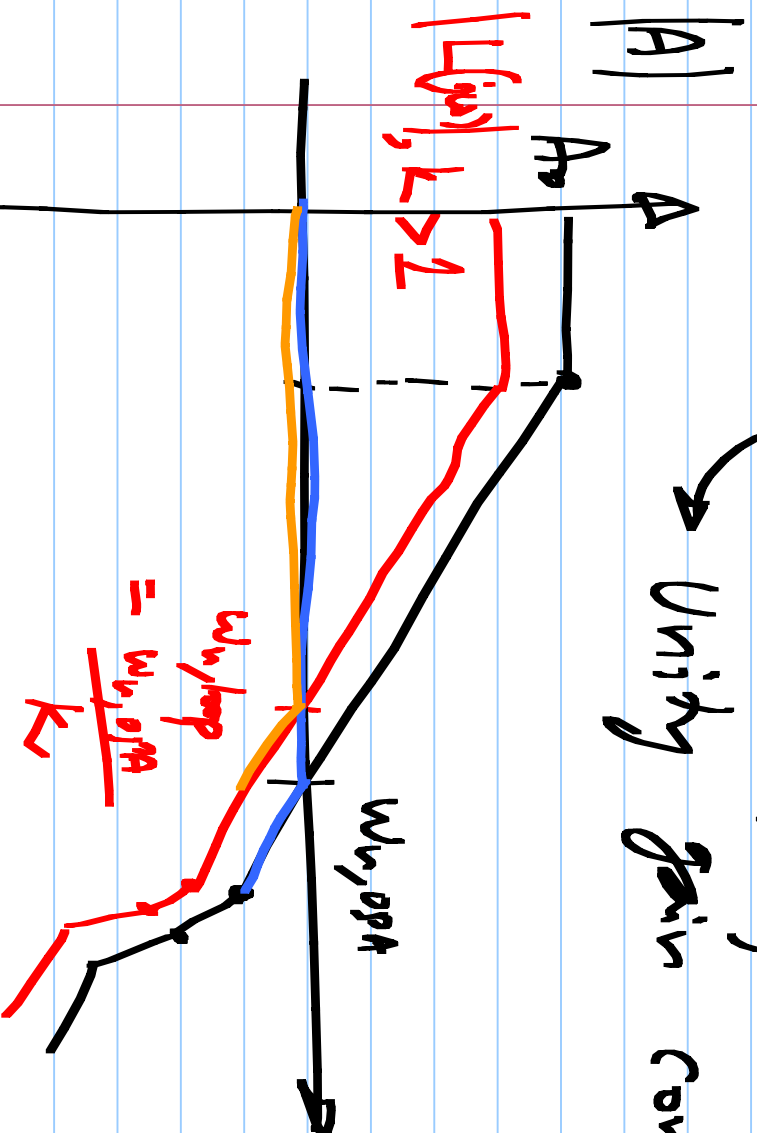


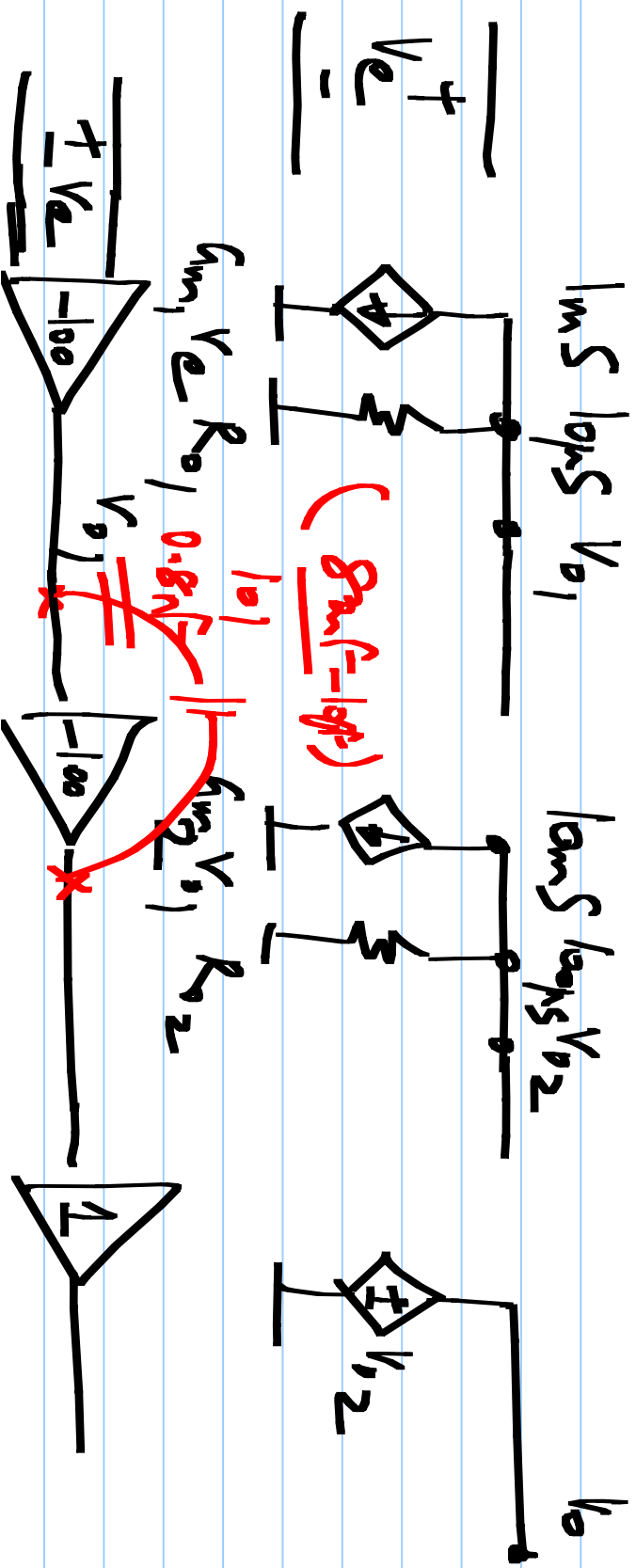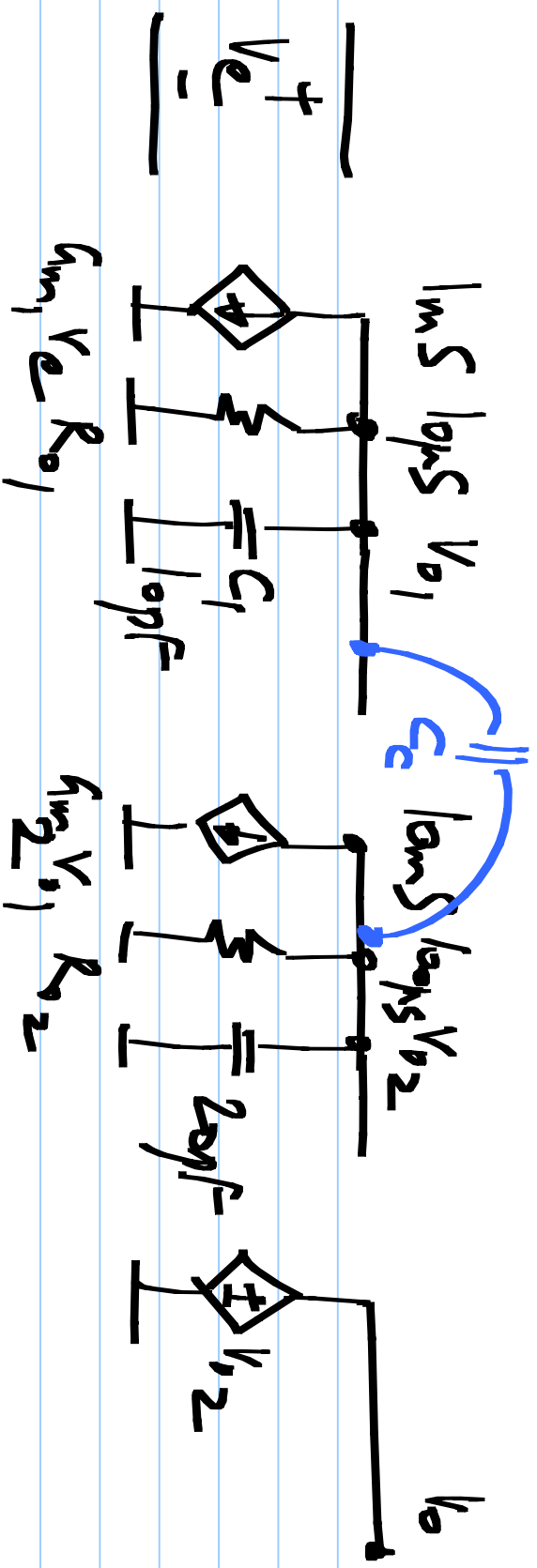

SC · V_{test}

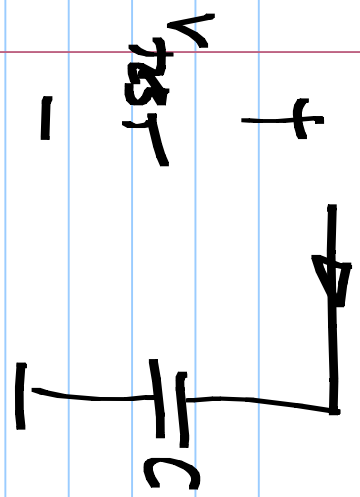


$$(1+A) V_x =$$

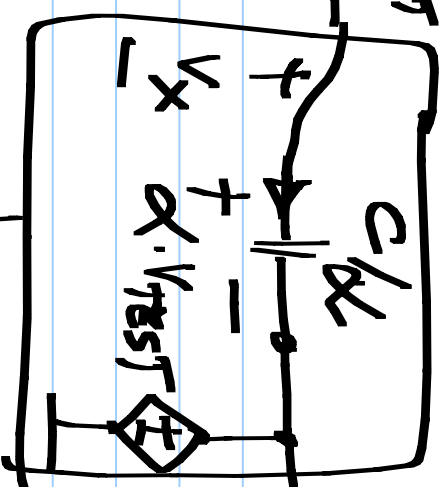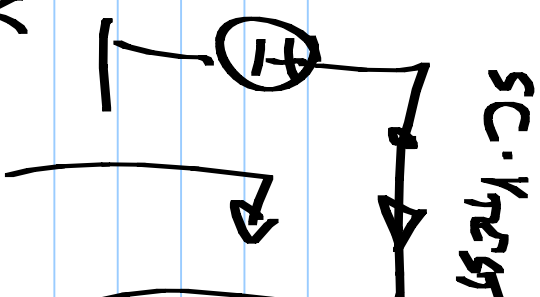

$\alpha > 1$


$$V_x(1-\alpha) < 0$$

SC · V_x

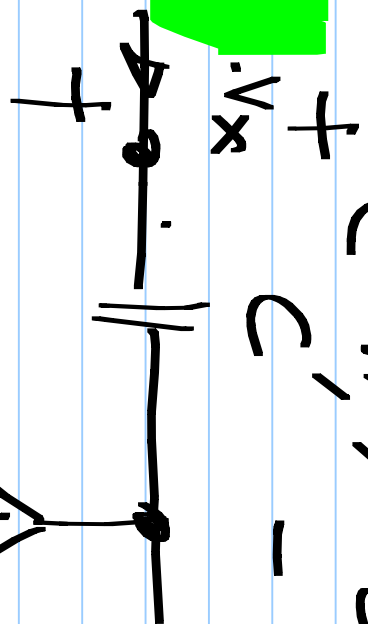


$$+ \alpha V_x$$

$$V_x \parallel V_x(1-\alpha)$$

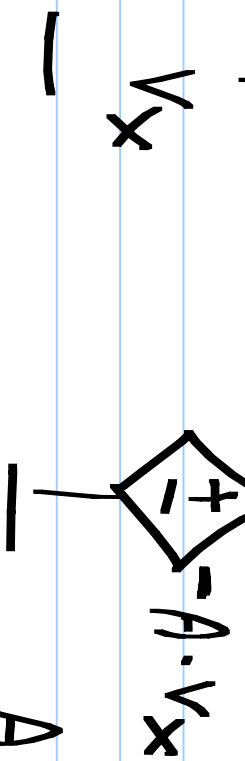



$A > 0$


Miller effect

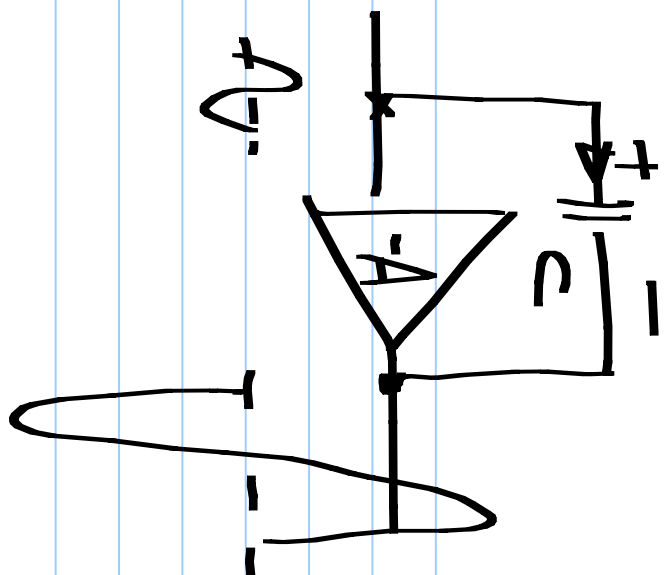

$$C(1+A)$$

≡

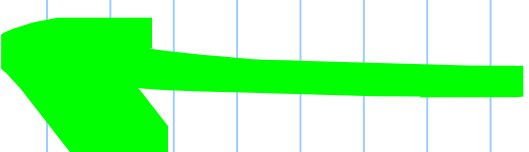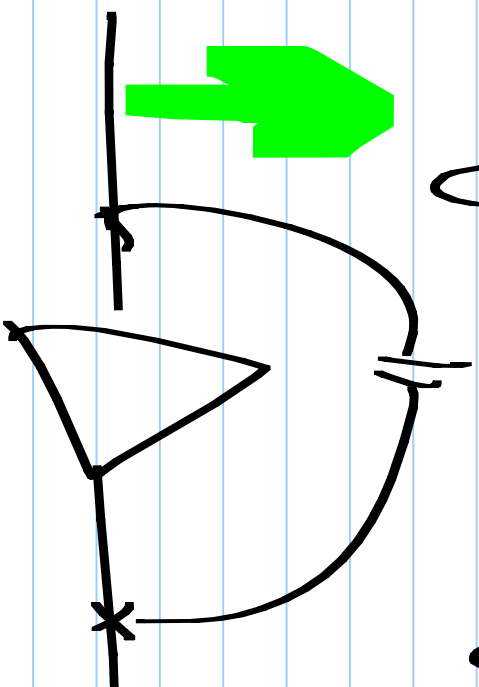

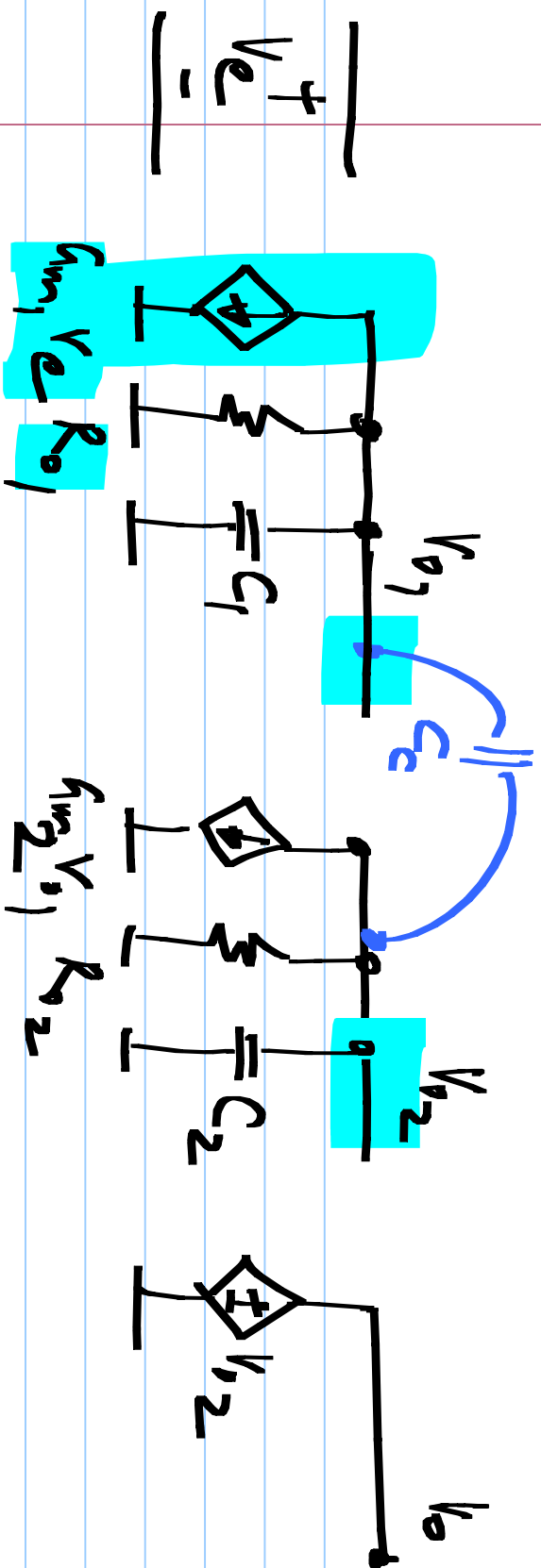

$$\begin{bmatrix} g_{m1} + s(C_1 + C_2) & -sC_2 \\ -sC_2 & g_{m2} + s(C_2 + C_2) \end{bmatrix} \begin{bmatrix} v_{o1} \\ v_{o2} \end{bmatrix} = \begin{bmatrix} -g_{m1}v_e \\ 0 \end{bmatrix}$$

$$V_{o2} = \frac{\begin{vmatrix} s(C_1 + C_2) + h_{o1} & -h_{m1}V_e \\ +h_{m2} - sC_2 & 0 \end{vmatrix}}{}$$

$$\begin{matrix} s \neq 0 \\ C_e = 0 \end{matrix} \quad \left| \begin{array}{cc} s(C_1 + C_2) + h_{o1} & -sC_2 \\ h_{m2} - sC_2 & s(C_1 + C_2) + h_{o2} \end{array} \right| + \frac{h_{m2}}{C_e}$$

Zero @

$$\frac{V_{o2}}{V_e} = \frac{s^2(C_1C_2 + C_2C_2 + C_2C_1) + s[C_2(h_{m2} + h_{o2} + h_{o1}) + C_1h_{o2} + C_2 \cdot h_{o1}] + h_{o1}h_{o2}}{h_{m1}(h_{m2} - sC_2)}$$

with $C_c = 0$, polar @ $-\frac{C_{o1}}{C_1}$, $-\frac{C_{o2}}{C_2}$

with $C_c \neq 0$, ?

$-b \pm \sqrt{b^2 - 4c}$

$$ax^2 + bx + c = 0$$

x_1, x_2

$$ax_2^2 + bx_2 + \cancel{c}$$

$x_2 = \left\{ b, -\frac{b}{a} \right\}$

$|x_2| \gg |x_1|$

$$ax_1^2 + bx_1 + c$$

$x_1 = -\frac{c}{b}$

X