

EE2019


$C_c \gg C_1$


8/3/2018

$$p_2 = \frac{g_{m2} \cdot \frac{C_c}{C_1 + C_c}}{C_2 + \frac{C_c \cdot C_1}{C_c + C_1}}$$

$$\tan^{-1} p_2 = \beta_M$$

$$p_2 \approx \frac{g_{m2}}{C_2 + C_1}$$

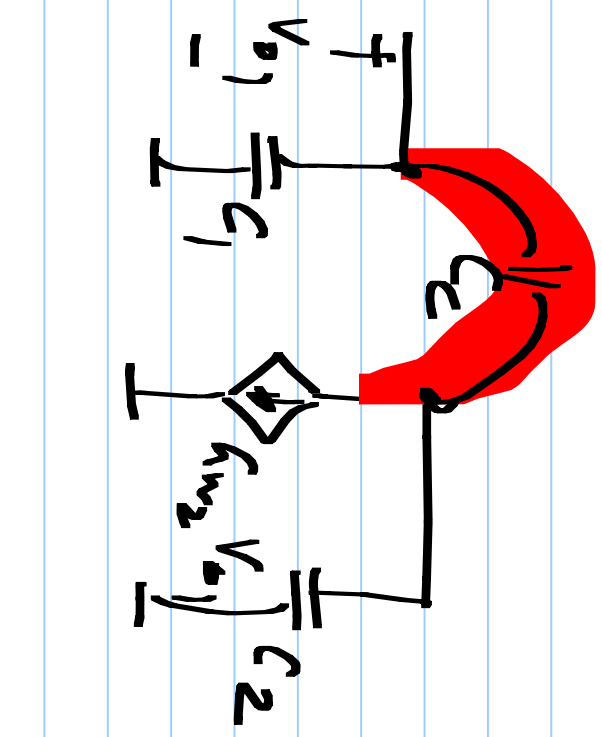

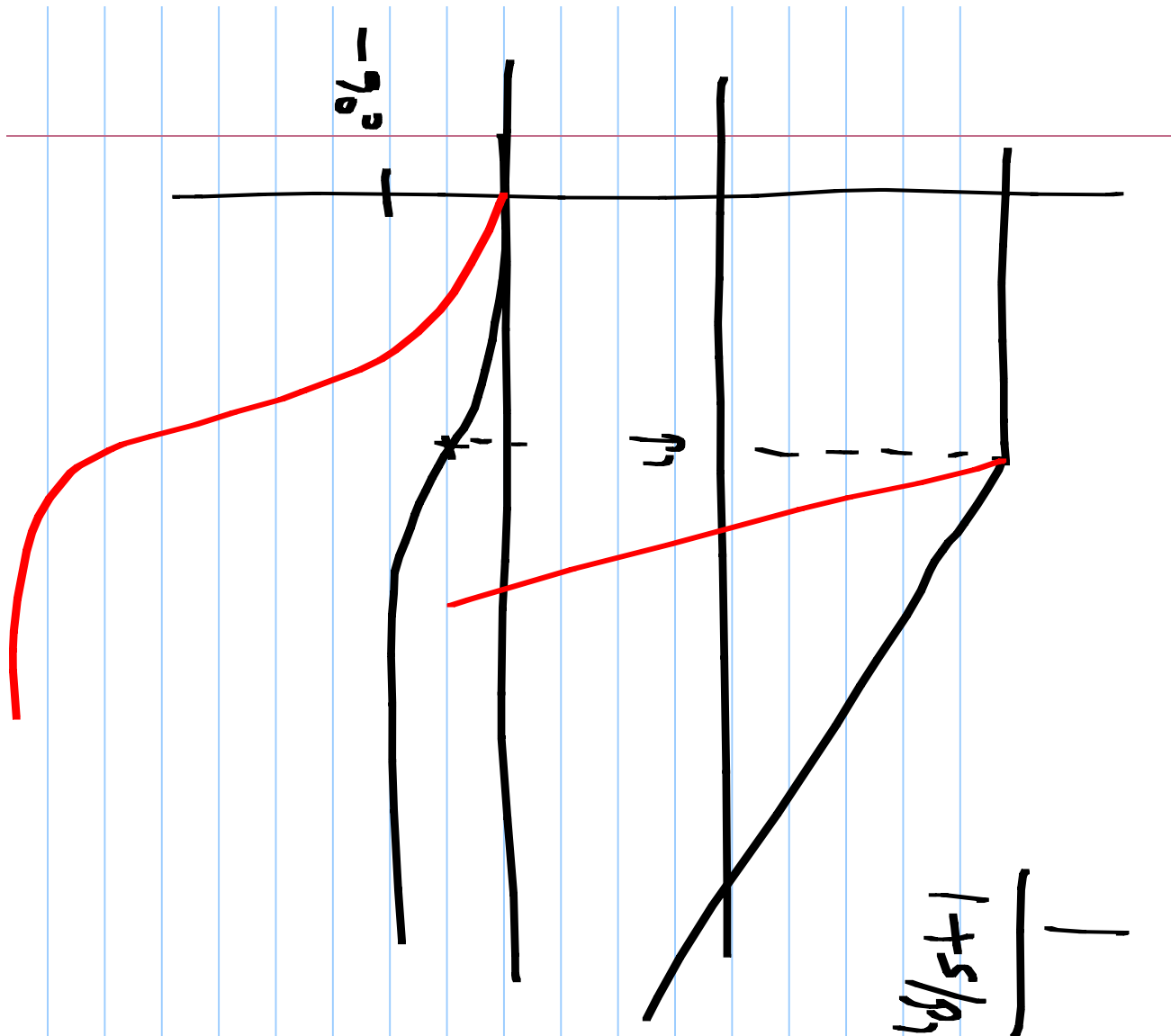

$|A(s)| \uparrow$


$A_0$

$\omega \rightarrow \infty$


$A_0 \rightarrow \infty$

$A(s)$
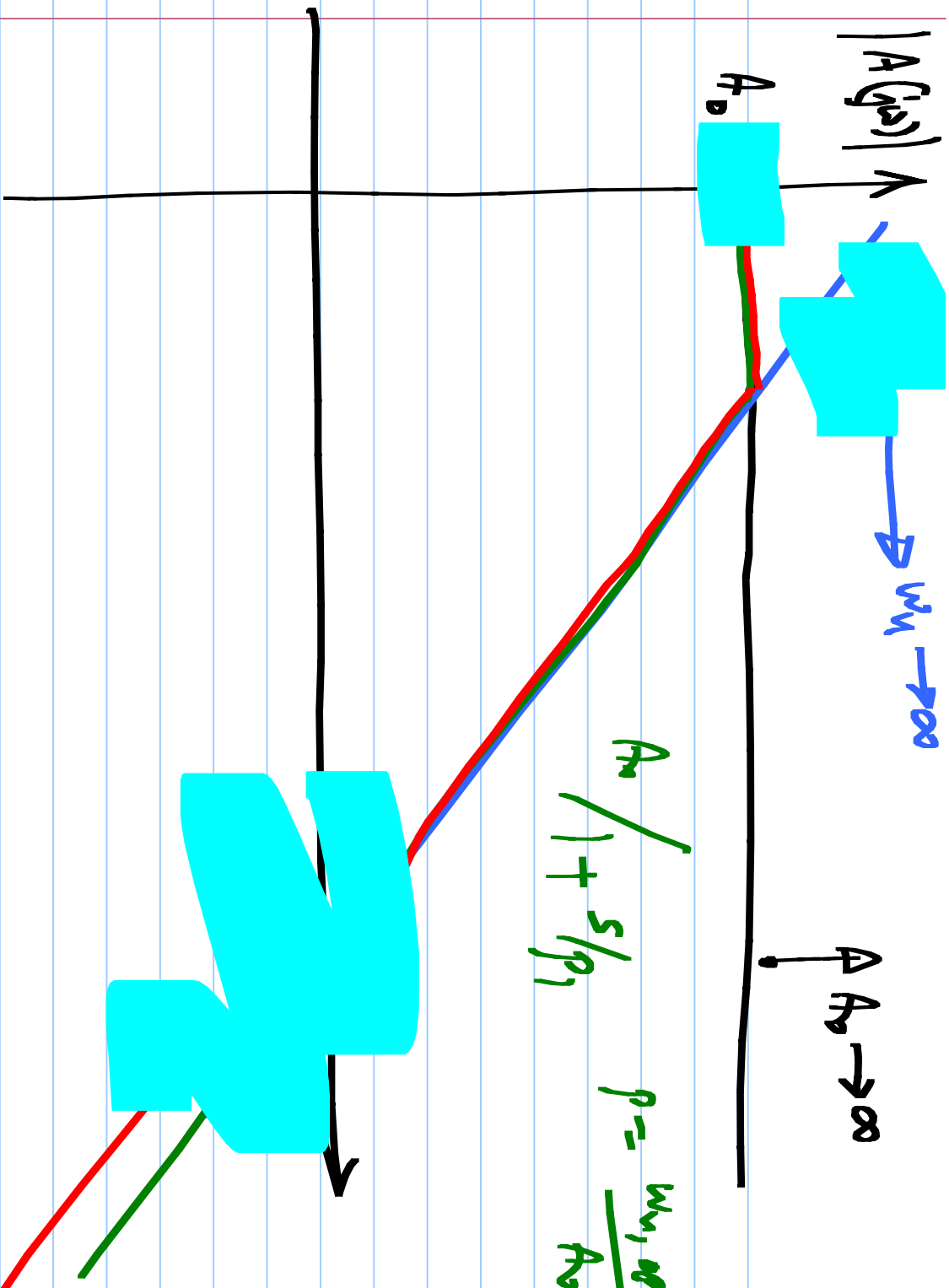
$$A_0 / (1 + s/p_1) \quad p_1 = \frac{\omega_{n,0A}}{A_0}$$






Battery voltage

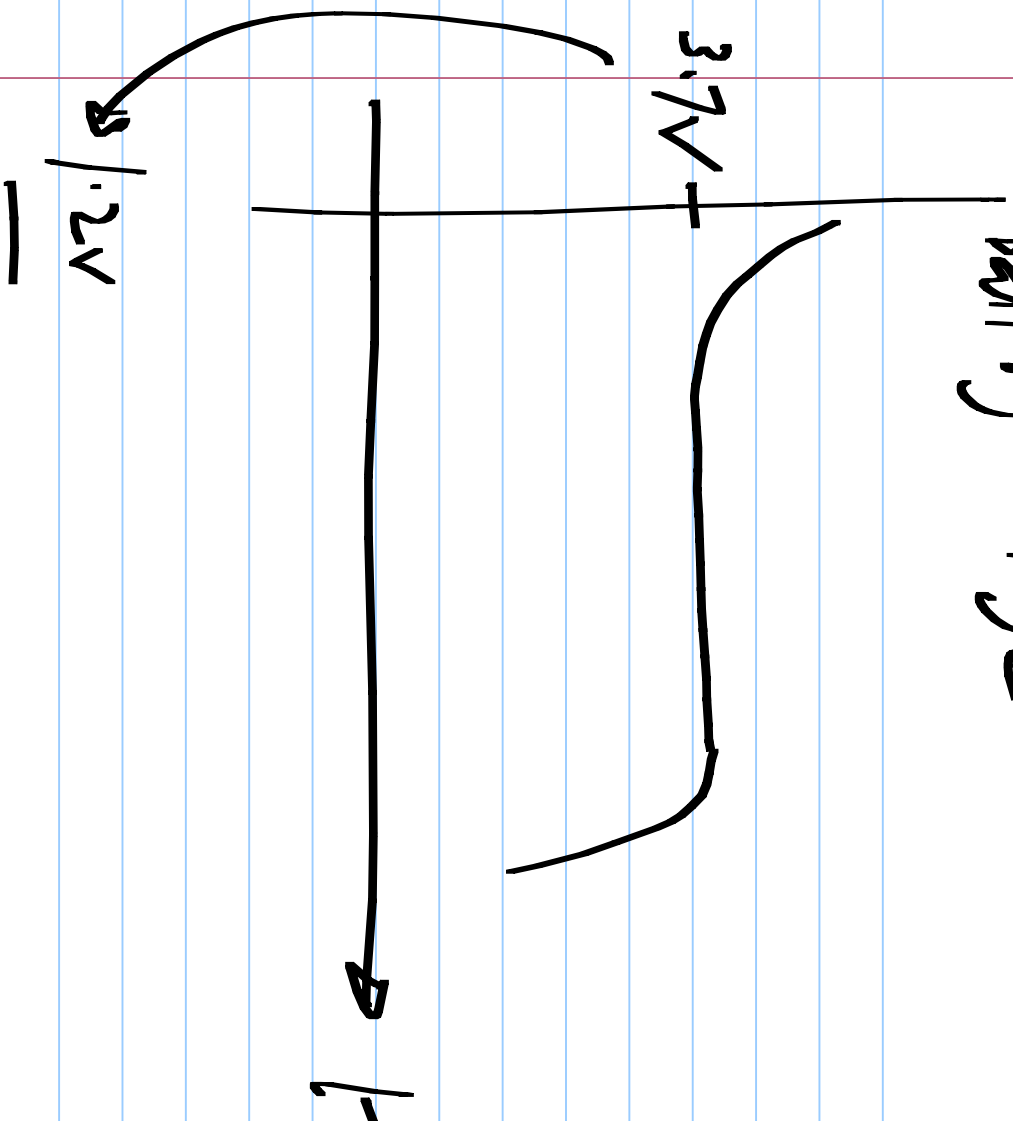

generate  
different voltages  
from a single voltage  
Regulate them  
accurately

Power management  
system

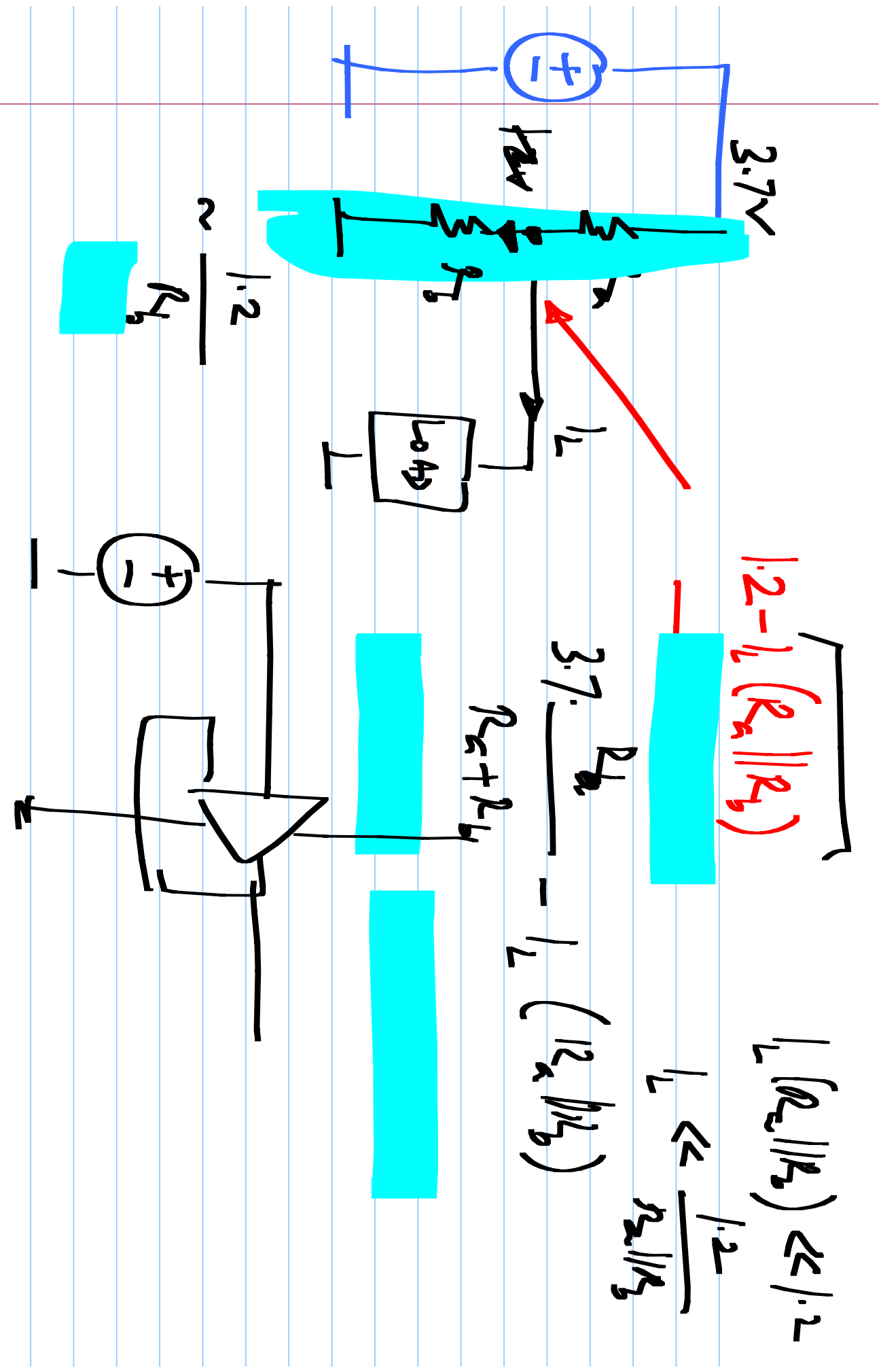


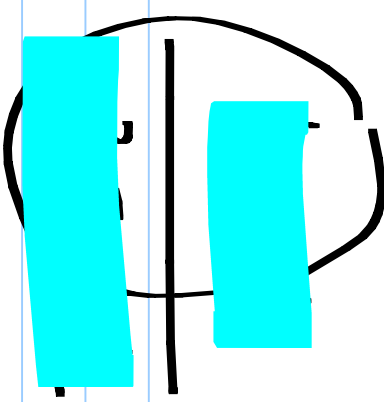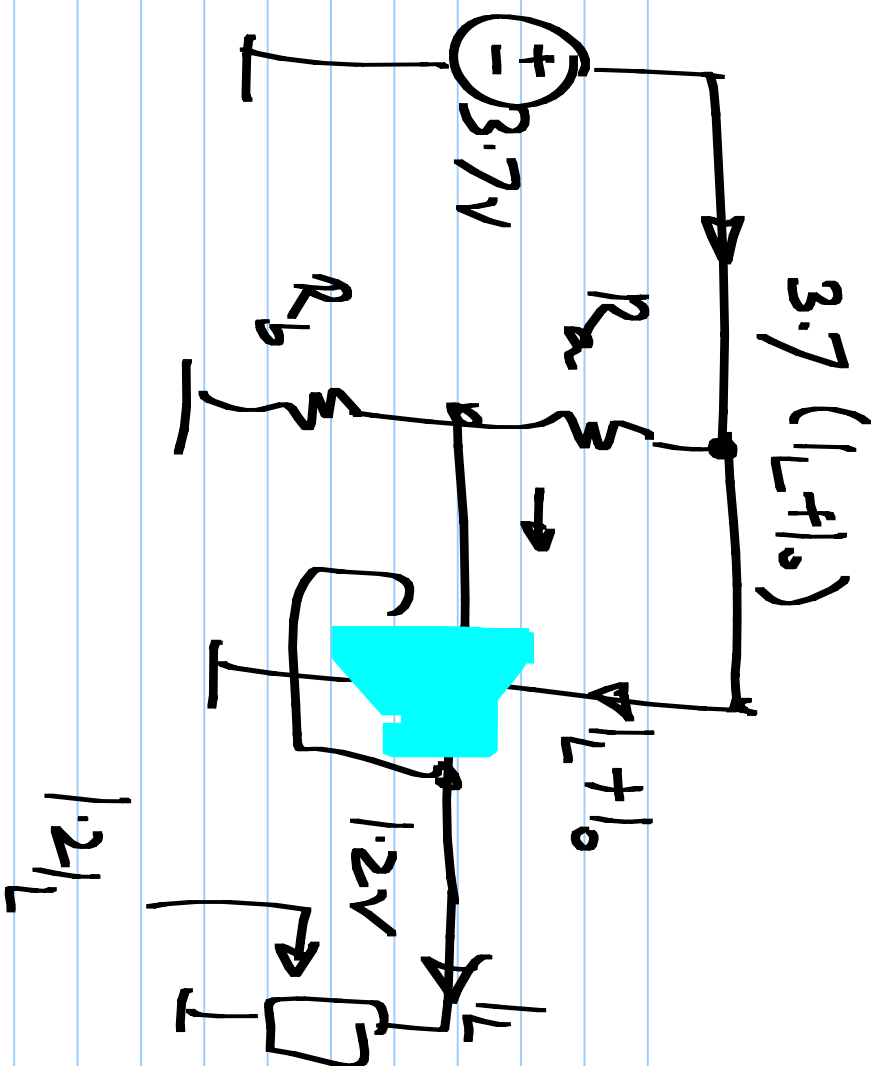


Use lossless components




Ideal switch linear

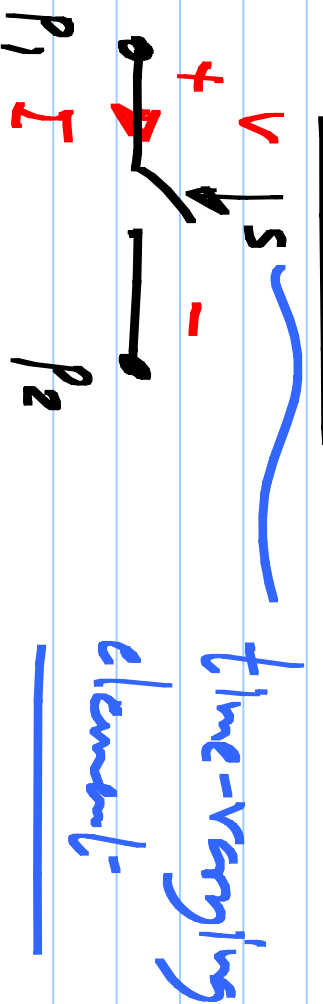



$s=1$   $V$   
Short

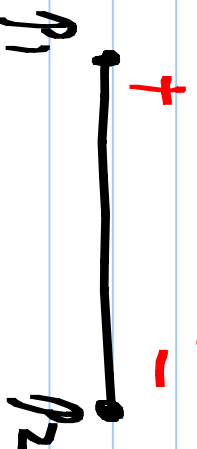



$s=0$   $V$   
 $p_1$   $p_2$  open

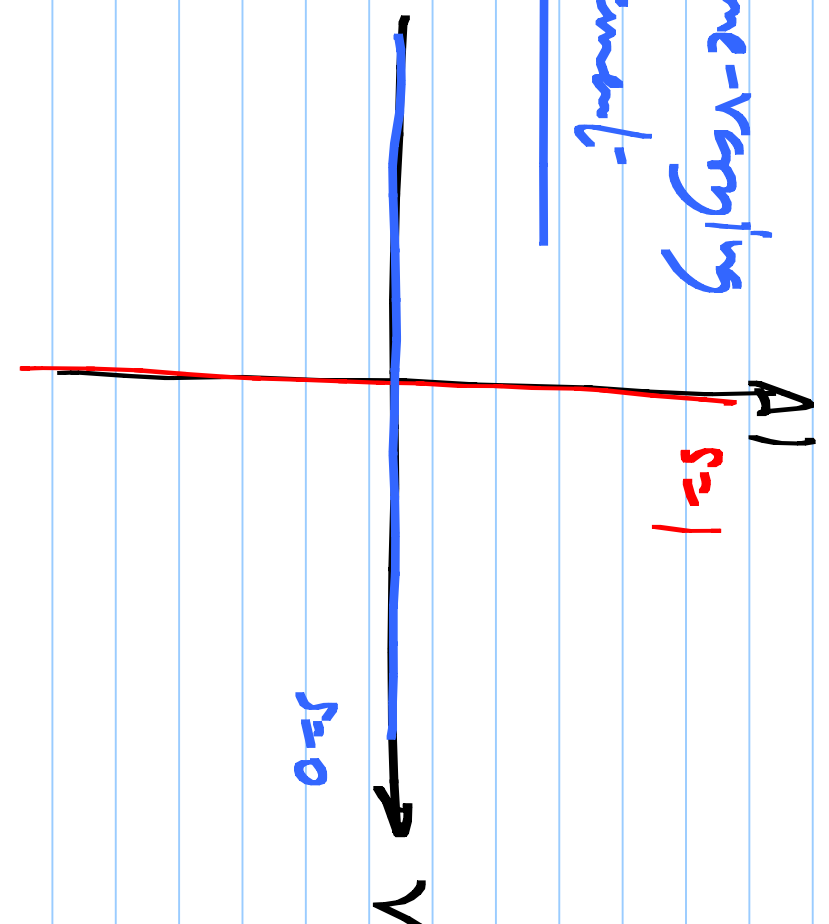


ac

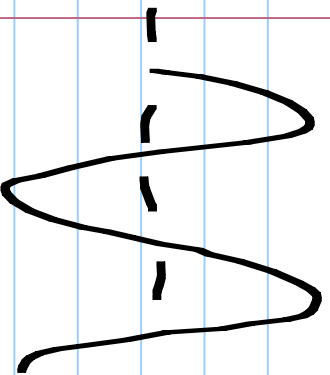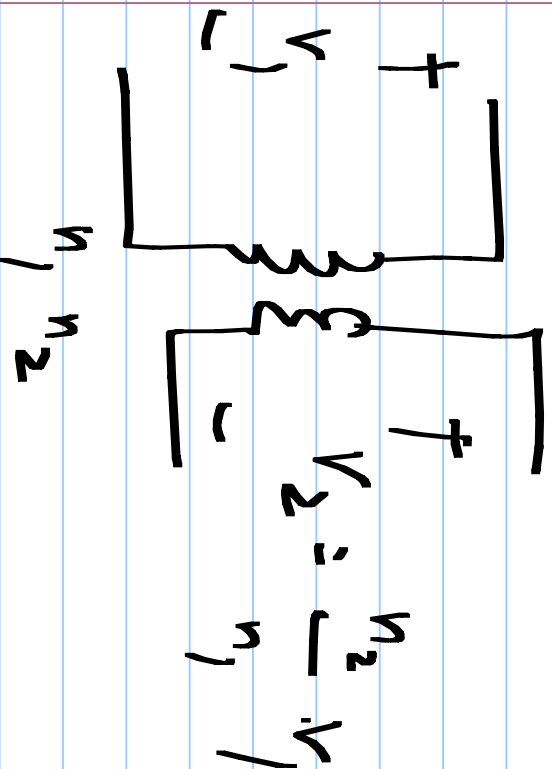

dc ?

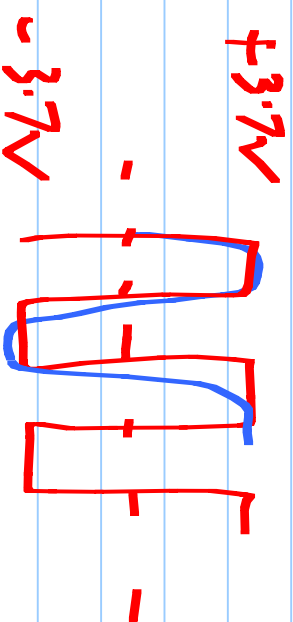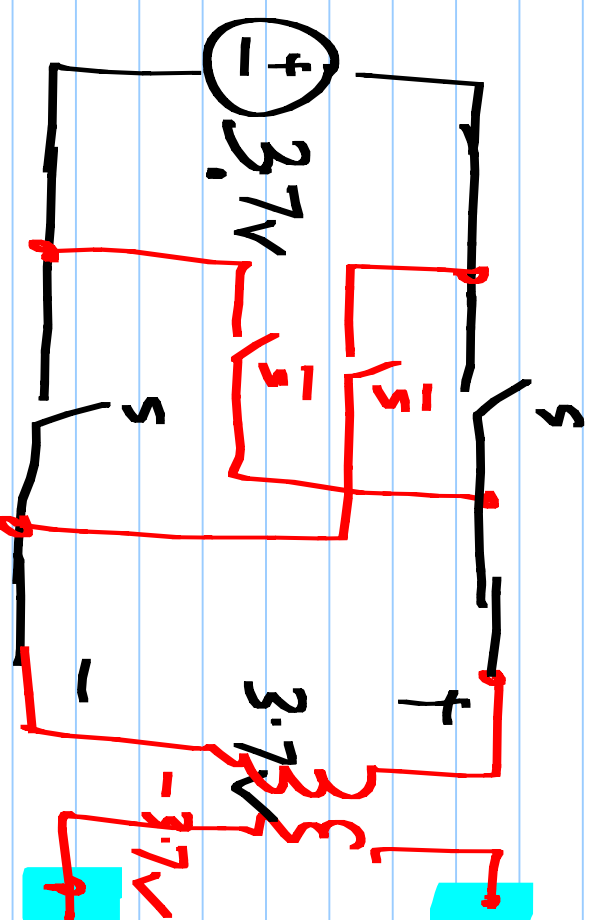




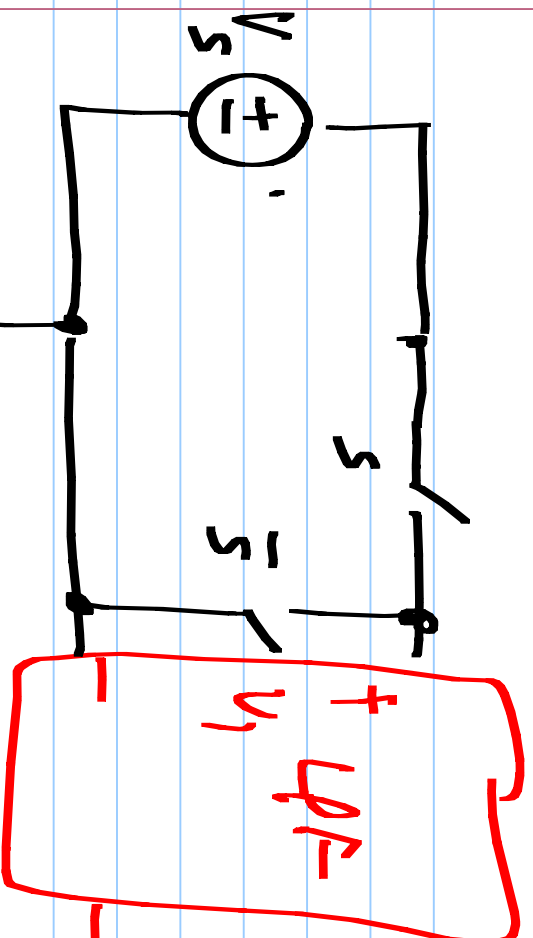

$$\omega_s = \frac{2\pi}{T}$$
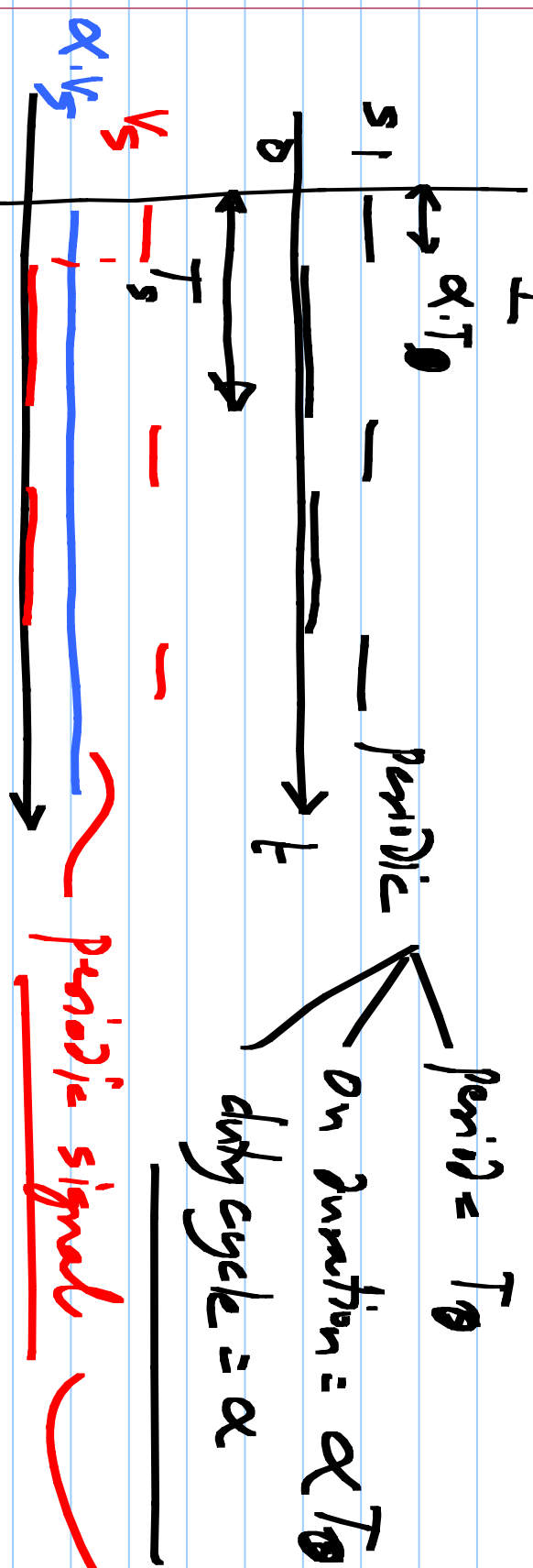
$$\sum_{k=0}^{\infty} V_k \cos(k\omega_s t + \phi_k)$$



periodic signal

$$v = \sum_{k=0}^{\infty} V_k \cos(k\omega t + \phi_k) \quad \underline{V_0 = \alpha V_s}$$

Filter out all harmonics @  $k \neq 0$ ,  $k \geq 1$   
to retain only the dc component

Lowpass filter