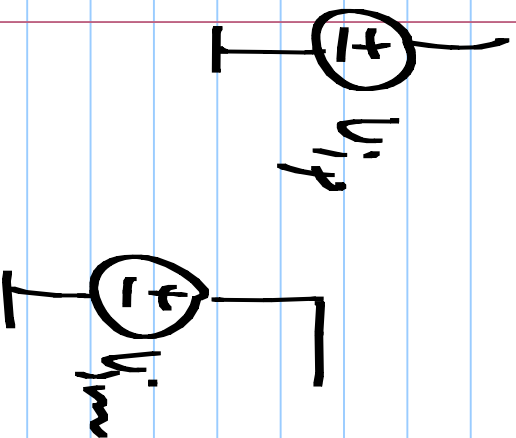



EE 2019


Difference amplifier

21/3/2018



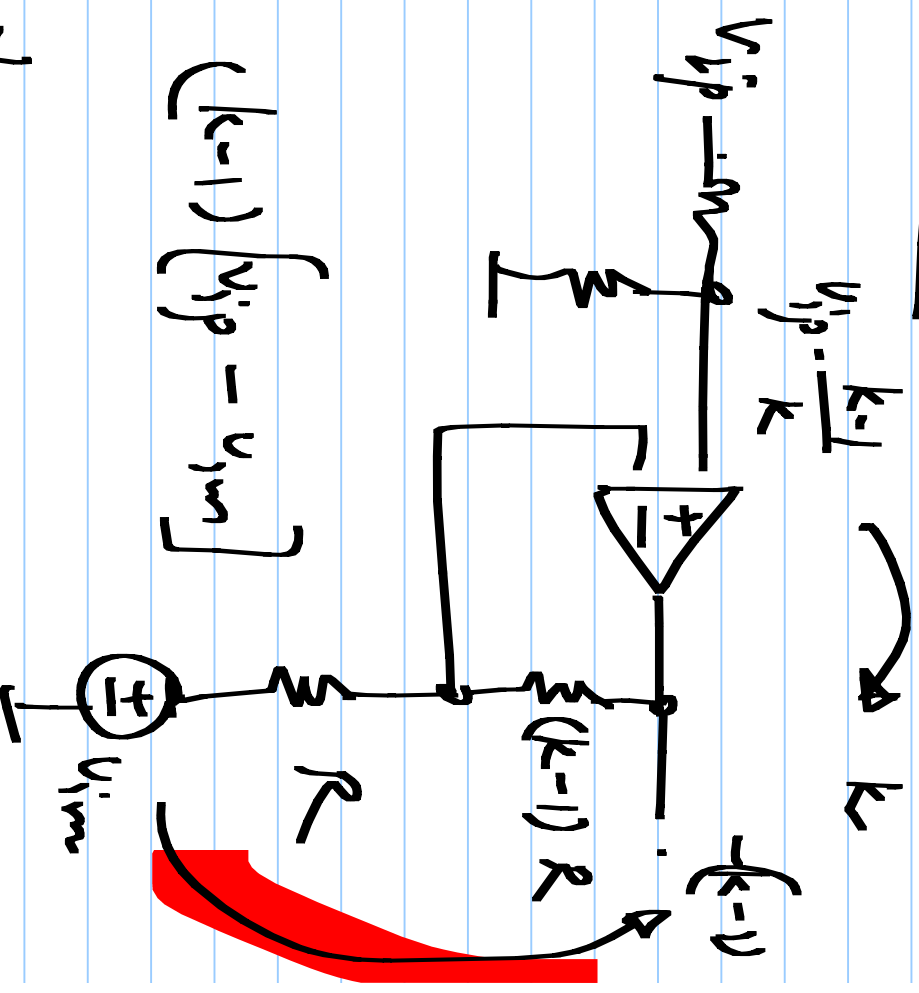Amplify the difference between v_{ip} & v_{im} .
& provide a single ended o/p.





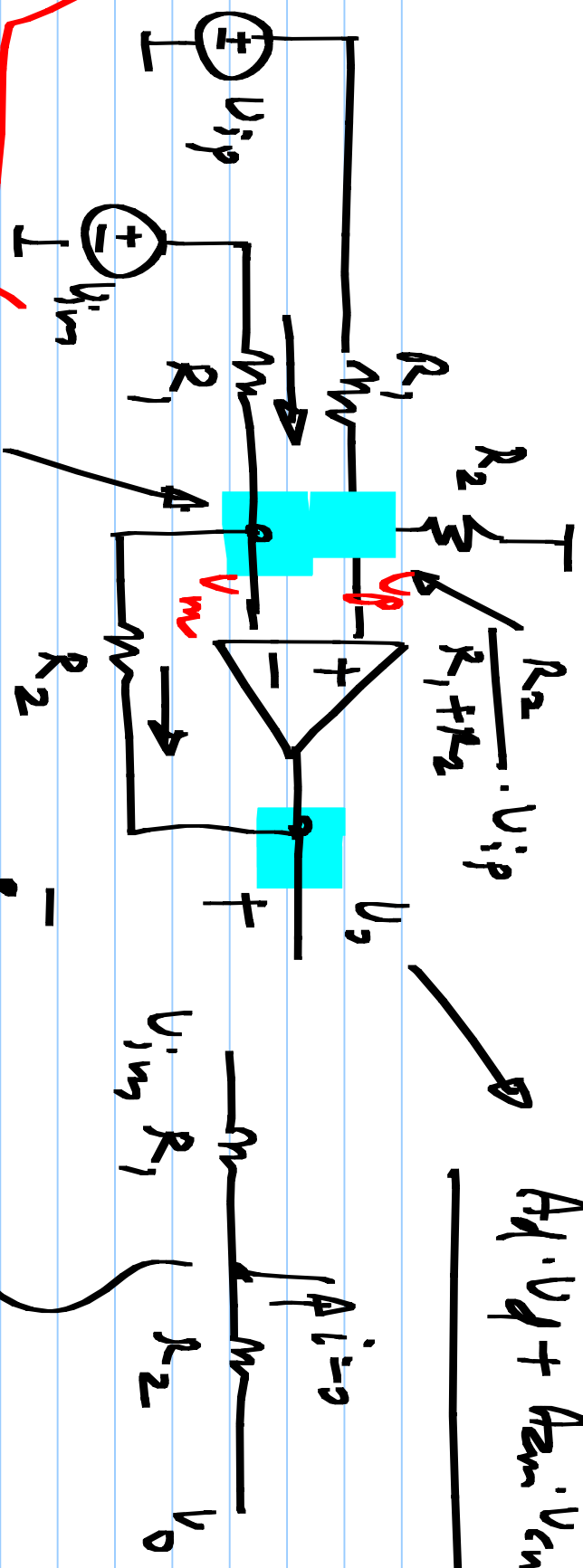

$$A_1 \cdot V_p + A_2 \cdot V_{cm}$$

$$\frac{R_2}{R_1 + R_2} \cdot V_{ip} = V_x = V_{im} \cdot \frac{R_2}{R_1 + R_2} + V_o \cdot \frac{R_1}{R_1 + R_2}$$
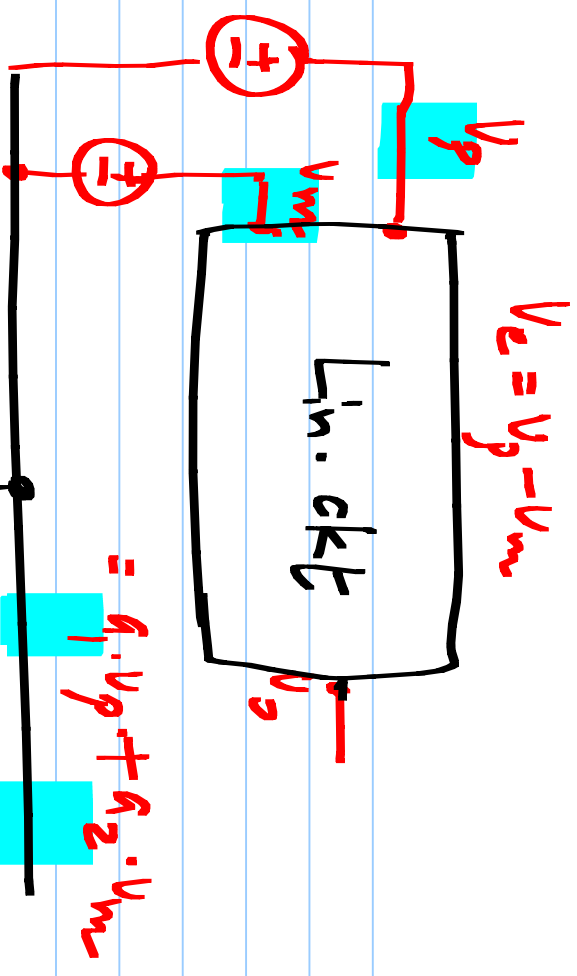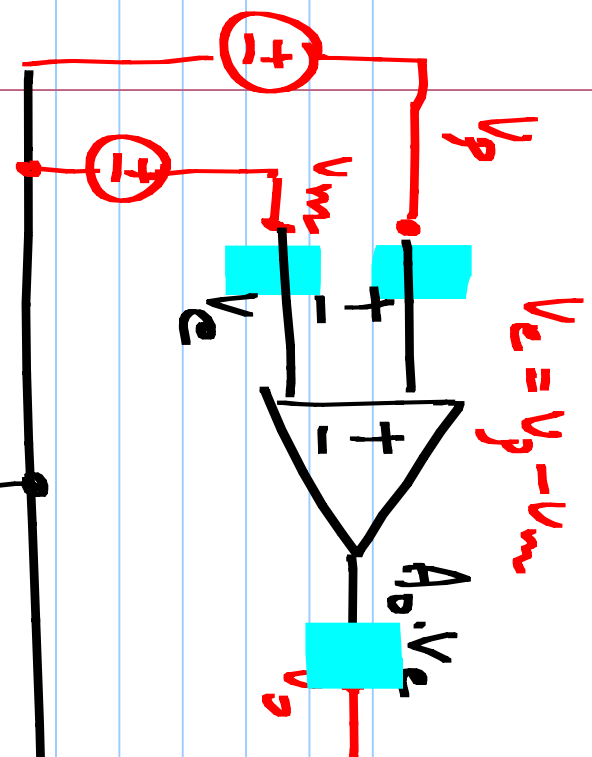
$$V_o = \frac{R_2}{R_1} (V_{ip} - V_{im})$$



$$V_{cm} = \frac{V_p + V_m}{2} \quad \text{Common-mode voltage}$$

$$V_e = V_p - V_m \quad \text{difference voltage}$$

$$V_m = \frac{V_p + V_m}{2} - \frac{V_p - V_m}{2}$$

$$V_D = a_1 \cdot V_p + a_2 \cdot V_m$$

$$= a_1 \left(\frac{V_p + V_m}{2} + \frac{V_p - V_m}{2} \right) + a_2 \left(\frac{V_p + V_m}{2} - \frac{V_p - V_m}{2} \right)$$

$$\boxed{\frac{A_d}{A_{cm}}}$$


$$= \left(\frac{a_1 - a_2}{2} \right) \cdot (V_p - V_m) + (a_1 + a_2) \left(\frac{V_p + V_m}{2} \right)$$

$$= A_d \cdot V_d + A_{cm} \cdot V_{cm}$$

difference voltage
difference gain


common-mode voltage
common-mode gain (Dead)

Inverting amplifier

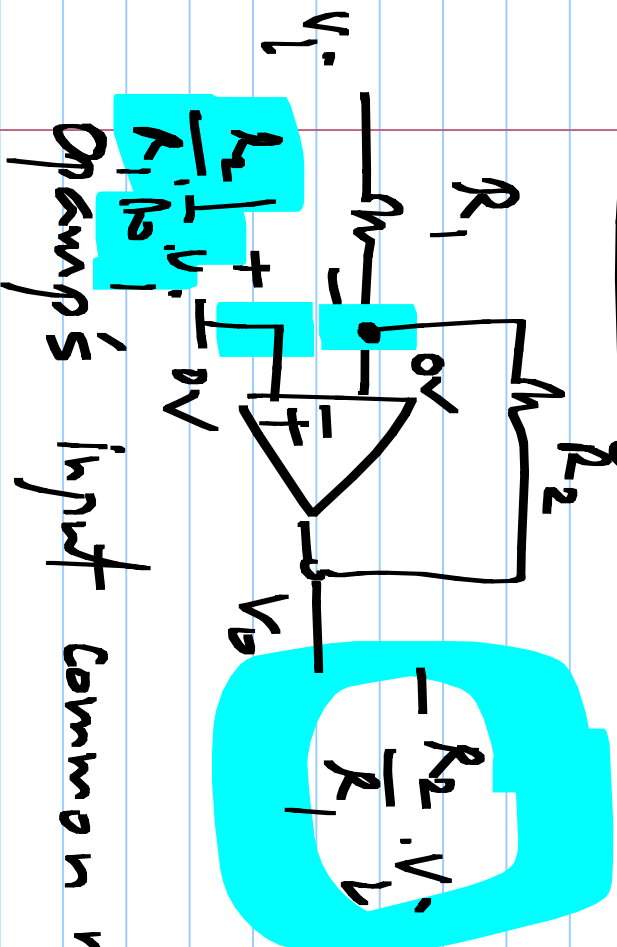


Voltage = Zero

Non-inverting amplifier

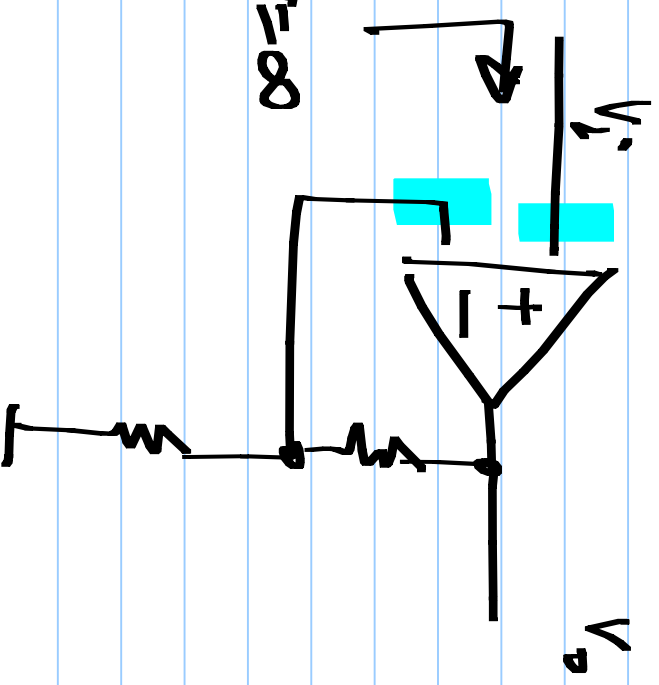

Common-mode input
 $= V_i$

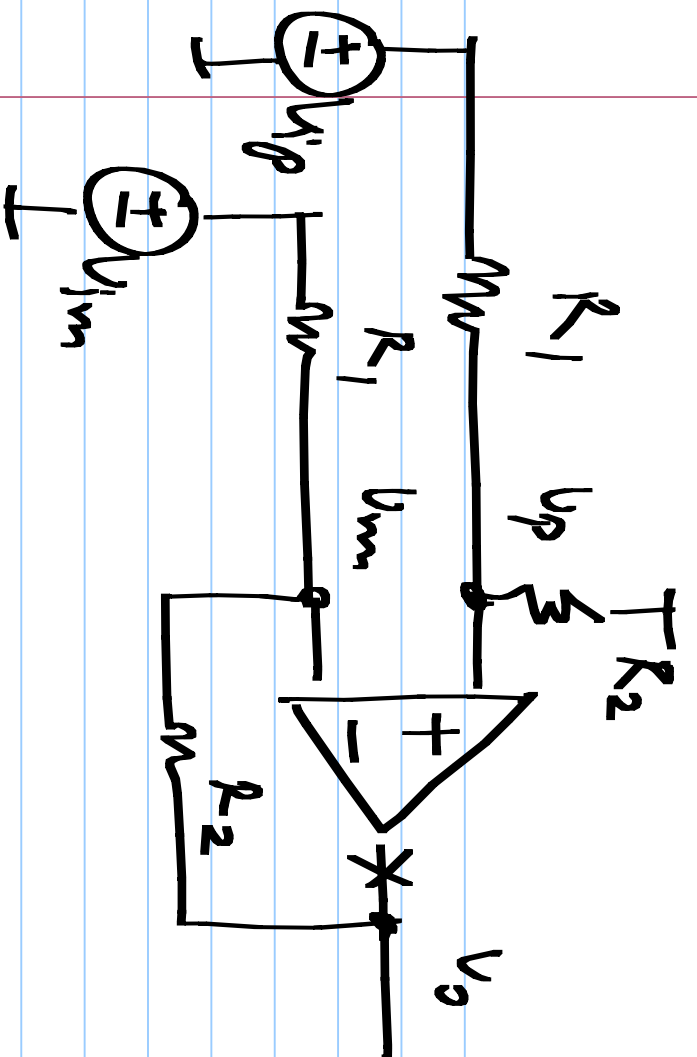

$$V_p = V_{ip} \cdot \frac{R_2}{R_1 + R_2}$$

$$V_m = V_{im} \cdot \frac{R_2}{R_1 + R_2} + V_0 \cdot \frac{R_1}{R_1 + R_2}$$

$$V_0 = A_d \cdot (V_p - V_m) + A_{cm} \left(\frac{V_p + V_m}{2} \right)$$

$$A_d \cdot \frac{R_2}{R_1 + R_2} (V_{ip} - V_{im}) - A_d \cdot V_0 \cdot \frac{R_1}{R_1 + R_2} + A_{cm} \cdot \frac{R_2}{R_1 + R_2} \frac{V_{ip} + V_{im}}{2} + \frac{A_{cm} \cdot V_0 \cdot \frac{R_1}{R_1 + R_2}}{2}$$

$$\frac{V_o}{A_d} \cdot \left(\frac{R_1 + R_2}{R_1} \right) =$$

$$\times \left(\frac{R_1 + R_2}{R_1} \right)$$

$$\cdot \frac{R_2}{R_1} (V_{ip} - V_{in}) - \cdot V_o +$$

$$\frac{1}{A_d R_1} + \frac{A_{cm} \cdot V_o}{\frac{R_2}{2 A_d}}$$

$$V_o = \frac{R_2}{R_1} (V_{ip} - V_{in}) + \frac{A_{cm}}{A_d} \cdot \frac{R_2}{R_1} \cdot \frac{V_{ip} + V_{in}}{2}$$


$$\left[+ \left(\frac{1}{A_d} \cdot \frac{R_1 + R_2}{R_1} \right) - \frac{A_{cm}}{2 A_d} \cdot \right]$$

$$V_o \approx \underbrace{\frac{R_2}{R_1} (V_{ip} - V_{im}) + \frac{A_{cm}}{A_d} \cdot \frac{R_2}{R_1} \cdot \frac{(V_{ip} + V_{im})}{2}}_{\text{difference input}} + \underbrace{\quad}_{\text{common-mode input}}$$

$$V_{ip} = 1 \text{ mV} \quad | 0.001 \text{ V}$$

$$V_{im} = -1 \text{ mV} \quad | 9.999 \text{ V} \quad | 1 \text{ mV}$$

$$\frac{R_2}{R_1} (1 \text{ mV}) + \frac{R_2}{R_1} \cdot \sqrt{10^{-4}} \quad | 1 \text{ mV}$$

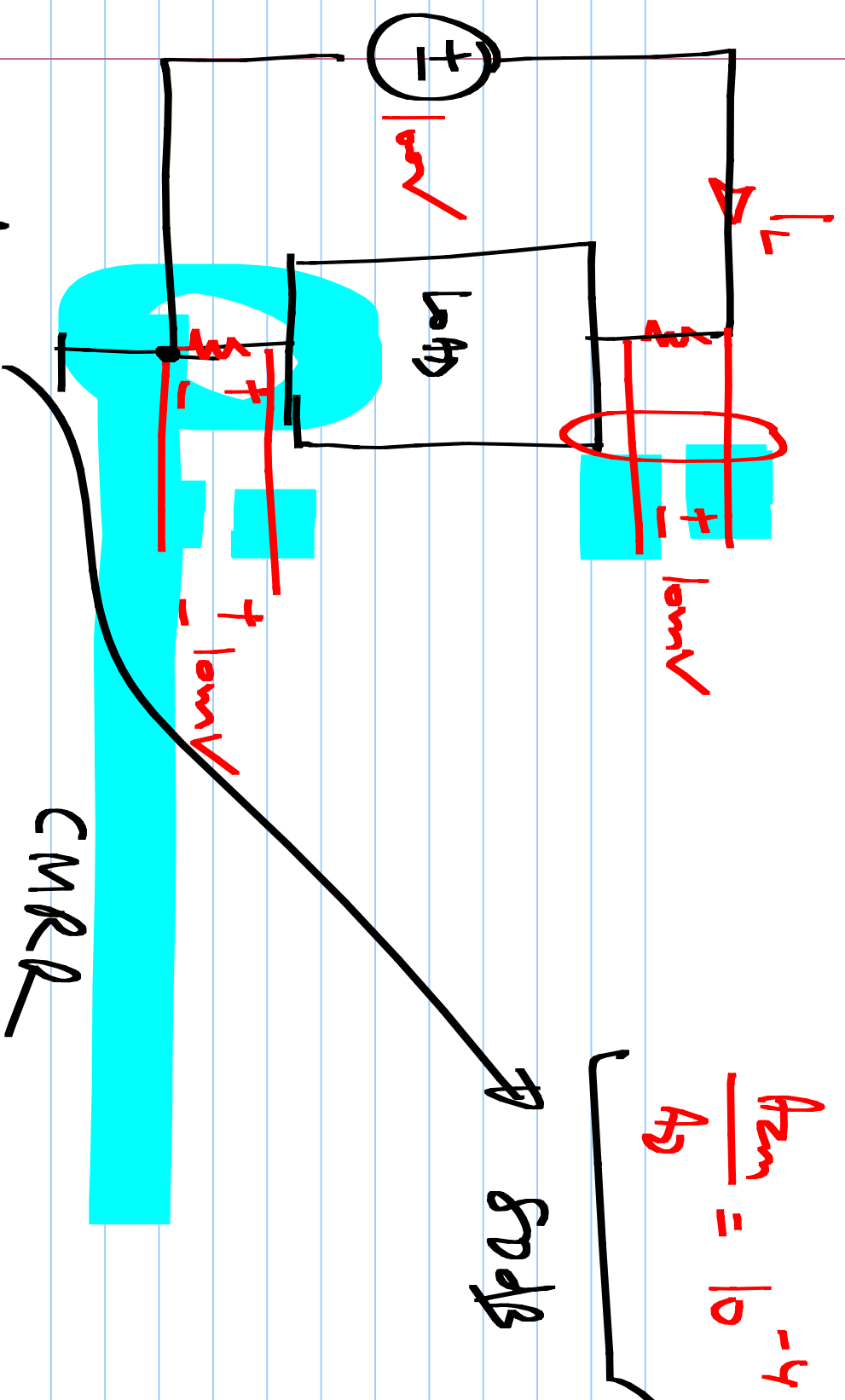

$$\frac{A_{cm}}{A_d} = 10^{-4}$$

$\rightarrow 80\text{dB}$

CMRR

20log $\left(\frac{A_d}{A_{cm}} \right)$: Common-mode rejection ratio

