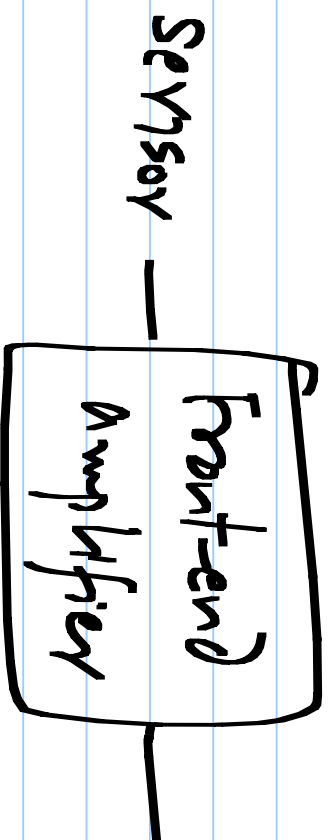



EE 2019

26/3/2018

* Amplifiers — instrumentation amplifier

* DC-DC converters



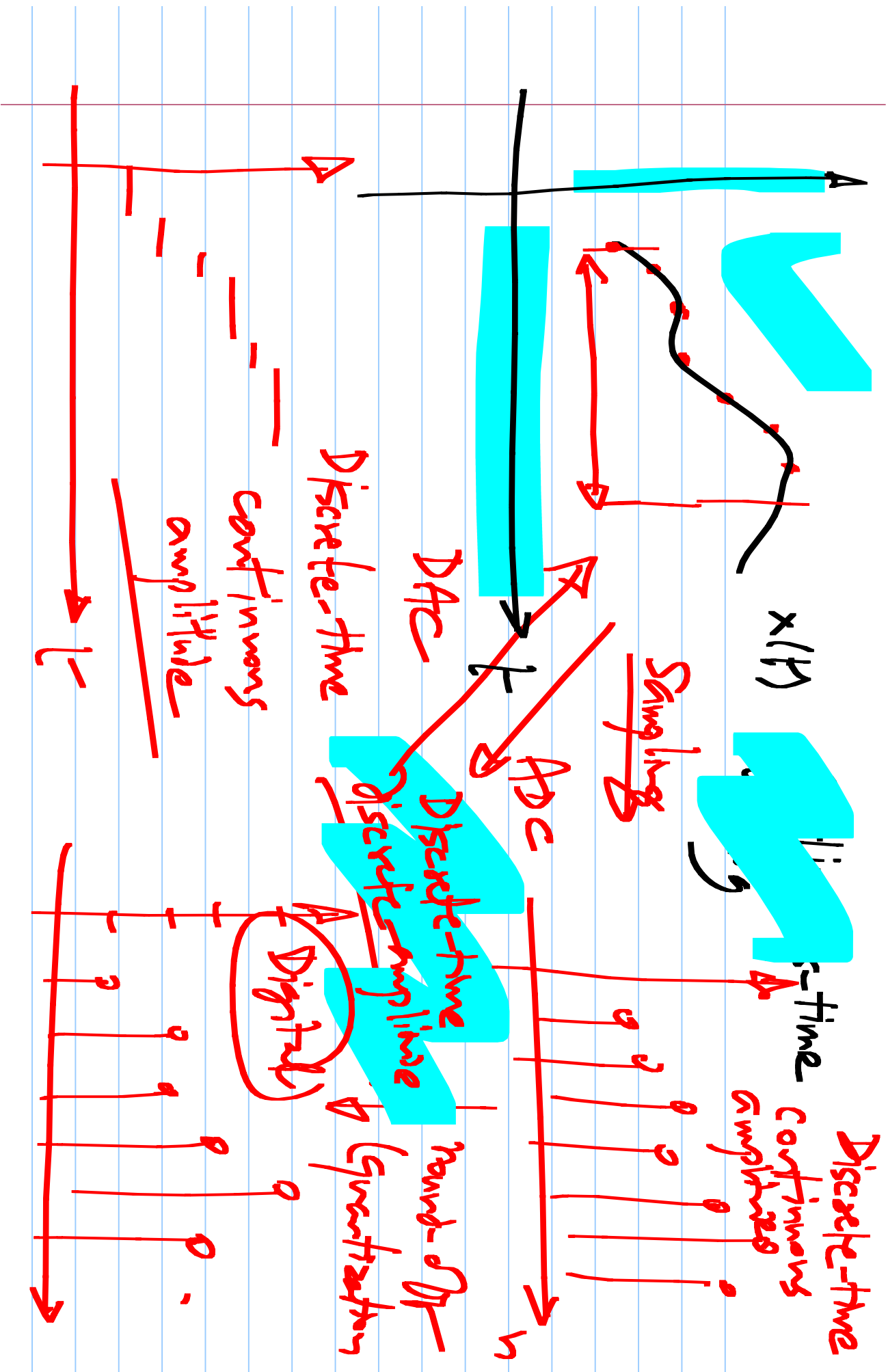


Sampling theorem: A continuous-time signal of bandwidth B can be reconstructed perfectly from its samples at a rate $2B$.


Sampling @ .

$$f_s \rightarrow < f_s/2$$


Nyquist rate

$$B \quad | \quad B$$

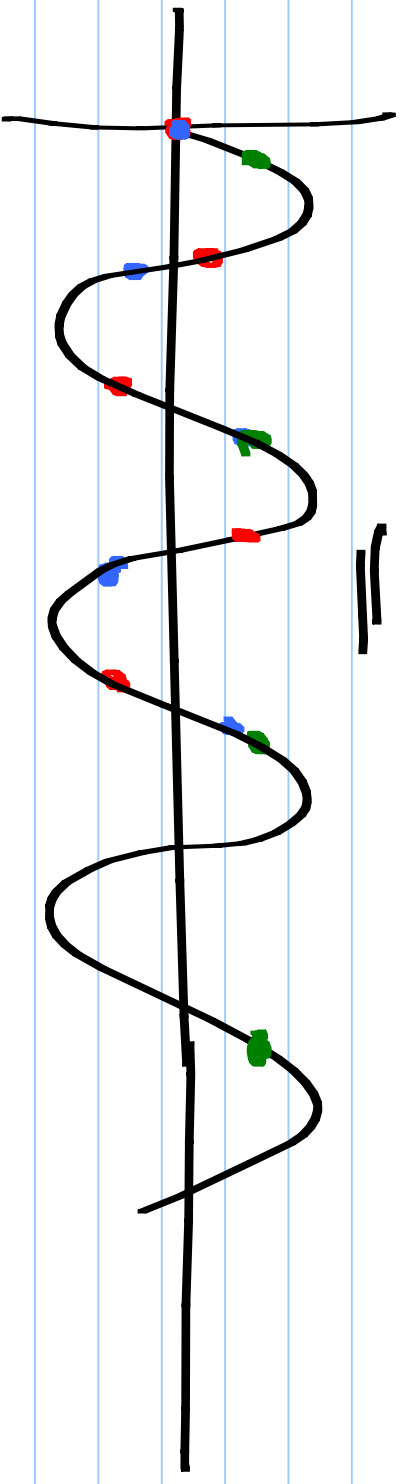


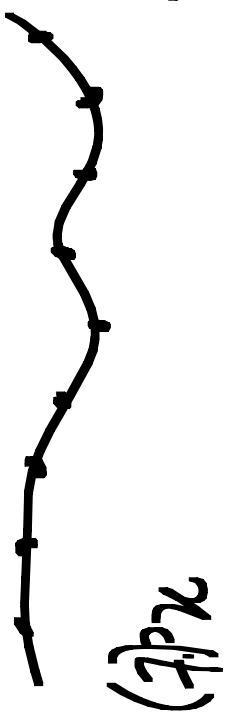


$$f_s = 1/T_s$$

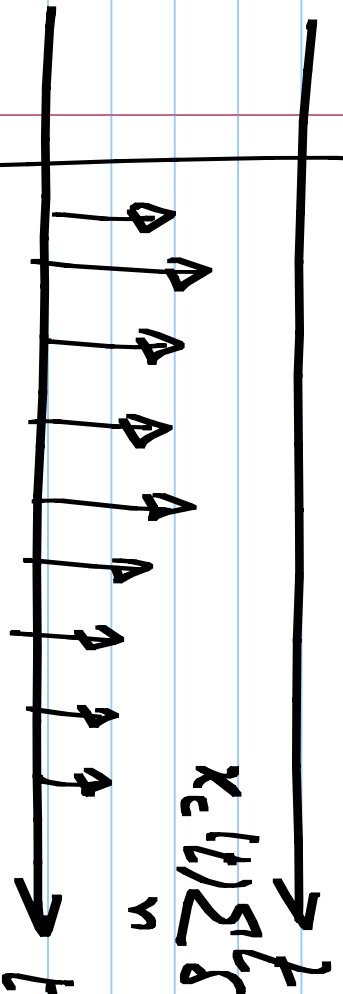

$$x_c(t) \sum_n \delta(t - nT_s)$$

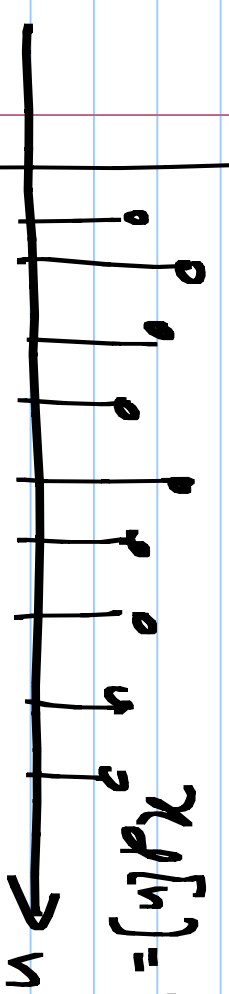


$$x_d[n] = x_c(nT_s)$$

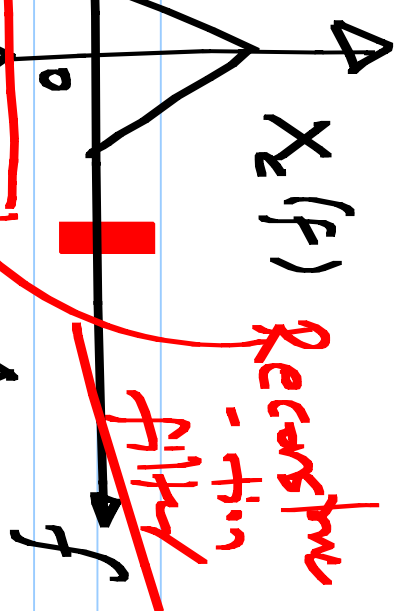


$$-1/2 \quad -1/2$$

$$1/2 \quad 1/2$$


Anti-aliasing filter

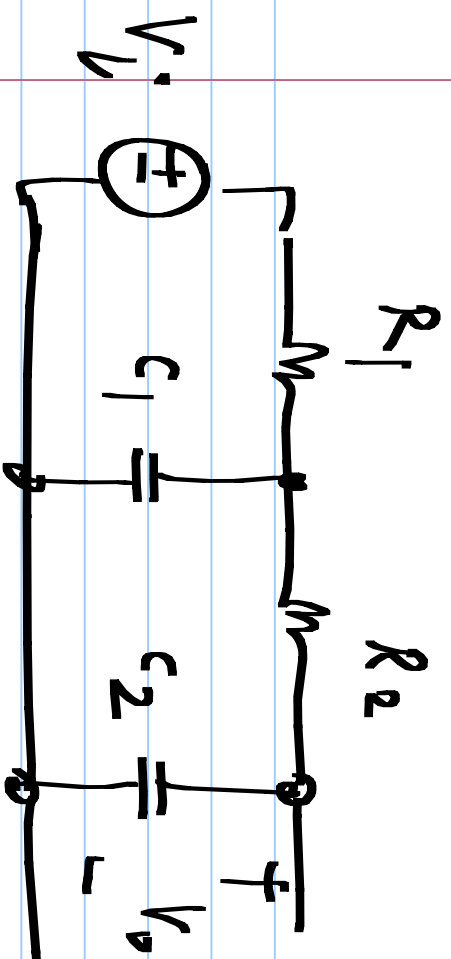

Low-pass filters:

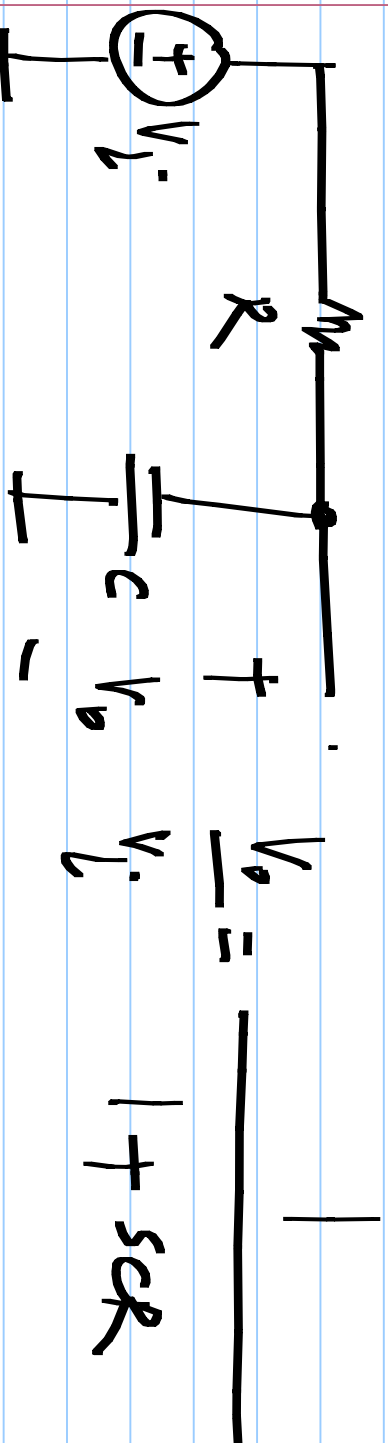


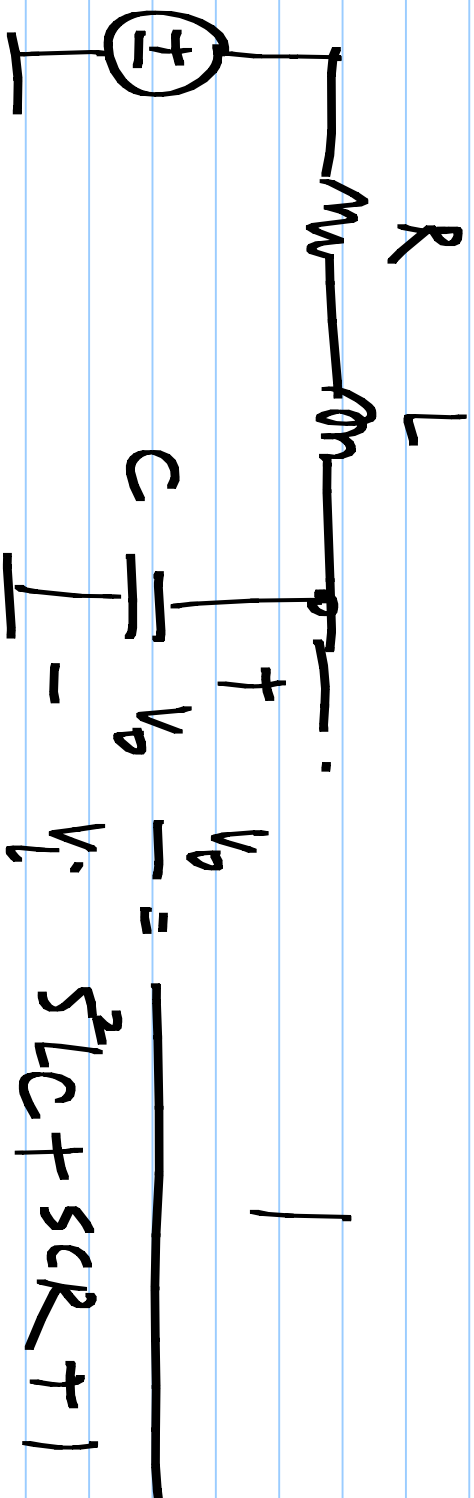
$$\frac{V_o}{V_i} = \frac{1}{1 + s\omega L}$$



$$\frac{V_o}{V_i} = \frac{1}{s\omega C + 1}$$

$$|H| \xrightarrow{\text{Passband}} |T_{\text{transmission}}| = \frac{N(\omega^2)}{D(\omega^2)}$$

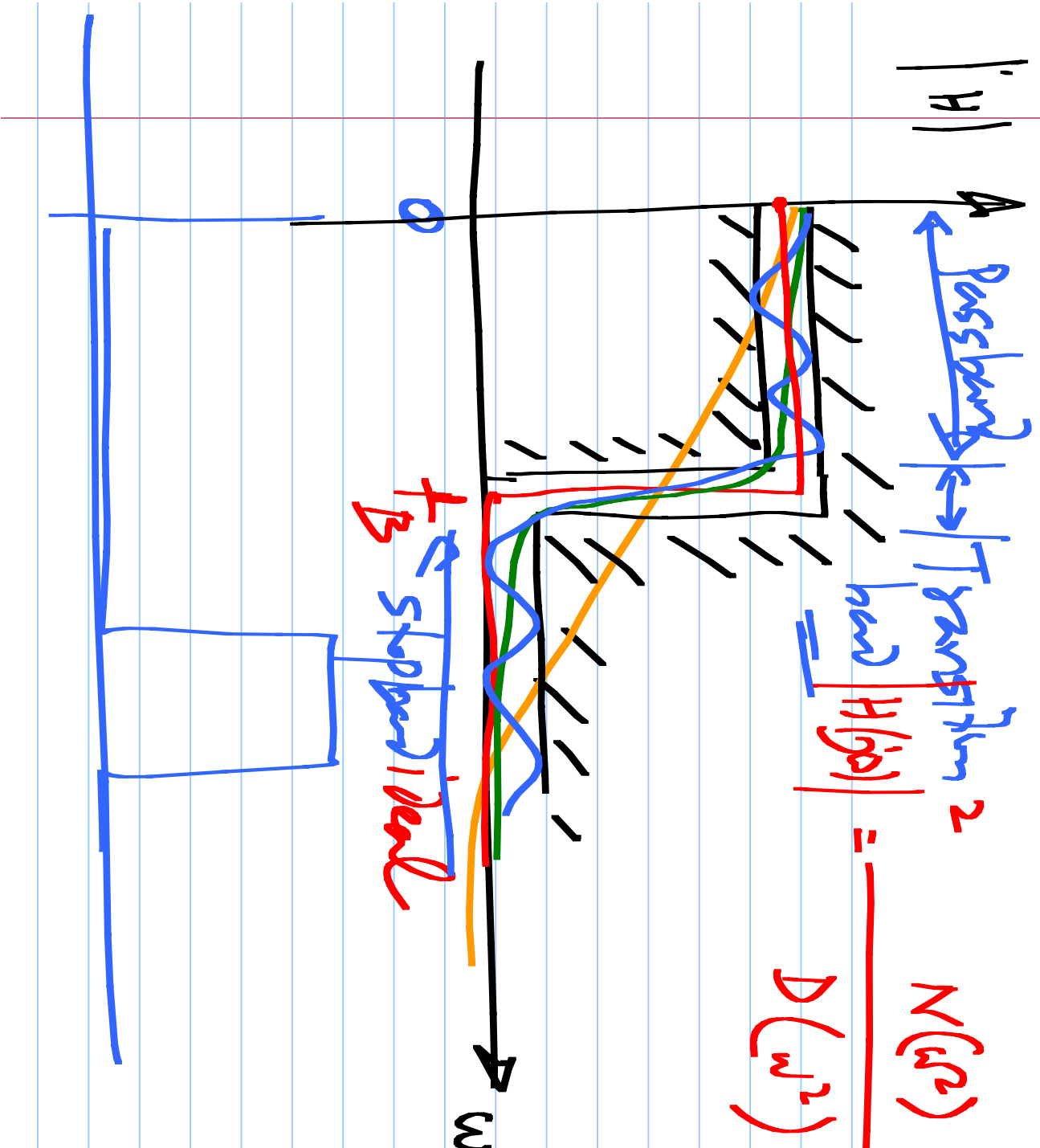


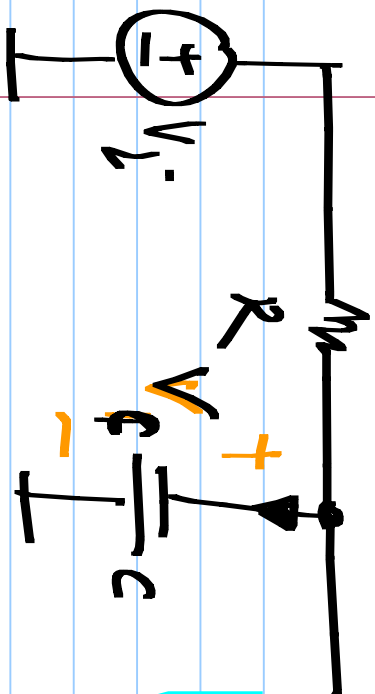

$$V_C = \frac{I_C}{S_C} = \frac{V_L - V_C}{S_C R}$$

$$V_C = \frac{V_L - V_C}{S_C R}$$

SCR

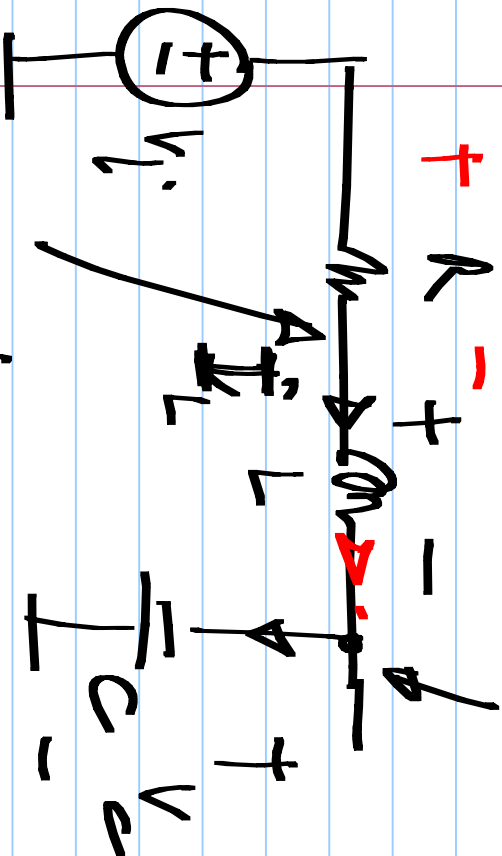


$$R_L = \frac{V_C - V_C}{S_L / R}$$

SCR

$$= \frac{V_C - V_C}{S_C R}$$

SCR

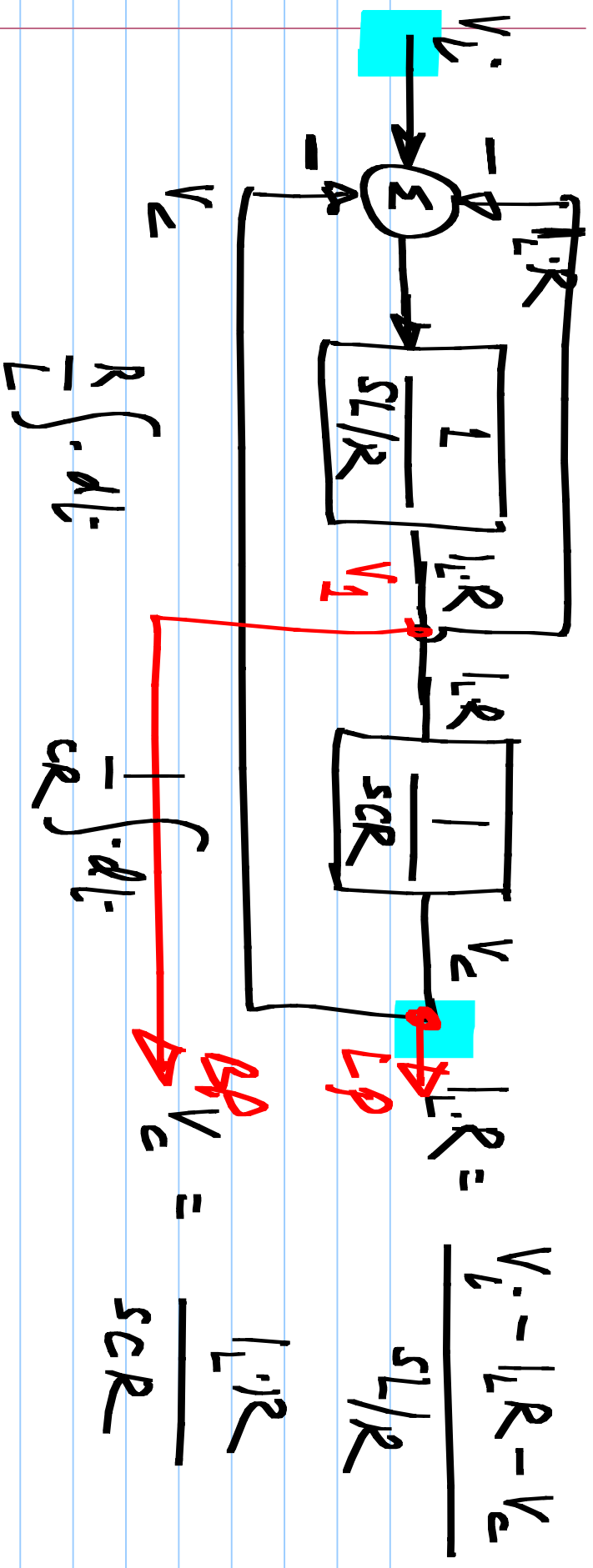

$$\frac{V_C}{V_L} = \frac{1}{s^2 LC + sCR + 1} \quad ; \quad \frac{V_1}{V_L} = \frac{sCR}{s^2 LC + sCR + 1}$$

