
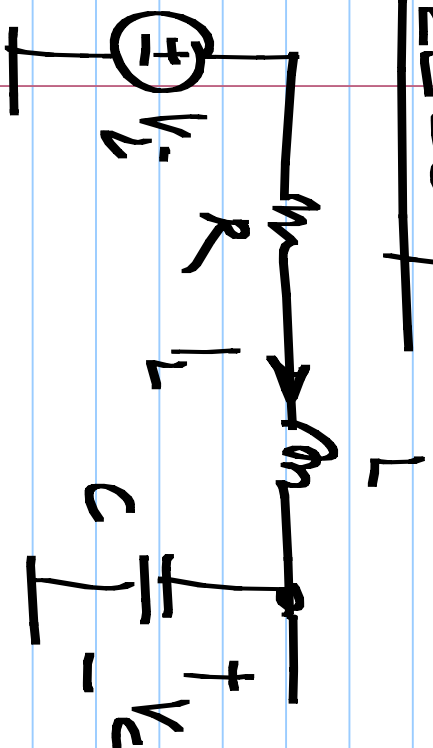




EE 2019


27/3/2018

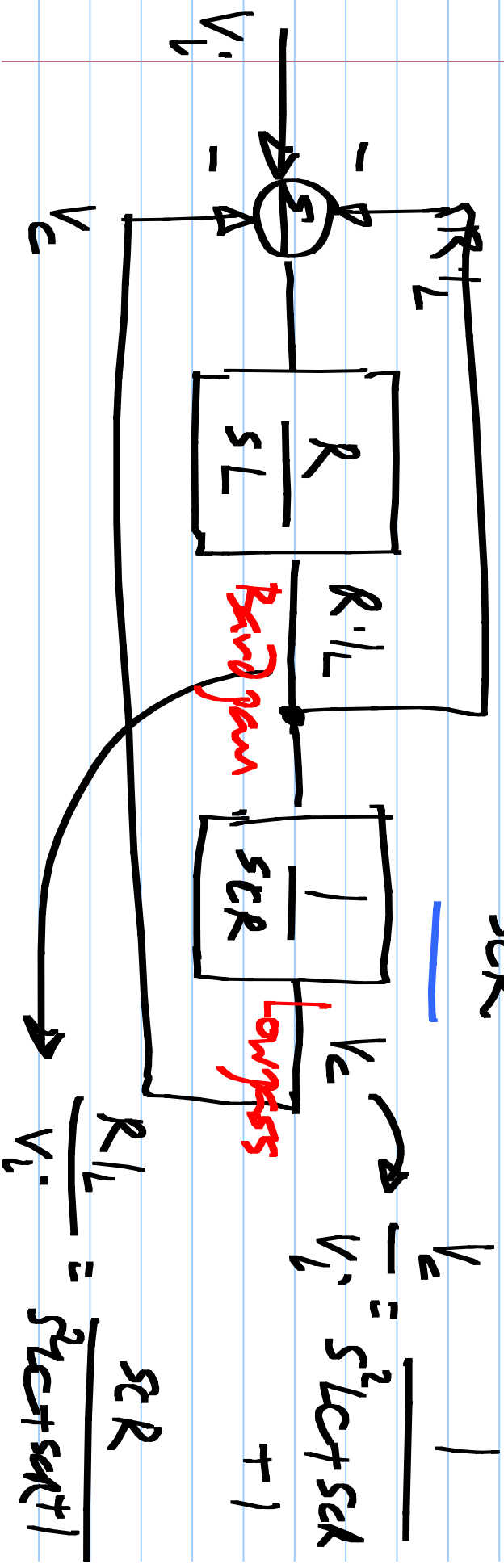

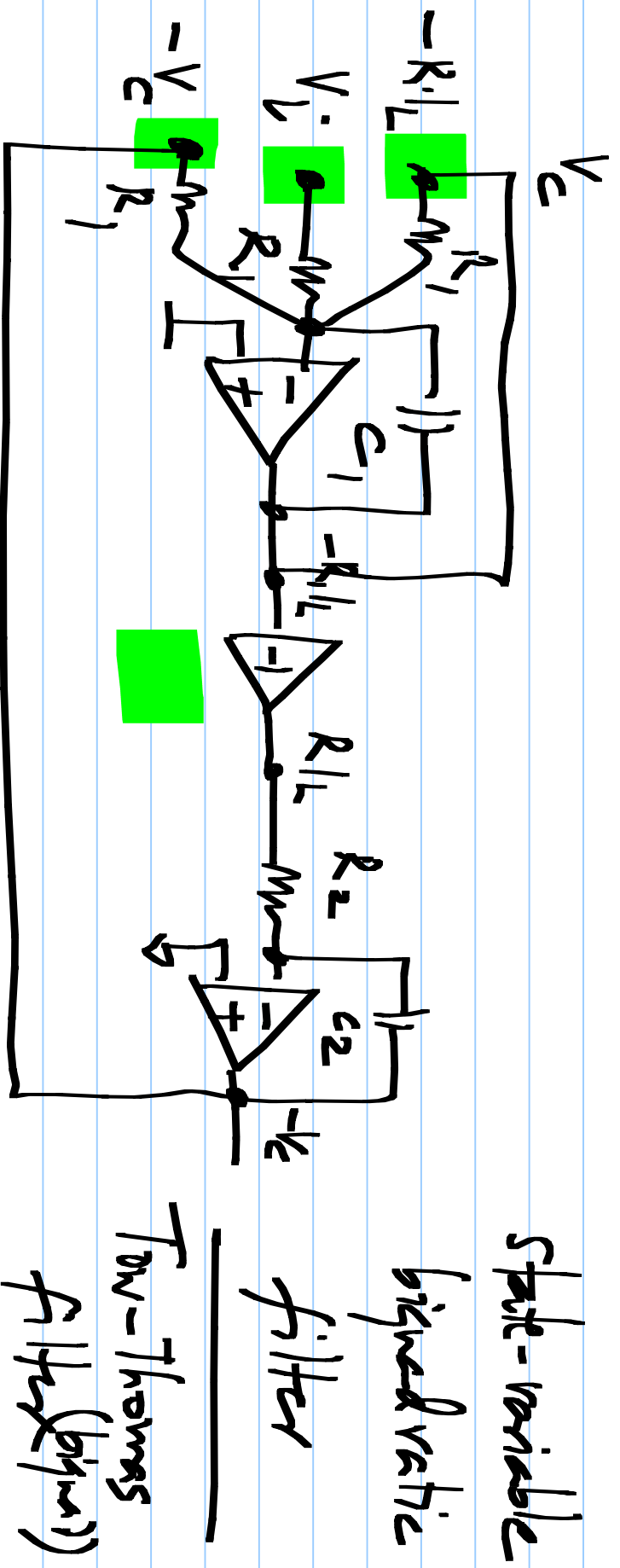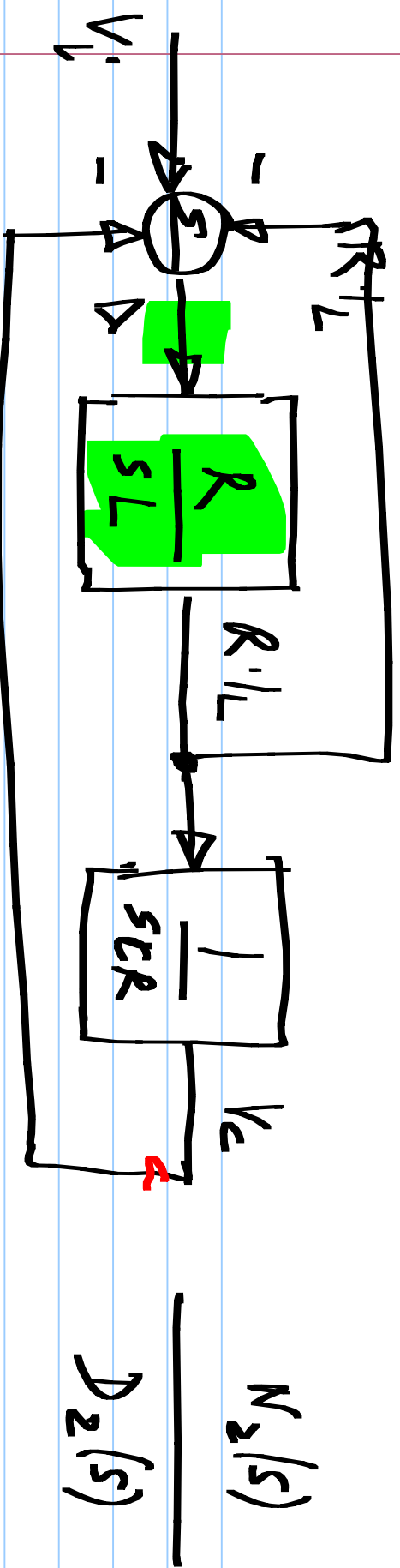
$$R/L = \frac{R}{sL} (V_i - I_L R - V_c)$$
$$V_c = \frac{1}{sCR} \cdot (I_L R)$$







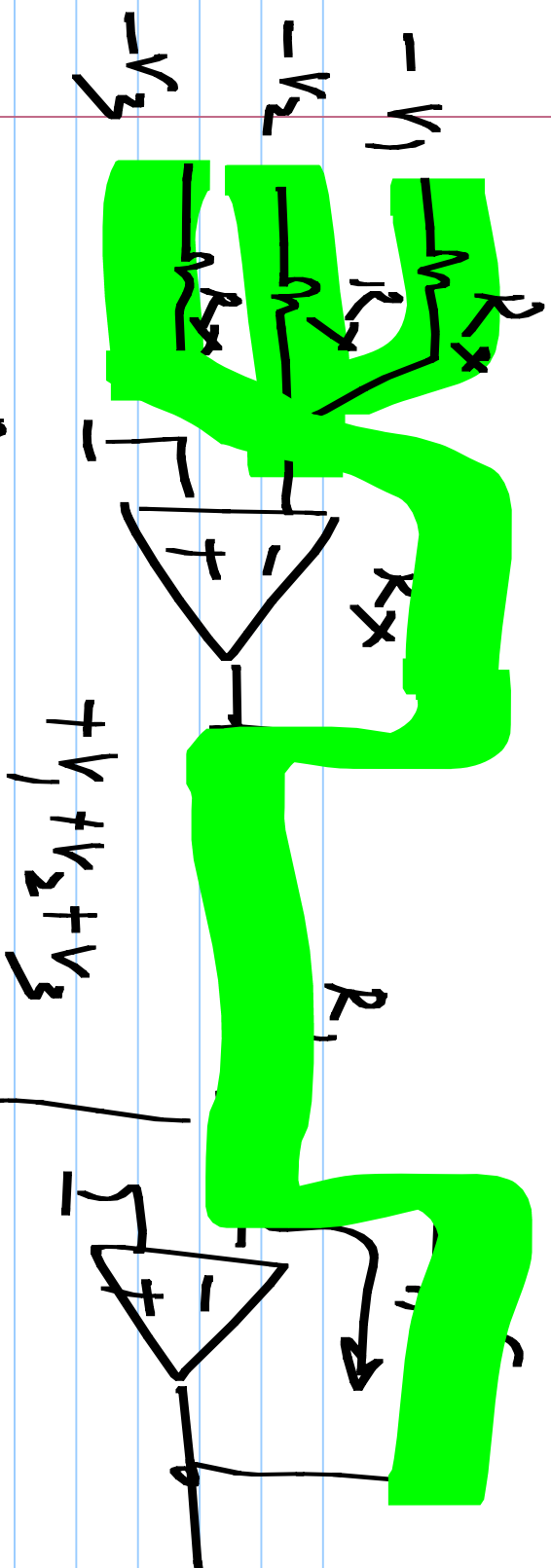
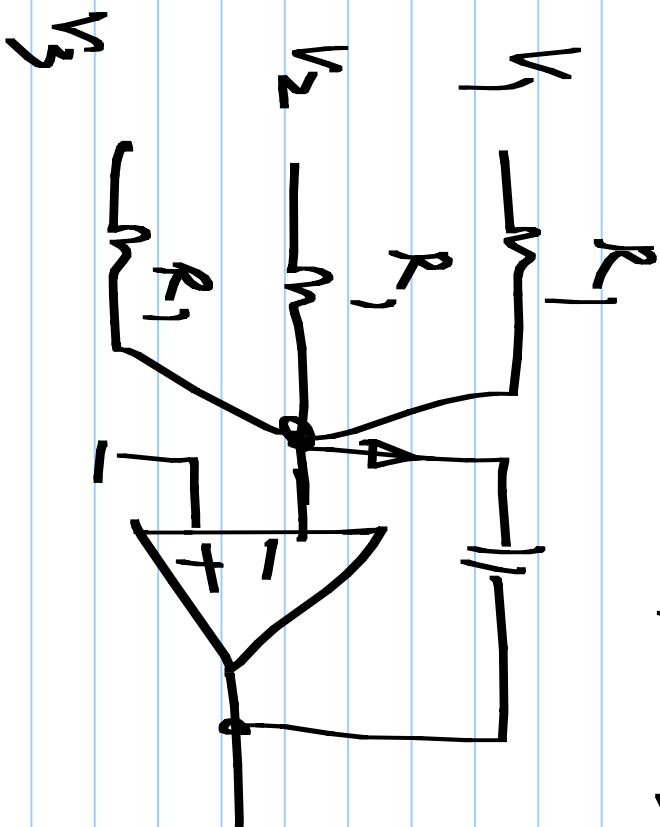
$$V_1 \frac{1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$



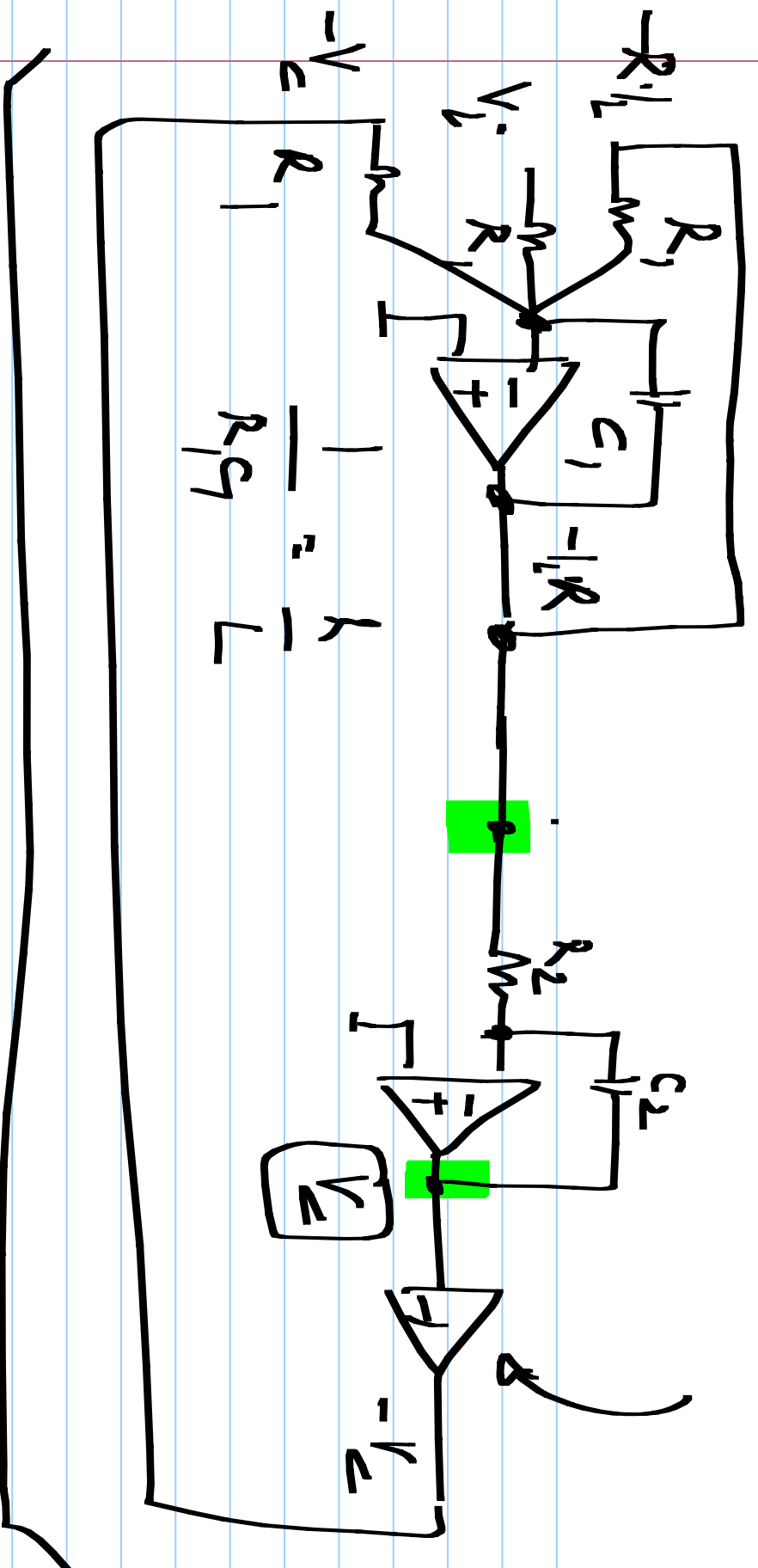

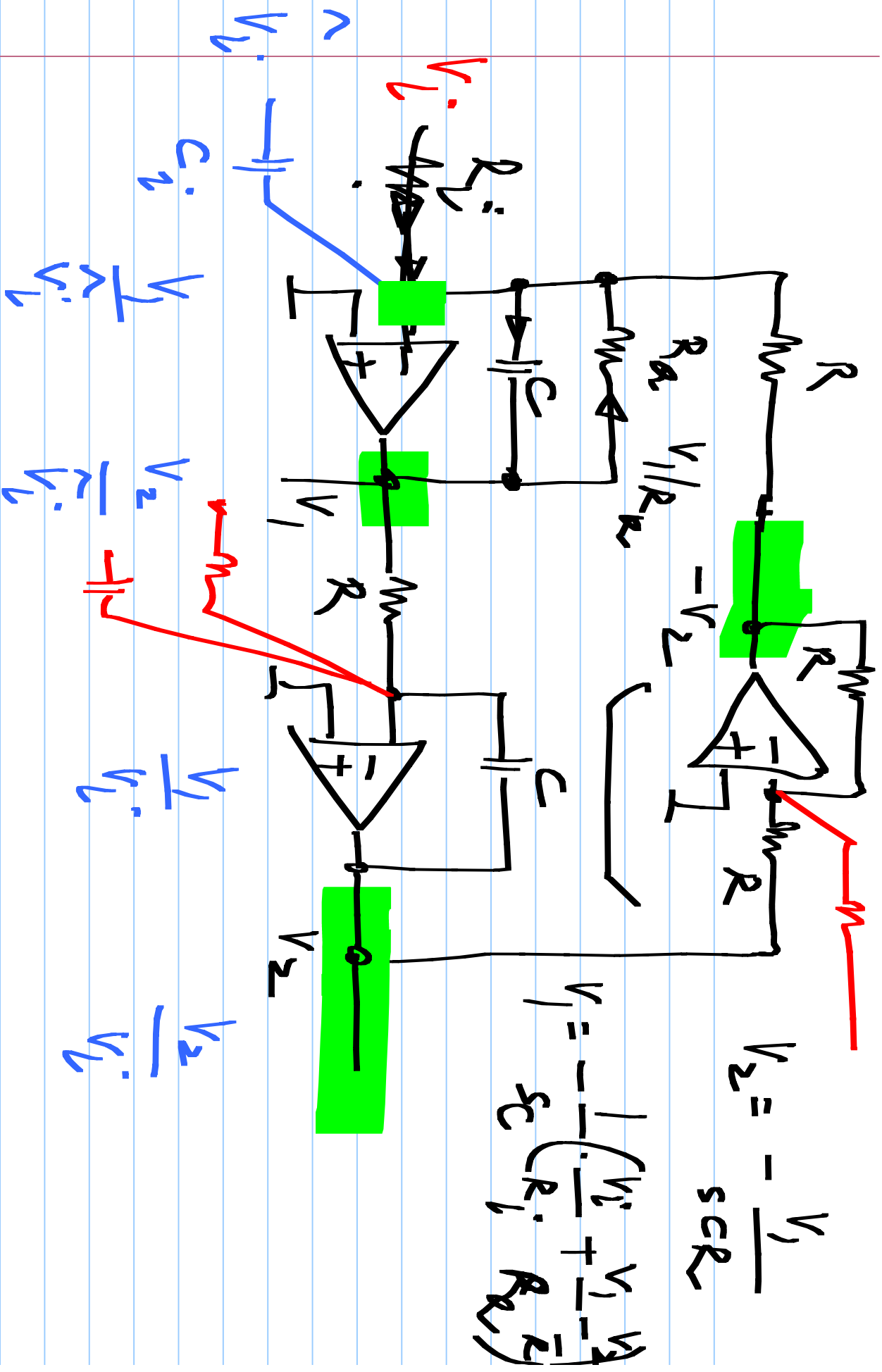

$$V_2 = -\frac{V_1}{sCR}$$

$$sCR \cdot V_2 = -V_1$$

$$sCR \cdot V_1 = -V_2 \cdot \frac{R}{R_L} - V_1 \cdot \frac{R}{R_Q} + V_2$$


$$V_1 = -\frac{1}{sC} \left(\frac{V_2}{R_L} + \frac{V_1}{R_Q} - \frac{V_2}{R} \right) - (sCR) \cdot V_2 = -V_2 \cdot \frac{R}{R_L} + (sCR) \cdot \frac{R}{R_Q} \cdot V_2 + V_2$$

$$\frac{V_1}{V_2} = \frac{-\frac{R}{R_L} \cdot (sCR)}{(sCR)^2 + sCR \cdot \frac{R}{R_Q} + 1}$$

$$\frac{V_2}{V_1} = \frac{R/R_L}{(sCR)^2 + sCR \cdot \frac{R}{R_Q} + 1}$$

$$\frac{V_2}{V_1} = \frac{R / \boxed{}}{(s \boxed{})^2 + s \cdot \frac{R}{R_2} + 1}$$

R_2

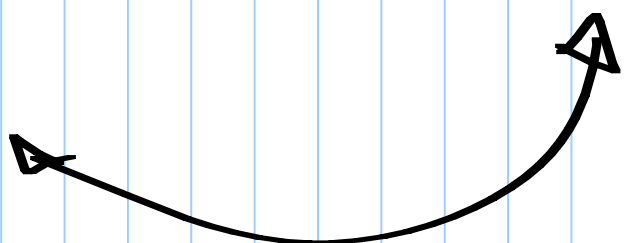

$$s^2 LC + sL/R + 1$$


$$\frac{1}{V_1} = - \frac{\frac{R}{R_1} \cdot (sCR)}{(sCR)^2 + sCR \cdot \frac{R}{R_2} + 1} D_2(s)$$

$$\frac{1}{V_2} = \frac{\frac{R}{R_1}}{(sCR)^2 + (sCR) \frac{R}{R_2} + 1}$$

$$\frac{1}{V_1} = \frac{- (sCR)^2 \cdot \frac{C_1}{C}}{D_2(s)} \quad , \quad \frac{1}{V_2} = \frac{(sCR) \cdot \frac{C_1}{C}}{D_2(s)}$$

High A Notch $H_1\left(\frac{s}{\omega_n}\right) = H\left(\frac{\omega_n}{s}\right)$

2nd order transfer fn.

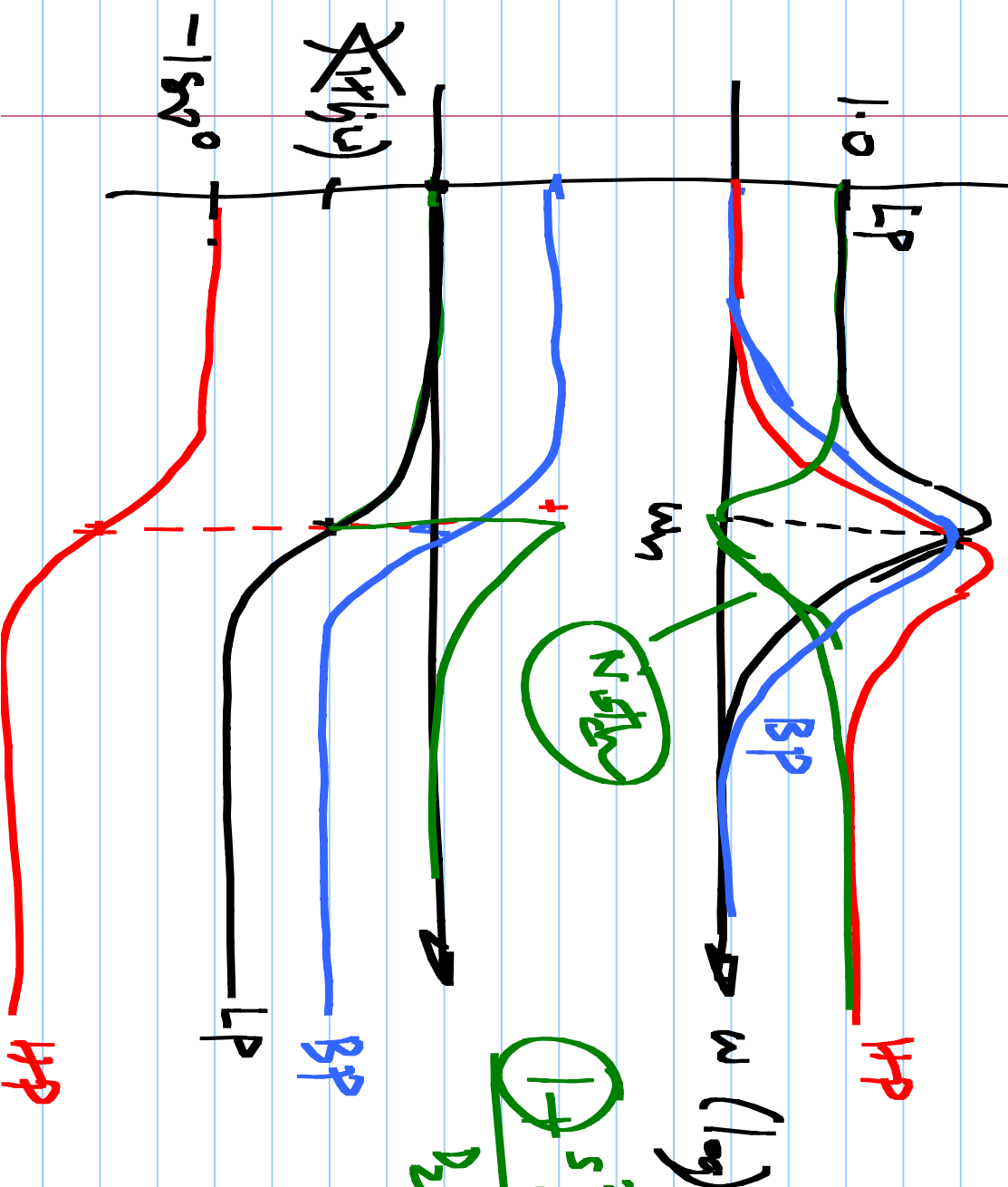

$$H(s) = \frac{1}{\frac{s^2}{\omega_n^2} + \frac{s}{Q\omega_n} + 1}$$

$$\frac{1 + s^2/\omega_n^2}{D_2(s)}$$

$$s = j\omega_n$$

$$H'(s) = \frac{s^2/\omega_n^2}{D_2(s)}$$

$$H_3(s) = \frac{s/\omega_n}{D_2(s)}$$

$$1 + \frac{s^2}{\omega_n^2}$$