

EE539: Analog Integrated Circuit Design; HW5

Nagendra Krishnapura (nagendra@iitm.ac.in)

due on 15 Mar. 2006

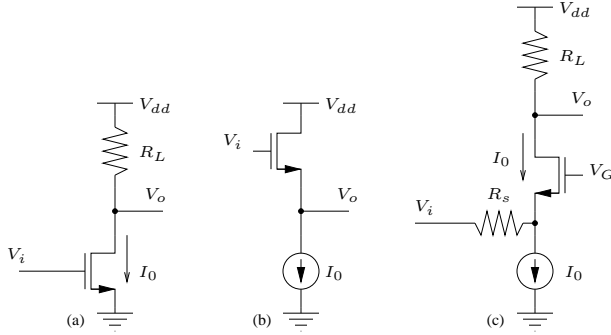


Figure 1: Problem 1

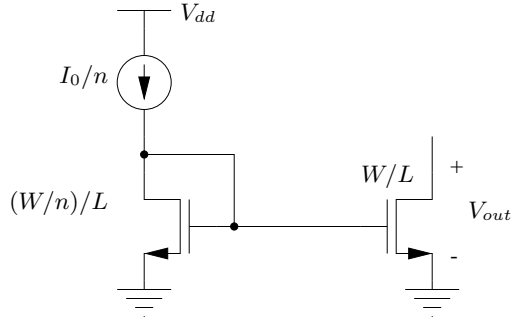


Figure 2: Problem 3

0.18 μm technology parameters: $V_{Tn} = 0.5 \text{ V}$; $V_{Tp} = 0.5 \text{ V}$; $K_n = 300 \mu\text{A}/\text{V}^2$; $K_p = 75 \mu\text{A}/\text{V}^2$; $A_{VT} = 3.5 \text{ mV } \mu\text{m}$; $A_\beta = 1\% \mu\text{m}$; $V_{dd} = 1.8 \text{ V}$; $L_{min} = 0.18 \mu\text{m}$, $W_{min} = 0.24 \mu\text{m}$; Ignore body effect unless mentioned otherwise. Ignore $1/f$ noise unless mentioned otherwise.

1. Determine the output and input referred noise voltages of the stages in Fig. 1.
2. A 1:1 current mirror has devices with sizes W/L and an output current I_0 has an rms current mismatch in the output of σ_{I_0} . Redesign the current mirror to have an rms mismatch of $\sigma_{I_0}/2$. (It should be usable in place of the original source).
3. A current mirror generating I_0 is realized as shown in Fig. 2. It is required to support a minimum output voltage of V_{out} . It is proposed that the reference branch have a current I_0/n in order to minimize “overhead” currents. How do

the power consumption and noise compare with a 1:1 current mirror?

4. Compute the contribution to output current noise from noise current i_{n1} and i_{n2} in the two devices in Fig. 3.
5. Compute the effect of threshold voltage mismatch ($\Delta V_{t1,2}$) and current factor mismatch ($\Delta\beta_{1,2}$) in the top and the bottom transistors in Fig. 4.
6. Compute v_o/v_i in the two circuits in Fig. 5. Calculate the tail node voltage in each case. Explain the results.
7. Compute the differential frequency response. Consider $g_m, C_{gs}, C_{gd}, C_{db}$ in the calculations. What is the purpose of C_f ? What value would you set it to?
8. Design and simulate a $100 \mu\text{A}$ pMOS cascode current mirror using $0.5 \mu\text{m}$ length transistors

 


Figure 5: Problem 6

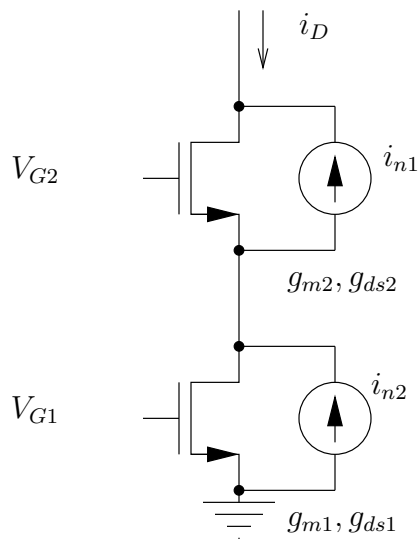


Figure 3: Problem 4

 


Figure 6: Problem 7

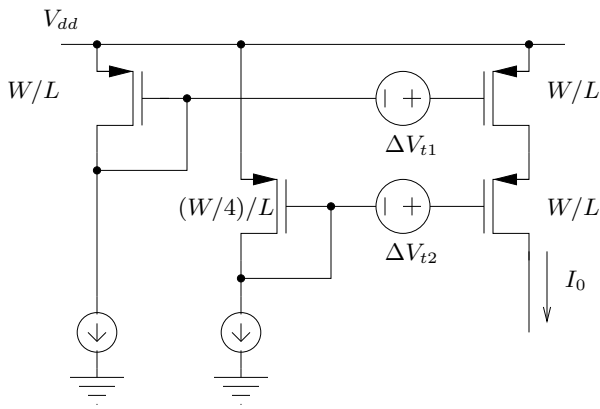


Figure 4: Problem 5

for $V_{out} = 300\text{ mV}$. Report the dc node voltages and the saturation voltages of each transistor. Plot the output impedance vs. frequency. Reduce W and L of the cascoding device by 2x and plot $|Z_{out}|$ vs. frequency on the same plot. What do you infer?