

EE539: Analog Integrated Circuit Design; Lecture 11

Nagendra Krishnapura (nagendra@iitm.ac.in)

30 Jan. 2006

Single Transistor Amplifiers

- MOSFET - a voltage controlled current source. By passing the current through a resistor, voltage gain can be obtained
- Transconductance (g_m) is higher in saturation region when compared to triode region
Saturation: $g_m = \frac{\mu C_{ox} W}{L} (V_{GS} - V_T)$
Triode: $g_m = \frac{\mu C_{ox} W}{L} V_{DS}$ where $V_{DS} < (V_{GS} - V_T)$
- Transconductance is almost independent of V_{DS} in the saturation region (there is a slight variation due to channel length modulation)
So, amplifiers are always biased in saturation region to get good amplification

Common Source Amplifier

Small signal analysis-DC

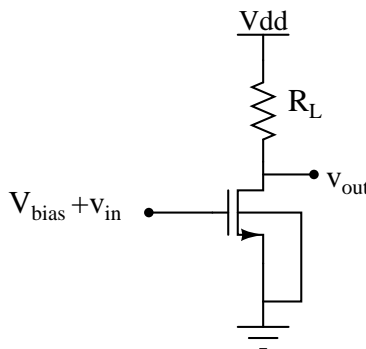


Figure 1: Common source amplifier

Assume that V_{dd} and V_{bias} bias the MOSFET in saturation.

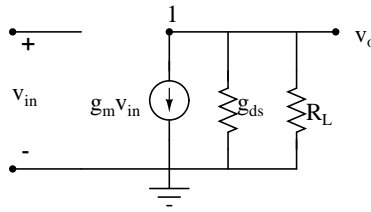


Figure 2: Small signal model at DC

Writing KCL at node 1,

$$V_{out}(g_{ds} + G_L) = -g_m V_{in}$$

$$\frac{V_{out}}{V_{in}} = -\frac{g_m}{g_{ds} + G_L} \approx -\frac{g_m}{G_L} \text{ if } g_{ds} \ll G_L$$

$$\text{Max DC gain} = -\frac{g_m}{g_{ds}} \text{ (at } R_L = \infty)$$

$$\text{Noting that } g_m = \sqrt{2\mu I_d C_{ox} \frac{W}{L}} \text{ and } g_{ds} = \lambda I_d$$

$$\text{Max DC gain} = \frac{\sqrt{2\mu C_{ox} \frac{W}{L}}}{\lambda} \frac{1}{\sqrt{I_d}}$$

We see that, to get the highest possible DC gain,

- Bias current should be as low as possible
- Width of the transistor can be increased while keeping the bias current constant
- Length of the transistor can be increased while keeping the bias current constant. This stems from the fact that λ is inversely proportional to length

We also see from the small signal model that

$$R_{in} = \infty$$

$$R_{out} = \frac{1}{g_{ds} + G_L}$$

Small signal analysis-AC (qualitative)

Fig. 3 shows the small signal model at high frequencies. If C_{gd} is neglected, then

$$\text{Gain} = -\frac{g_m}{g_{ds} + G_L + sC_{db}}$$

There will be one pole at $\frac{g_{ds} + G_L}{C_{db}}$

We also note that as R_L increases, gain increases and BW decreases. Also, C_{gs} has no effect since it is just a capacitor in parallel with the input voltage source.(Fig. 4)

Now, if C_{gd} is included, a zero is added at g_m/C_{gd} and we see that the output voltage doesn't go to zero at very high freqs, but settles to a non-zero value depending on the relative values of C_{db} and C_{gd} .(Fig. 5)

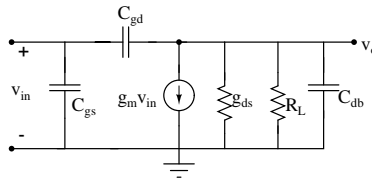
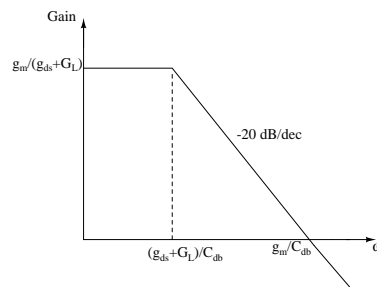
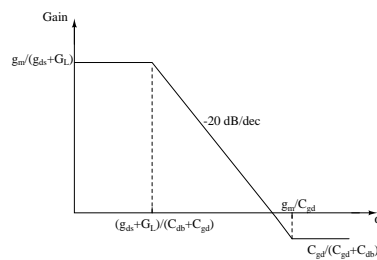


Figure 3: Small signal model at high frequencies

Figure 4: Gain without C_{gd} Figure 5: Gain with C_{gd}