

# ANALOG IC DESIGN.

01 FEBRUARY 2006

1


$$\frac{V_0}{V_i} = \frac{g_m}{g_{ds} + G_L} = \frac{1 - \frac{sC_{gd}}{g_m}}{\left(1 + \frac{s}{P_1}\right)\left(1 + \frac{s}{P_2}\right)}$$



$$P_1 \approx \frac{1}{R_S(C_{gs} + C_{gs}A_{dc})}$$

$$P_2 \approx \frac{g_m + g_{ds} + G_L + G_s}{C_{gs} + C_L}$$

- $C_{GD}$  causes pole spitting - i.e poles move apart as  $C_{GD}$  increases
- The zero of the transfer function is at  $Z = \frac{g_m}{C_{GD}}$

## Common Source Amplifier :

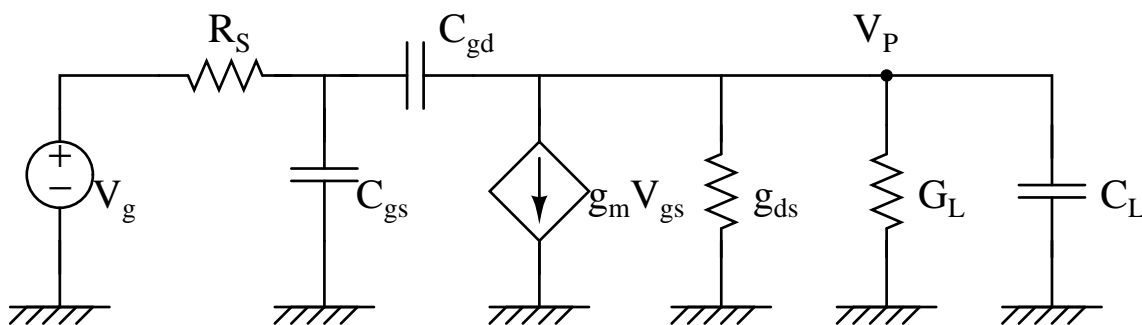

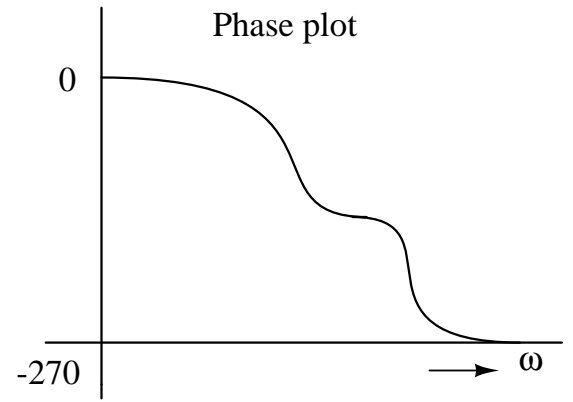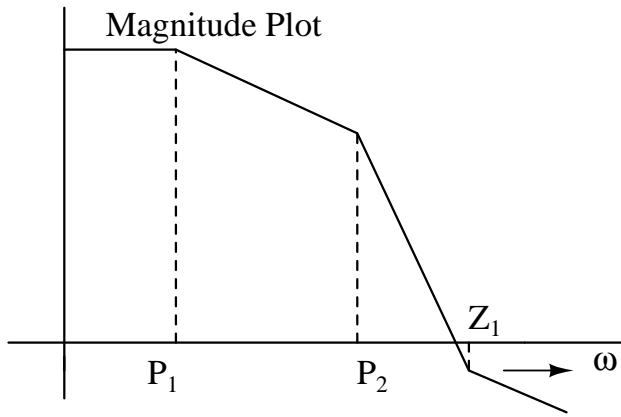

The zero can be before or after the second pole



## 2

loading increases as the size increases

⇒ Amplifier stages of Common source amplifier has moderate  $Z_{out}$

$$Z_{out} = \frac{1}{g_{ds} + sC_L + sg_{gd}}$$

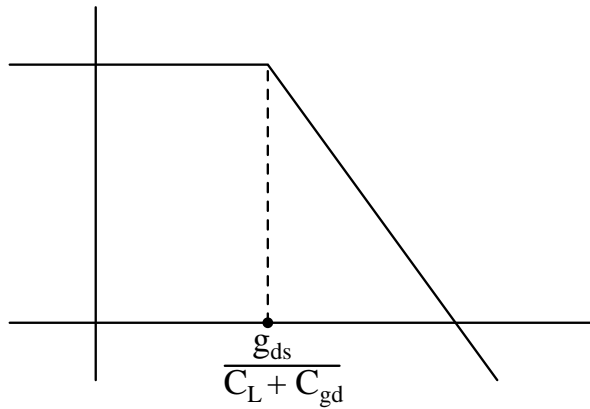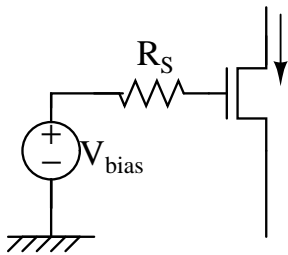As we increase frequency; it becomes a worse current source.



### 3

At high frequencies; we can neglect  $R_s$  compared to  $C_{gs}$ ;  $C_{gs}$  and  $C_{gd}$  will come in series and will have a low impedance

At high frequencies..

To simplify analysis,  
remove  $C_{gs}$

$$\text{Low } f \Rightarrow Z_{\text{out}} = \frac{1}{g_{ds}}$$

$$\text{High } f \Rightarrow Z_{\text{out}} = \frac{1}{g_{ds} + G_s + g_m}$$

