

EE539: Analog Integrated Circuit Design; Lecture 15

Nagendra Krishnapura (nagendra@iitm.ac.in)

06 Feb. 2006

Input Referred noise

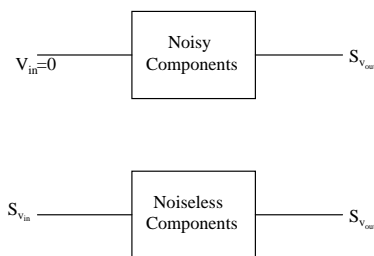


Figure 1: Input Referred noise

Consider a network whose output noise power spectral density is $S_{v_{out}}$. Now, if we make all the components in the network noiseless, then the noise that should be present at the input of the network in order to get the same $S_{v_{out}}$ at the output is called the "input referred noise".

PSD of the input referred noise ($S_{v_{in}}$) is given by

$$S_{v_{in}} = \frac{S_{v_{out}}}{|H(f)|^2} \text{ where } |H(f)| \text{ is the transfer function from input to output.}$$

Input referred noise is useful when we need to compare the noise and input signal level.

For e.g. Let us calculate the input referred noise for a MOSFET. (Fig. 2)

$$S_{v_{in}} = \frac{S_{I_D} + S_{I_R}}{g_m^2} = \frac{\frac{4kT}{R} + \frac{8kTg_m}{3}}{g_m^2} = \frac{4kT}{g_m} \left(\frac{1}{g_m R} + \frac{2}{3} \right)$$

Dynamic Range

Let us calculate the Dynamic Range of a MOSFET amplifier.

Let the input signal have a peak amplitude V_p . Neglecting noise due to load resistance and assuming a bandwidth of B,

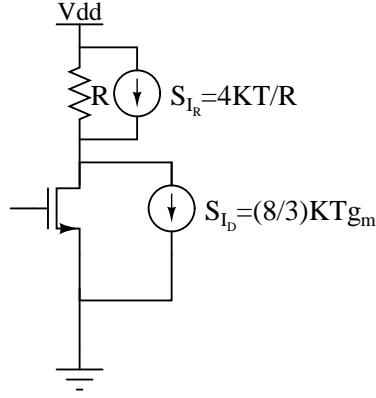


Figure 2: MOSFET noise

$$\left(\frac{S}{N}\right)_i = \frac{\left(\frac{V_p}{\sqrt{2}}\right)}{\left(\sqrt{\frac{8kTB}{3g_m}}\right)}$$

For an SNR of 0dB,

$$V_{pmin} = \sqrt{\frac{16kTB}{3g_m}}$$

For a max Harmonic Distortion of x%,

$$\begin{aligned} \frac{V_{pmax}}{V_{pmin}} &= \frac{4(V_{GS} - V_T)x}{\sqrt{\frac{16kTB}{3g_m}}} \\ &= \frac{4x}{\sqrt{\frac{16kTB}{3}}} \sqrt{\frac{\mu C_{ox} W}{L}} (V_{GS} - V_T)^{\frac{3}{2}} \\ &= \frac{V_{pmax}}{V_{pmin}} = \frac{4x}{\sqrt{\frac{16kTB}{3}}} \frac{1}{\left(\frac{\mu C_{ox} W}{L}\right)^{\frac{1}{4}}} (2I_D)^{\frac{3}{4}} \end{aligned}$$

$$\text{Dynamic Range} = 20 * \log \left(\frac{V_{pmax}}{V_{pmin}} \right)$$

From these equations, we see that the dynamic range can be increased by

- increasing the overdrive for the same aspect ratio
- decreasing the aspect ratio while keeping the bias current constant. (But it is a weak function of aspect ratio)

Common Drain Amplifier(Source Follower)

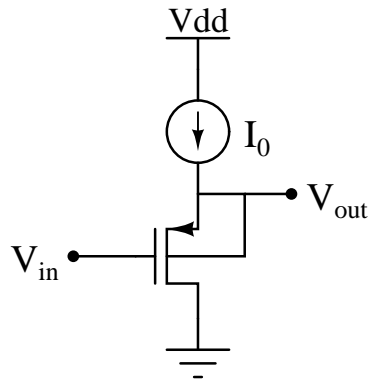


Figure 3: Source Follower

Consider the source follower (Fig. 3)

$$V_{out} = V_{in} + V_{GS} = V_{in} + V_T + \sqrt{\frac{2I_0}{\left(\frac{\mu C_{ox} W}{L}\right)}}$$

Small signal gain = 1 (if there is no body effect)