

COMMON DRAIN AMPLIFIER.

7 FEBRUARY 2006

COMMON DRAIN AMPLIFIER.

The output voltage is

$$V_{out} = V_{in} - V_{gs} \quad (1)$$

$$V_{out} = V_{in} - V_T - \sqrt{\frac{I_{bias}}{\frac{\mu_n C_{ox} W}{2L}}} \quad (2)$$

$$V_T = f(V_{BS}) \quad (3)$$

SMALL SIGNAL EQUIVALENT.

$$v_{gs} = v_{in} - v_{out} \quad (4)$$

$$v_{bs} = -v_{out} \quad (5)$$

$$v_{ds} = -v_{out} \quad (6)$$

$$(7)$$

Writing KCL at the source node

$$g_m(v_{in} - v_{out}) - g_{mbs}v_{out} - g_{ds}v_{out} = 0 \quad (8)$$

$$\frac{v_{out}}{v_{in}} = \frac{g_m}{g_m + g_{mbs} + g_{ds}} \quad (9)$$

☞ Therefore gain is less than one.

☞ Typically g_{mbs} varies from $\frac{g_m}{4}$ to $\frac{g_m}{2}$

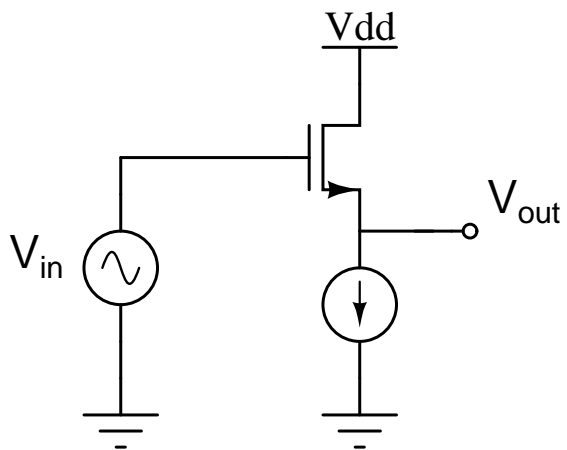


Figure 1: COMMON DRAIN AMPLIFIER

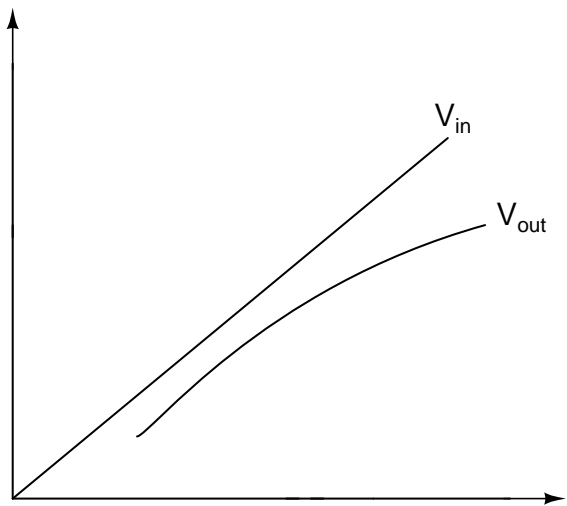


Figure 2: VARIATION OF V_{out} WITH V_{in}

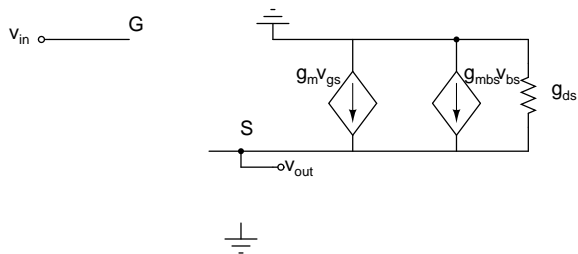


Figure 3: SMALL SIGNAL EQUIVALENT

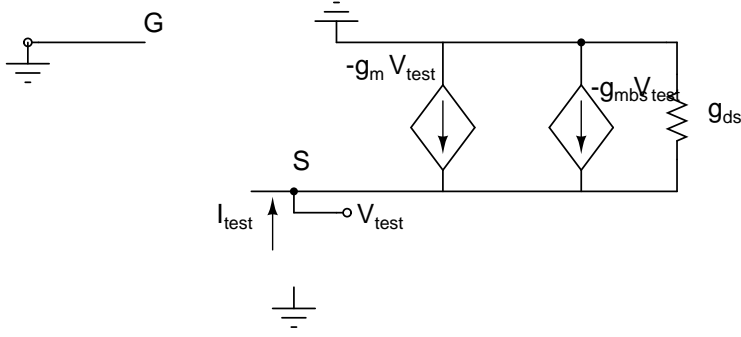


Figure 4: EQUIVALENT CIRCUIT TO FIND OUTPUT RESISTANCE

INPUT AND OUTPUT RESISTANCE.

Input resistance

$$R_{in} = \infty \quad (10)$$

Output resistance

To find the output resistance we apply a test voltage V_{test} and find the current I_{test} through it.

$$I_{test} = g_m V_{test} + g_{mbs} V_{test} + g_{ds} V_{test} \quad (11)$$

$$G_{out} = g_m + g_{mbs} + g_{ds} \quad (12)$$

✎ It is mostly used as a buffer.

HIGH FREQUENCY ANALYSIS.

For High frequency analysis we have to include the effect of C_{gs} , C_{gd} , C_{sb} and C_{db}

The transfer function is obtained as

$$\frac{V_{out}}{V_{in}} = \frac{g_m + sC_{gs}}{g_m + g_{mbs} + g_{ds} + s(C_{gs} + C_{sb})} \quad (13)$$

INPUT AND OUTPUT ADMITTANCE.

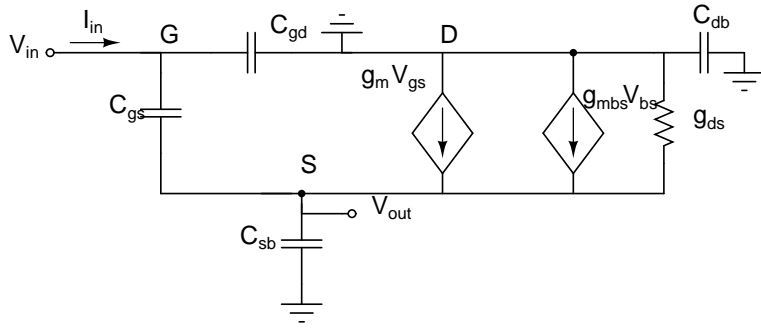


Figure 5: HIGH FREQUENCY EQUIVALENT CIRCUIT

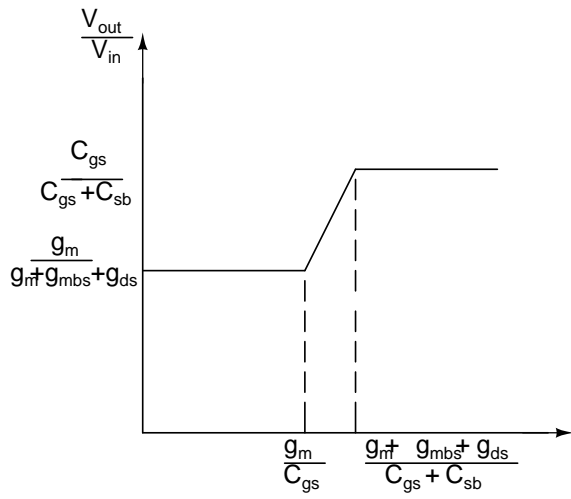


Figure 6: BODE PLOT FOR GAIN

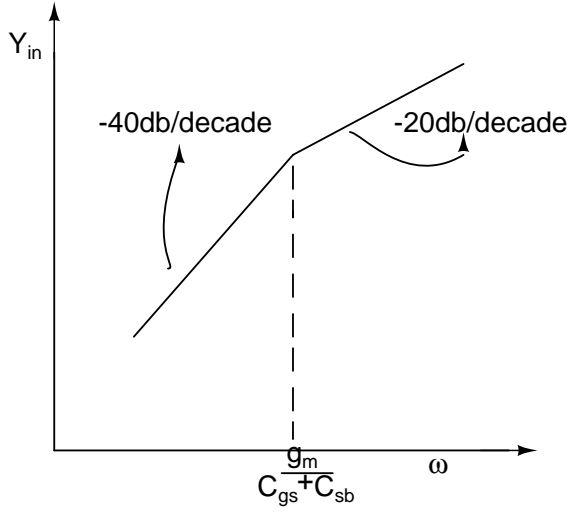


Figure 7: BODE PLOT OF OUTPUT ADMITTANCE

Output admittance

$$Y_{out} = g_m + g_{mbs} + g_{ds} + s(C_{gs} + C_{sb}) \quad (14)$$

Input admittance

$$I_{in} = (V_{in} - V_{out})sC_{gs} \quad (15)$$

$$I_{in} = V_{in} \frac{g_{mbs} + g_{ds} + sC_{sb}}{g_m + g_{mbs} + g_{ds} + s(C_{gs} + C_{sb})} sC_{gs} \quad (16)$$

Approximating,

$$I_{in} = V_{in} \frac{s^2 C_{sb} C_{gs}}{g_m + s(C_{gs} + C_{sb})} \quad (17)$$

$$Y_{in} = \frac{s^2 C_{sb} C_{gs}}{g_m + s(C_{gs} + C_{sb})} \quad (18)$$

☞ This shows it acts as a negative resistance and can be used in oscillators