

EE539: Analog Integrated Circuit Design; Lecture 1

Nagendra Krishnapura (nagendra@iitm.ac.in)

06 Mar. 2006

1

 


Figure 1:

Current i can also be pushed in then upper limit of i is $|i| < I_0$ for both the transistors to be in saturation the limits on gate voltage V_G is given as

$$V_{Dsat0} + V_{Dsat1} + V_T < V_G < V_{DD} - I_0 R_L + V_T$$

2

 


Figure 2:

2

for both the transistors to be in saturation the limits on gate voltage V_G is given as

$$V_{Dsat0} + V_{Dsat1} + V_T < V_{bias} + v < V_{DD} + V_T$$

But in practice the upper limit on $V_{bias} + v$ is only V_{dd} .

To get max. signal swing place V_{bias} at the middle.

3

 


Figure 3:

differential input \Rightarrow differential output.

it also gives flexibility in biasing the transistors.

4

 


Figure 4:

To maximize gain $\uparrow g_m \Rightarrow \uparrow W$ or $\uparrow I_D$.

$$g_m = \frac{2I_0}{V_{GS} - V_T}$$

$$|gain| = \frac{2I_0 R_L}{V_{GS} - V_T} = \frac{2V_R}{V_{GS} - V_T}$$

so to increase gain $\Rightarrow \uparrow V_R$ or $\downarrow V_{GS} - V_T$

but max. value of V_R is $V_{dd} - V_{Dsat}$.

This is a certain limitation in increasing gain.

We can increase gain by increasing bias size of transistors or R_L .

$$\text{Actual gain} = \frac{g_m}{G_L + g_{ds}}$$

To set $G_L = 0$ the load should be a current source.

5

 


Figure 5:

small changes in I_1 causes large change in V_{DS}

for a fixed V_G , adjust I_1 by feedback.

6

 


Figure 6:

We can terminate load R not only to V_{dd} but also to any other V_{bias} .

(The intersection of the load line and the I_D vs V_{DS} characteristics gives V_0)

4

7

To change Bias point without changing the gain; change I_0

But I_D is very sensitive to variations in V_G ; so to get correct value of V_G a current mirror is used

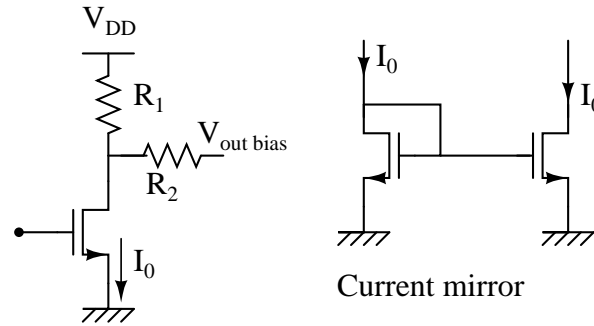


Figure 7:

8

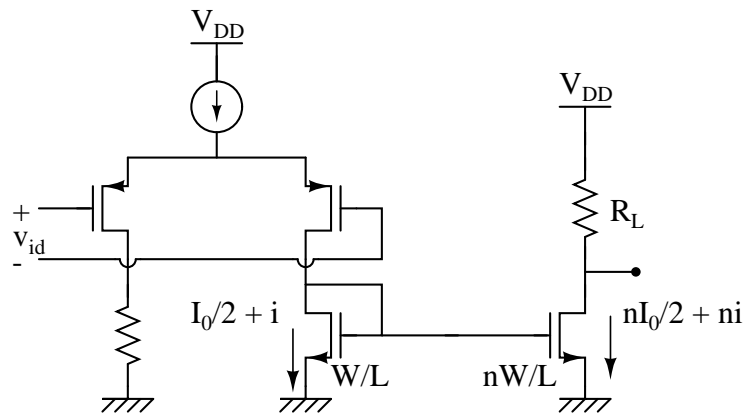


Figure 8:

$$gain = \frac{g_m}{2} v_{id}$$

$$n_i = \frac{ng_m}{2} v_{id}$$

$$v_0 = \frac{ng_m}{2} v_{id} R_L$$

$$Total\ gain = \frac{v_0}{v_{id}} = \frac{ng_m}{2} v_{id} R_L$$

9

To get a gain of g_m / g_{ds}

The problem here is, the output bias point keeps changing
we can also have a problem with mismatch.

 


Figure 9: