

EE539: Analog Integrated Circuit Design;

Nagendra Krishnapura (nagendra@iitm.ac.in)

07 Mar. 2006

1 OUTPUT COMMON MODE FEEDBACK

To fix the output bias point, we can use the configuration shown in fig(1).

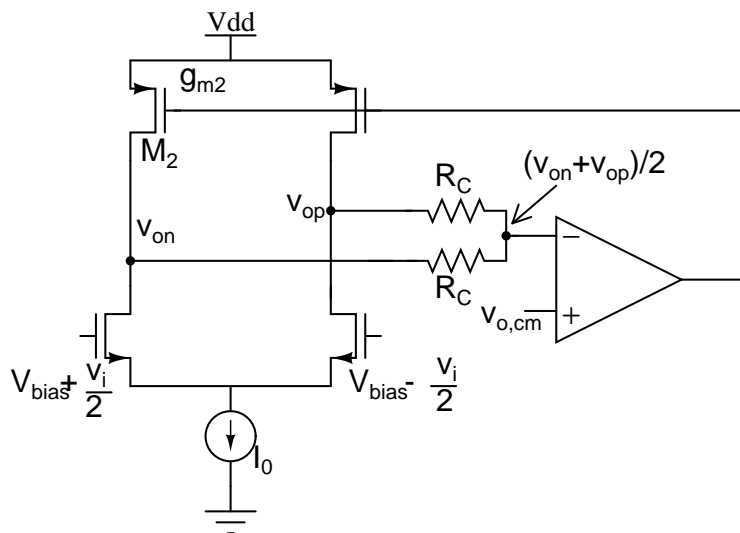


Figure 1: OUTPUT COMMON MODE FEEDBACK

If $\frac{V_{op} + V_{on}}{2} > V_{o,CM}$, then the gate voltage of M_2 increases such that the value of current flowing through the transistors remains constant and make the output voltage bias at $V_{o,CM}$

So, here we can connect $\frac{V_{op} + V_{on}}{2}$ directly to the gate of the transistor M_2 .

Here the output bias point is

$$V_{o,CM} = V_{dd} - V_T + V_{Dsatp}$$

To find the common mode and differential mode loading,

$$R_{CM} = \frac{1}{g_m + g_{ds}}$$

$$R_{diff} = 2R_C \parallel \frac{2}{g_{ds}}$$

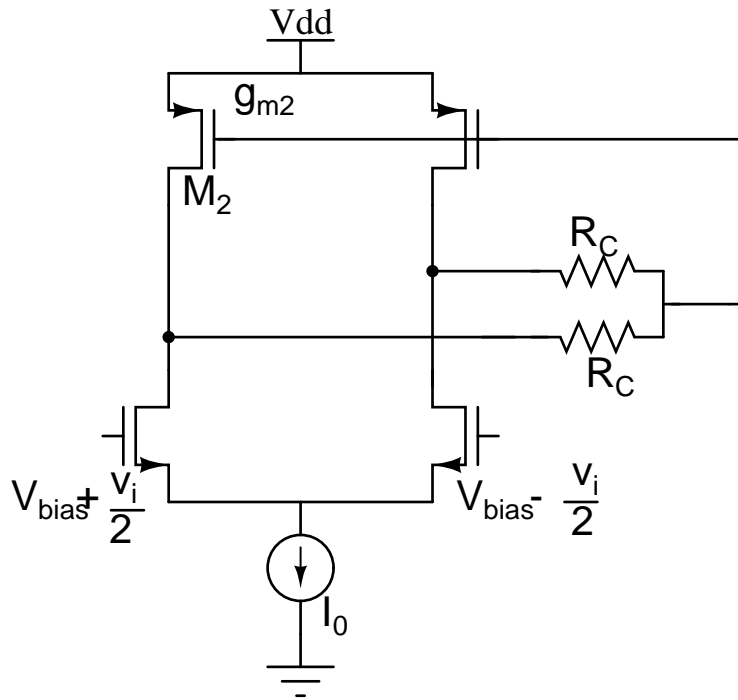


Figure 2: OUTPUT COMMON MODE FEEDBACK

If we observe the above two equations then,

$$R_{CM} \ll R_{diff}$$

That implies the configuration shown gives the fixed output bias point and very large gain.

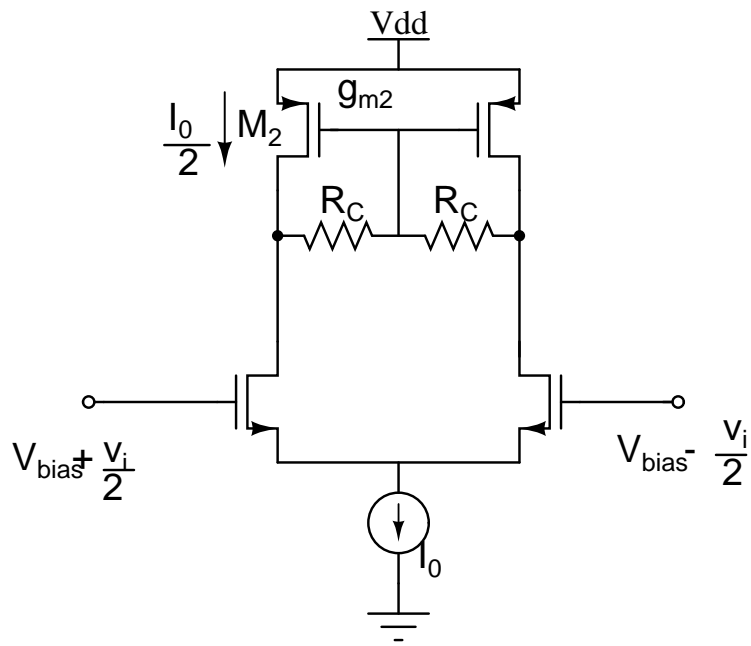


Figure 3: OUTPUT COMMON MODE FEEDBACK

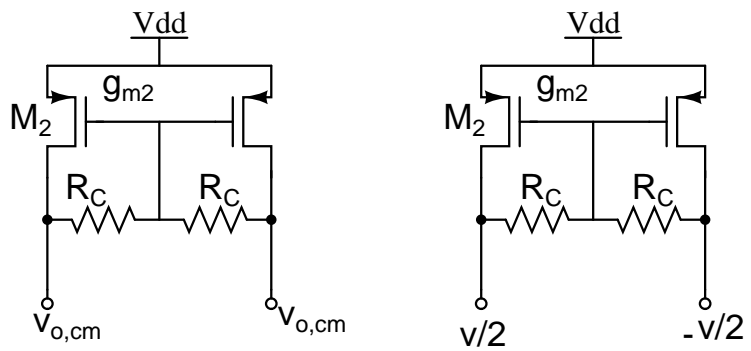


Figure 4: COMMON MODE AND DIFFERENTIAL LOADING

2 NEGATIVE FEEDBACK

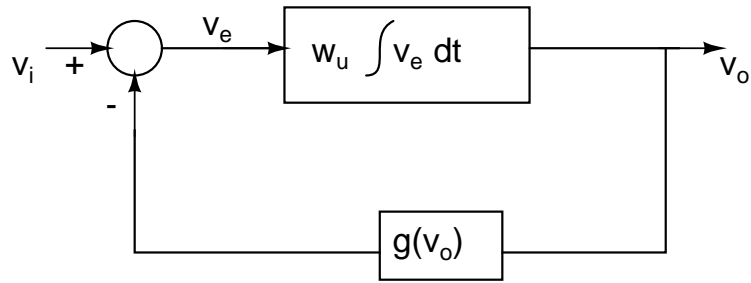


Figure 5: NEGATIVE FEEDBACK SCHEMATIC DIAGRAM

Steady state integrator input (error) = 0

The frequency response of the integrator is shown in the below figure.

$$H(s) = \frac{w_u}{s}$$

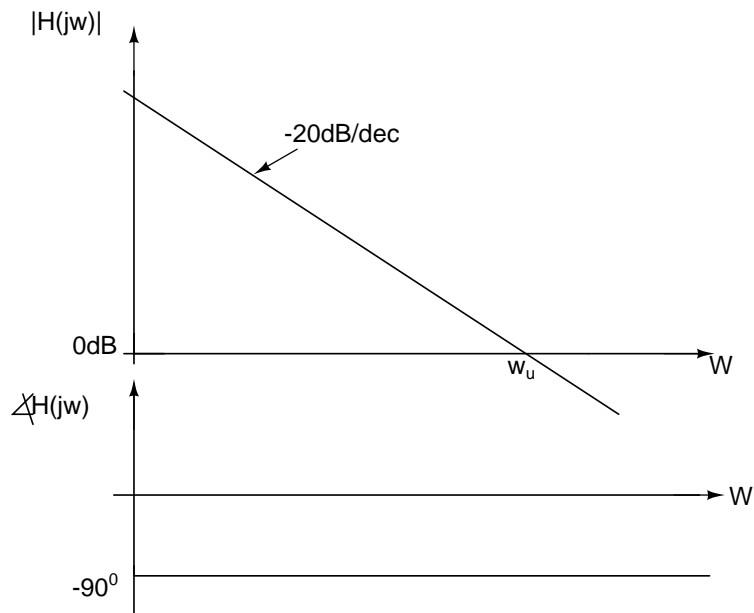


Figure 6: FREQUENCY RESPONSE OF THE INTEGRATOR