

EE539: Analog Integrated Circuit Design;

Nagendra Krishnapura (nagendra@iitm.ac.in)

24 March 2006

1 Single stage opamp

Single stage opamp is nothing but differential amplifier, and is shown in figure(1).

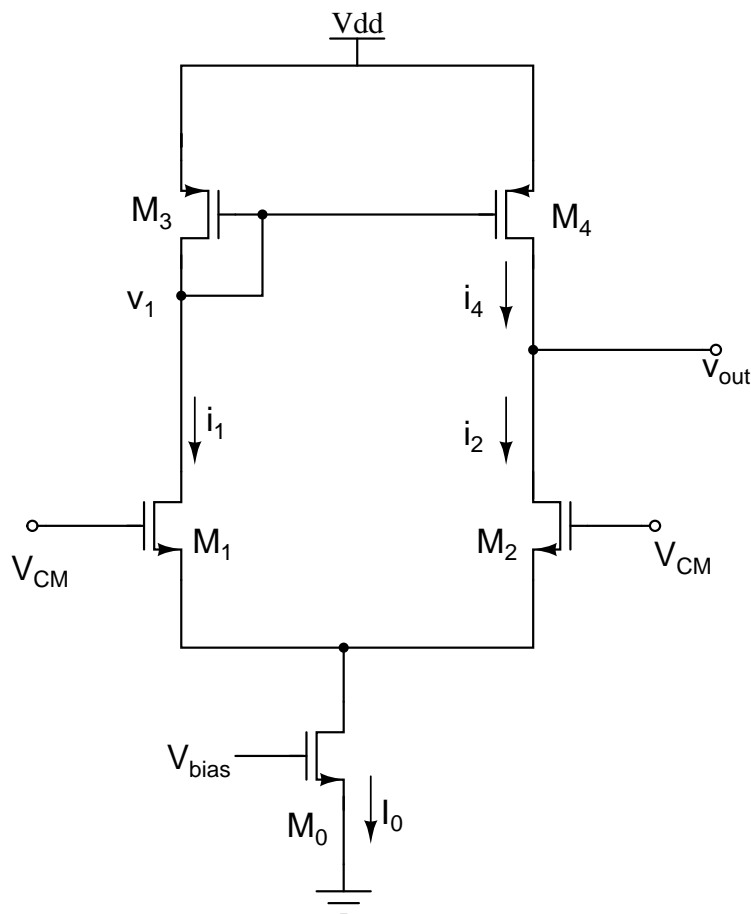


Figure 1: Single stage opamp

In figure(1),DC gain,

$$A_{dc} = g_{m1} \cdot R_{out} = \frac{g_{m1}}{g_{ds1} + g_{ds3}}$$

To increase DC gain, increase r_{ds1}, r_{ds3} . To achieve large R_{out} , we can choose cascode configuration.

2 Telescopic cascode opamp

Let the upper part of differential pair, and convert it into cascode.

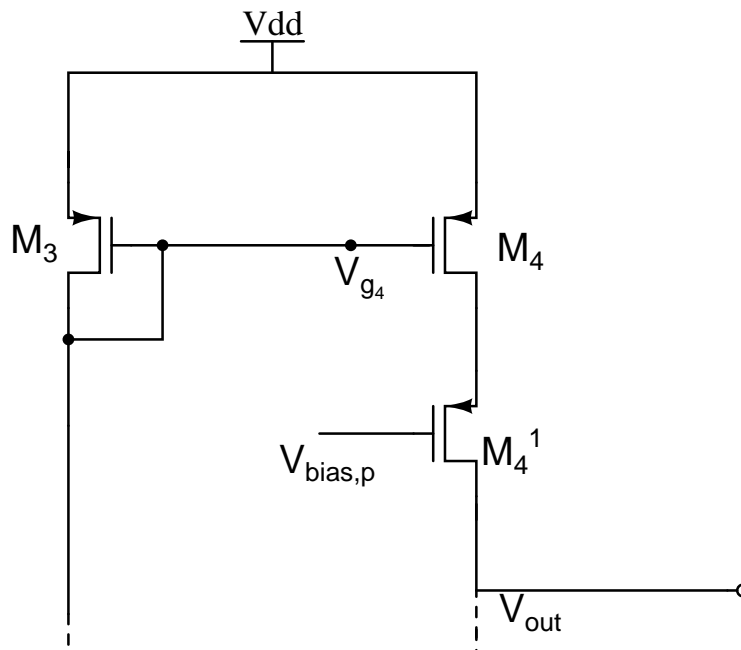


Figure 2: CASCODE CURRENT MIRROR

In the above figure,

$$V_{bias,p} < V_{dd} - V_T - 2V_{dsat}$$

$$V_{out,max} = V_{bias,p} + V_T$$

We can also use the configuration shown below,

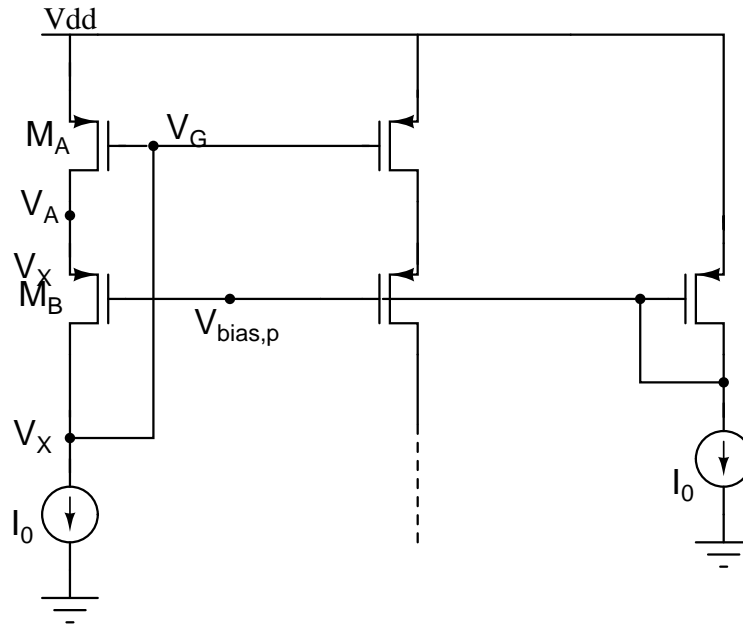


Figure 3: CASCODE CURRENT MIRROR

Similarly, bottom part of differential pair, can be convert it into cascode.

Now by putting all together,

For the Telescopic cascode opamp,

$$G_{out} = \frac{g_{ds1}^2}{g_{m1}} + \frac{g_{ds3}^2}{g_{m3}}$$

$$A_{dc} = g_{m1} \cdot R_{out} = \frac{g_{m1}}{\frac{g_{ds1}^2}{g_{m1}} + \frac{g_{ds3}^2}{g_{m3}}}$$

$$A_{dc} \approx \frac{g_m^2}{2 \cdot g_{ds}^2}$$

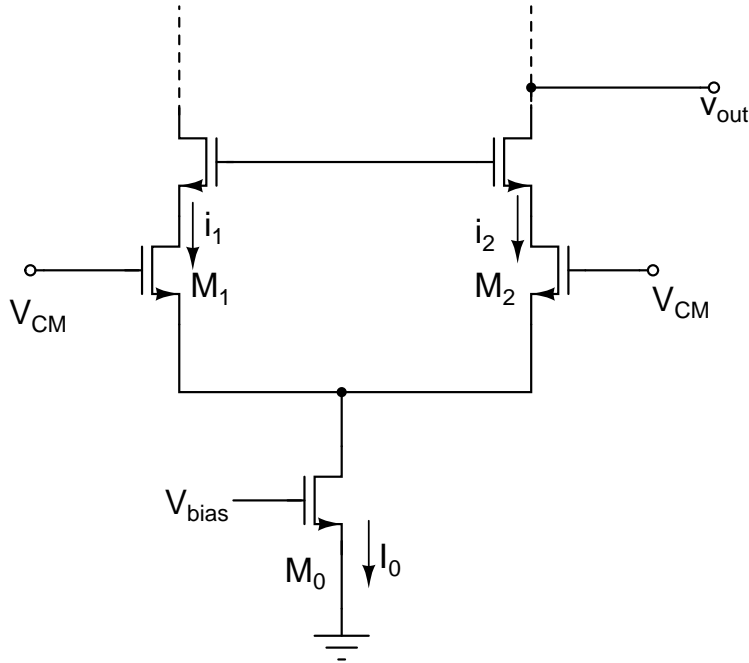


Figure 4:

2.1 Frequency response of telescopic cascode opamp

For the Telescopic cascode opamp,

If C_1 is zero,

$$A = \frac{v_{out}(s)}{v_{in}(s)} = \frac{g_{m1}}{\frac{g_{ds1}^2}{g_{m1}} + \frac{g_{ds3}^2}{g_{m3}} + sC_L}$$

If C_1 is present then,

$$P_1 = \frac{\frac{g_{ds1}^2}{g_{m1}} + \frac{g_{ds3}^2}{g_{m3}}}{C_L}$$

$$P_2 = \frac{g_{m3}}{C_1}$$

$$Z_1 = \frac{2g_{m3}}{C_1}$$

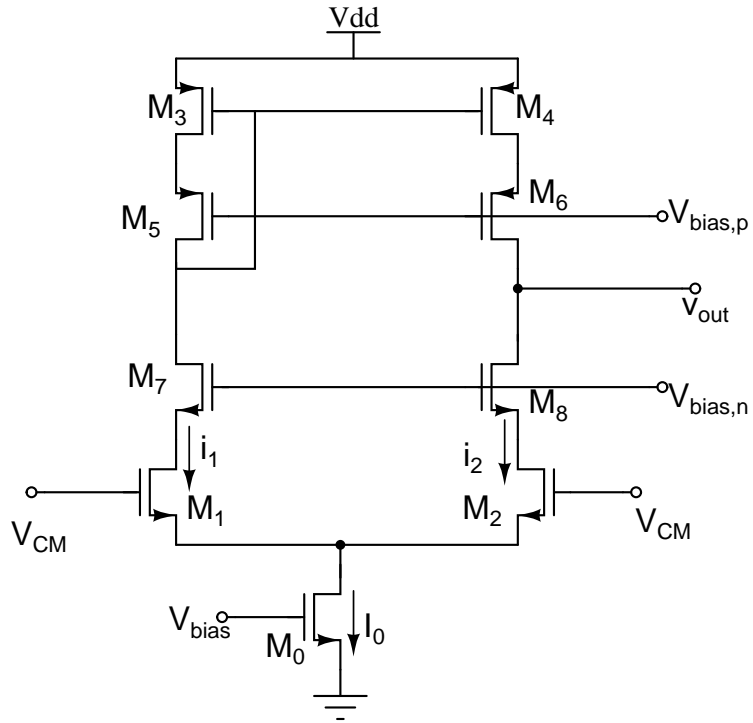


Figure 5: Telescopic cascode opamp

$$w_u = \frac{g_{m1}}{C_L}$$

Frequency response of telescopic cascode opamp is shown in the below figure.

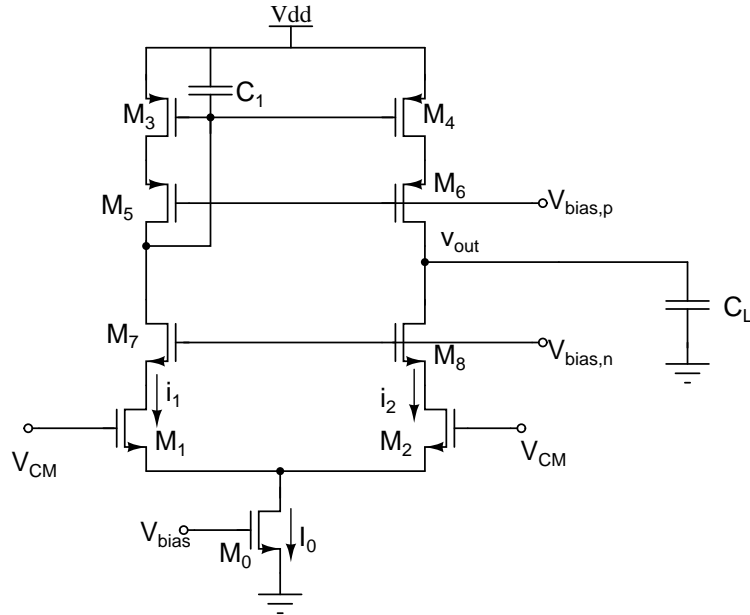


Figure 6: Telescopic cascode opamp

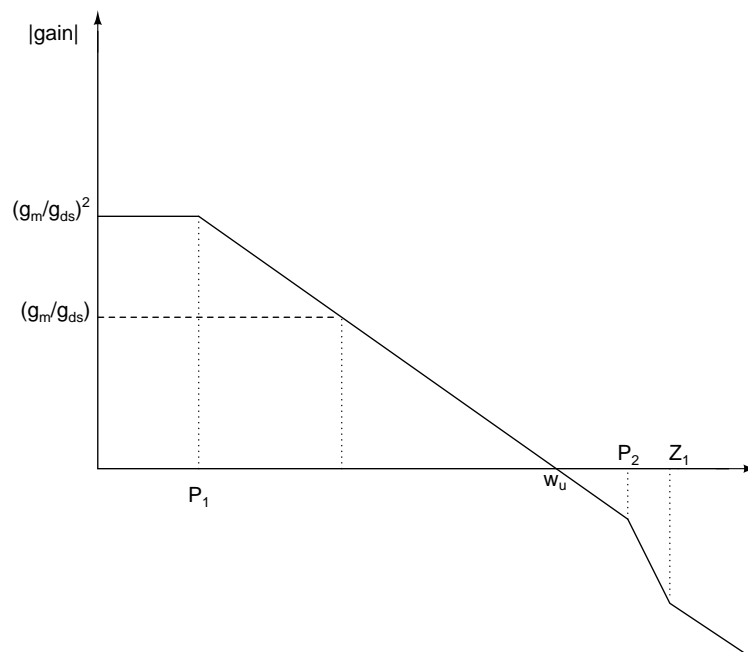


Figure 7: Frequency response Telescopic cascode opamp