

EE539: Analog Integrated Circuit Design

Nagendra Krishnapura (nagendra@iitm.ac.in)

28/3/06

NOISE ANALYSIS OF TELESCOPIC CASCODE.

TRANSISTOR	NOISE CURRENT CONTRIBUTED TO OUTPUT
M_0	0
M_1	i_1
M_2	i_2
M_3	i_3
M_4	i_4
M_5	0
M_6	0
M_7	0
M_8	0

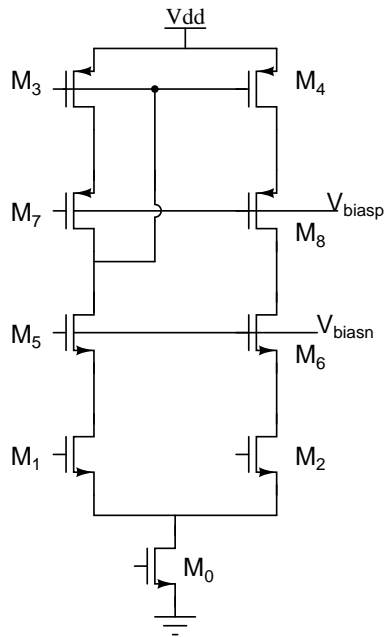


Figure 1: TELESCOPIC CASCODE

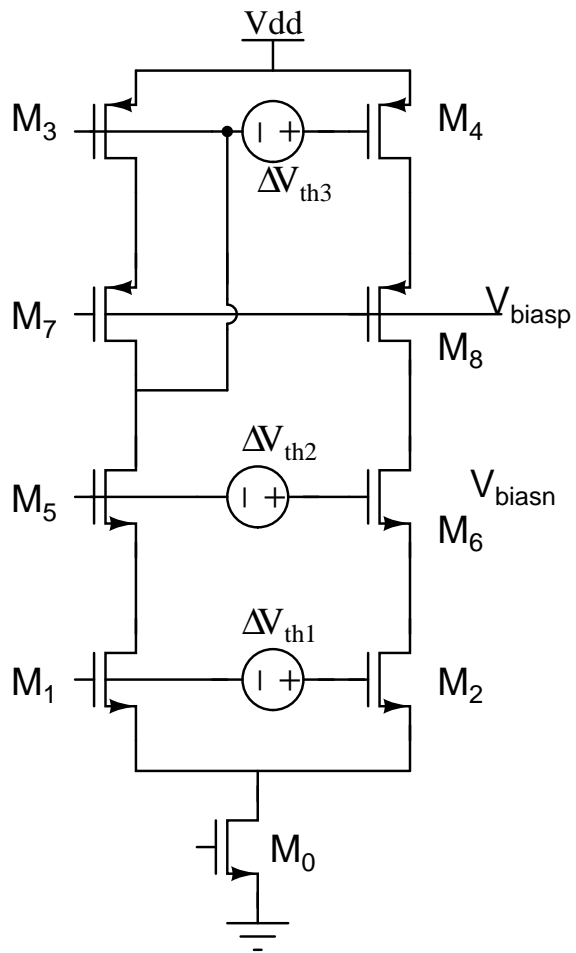


Figure 2: TELESCOPIC CASCODE

EFFECT OF V_{th} MISMATCH

If g_{ds} is neglected, there is no effect for ΔV_{th2}

TRANSISTOR	NOISE CURRENT CONTRIBUTED TO OUTPUT
M_0	0
M_1 and M_2	$g_{m1}\Delta V_{th1}$
M_3 and M_4	$g_{m3}\Delta V_{th3}$
M_5 and M_6	0
M_7 and M_8	0

$$\sigma_{os,in} = \sqrt{\sigma_{V_{th1}}^2 + \sigma_{V_{th3}} \frac{2g_{m3}^2}{g_{m1}^2}}$$

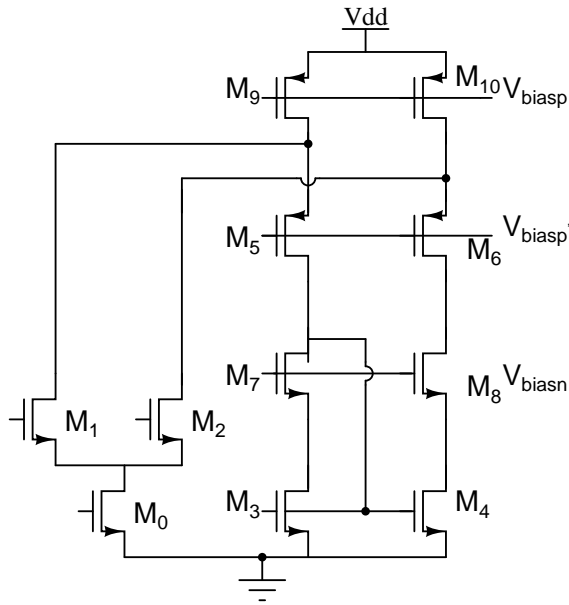


Figure 3: FOLDED CASCODE

NOISE ANALYSIS OF FOLDED CASCODE.

TRANSISTOR	NOISE CURRENT CONTRIBUTED TO OUTPUT
M_0	0
M_1	i_1
M_2	i_2
M_3	i_3
M_4	i_4
M_5	0
M_6	0
M_7	0
M_8	0
M_9	i_9
M_{10}	i_{10}

$$S_{out} = \frac{16kT}{3}(g_{m1} + g_{m3} + g_{m9}) \quad (1)$$

$$S_{in} = \frac{S_{out}}{g_{m1}^2} \quad (2)$$

$$S_{in} = \frac{16kT}{3g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} + \frac{g_{m9}}{g_{m1}}\right) \quad (3)$$

so folded cascode has more noise compared to telescopic cascode.