


EE539: Analog Integrated Circuit Design

Introduction

Nagendra Krishnapura

Department of Electrical Engineering
Indian Institute of Technology, Madras
Chennai, 600036, India

1 Jan. 2008

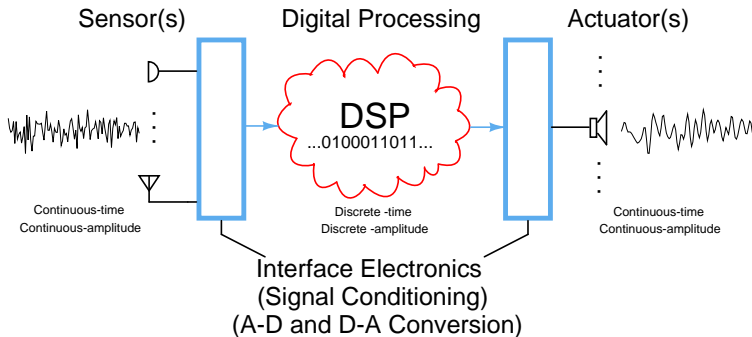


Analog circuits in modern systems on VLSI chips

- Analog to digital conversion
- Digital to analog conversion
- Amplification
- Signal processing circuits at high frequencies
- **Power management-voltage references, voltage regulators**
- **Oscillators**


The last two are found even on many “digital” ICs

Chip Micrograph

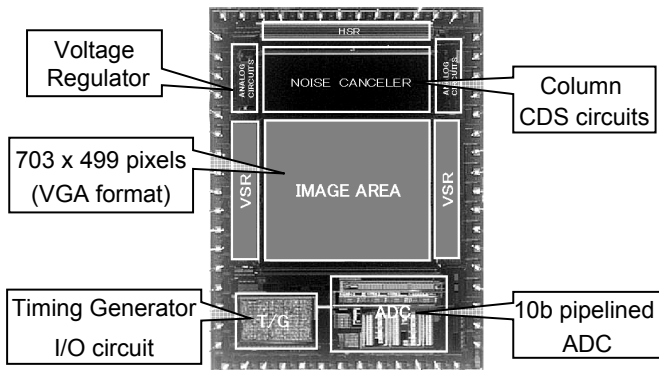


Chip size: 4.74mm x 6.34mm

Die Micrograph

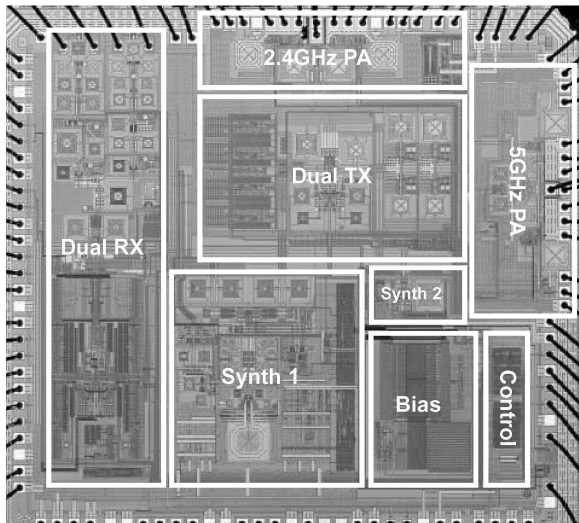

DRAM[ISSCC 2004]

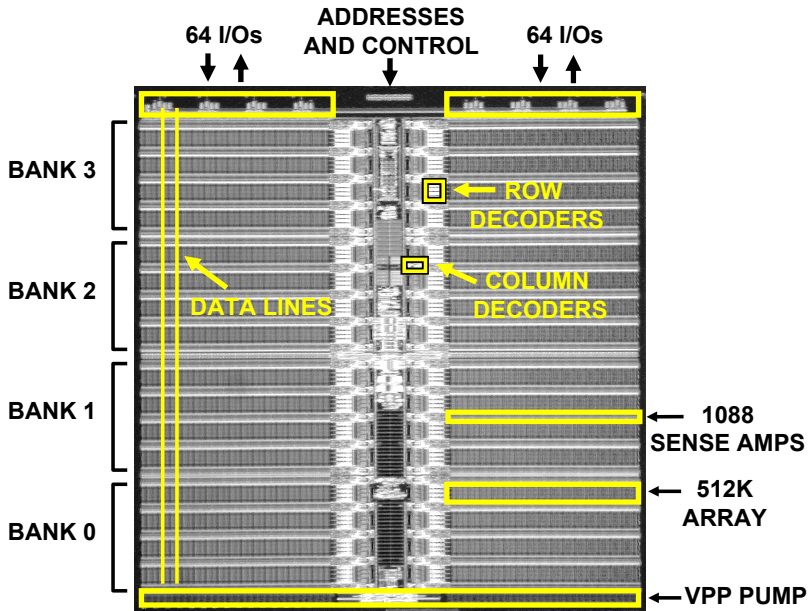

Analog IC design in India

- Many companies starting analog centers
- Multinationals-TI, National, ST, ADI etc.
- Indian start ups-Cosmic, Karmic, Sankalp etc.
- Big demand for skilled designers
- Interesting and profitable activity 😊

Learn to design negative feedback amplifiers on CMOS ICs

- Negative feedback for controlling the output
- Amplifiers, voltage references, voltage regulators, biasing

Course prerequisites

- Circuit analysis
- Small and large signal analysis
- Laplace transforms, frequency response, Bode plots
- Differential equations
- Opamp circuits
- Basic transistor models and circuits

Course contents-Introduction/Review

- Circuit analysis, laplace transforms, differential equations
- Amplifiers using negative feedback
- Negative feedback circuits using opamps

Course contents-Amplifiers on ICs

- Components available in CMOS integrated circuit (IC) processes
- Device models-dc small signal, dc large signal, ac small signal, mismatch, noise
- Basic single transistor amplifier stages
- Transistor biasing, compound amplifier stages
- Differential amplifiers
- Fully differential amplifiers and common mode feedback

Course contents-Design of opamps

- Single stage opamp
- Folded, telescopic cascode opamps
- Two stage opamp
- Fully differential opamps and common mode feedback
- Applications: Bandgap reference, constant g_m bias generation

Design versus Analysis

- Design: Create something that doesn't yet exist
- Analysis: Analyze something that exists

To be able to design

- Knowing analysis is necessary, not sufficient
- Multiple ways of looking at building blocks
- Trial and error approaches
- Intuitive thinking/understanding
- Curiosity
- Open mind
- Thoroughness

- Intuitive thinking **is not** sloppy thinking!
- Relate problems to other problems already solved
- Use boundary conditions, dimension checks etc.
- Build your intuition
 - Solve many problems
 - Think about why the answer is what it is
 - Come up with the form of the solution before applying full blown analysis

Circuit analysis

- Nodal analysis-Kirchoff's Current Law (KCL) at each node
- Solve N simultaneous equations for an N node circuit
- Mesh analysis-Kirchoff's Voltage Law (KVL) around each loop
- Solve M simultaneous equations for a circuit with M independent loops

Nodal analysis

$$\begin{aligned}i_{11}(\bar{v}) + i_{12}(\bar{v}) + \dots + i_{1N}(\bar{v}) &= i_1 \\i_{21}(\bar{v}) + i_{22}(\bar{v}) + \dots + i_{2N}(\bar{v}) &= i_2 \\&\vdots \\i_{N1}(\bar{v}) + i_{N2}(\bar{v}) + \dots + i_{NN}(\bar{v}) &= i_N\end{aligned}$$

- i_{kl} : Current in the branch between nodes k and l
- i_{kk} : Current in the branch between node k and ground
- v_k : Voltage at node k ; $\bar{v} = [v_1 v_2 \dots v_N]^T$
- i_k : Current source into node k

i_{kl} can be a nonlinear function of \bar{v}

Nodal analysis—Linear circuits

$$\begin{aligned}g_{11}v_1 + g_{12}v_2 + \dots + g_{1N}v_N &= i_1 \\g_{21}v_1 + g_{22}v_2 + \dots + g_{2N}v_N &= i_2 \\&\vdots \\g_{N1}v_1 + g_{N2}v_2 + \dots + g_{NN}v_N &= i_N\end{aligned}$$

- g_{kl} : Conductance between nodes k and l
- g_{kk} : Conductance between node k and ground
- v_k : Voltage at node k
- i_k : Current source into node k

Nodal analysis—Independent voltage source

$$\begin{array}{r} \vdots \\ g_{k1}v_1 + g_{k2}v_2 + \dots + g_{kN}v_N = i_k \quad \text{node } k \\ \vdots \\ v_k = V_o \quad \text{node } k \end{array}$$

- Ideal voltage source V_o connected to node k

Nodal analysis—Controlled voltage source

$$\begin{array}{rcl} & \vdots & \\ \mathcal{G}_{k1}v_1 + \mathcal{G}_{k2}v_2 + \dots + \mathcal{G}_{kN}v_N & = & i_k \quad \text{node } k \\ & \vdots & \\ v_k - kv_I & = & 0 \quad \text{node } k \end{array}$$

- Voltage controlled voltage source $v_k = kv_I$ driving node k

Nodal analysis—Controlled voltage source

$$g_{k1}v_1 + g_{k2}v_2 + \dots + g_{kI}v_I + \dots + g_{kN}v_N = i_k \quad \text{node } k$$

$$g_{k1}v_1 + g_{k2}v_2 + \dots + \frac{v_k}{R_m} + \dots + g_{kN}v_N = i_k \quad \text{node } k$$

$$g_{l1}v_1 + g_{l2}v_2 + \dots + g_{lK}v_K + \dots + g_{lN}v_N = i_l \quad \text{node } l$$

$$g_{l1}v_1 + g_{l2}v_2 + \dots - \frac{v_k}{R_m} + \dots + g_{lN}v_N = i_l \quad \text{node } l$$

- Current controlled voltage source $v_k = R_m i_{kl}$ driving node k

Nodal analysis—Controlled current source

$$\begin{aligned}g_{k1}v_1 + g_{k2}v_2 + \dots + g_{kl}v_l + \dots + g_{kN}v_N &= i_k + g_m v_l \\g_{k1}v_1 + g_{k2}v_2 + \dots + g_{kl}v_l - g_m v_l + \dots + g_{kN}v_N &= i_k\end{aligned}$$

- Current controlled voltage source $i_0 = g_m v_l$ driving node k

Nodal analysis—Ideal opamp

$$\begin{array}{rcl} & \vdots & \\ \cancel{g_{m1}v_1} + \cancel{g_{m2}v_2} + \dots + \cancel{g_{mN}v_N} & = & i_m \quad \text{node } m \\ & \vdots & \\ v_k - v_l & = & 0 \quad \text{node } m \end{array}$$

- Ideal opamp with input terminals at nodes k , l and output at node m

Nodal analysis—solution

$$\begin{bmatrix} g_{11} & g_{12} & \cdots & g_{1N} \\ g_{21} & g_{22} & \cdots & g_{2N} \\ \vdots & & & \\ g_{N1} & g_{N2} & \cdots & g_{NN} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{bmatrix}$$
$$G\bar{v} = \bar{i}$$
$$v = G^{-1}\bar{i}$$

- g_{kl} : Conductance between nodes k and l
- g_{kk} : Conductance between node k and ground
- v_k : Voltage at node k
- i_k : Current source into node k
- Modified terms for voltage sources or controlled sources
- Matrix inversion yields the solution

Nodal analysis—solution

$$V_k = \frac{\begin{vmatrix} g_{11}g_{12} \dots i_1 \dots g_{1N} \\ g_{21}g_{22} \dots i_2 \dots g_{2N} \\ \vdots \\ g_{N1}g_{N2} \dots i_N \dots g_{NN} \end{vmatrix}}{\begin{vmatrix} g_{11}g_{12} \dots g_{1k} \dots g_{1N} \\ g_{21}g_{22} \dots g_{2k} \dots g_{2N} \\ \vdots \\ g_{N1}g_{N2} \dots g_{Nk} \dots g_{NN} \end{vmatrix}}$$

- Cramer's rule can be used for matrix inversion

Circuits with capacitors and inductors

$$\begin{bmatrix} Y_{11}(s) & Y_{12}(s) & \dots & Y_{1N}(s) \\ Y_{21}(s) & Y_{22}(s) & \dots & Y_{2N}(s) \\ & & \vdots & \\ Y_{N1}(s) & Y_{N2}(s) & \dots & Y_{NN}(s) \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \\ \vdots \\ V_N(s) \end{bmatrix} = \begin{bmatrix} I_1(s) \\ I_2(s) \\ \vdots \\ I_N(s) \end{bmatrix}$$

$$\mathbb{Y}(s)\bar{V}(s) = \bar{I}(s)$$

$$\bar{V}(s) = \mathbb{Y}^{-1}\bar{I}(s)$$

- Conductances g_{kl} replaced by admittances $Y_{kl}(s)$
- Roots of the determinant of $\mathbb{Y}(s)$ are system poles

Laplace transform analysis for linear systems

Input Output

$$X(s) \quad H(s)X(s)$$

$$e^{st} \quad H(s)e^{st}$$

$$X(j\omega) \quad H(j\omega)X(j\omega)$$

$$e^{j\omega t} \quad H(j\omega)e^{j\omega t}$$

$$\cos(\omega t) \quad |H(j\omega)| \cos(\omega t + \angle H(j\omega)) \quad (\text{Steady state solution})$$

- Linear time invariant system described by its transfer function $H(s)$
- $H(s)$ is the laplace transform of the impulse response
- $s = j\omega$ represents a sinusoidal frequency ω

Laplace transform analysis for linear systems

Transfer function $H(s)$ (no poles at the origin)

$$\begin{aligned} H(s) &= A_{dc} \frac{1 + b_1 s + b_2 s^2 + \dots + b_M s^M}{1 + b_1 s + b_2 s^2 + \dots + b_N s^N} \\ &= A_{dc} \frac{\prod_{k=1}^M 1 + s/z_k}{\prod_{k=1}^N 1 + s/p_k} \end{aligned}$$

Single pole at the origin

$$H(s) = \frac{\omega_u}{s} \frac{\prod_{k=1}^M 1 + s/z_k}{\prod_{k=2}^N 1 + s/p_k}$$

- All poles p_k must be in the left half plane for stability

Frequency and time domain analyses

Frequency domain

- Algebraic equations-easier solutions
- Only for linear systems

Time domain

- Differential equations-more difficult to solve
- Can be used for nonlinear systems as well
- Piecewise linear systems occur quite frequently (e.g. saturation)

Bode plots

- Sinusoidal steady state response characterized by $|H(j\omega)|$, $\angle H(j\omega)$
- Bode plot: Plot of $20 \log |H(j\omega)|$, $\angle H(j\omega)$ versus $\log \omega$ approximated by straight line segments
- Good approximation for real poles and zeros

Very power tools, indispensable for complex calculations, but GIGO!

- Matlab: System level analysis (Frequency response, pole-zero, transfer functions)
- Spice: Circuit analysis
- Maxima: Symbolic analysis

References

- Behzad Razavi, *Design of Analog CMOS Integrated Circuits*, McGraw-Hill, August 2000.
- Hayt and Kemmerly, *Engineering Circuit Analysis*, McGraw Hill, 6/e.
- B. P. Lathi, *Linear Systems and Signals*, Oxford University Press, 2 edition, 2004.
- Sergio Franco, *Design with operational amplifiers and analog ICs*, Tata McGraw Hill.
- H. Takahashi et al., "A 3.9 μm pixel pitch VGA format 10b digital image sensor with 1.5-transistor/pixel," *IEEE International Solid-State Circuits Conference*, vol. XVII, pp. 108 - 109, February 2004.
- M. Zargari et al., "A single-chip dual-band tri-mode CMOS transceiver for IEEE 802.11a/b/g WLAN," *IEEE International Solid-State Circuits Conference*, vol. XVII, pp. 96 - 97, February 2004.
- K. Hardee et al. "A 0.6V 205MHz 19.5ns tRC 16Mb embedded DRAM," *IEEE International Solid-State Circuits Conference*, vol. XVII, pp. 200 - 201, February 2004.