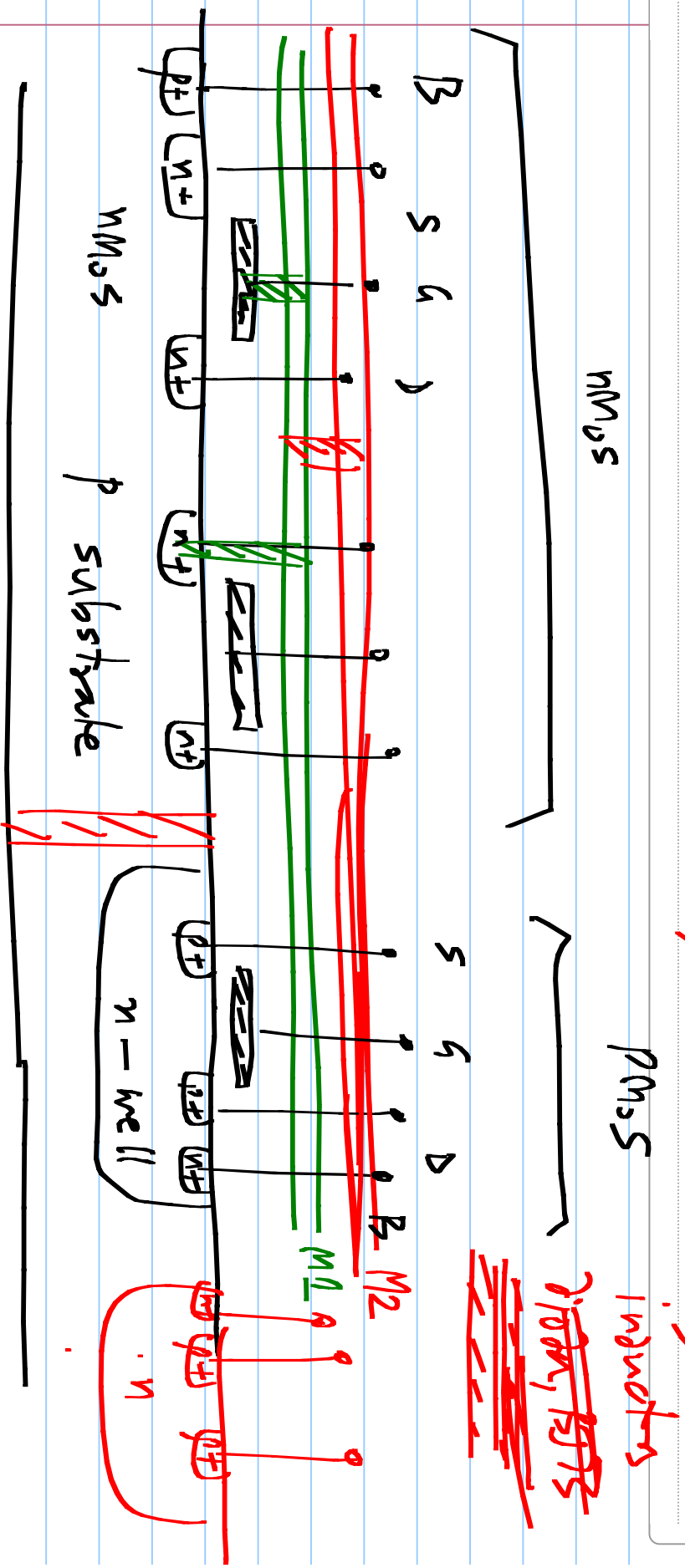


Lecture 2



12/1/2016

pnms, pnms, resistors, capacitors




Resistors in a CMOS process

$$R = \frac{\rho L}{wt}$$

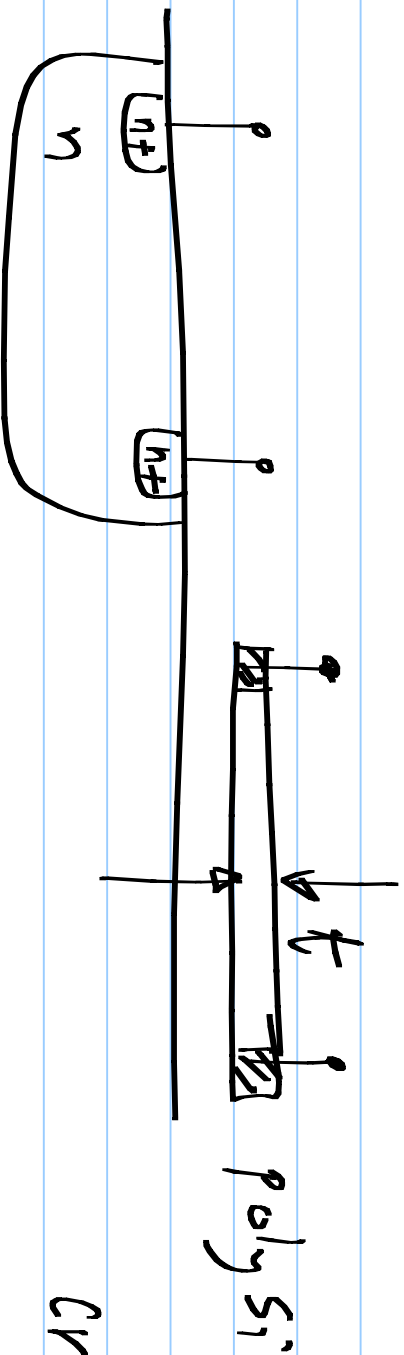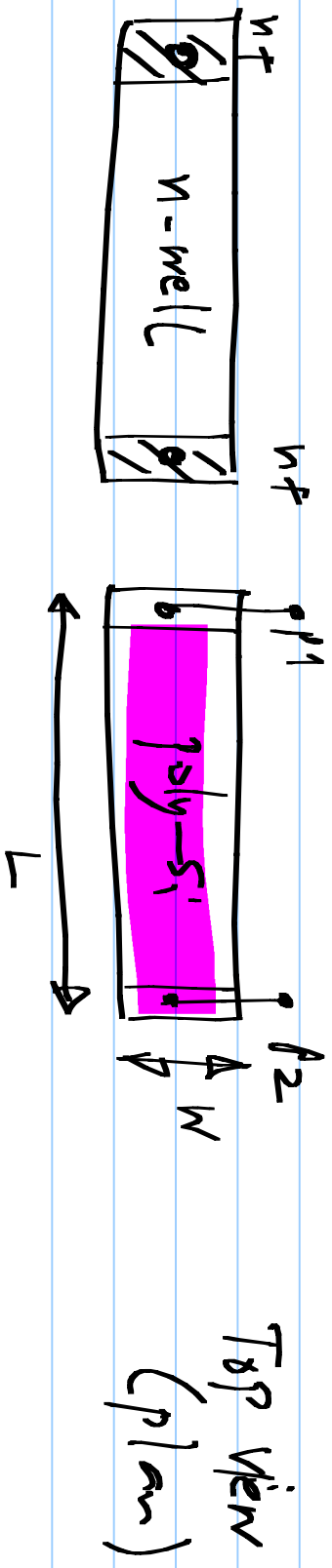

$$R = \left(\frac{f}{t} \right) \frac{L}{W} = R_{sh} \cdot \frac{L}{W}$$


sheet resistance ($\Omega/\square$)


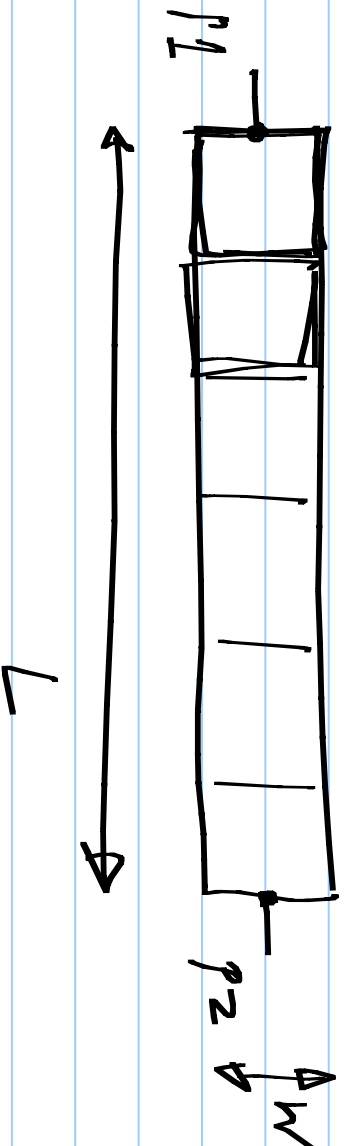


$$\frac{100\Omega/\square}{L} \cdot \frac{W}{L} = 10 \Rightarrow R = \underline{1k\Omega}$$


loop

Mandered layout for high resistances


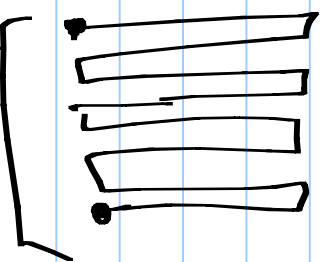


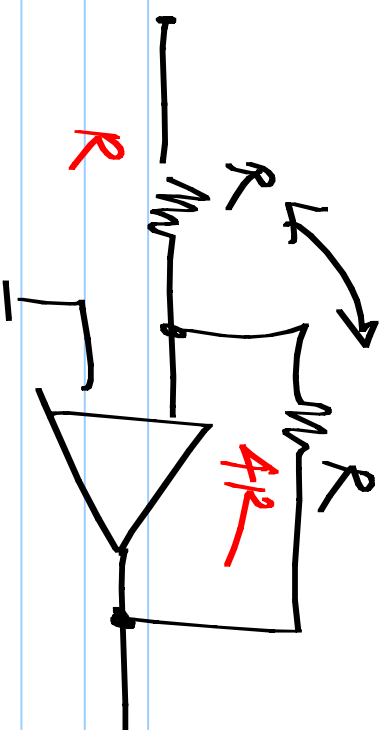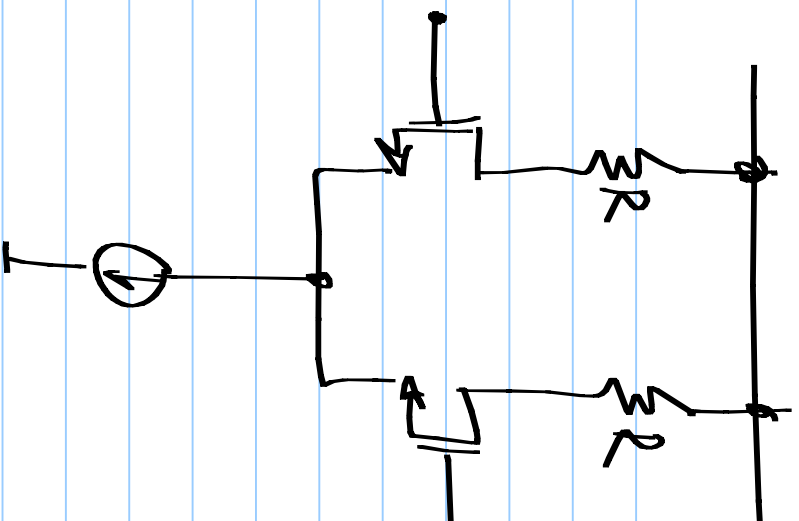

Identical resistors

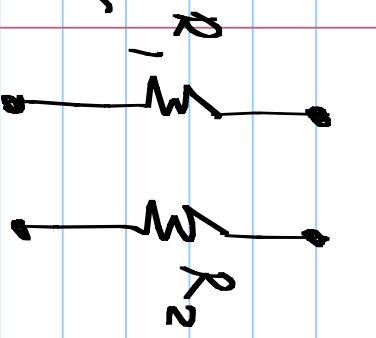


$$\frac{R_1 + R_2}{2} = R$$

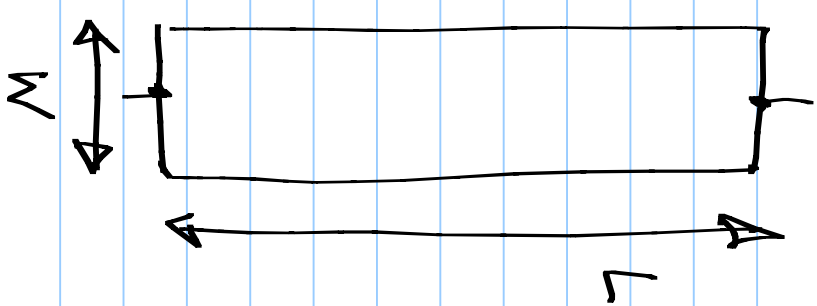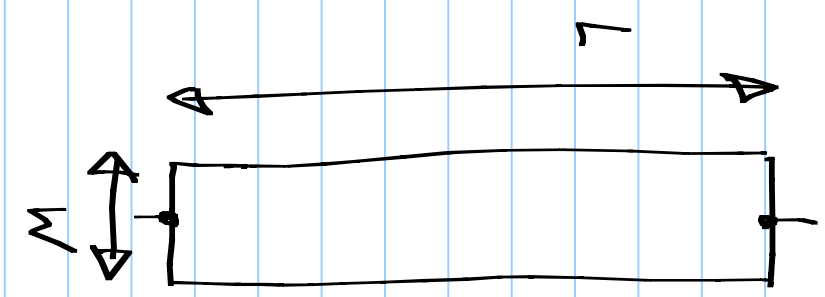

Random mismatch

$$(R_{sh}) \cdot \frac{L}{W}$$

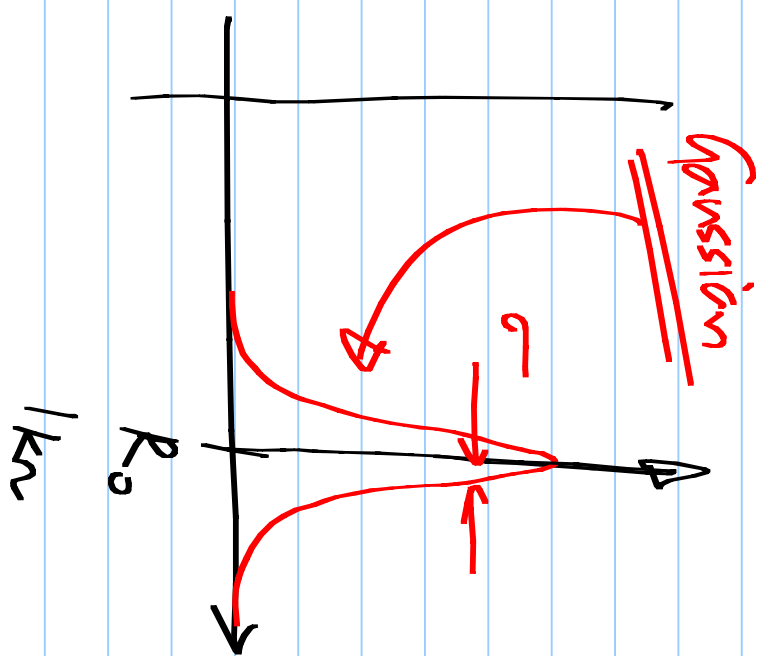


$$R = \frac{\Delta R}{2}$$

$$\Delta R = R_2 - R_1$$

$$\sqrt{\pm (R_1 - R_0)^2}$$

$$\sigma(R)$$

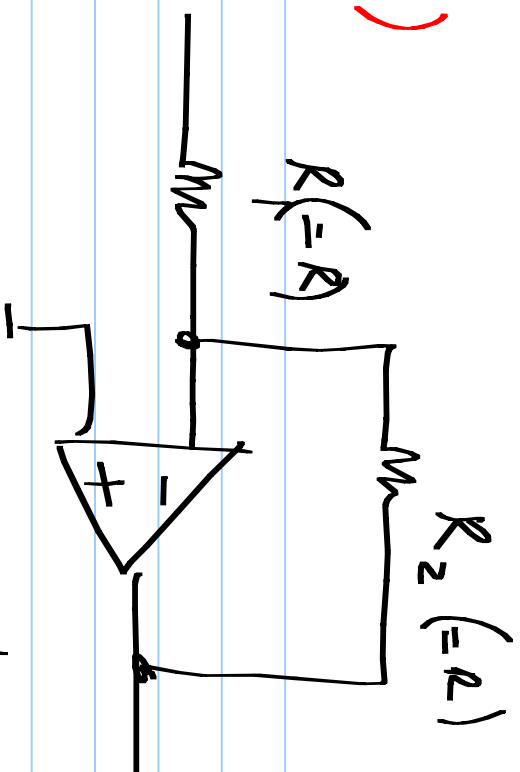
$$\sigma_{R_1} = \sigma \left(\frac{R}{R_0} \right)$$



$$| \text{would like} \quad 0.999 < |A| < 1.001$$

| have

$$0.998 < |A| < 1.002$$

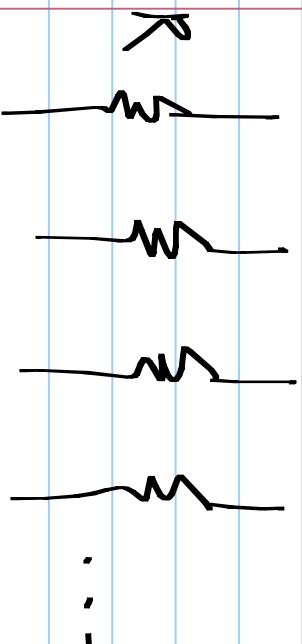

$$\sigma_R = \sigma \left(\frac{R}{R_0} \right) = 1\%$$

mean

$$|A_v| = \left| \frac{V_o}{V_i} \right|$$