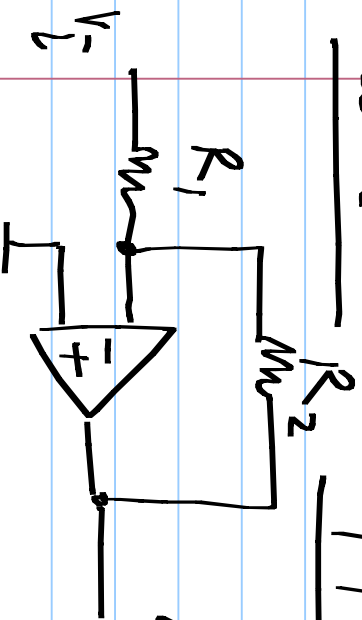


Lecture 3

13/1/2016

I'd like $\sigma(A_v) = 0.001$



$$A_v = \left| \frac{v_o}{v_i} \right| = \frac{R_2}{R_1} = \frac{R_o + \Delta R_2}{R_o + \Delta R_1}$$

$$R_1 = R_2 = R_o$$

$$= \frac{R_o \left(1 + \frac{\Delta R_2}{R_o} \right)}{R_o \left(1 + \frac{\Delta R_1}{R_o} \right)} \approx 1 + \frac{\Delta R_2}{R_o} - \frac{\Delta R_1}{R_o}$$

$$\text{mean} = R_o$$

$$\text{mean}(A_v) = 1, \quad 2\sigma_R^2$$

$$\sigma\left(\frac{\Delta R}{R_o}\right) = \sigma_R$$

$$\sigma^2(A_v) = \sigma^2\left(\frac{\Delta R_2}{R_o}\right) + \sigma^2\left(\frac{\Delta R_1}{R_o}\right)$$

$$\Delta R = R_k - R_o$$


$$\sigma(A_v) = \sqrt{2} \sigma_R \quad \text{e.g. } 0.002$$

$$\left[\begin{array}{l} R_a = R_o + \Delta R_o \\ R_b = R_o + \Delta R_b \end{array} \right] \quad \left[\begin{array}{l} R_x \\ 2R_o + \Delta R_a + \Delta R_b \end{array} \right]$$

$$\sigma \left(\frac{\Delta R_o}{R_o} \right) = \sigma_R$$

$$\sigma^2 \left(\frac{\Delta R_a}{2R_o} \right) = \frac{\sigma_R^2}{4}$$
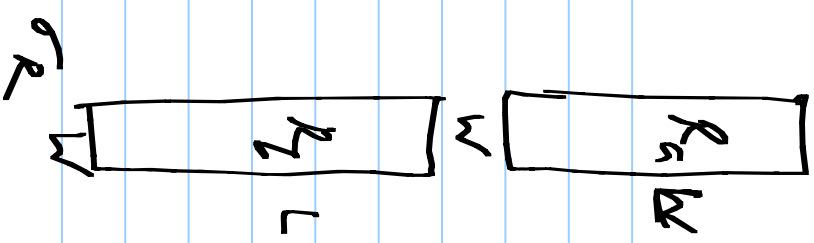
$$\sigma^2 \left(\frac{\Delta R_x}{2R} \right) = \frac{\sigma_R^2}{2}$$




$$2R_o \left(1 + \frac{\Delta R_a + \Delta R_b}{2R_o} \right)$$

$$\underbrace{\hspace{10em}}_{\sigma_R^2/2} \quad \underbrace{\hspace{10em}}_{2wL} \quad \underbrace{\hspace{10em}}_{\sigma_R/\sqrt{2}}$$

deviations from R_0

$$\sigma_R = \sigma \left(\frac{\Delta R}{R_0} \right) = \frac{A_R}{\sqrt{WL}}$$

mean

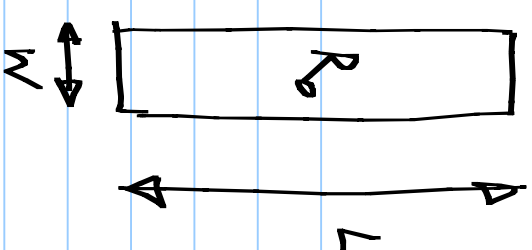


$$R_0 = R_{sl} \cdot \frac{L}{W}$$

$$\frac{1}{\mu m^2} \left[\frac{10 \mu m}{0.1 \mu m} \right] \left[\frac{100 \mu m}{1 \mu m} \right] 100 \mu m^2$$



ϕ_0 / σ $0.18 / \sigma$

~~Random~~

mismatch

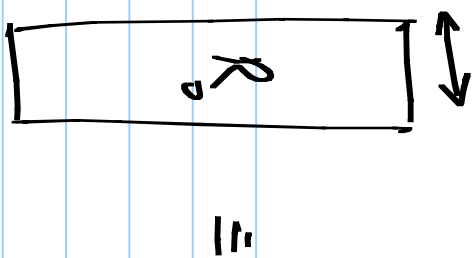


✓

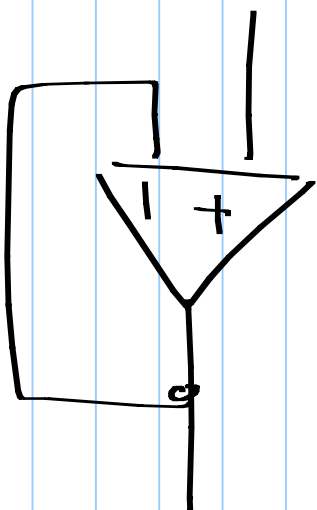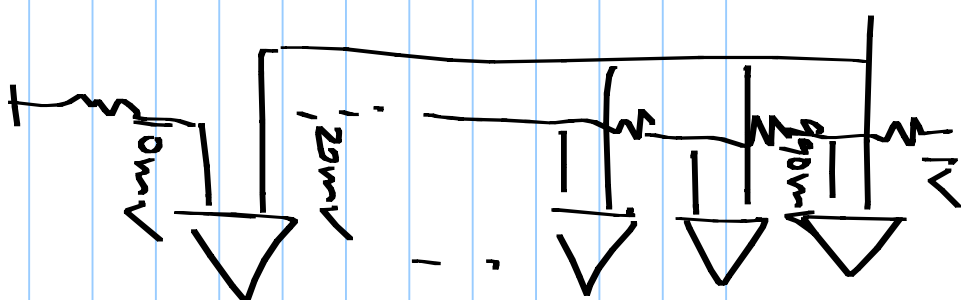




Systematic mismatch


$$R = R_{sh} \cdot \frac{L}{W}$$

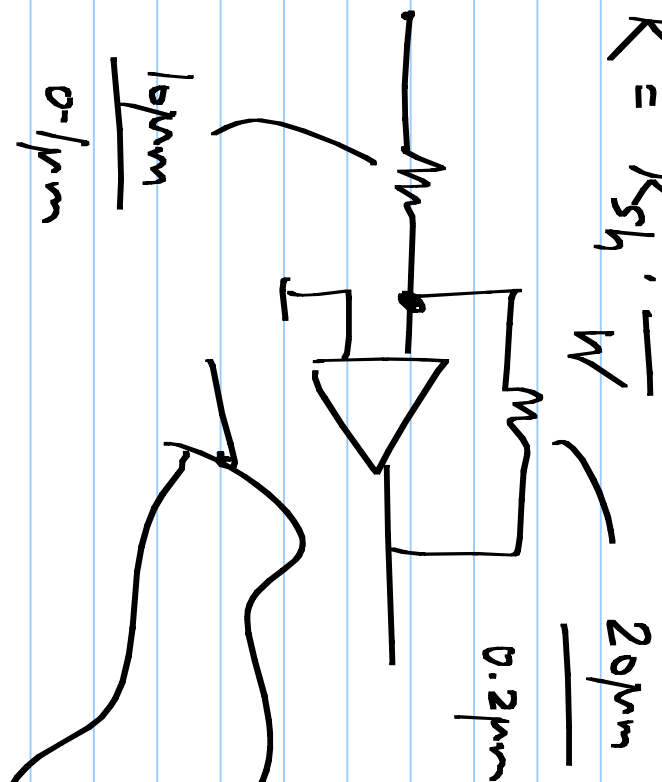


$$R = \rho \cdot \frac{L}{Wt}$$

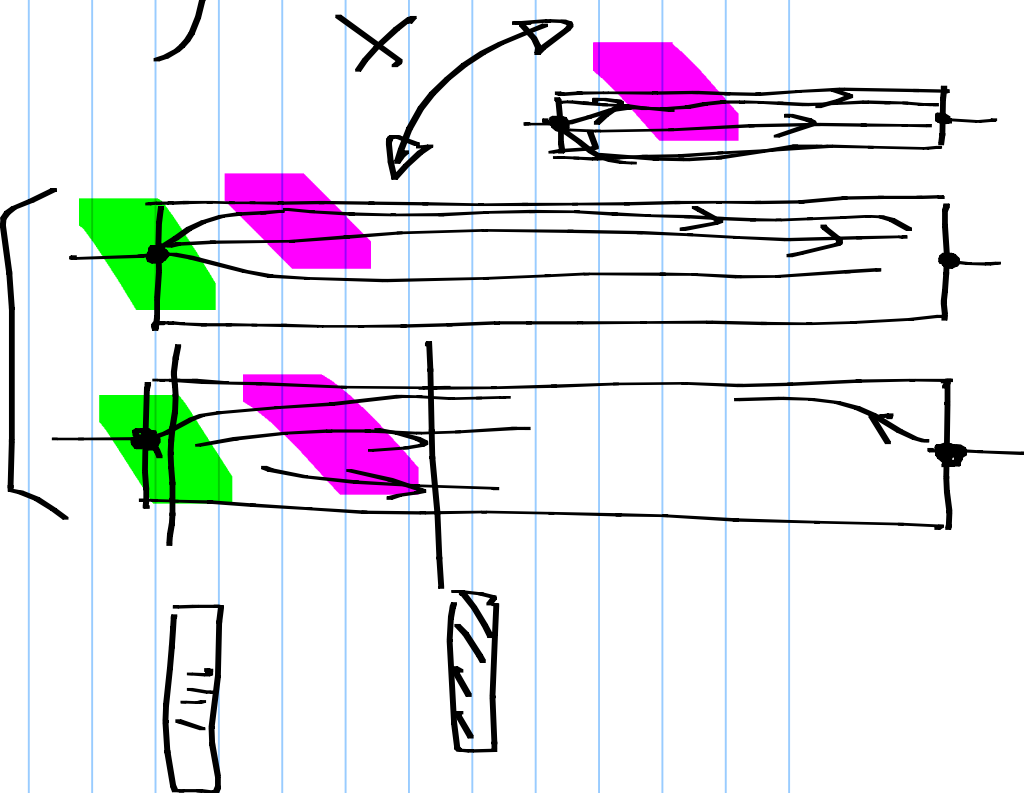

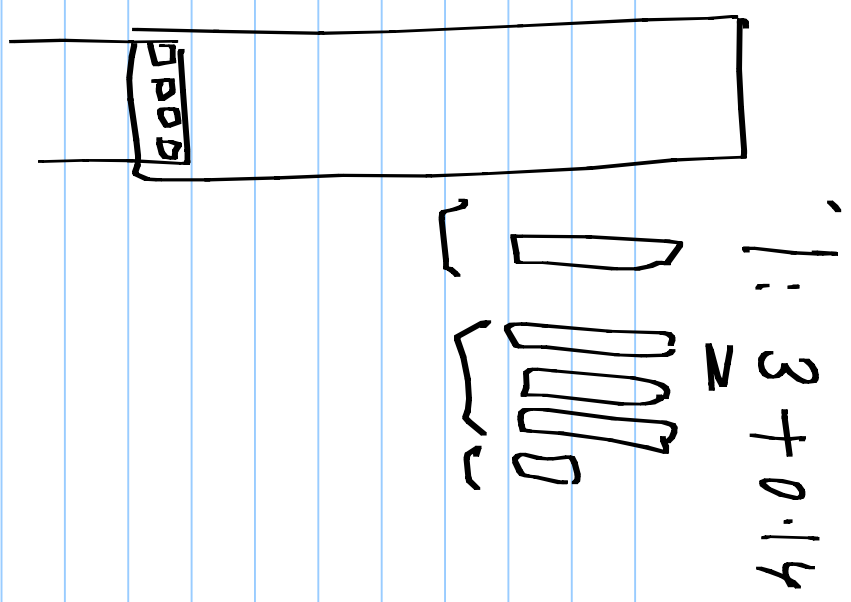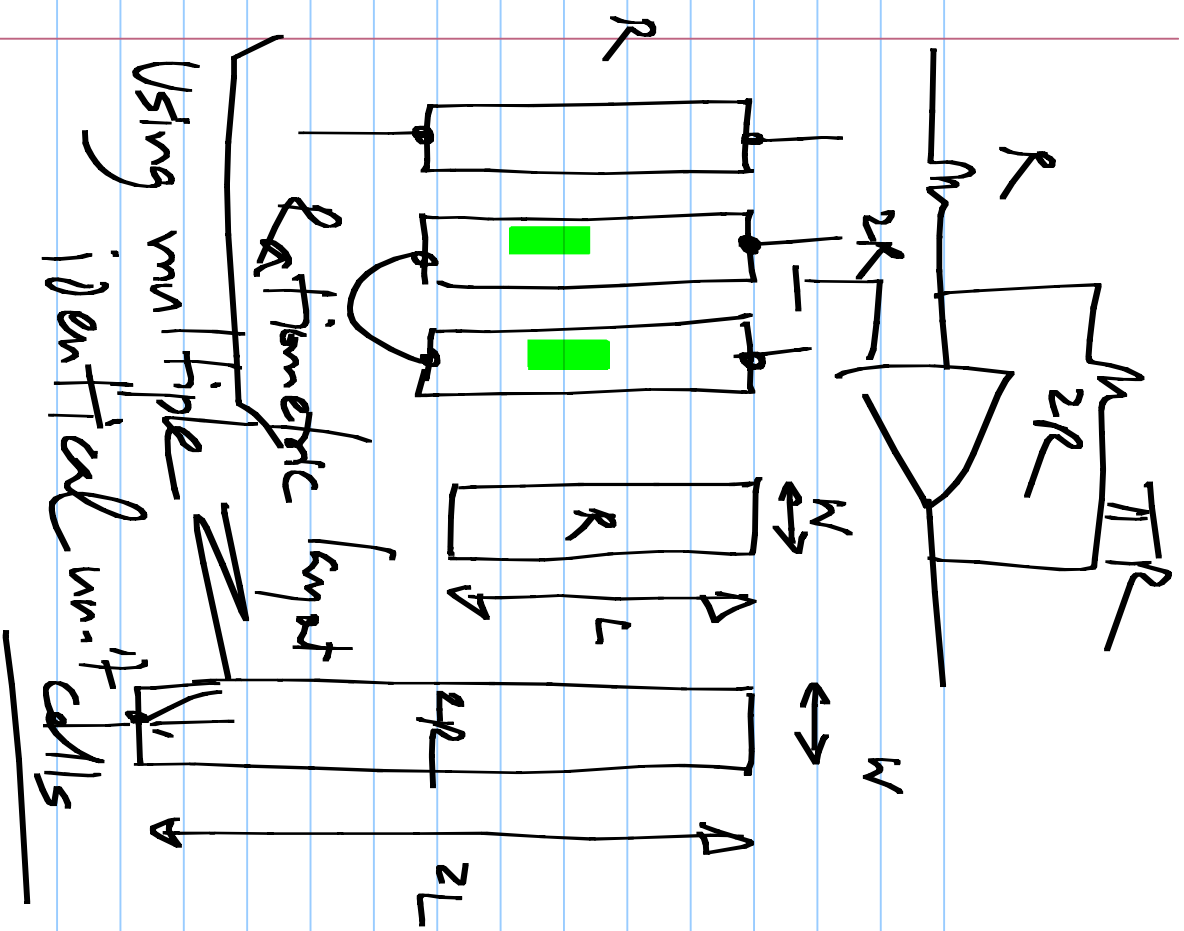

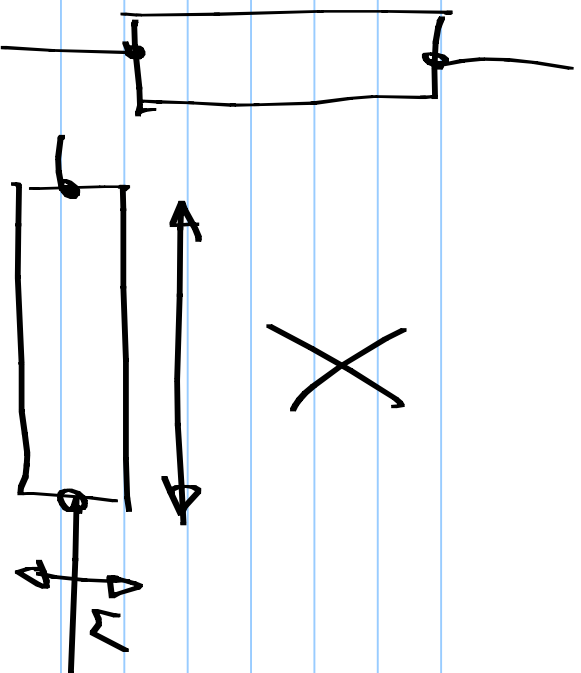

lay them out in
the same orientation

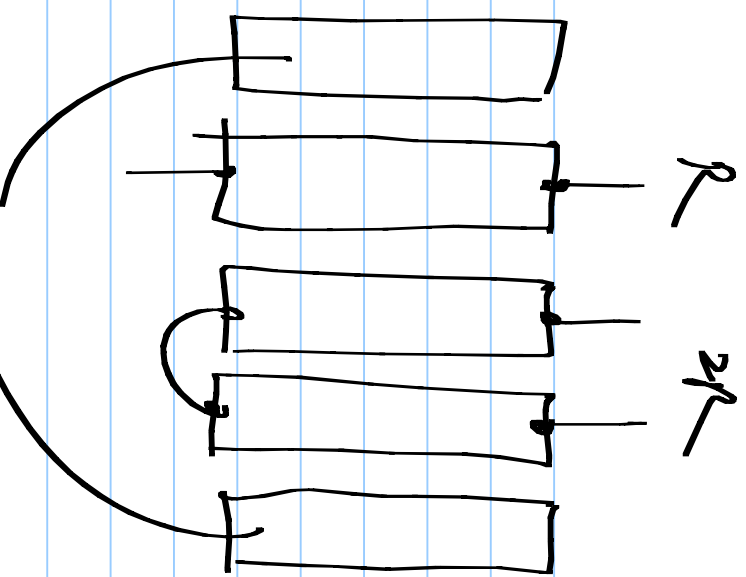

clummy device



Resistor on a chip $R = \underbrace{R_{sh}}_{\text{process constant}} \cdot \frac{L}{W}$

* Random mismatch $\sigma_R = \sigma\left(\frac{\Delta R}{R_0}\right) = \sqrt{\frac{A_R}{WL}}$
— Large size to reduce mismatch


* Systematic mismatch
— Identical unit layouts (same orientation)
— Dummy devices

Process variation: $R_{sh} = 100\Omega_{\text{typ.}} \pm 20\%$ Accuracy
poor

Resistor model

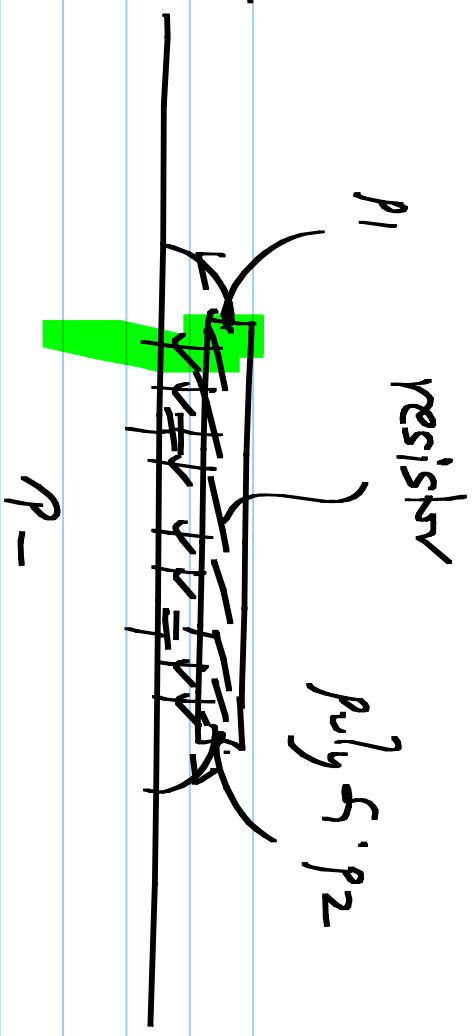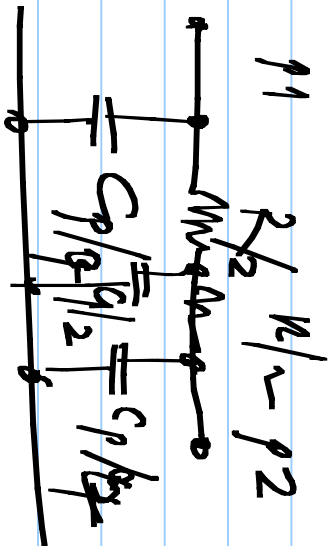
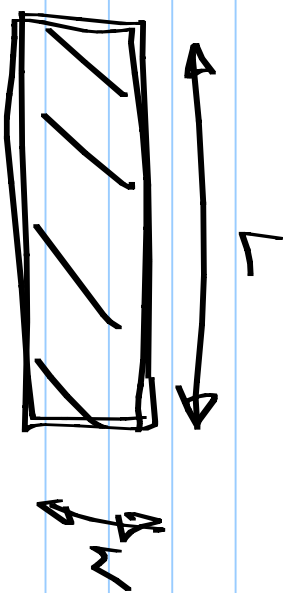
$$C_p = C'_R \cdot WL + C''_R (2W + 2L)$$



cap. per area
fringe cap.
per unit perimeter ft/μm