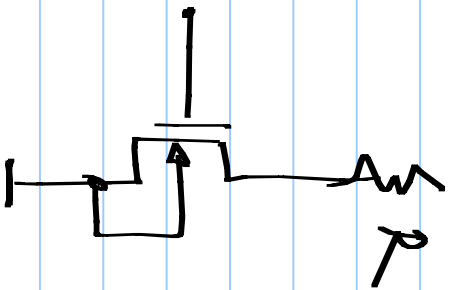


19/1/2016

Lecture 6

CS

Body effect in a common source amplifier




Both source & bulk are incrementally grounded, $v_{bs} = 0$

No change : gain = $-g_m R$

$$g_m, g_{ds} = 0$$

g_{mb}

Common gate amplifier

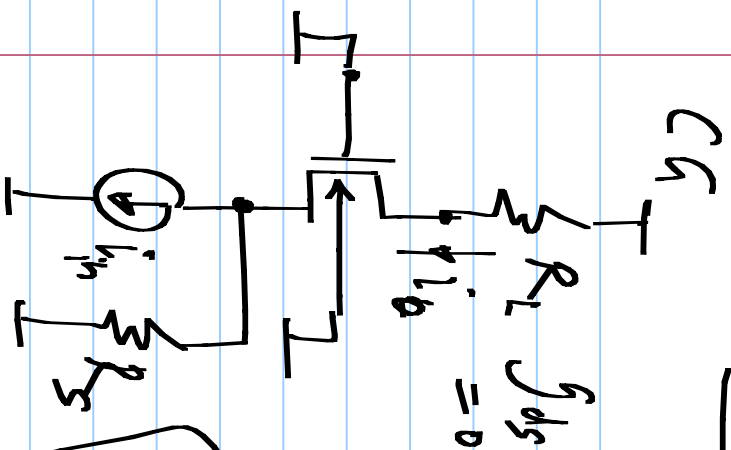


$$\text{gain} : \frac{i_o}{i_{in}} = \frac{R_L}{(g_m + g_{mb}) + r_s}$$

$$R_L : \frac{1}{(g_m + g_{mb}) \cdot r_{ds} \cdot R_s + r_{ds} + R_s}$$

Body effect improves the performance

$g_m, g_{ds} \rightarrow g_{mb}$

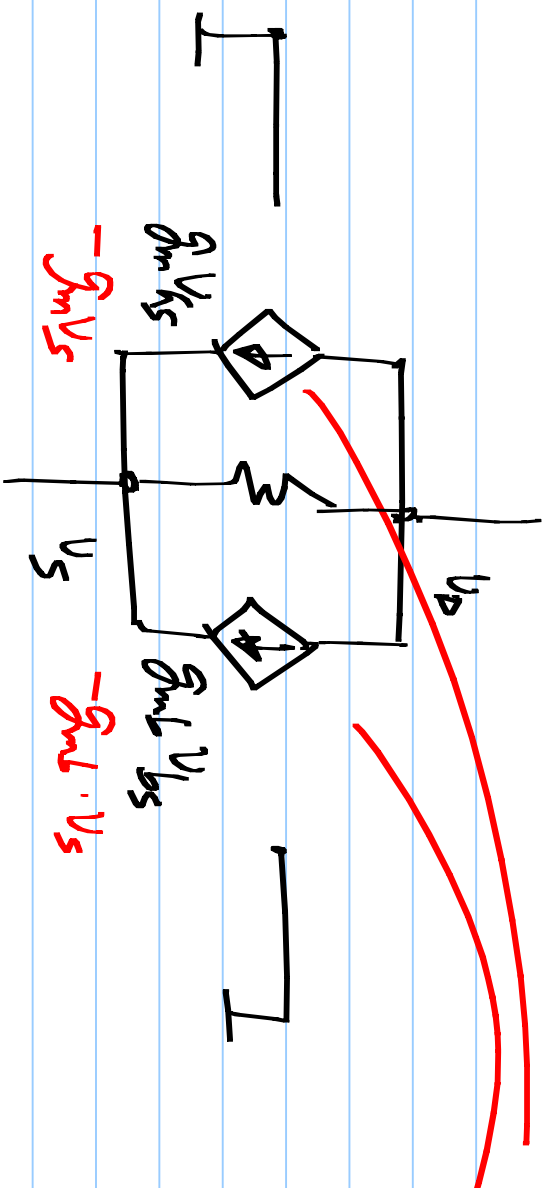


$$g_m + g_{mb} V_s$$

Common drain amplifier

CD gain: $\frac{v_o}{v_i} = \frac{g_m}{g_m + g_{mb} + g_L} \approx \frac{g_m}{g_m + g_{mb}}$

$$R_o: \frac{1}{g_m + g_{mb}}$$

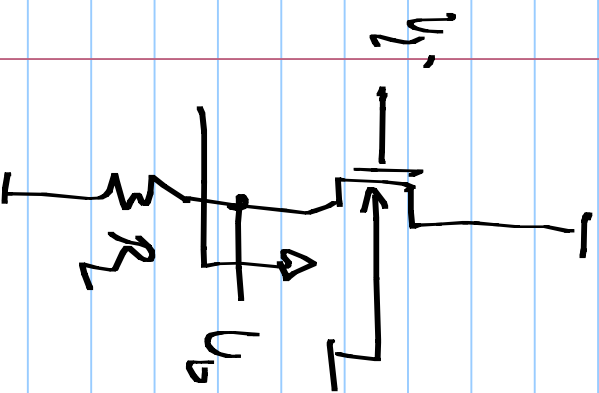


$$\frac{g_m}{g_{mb}} : 4 - 10$$

Evaluate the effect of body effect on
single transistor V_{GS} & V_{DS}



Constant

V_{GS} bias

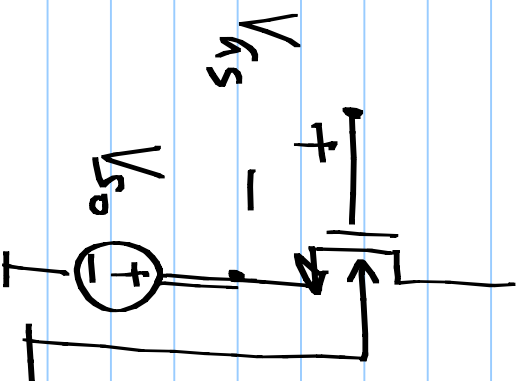



Constant I_D bias — small signal parameters: same

Drain feedback

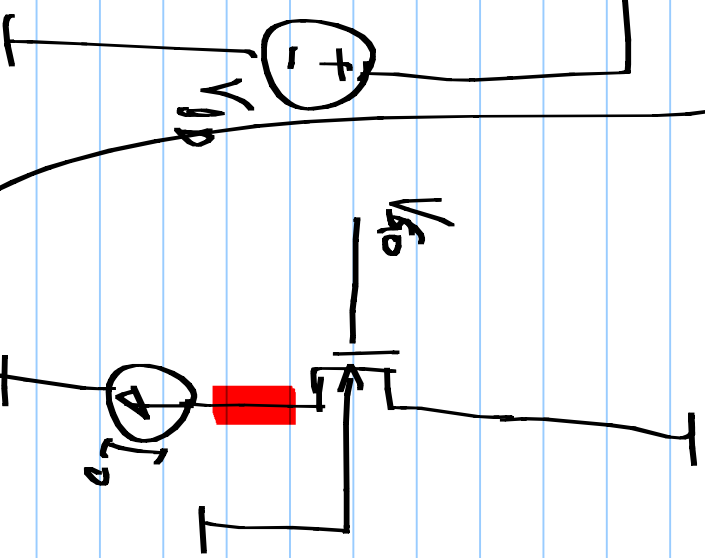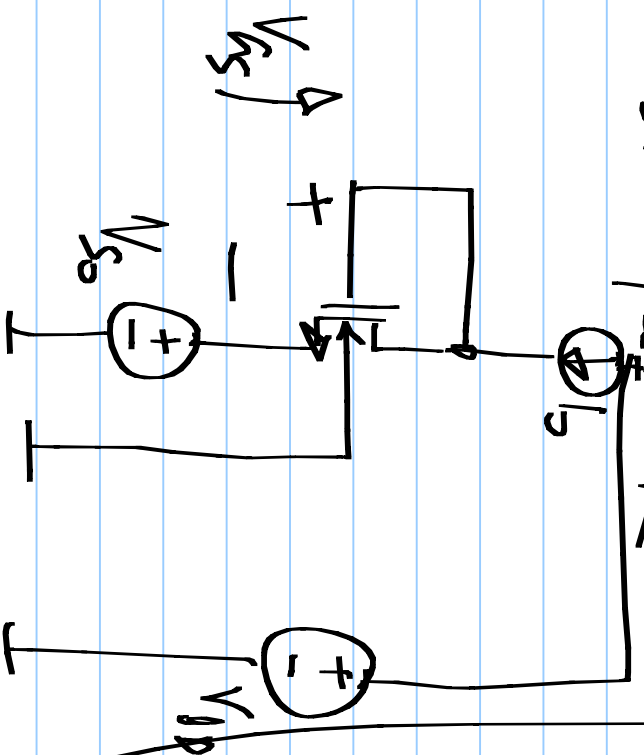

$$g_m = \sqrt{\frac{2I_D}{\mu_n C_{ox} W/L}} \quad (\text{swing limits}) \quad \text{check}$$

Source follower:

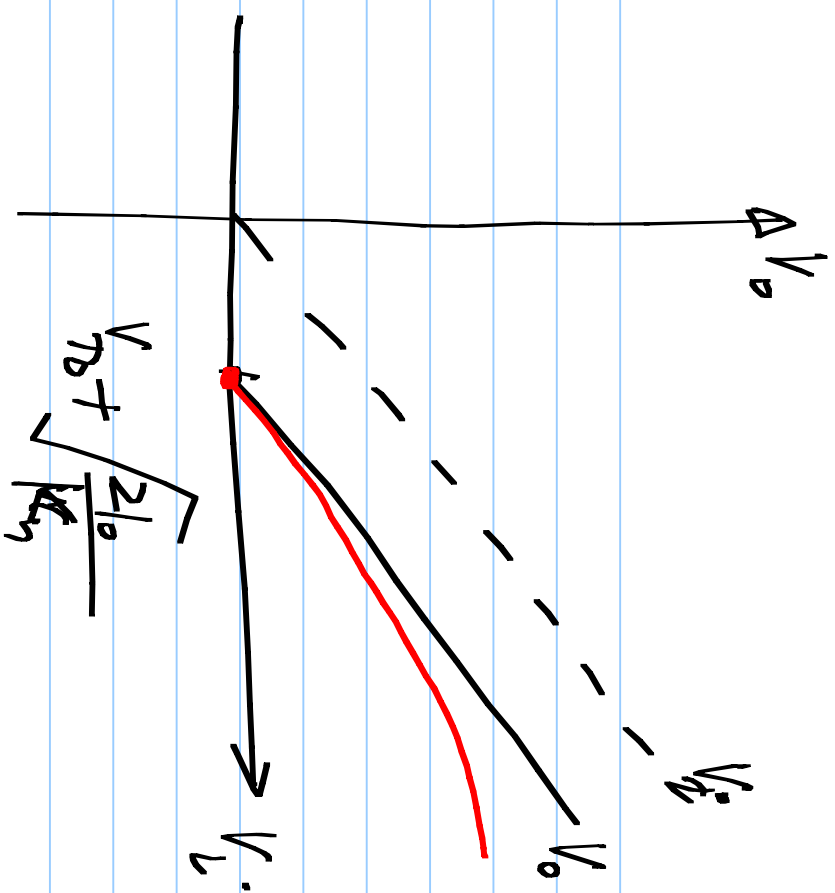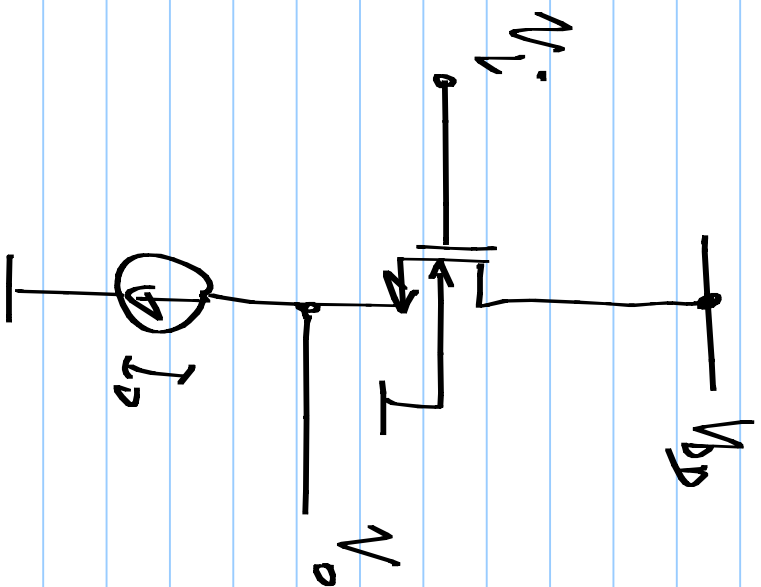

$$N_o = V_i - V_{as}$$

$$= V_i - \left(V_{T_o} + \gamma \left(\sqrt{V_o + 2\gamma f} - \sqrt{2\gamma f} \right) \right)$$

$$+ \sqrt{\frac{2\gamma 2I_o}{\mu_{n,sat} W_L}}$$