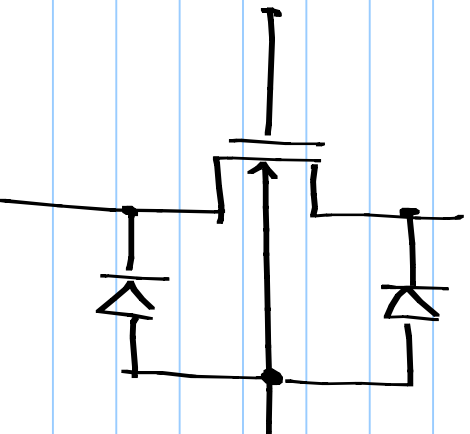


Lecture 7 20/1/2016


negative V_{SB} ($|V_{SB}| < 200mV$)

to reduce the threshold voltage




$$V_{th} + \gamma \left(\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right)$$

Small signal model of the MOS transistor

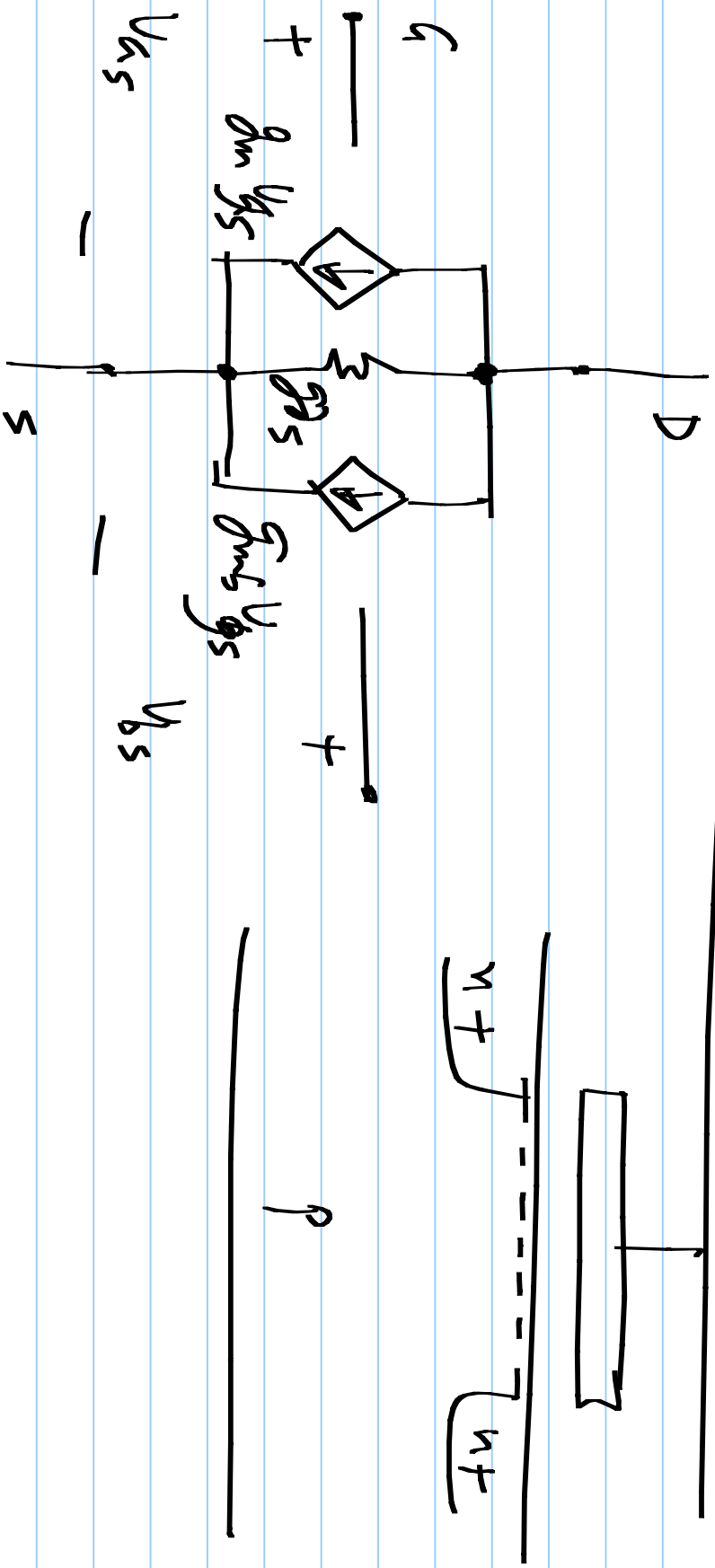


dc model of the MOS transistor

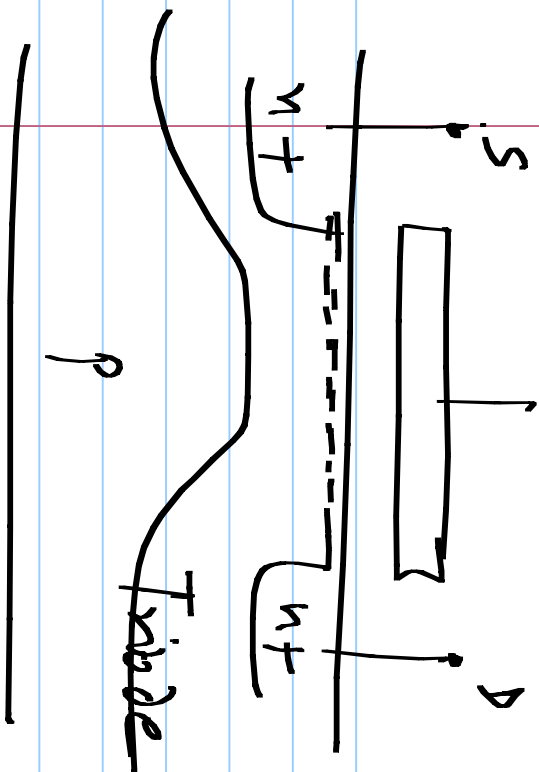

$$C_{gs} = C_{gd} = \frac{WL C_{ox}}{2}$$

$$V_{gs} > V_t$$

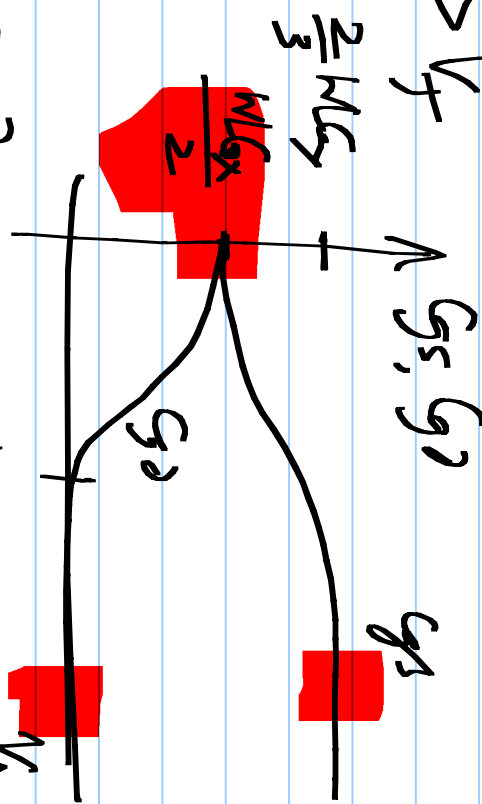


$$C_{gd} = 0$$

$$C_{gs} = \frac{2}{3} WL C_{ox}$$

Saturation

Intrinsic Capacitors C_{gs}, C_{gd}

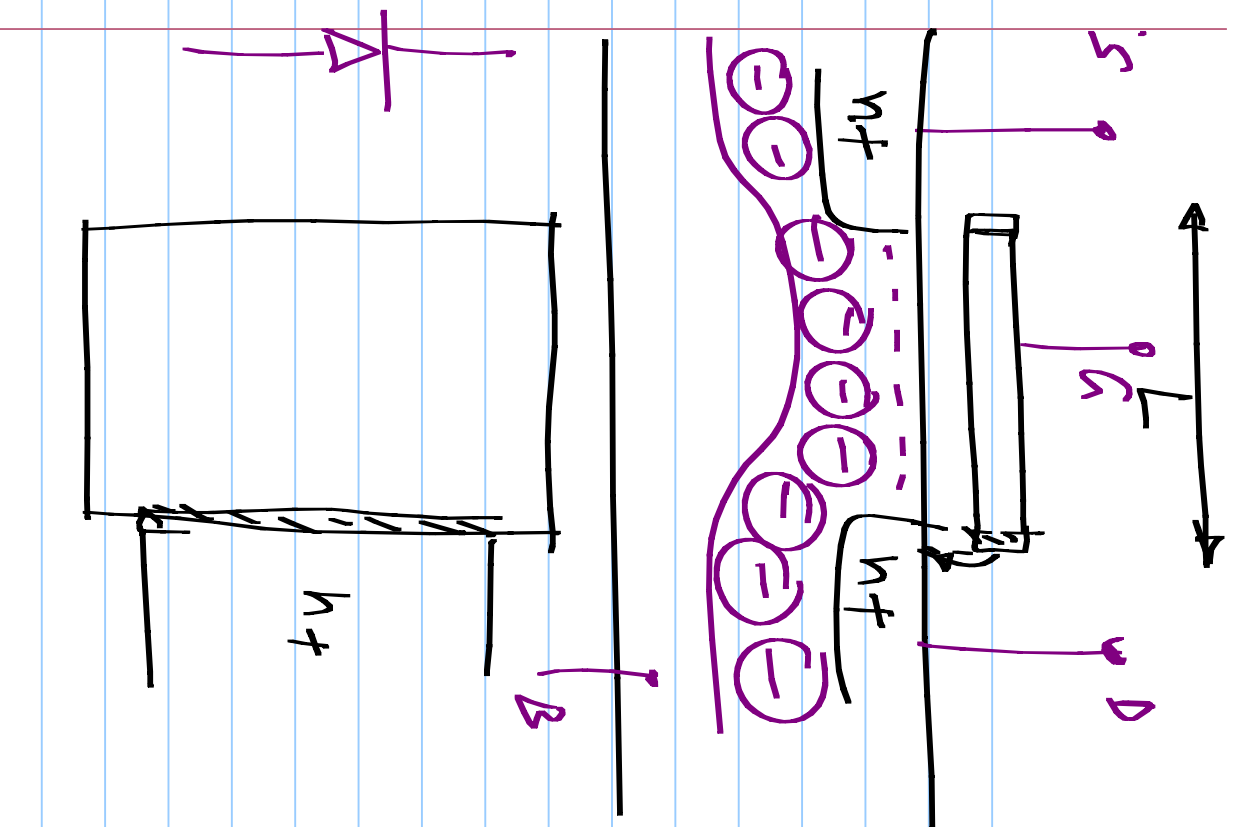


$$C_{gs} = C_{gs,i} + C_{ov}$$


$$C_{gd} = C_{gd,i} + C_{ov}$$

$$\underline{C_{ov} \cdot W}$$

Intrinsic + overlap

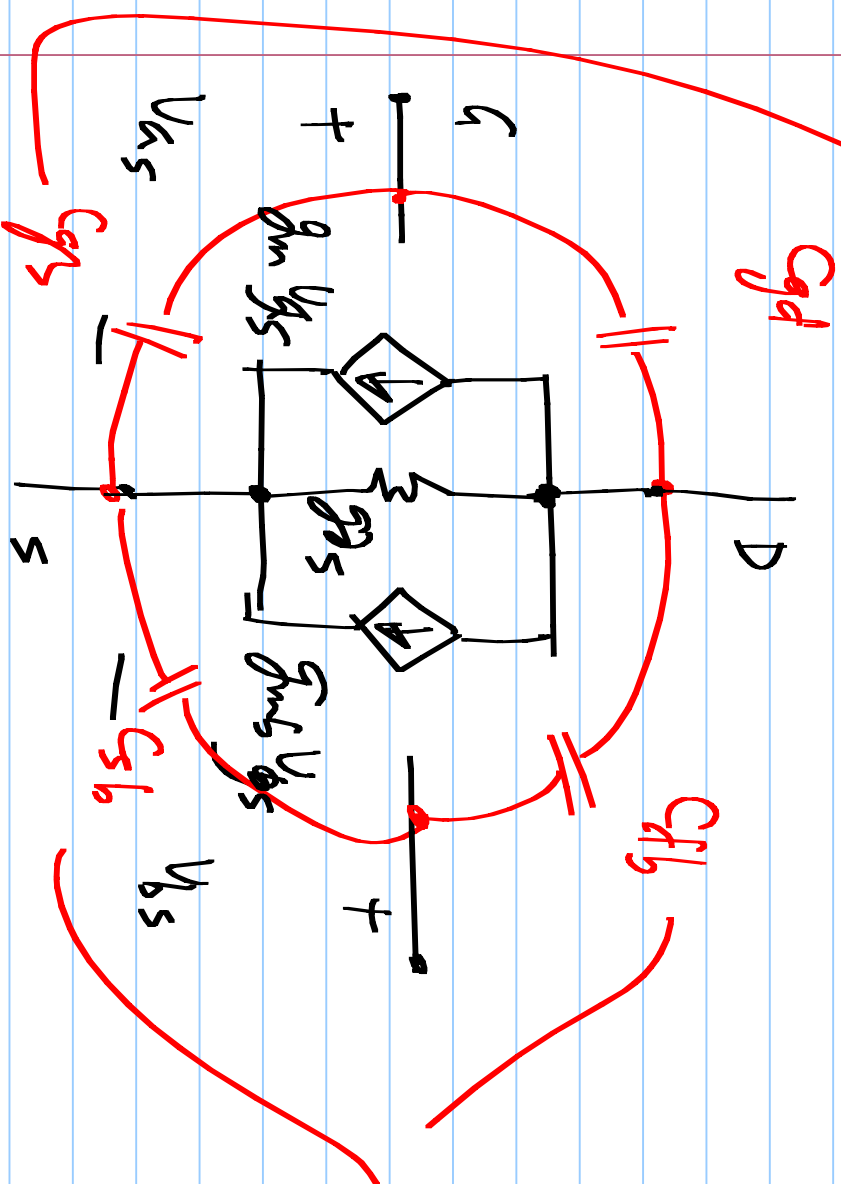

depletion cap. of the
reverse biased jn.

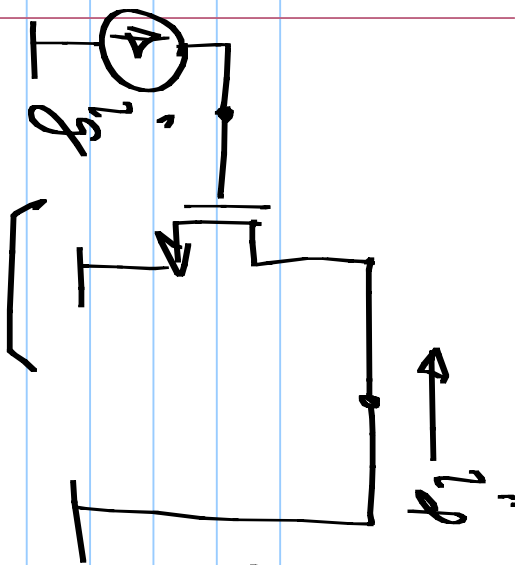



incremental short

$$\frac{i_d}{i_g} = \frac{I_D(s)}{I_g(s)} = \frac{g_m}{s C_{gs}}$$

Binned in

saturation
 $I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$
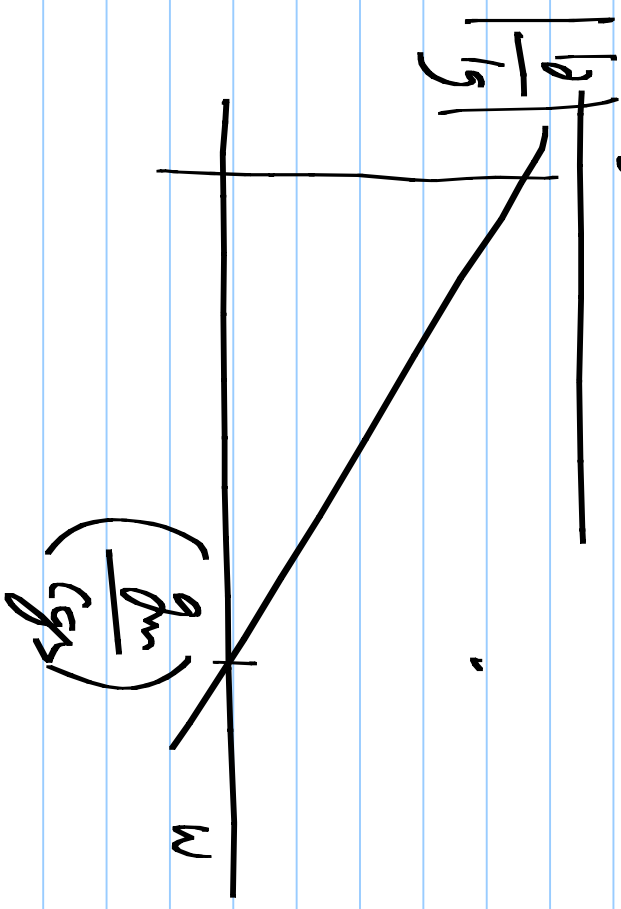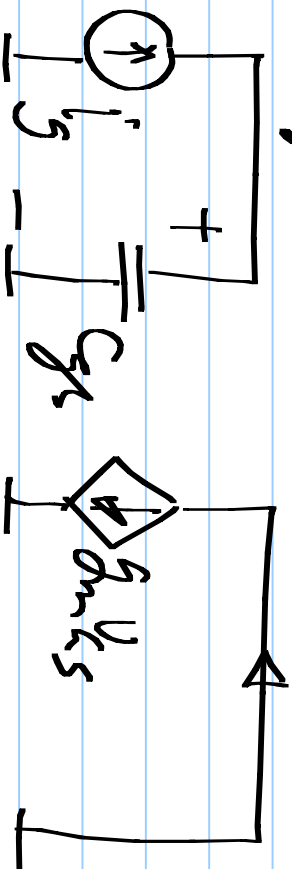
$$I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$



$$\omega_T = \frac{g_m}{g_s} = \frac{\mu_n C_{ox} \frac{W}{L} (V_{gs} - V_T)}{\frac{2}{3} \mu_n C_{ox}}$$

$$\omega_T = \frac{3}{2} \frac{\mu_n (V_{gs} - V_T)}{L^2}$$
