

Lecture 9

8/2/2016

Transit frequency:

$$\omega_T = \frac{g_m}{C_{gs}} = \frac{3}{2} \mu_n \underbrace{(V_{as} - V_T)}_{\text{h.f. circuits}}$$

Bias @ large

$V_{as} - V_T$ in

h.f. circuits

$$\frac{3}{4} \frac{V_{SAT}}{L}$$

velocity saturated

MOS transistor mismatch

$$I_D = \left[\frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 \right] \text{ Saturation region}$$
$$= \frac{K_n}{2} (V_{GS} - V_T)^2$$

Random mismatch: Current factor K_n & threshold voltage V_T randomly distributed.

$V = I \cdot R$ std deviation of $\frac{\Delta R}{R_0}$ $\nwarrow$ mean value

$$I = C \cdot \frac{dV}{dt} \quad , \quad \frac{\Delta C}{C_0}$$

$$I = \frac{K_n}{2} \underbrace{(V_{GS} - V_T)^2}_{\text{std deviation of } \frac{\Delta K_n}{K_{n0}} \nearrow \text{mean value}}$$

std deviation of ΔV_T

$$\text{std deviation of } \frac{\Delta k_n}{k_n} \quad \sigma_{k_n} = \sigma \left(\frac{\Delta k_n}{k_n} \right) = \frac{A_\beta}{\sqrt{WL}}$$

$$k_n \equiv \beta_n$$


$$\text{std deviation of } \frac{V}{I} : \sigma_{V/I} = \sigma \left(\frac{V}{I} \right) = \frac{A_{V/I}}{\sqrt{WL}}$$

$$A_p \equiv A_c, A_2 : \left(\frac{1}{2} \right) \cdot \mu m$$


$$A_A : 5 \text{ mV} \cdot \mu m \quad \sigma_{V/I}$$

$$A_A : \frac{\text{mV} \cdot \mu m}{10 \mu m}$$


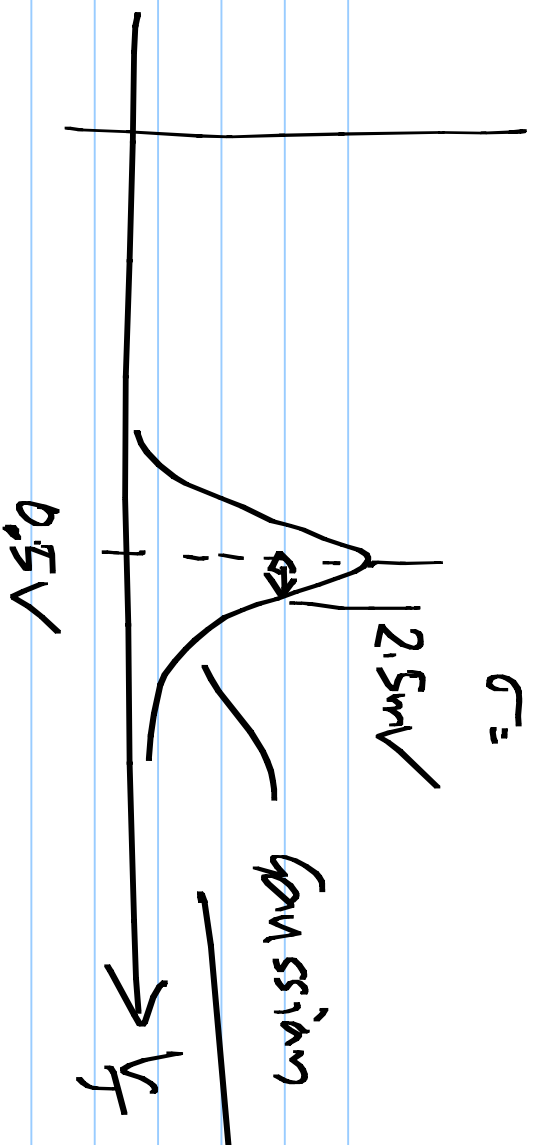
$$\frac{10 \mu m}{2-4 \mu m} : \left. \vphantom{\frac{10 \mu m}{2-4 \mu m}} \right\} = 2.5 \text{ mV}$$



$$\frac{10\mu m}{0.4\mu m}$$

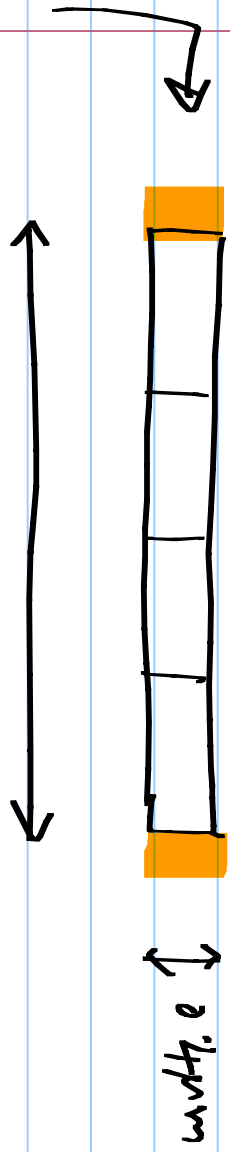

width, e

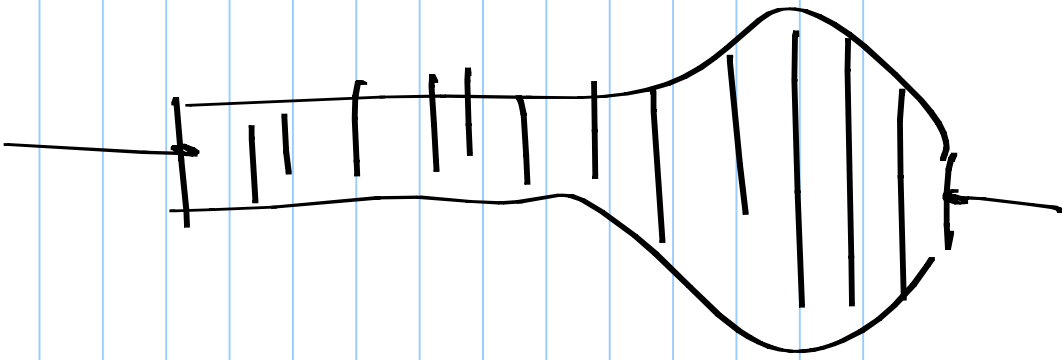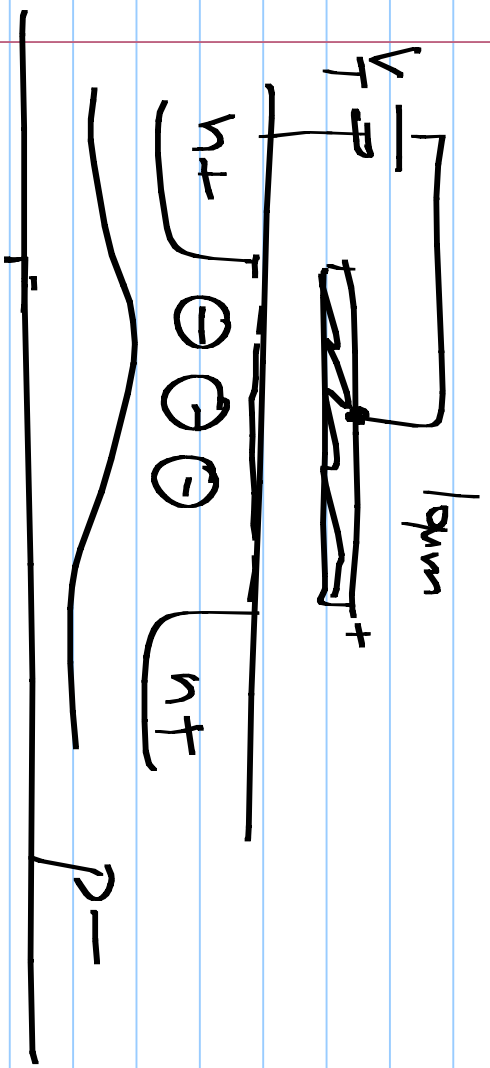




$$V_{gs} - V_{th} = V_{gs} - (V_{th} + \Delta V_{th})$$

$$= V_{gs} - V_{th} - \Delta V_{th}$$

$$= V_{gs} - V_{th}$$

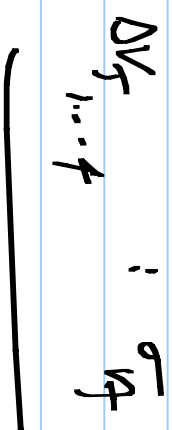


$$I_{1 \dots 4} = \frac{k_n}{2} (V_{GS} - V_{T0} - \Delta V_{1 \dots 4})^2$$

$$j = 1 + 1_2 + 1_3 + 1_4$$

$$\frac{4k_n}{2} (V_{GS} - V_{T0})^2 \quad N_0 \text{ mismatch}$$

$$\frac{4k_n}{2} (V_{GS} - V_{T0} - \Delta V_{Tx})^2 \quad w / \text{mismatch}$$

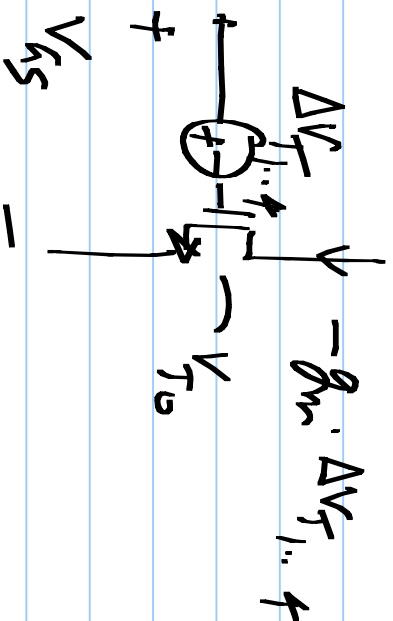
$$\Delta I_D = -g_m (\Delta V_{T1} + \Delta V_{T2} + \Delta V_{T3} + \Delta V_{T4})$$



$$\Delta I_D = \underbrace{-g_m \cdot \Delta V_{T1}}_{1 \dots 4}$$


$$\sigma^2(\Delta I_D) = g_m^2 \cdot 4 \sigma_{V_T}^2$$


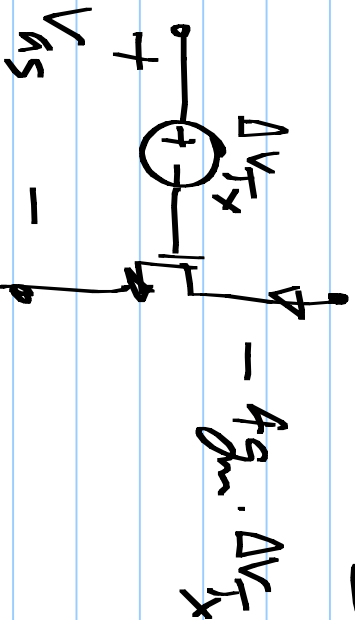
$$\begin{aligned} \text{op drain current} &= \frac{k_n}{2} (V_{gs} - V_{to})^2 \\ &= \frac{1}{6} g_m^2 \cdot \sigma_{V_{T1}}^2 \end{aligned}$$



$$\sigma_{V_{T1}}^2 = \frac{\sigma_{V_T}^2}{4}$$

$$\sigma_{V_{gs}} = \sigma_{V_T}/2$$

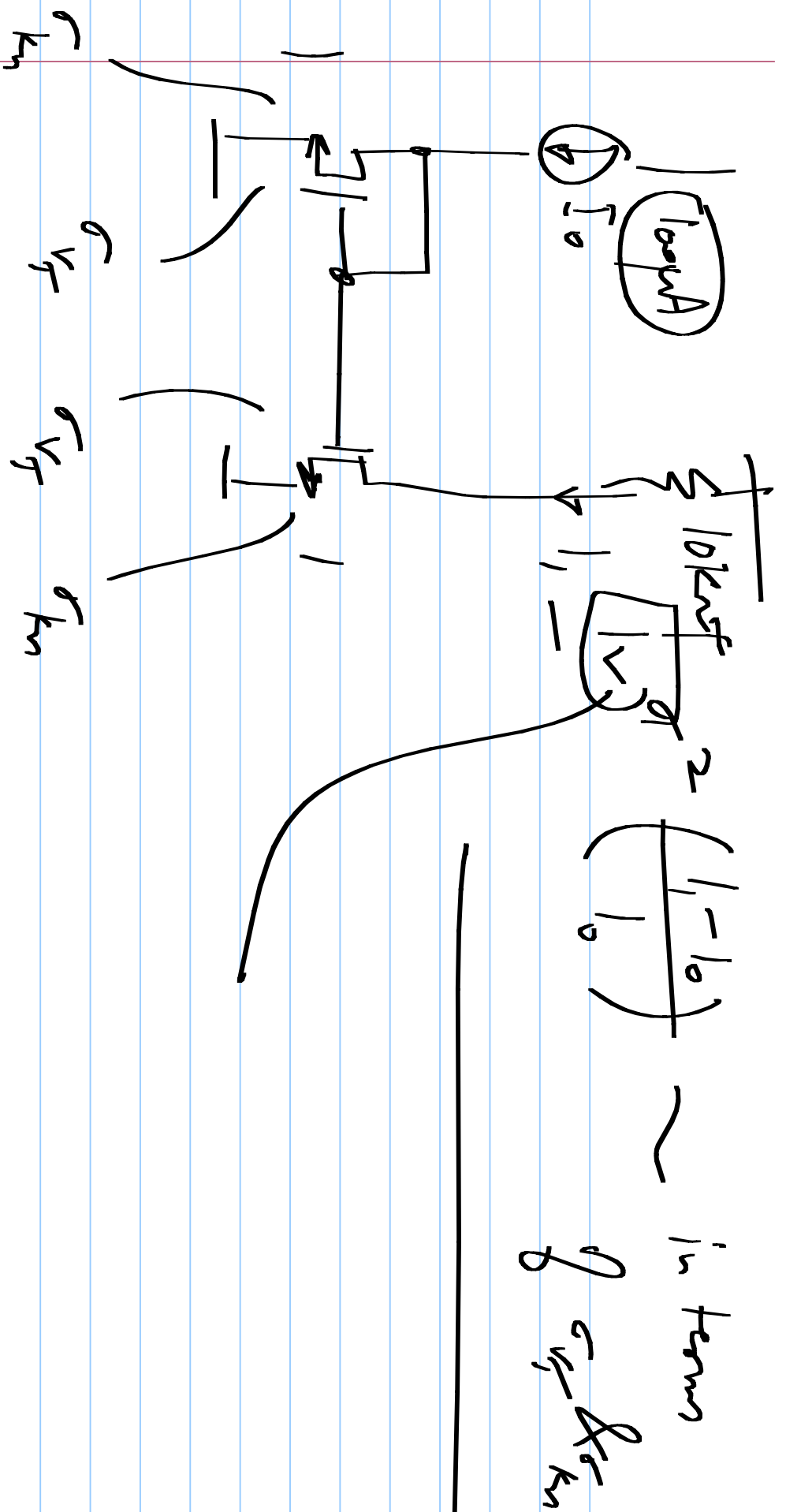

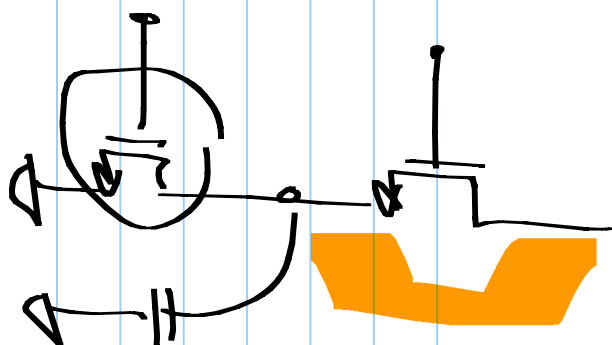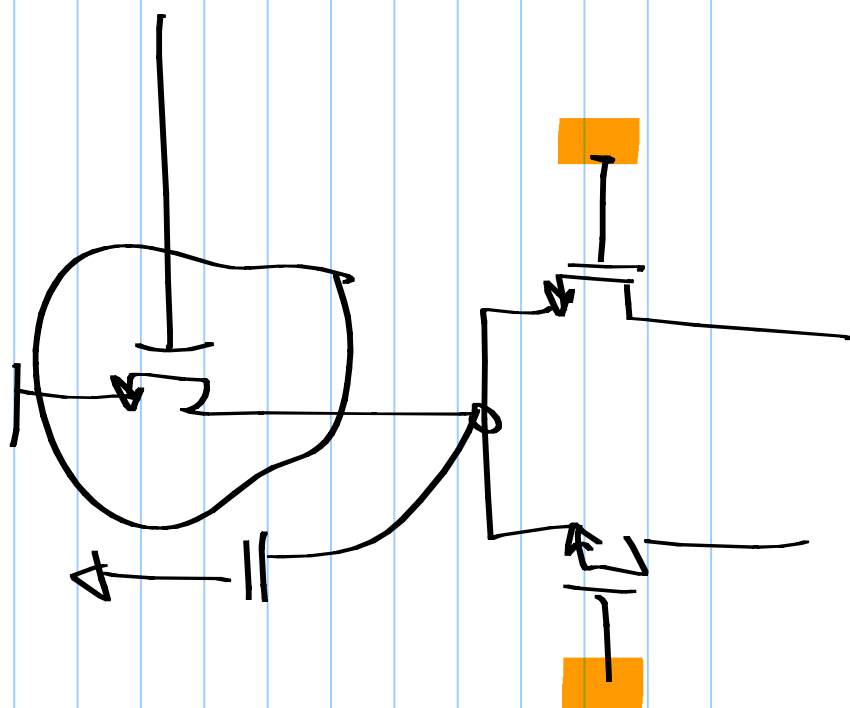

Noise : Random noise

