

Lecture 11

10/2/2016

$$S_x(f) = 2 \cdot \int_{-\infty}^{\infty} R_x(\tau) \exp(j2\pi f \tau) d\tau$$

$x(t)$: random process. current (A)

Zero mean.



$$E[x^2(t)]: \text{variance } A^2$$

$$\text{Autocorrelation: } E[x(t)x(t+\tau)] = R_x(\tau) = R_x(-\tau)$$

$$R_x(0) = \int_0^{\infty} S_x(f) df$$

$$\text{Power spectral density: } \mathcal{F}[R_x(\tau)] = \underbrace{S_x(f)}_{\text{one sided PSD}} \frac{A^2}{\text{Hz}}$$

Fourier transform

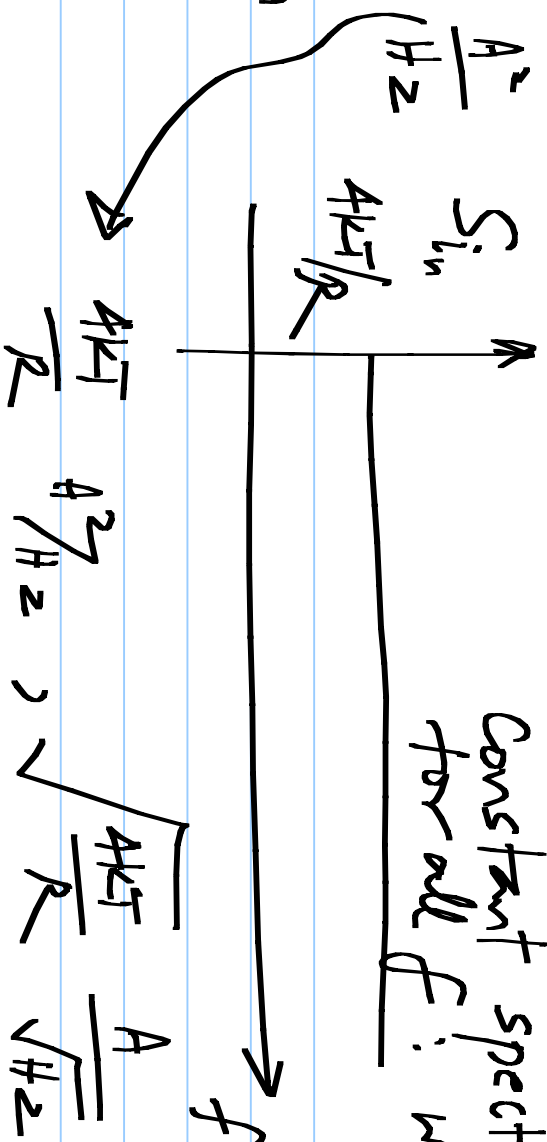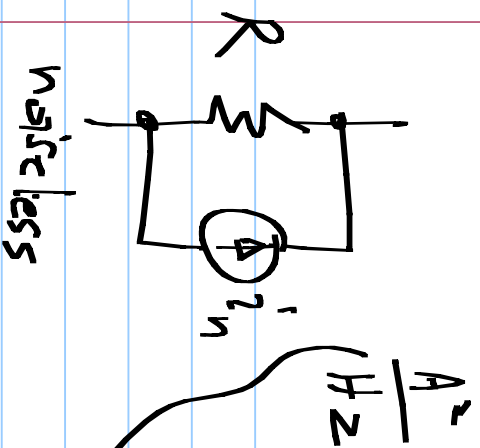

k : Boltzmann's constant



T : absolute temp.

$$kT: 4 \times 10^{-21} \text{ J} \quad @ 300 \text{ K}$$

$$4 \times 10^{-21} \frac{\text{W}}{\text{Hz}}$$

$$\frac{4 \cdot 4 \cdot 10^{-21}}{10^3} \frac{\text{A}^2}{\text{Hz}} = 16 \cdot 10^{-24} \frac{\text{A}^2}{\text{Hz}}$$
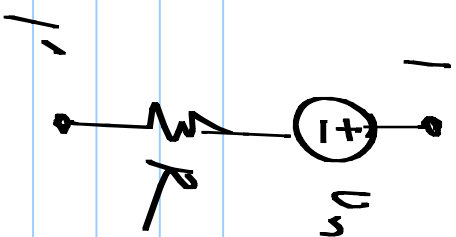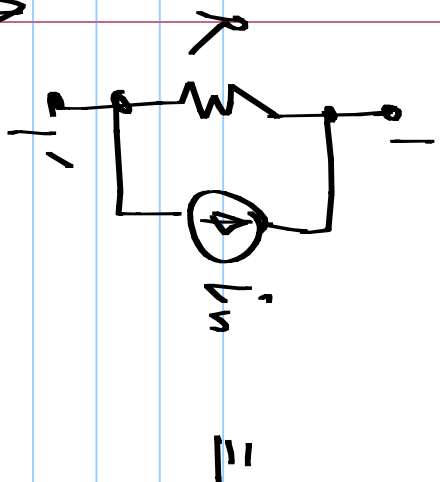
$$4 \cdot 10^{-12} \frac{\text{A}}{\sqrt{\text{Hz}}} = \frac{4 \mu\text{A}}{\sqrt{\text{Hz}}}$$



$$u_n = i_n \cdot R$$

$$S_{u_n} = S_{i_n} \cdot R^2$$

$$= \frac{4k\Omega}{R} \cdot R^2 = 4k\Omega R$$



$$V^2/Hz$$


$$4k\Omega R$$

$$1k\Omega : 16 \times 10^{-18} V^2/Hz$$




$$4nV / \sqrt{Hz}$$


$\rightarrow f$

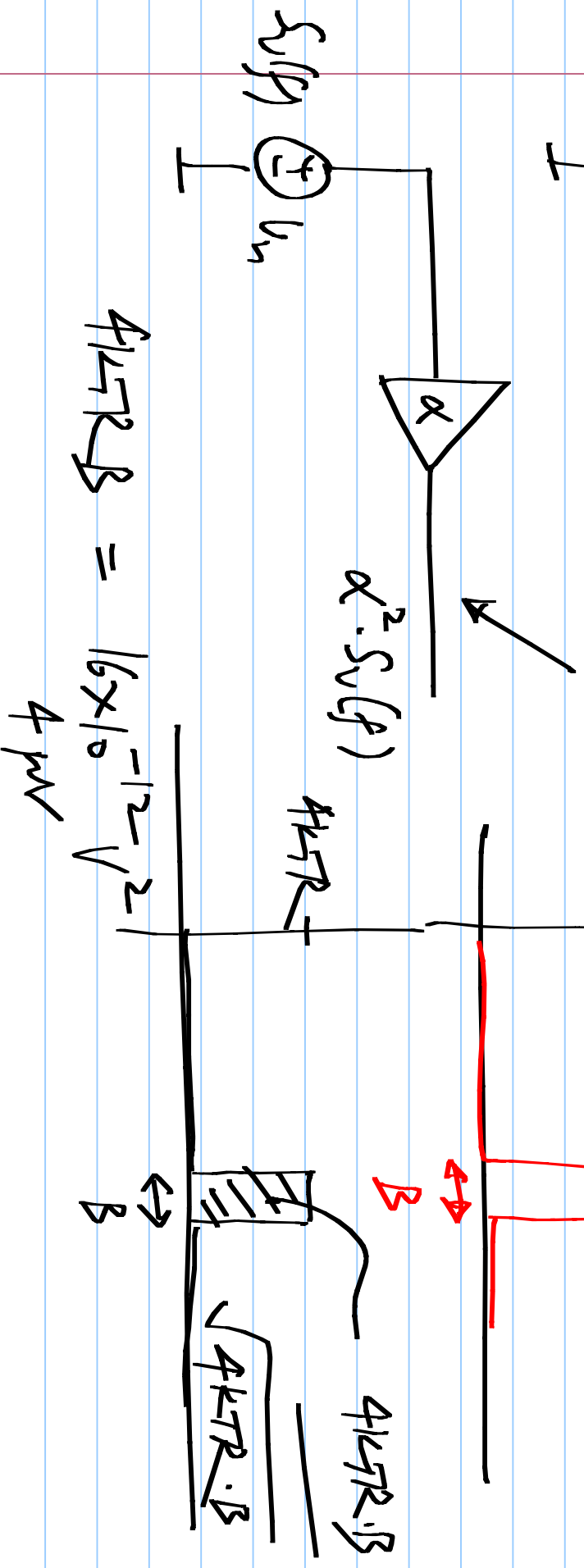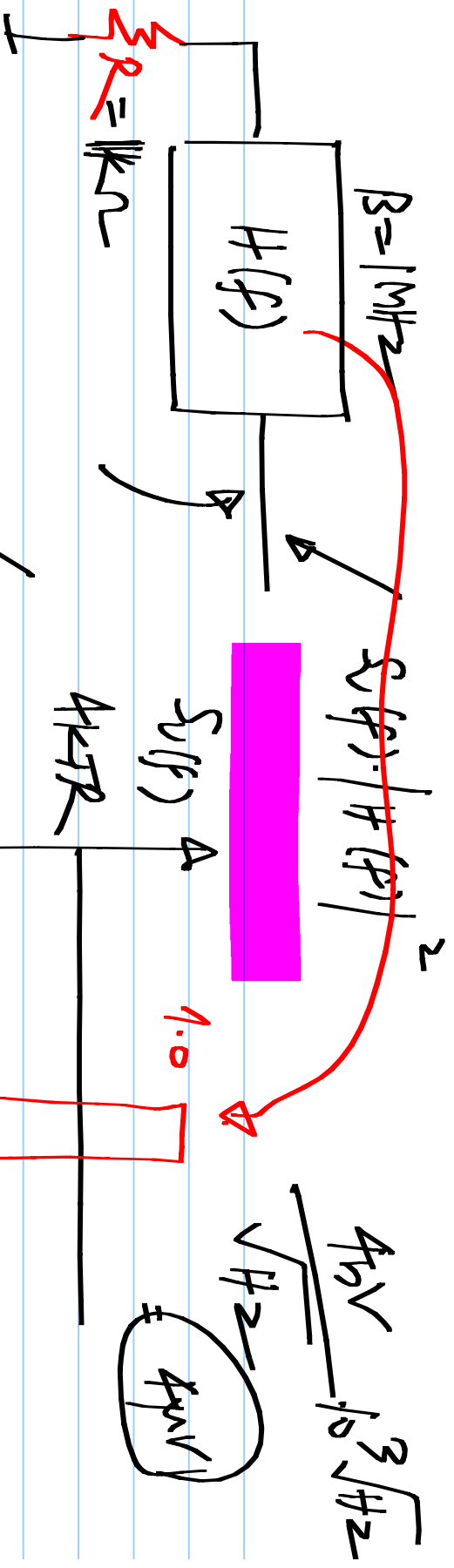

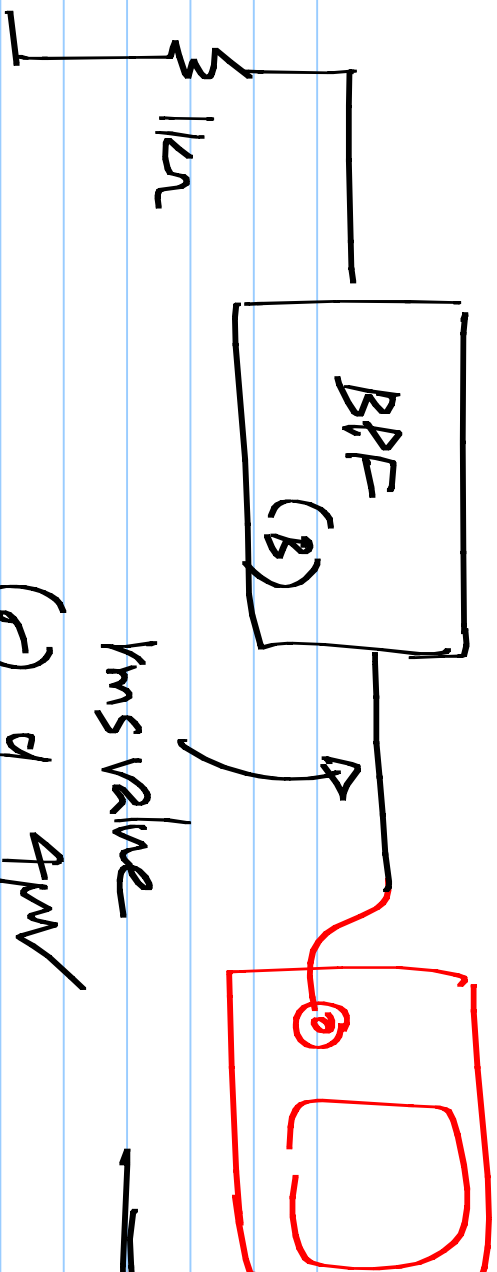

rms value
(c) of $4\mu V$

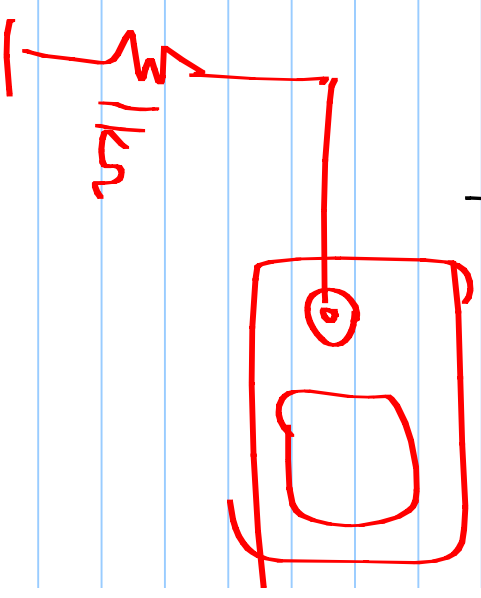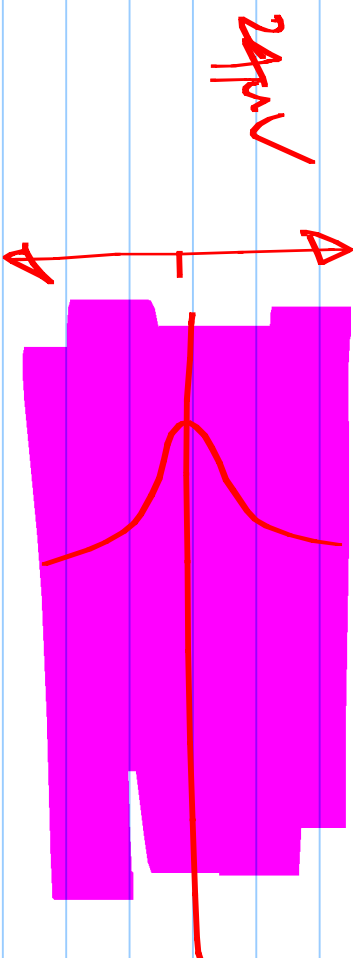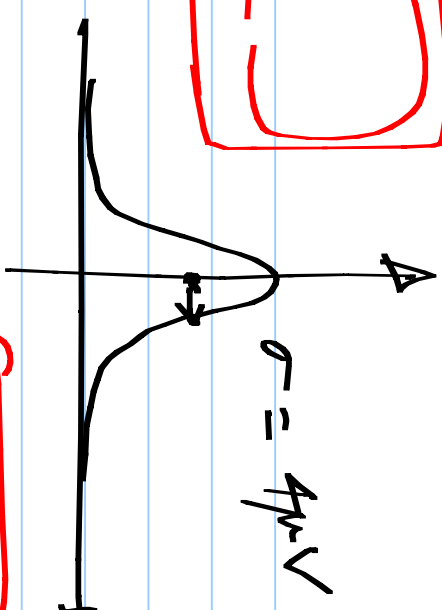


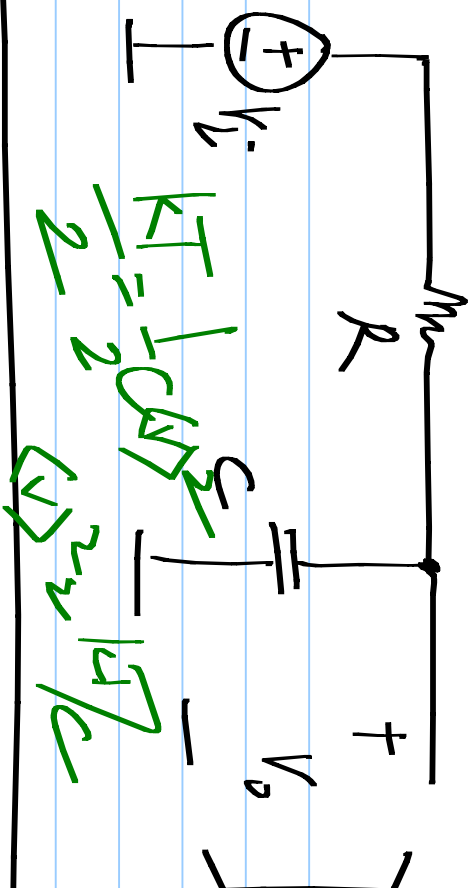

$$kT = \frac{1}{2} C \Delta V^2$$

$$\Delta V = \sqrt{\frac{2kT}{C}}$$


spectral density
&
mean square value

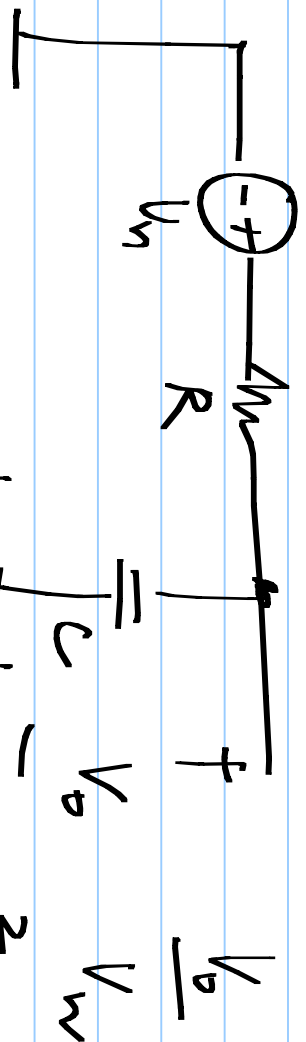

$$S = j2\pi f$$

$$\frac{v_o}{v_n} = \frac{1}{1 + sCR}$$
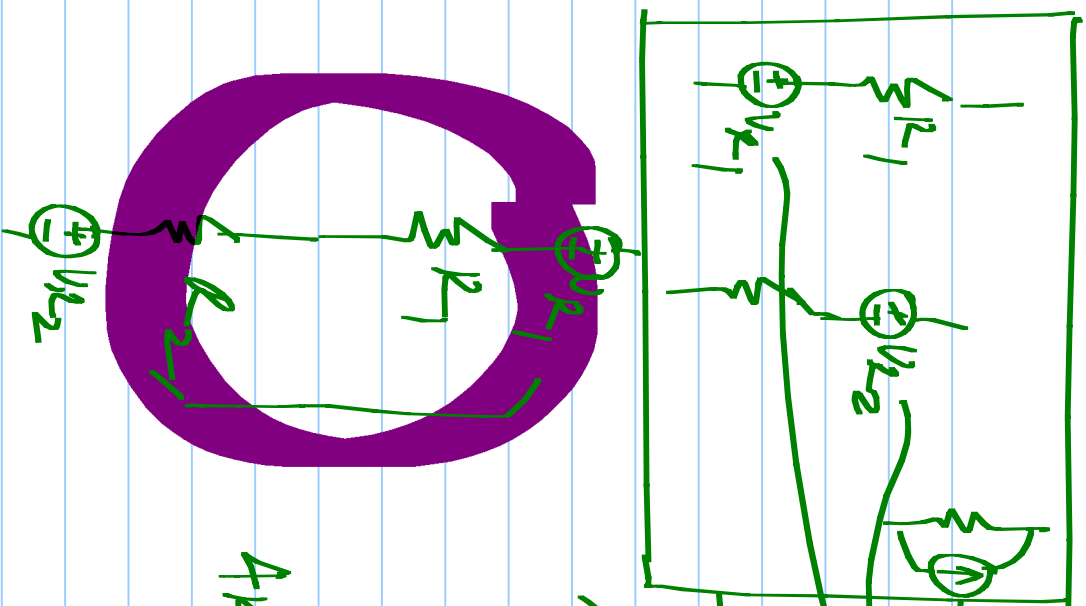
$$S_{v_o}(f) = 4kTR \cdot \frac{1}{1 + j2\pi fCR} = \frac{4kTR}{1 + 4\pi^2 f^2 C^2 R^2}$$




$$4kR_1 + 4kR_2 = 4k(R_1 + R_2)$$

$$\underbrace{4kR_1 + 4kR_2 + 4kR_3}_{\substack{\text{dim} \\ \text{len}}} \underbrace{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}_{\substack{V^2 \\ H^2}} = \frac{4k}{R_1 + R_2 + R_3}$$



Noise in a Mos transistor :

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$g_{DS} = \frac{\partial I_D}{\partial V_{DS}} \bigg|_{V_{GS}=0} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

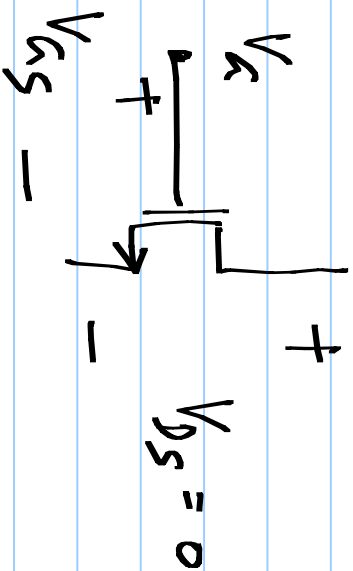

$V_{DS}=0$

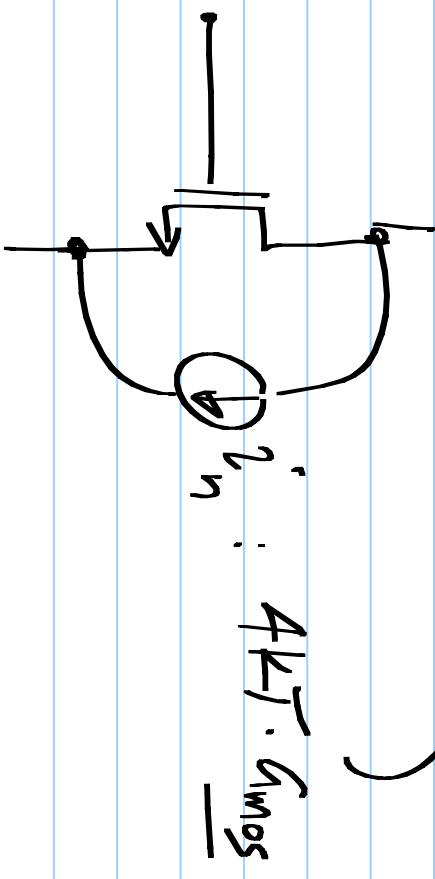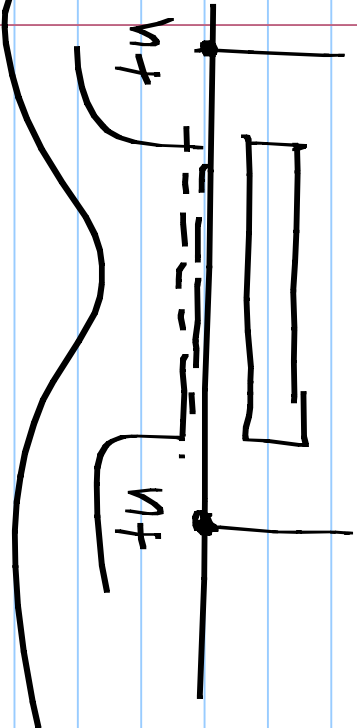

$I_n : 4kT \cdot C_{mos}$