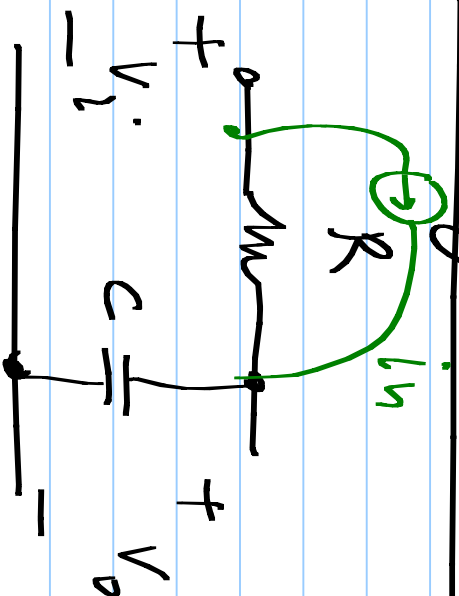


Lecture 13


15/2/2016

Reducing noise in a circuit-



$$\frac{V_o}{V_i} = \frac{1}{1 + sCR}$$


$$\frac{V_o}{V_{on}} = \frac{kT}{C}$$

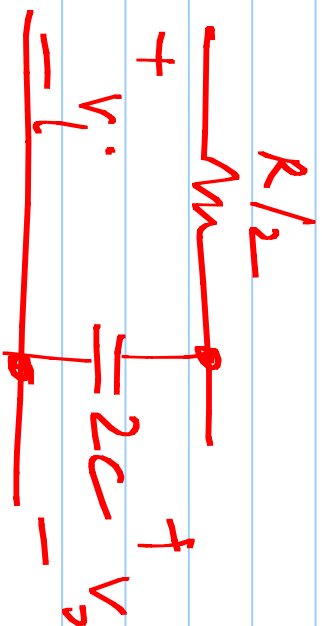

$$\frac{V_o}{V_{on}} = \frac{kT}{2C} \frac{1 + sCR}{1 + sCR}$$

Power dissipated $P_n \propto$

by a factor n

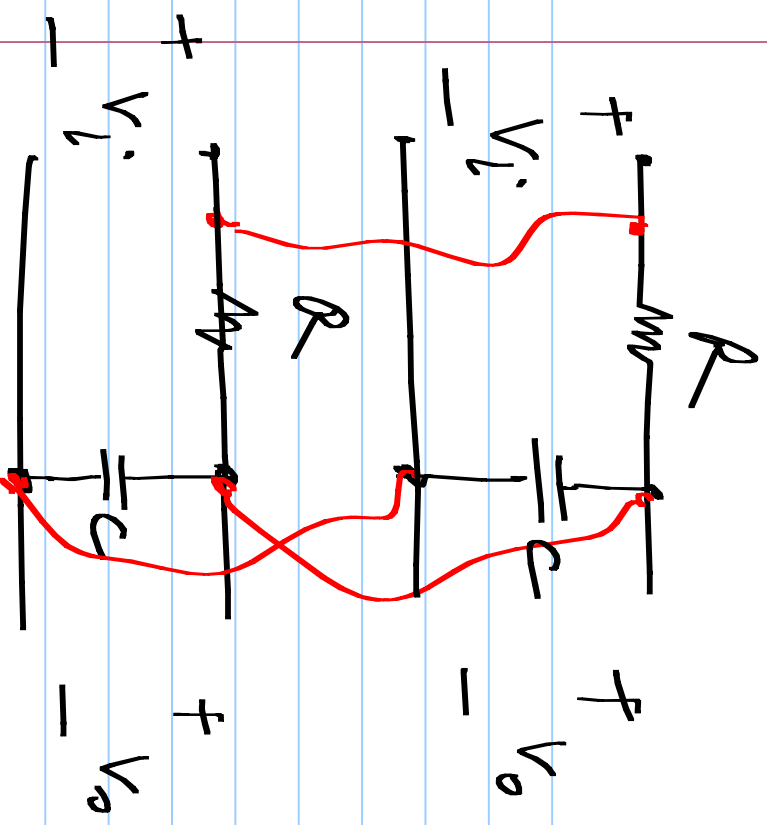

Impedance scaling


$$\{R, L, C\} \rightarrow \{R/2, L/2, 2C\}$$

$\{R/n, L/n, nC\}$ / Preserves TF

Reduces mean

squared voltage noise

or voltage noise PSD



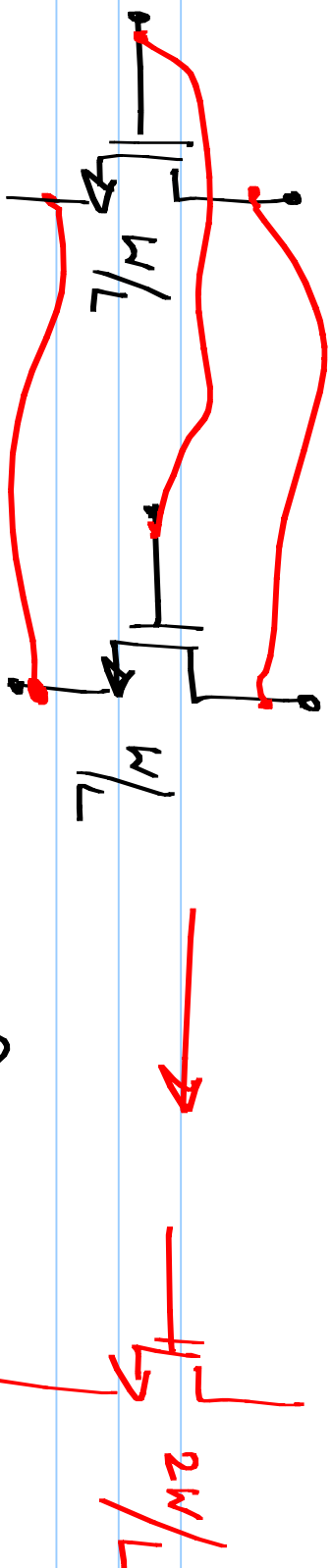


$$\{ g_m, g_{ds}, g_{mb} \} \xrightarrow{2\times} \{ 2g_m, 2g_{ds}, 2g_{mb} \}$$

$$\text{Noise voltage} = \text{Noise current} \times \left\{ \text{Impedance} \right\}$$

$$P_{SD} = \uparrow_n \text{ Noise } P_{SD} \times \left| \text{Transimpedance} \right|^2 \downarrow_n$$

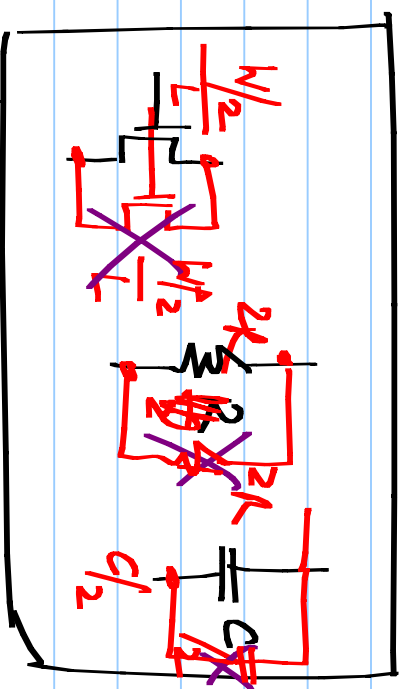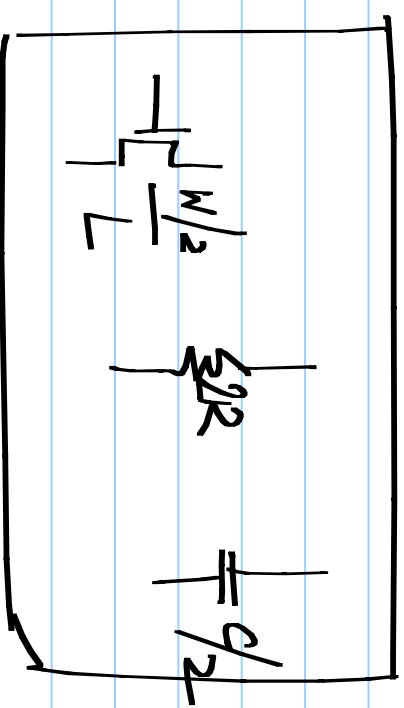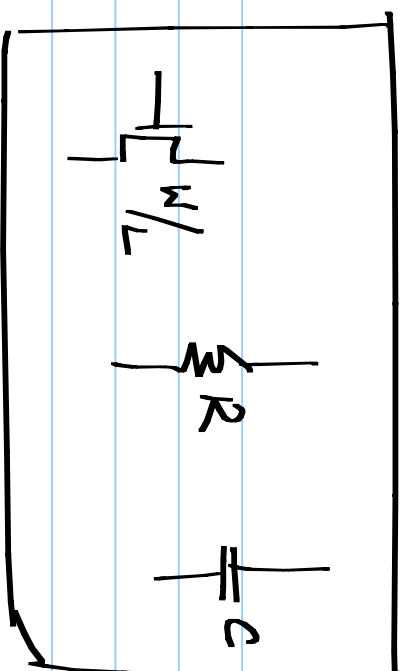- * Parasitic capacitances of the device; Body effect
- * Mismatch
- * Noise



$$+ R - \frac{V_p}{\sqrt{2}} \cos\left(\frac{t}{R_C} + \frac{\pi}{4}\right)$$

$$+ \frac{V_p}{\sqrt{2}} \cos\left(\frac{t}{R_C} - \frac{\pi}{4}\right)$$

$$V_p \cos\left(\frac{t}{R_C}\right) \quad \frac{V_p}{\sqrt{2}R} \cos\left(\frac{t}{R_C} + \frac{\pi}{4}\right)$$


output voltage signal



(mean sq.) noise

Resistor current

$$\frac{kT/C}{V_p^2/4R^2} \quad \frac{kT/2C}{V_p^2/R^2}$$

Single stage opamp.

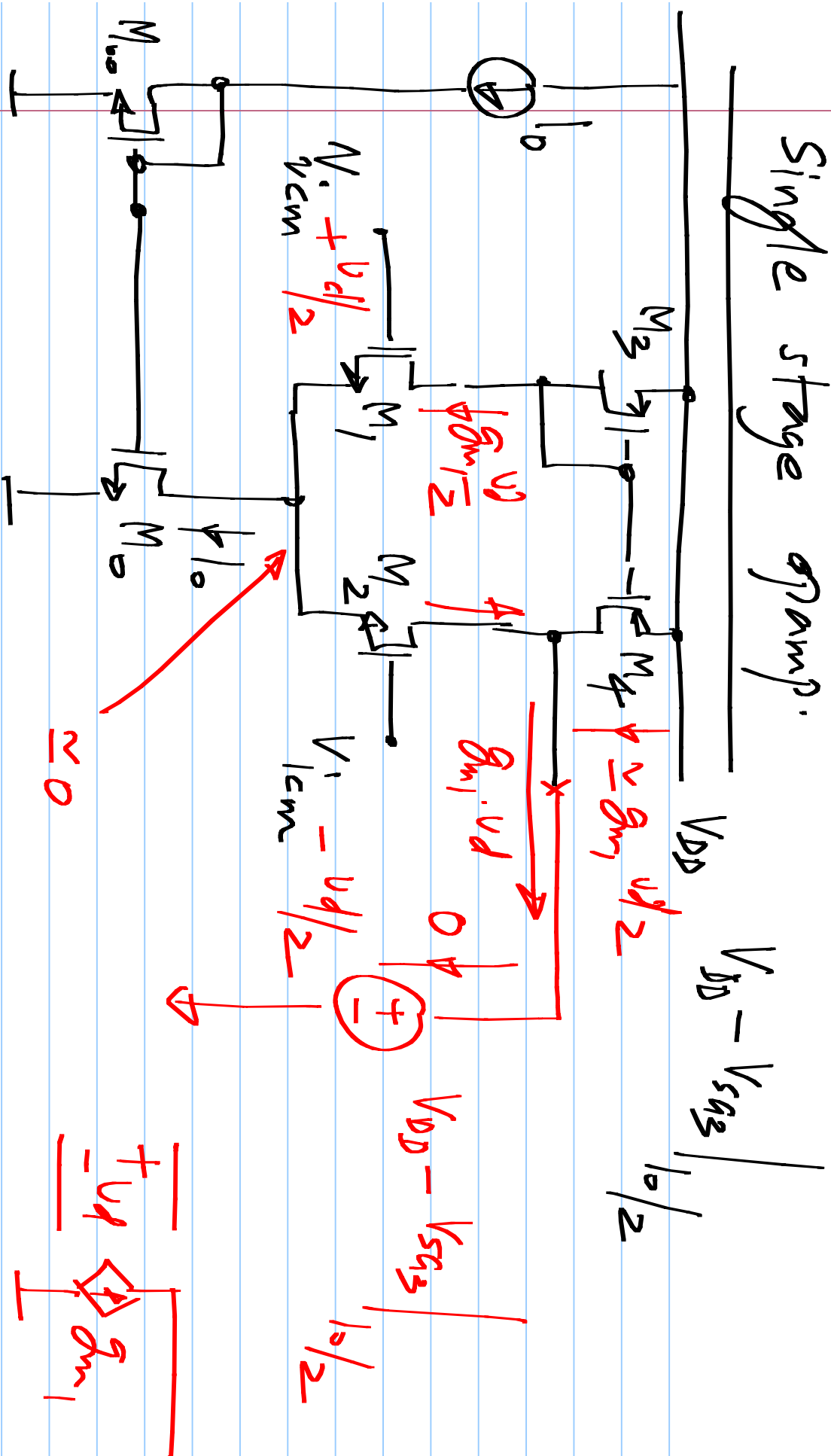

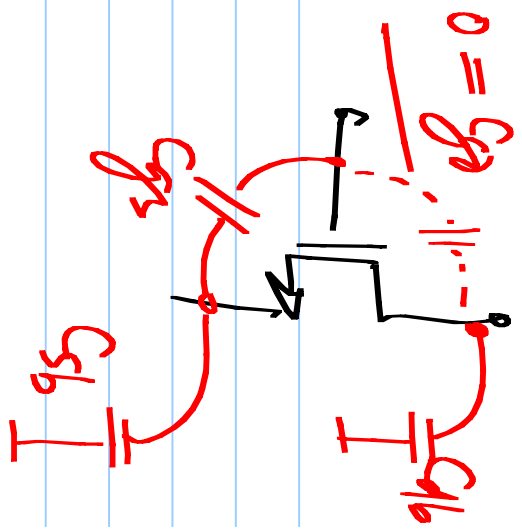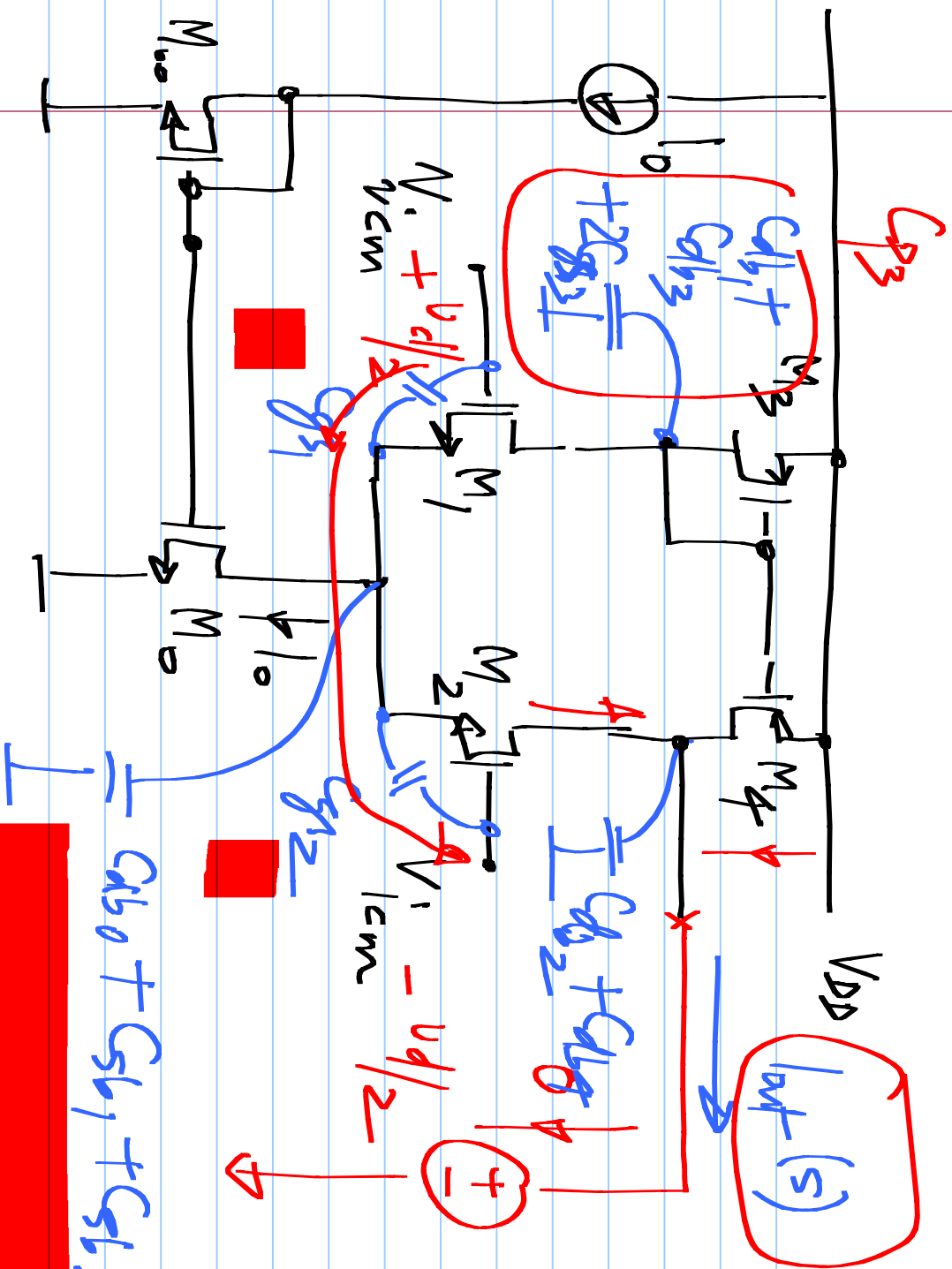

$$l_{out}(s) = \frac{V_d(s)}{V_{cm}(s)}$$

$$C_{db0} + C_{db1} + C_{db2}$$