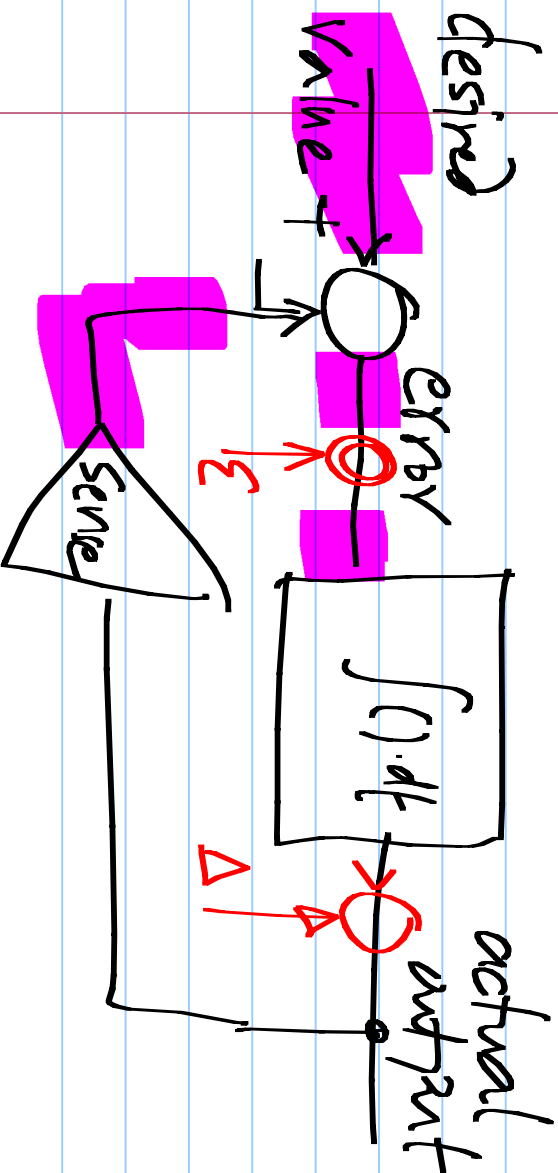


Lecture 21


2/3/2016

Negative feedback systems



Zero in steady state

$$V_o = K V_i$$

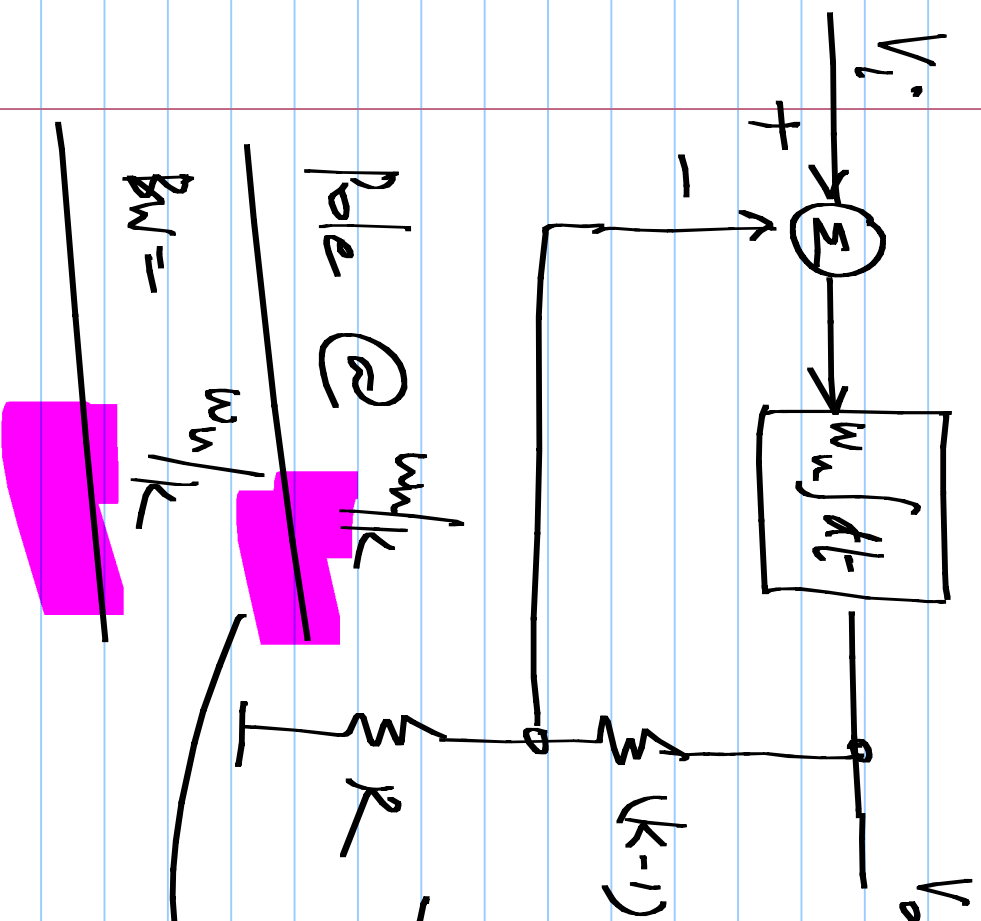

$$\frac{k}{w_u} \cdot \frac{dV_o}{dt} + V_o = K V_i$$

$$V_i = V_p u(t)$$

$$\tau = \frac{k}{w_u}$$

$$V_o(t) = K V_p (1 - \exp(-t/\tau)) + V_o(0) \exp(-t/\tau)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{k}{1 + \frac{s}{(w_n/k)}}$$


$$\frac{V_o(s)}{V_i(s)} = \frac{k}{1 + \frac{s}{(\omega_n/k)}} \quad \text{closed loop } f_c$$

$$v_i(t) = V_p \cos(\omega_i t)$$

$$v_o(t) = \frac{k V_p}{\sqrt{1 + \left(\frac{\omega_i}{\omega_n/k}\right)^2}} \cdot \cos\left(\omega_i t - \tan^{-1} \frac{\omega_i}{\omega_n/k}\right)$$

$$\omega_i \ll \omega_n/k \quad \approx k V_p \cos\left(\omega_i t - \frac{1}{\omega_n/k}\right)$$
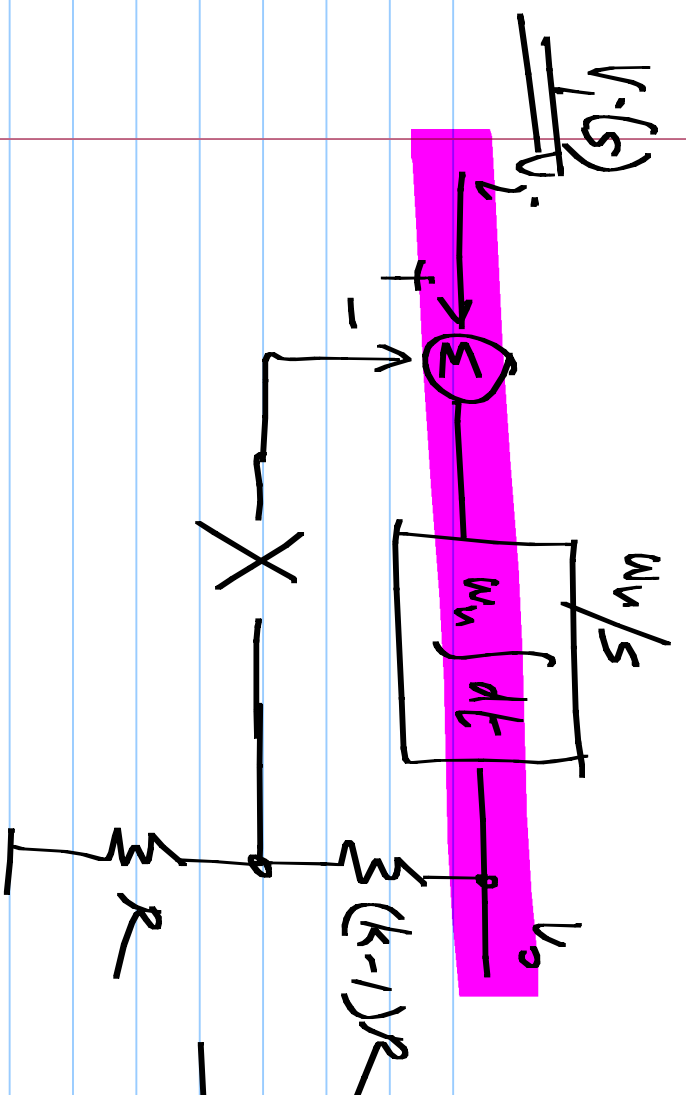
$$\omega_i \gg \omega_n/k \quad \frac{\omega_n}{\omega_i} V_p \sin(\omega_i t)$$




Negative feedback :
quantified by loop gain

$$\frac{V_{\text{error}}}{V_{\text{ref}}} = - \frac{\frac{w_n}{k \cdot s}}{L(s)}$$

$$L(s) = \frac{w_n}{k \cdot s}$$

$$\frac{w_n}{s} \cdot V_i(s) \quad V_i(t) = V_p \cos w_i t$$

$$\frac{w_n}{w_i} V_p \sin w_i t$$

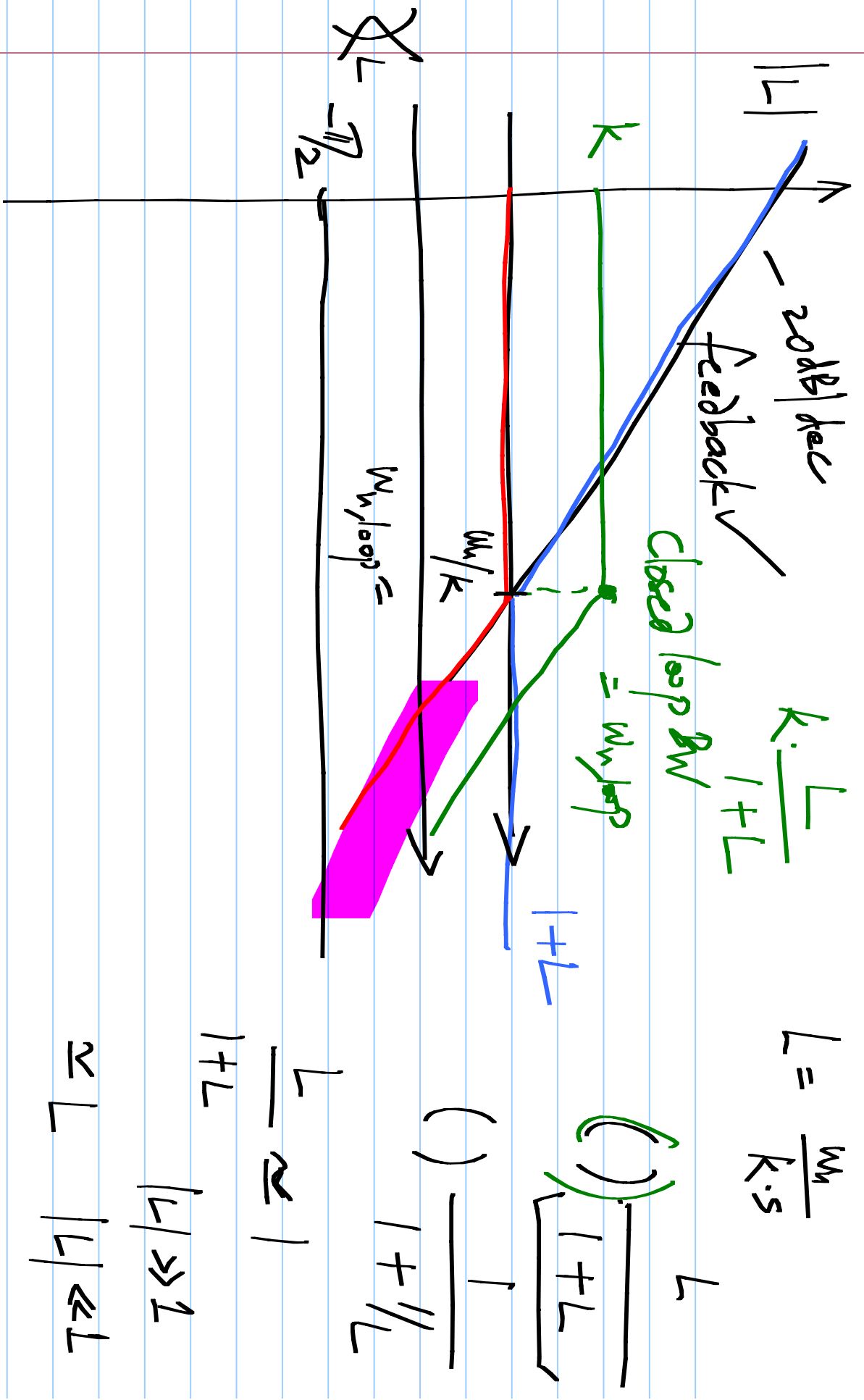

$$L = \frac{\omega_n}{k \cdot s}$$


$$L \cdot \frac{1}{1+L}$$

$$\frac{1}{1+1/L}$$

$$\frac{L}{1+L} \approx 1$$

$$|L| \gg 1$$

$$\approx L \quad |L| \ll 1$$

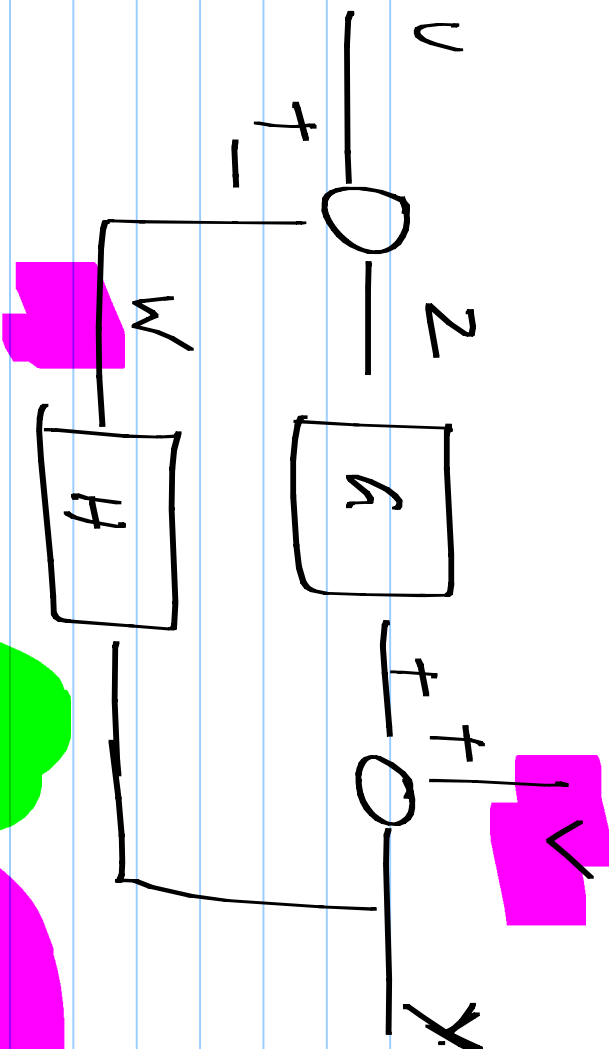

$$\frac{Y}{V} = \frac{G}{G_H + 1}$$

$$= \frac{1}{H + 1} \cdot \frac{G_H}{G_H + 1}$$

$$\frac{Y}{V} =$$

$$\frac{1}{1 + G_H}$$

$$\frac{Y}{V} = \frac{M}{H + 1}$$

$$\frac{1}{1 + G_H}$$

$$\frac{G_H}{1 + G_H}$$

Integrator : Current into a capacitor

