

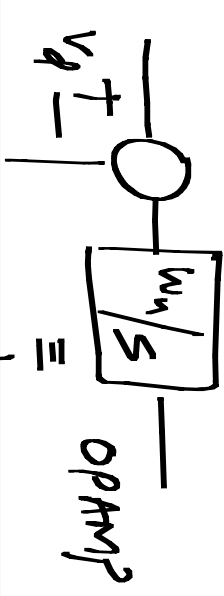
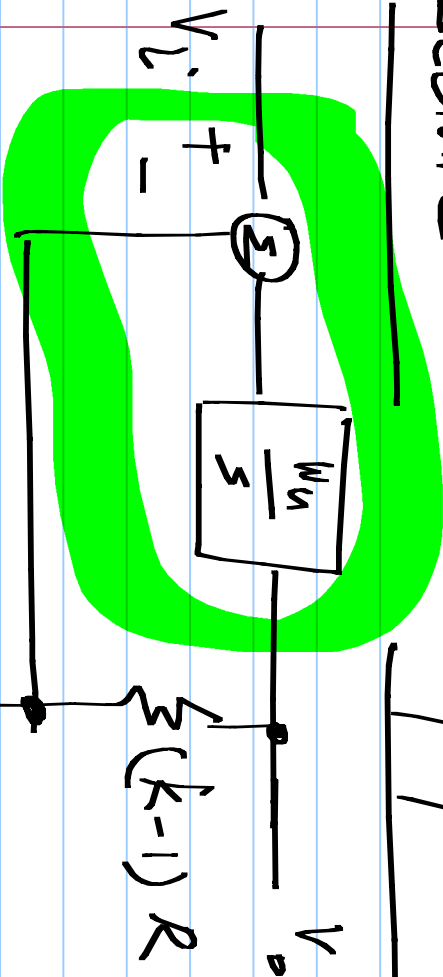




Lecture 22

3/3/2016

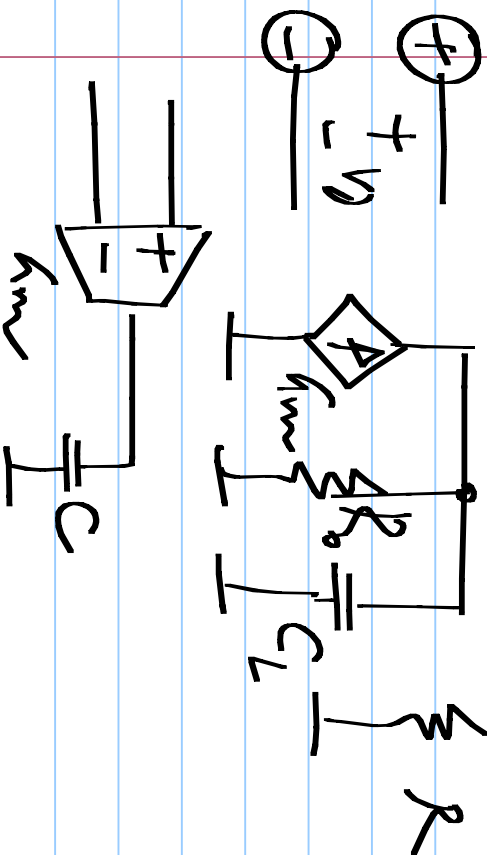

$$BW = \frac{w_n}{K}$$

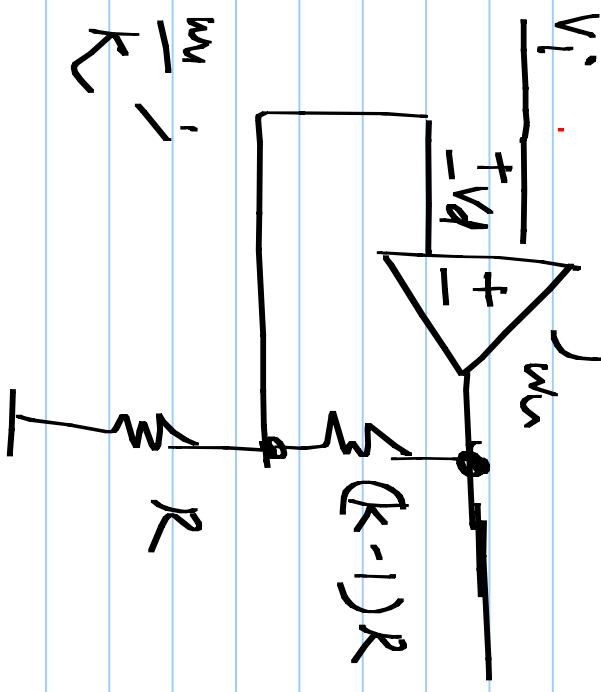

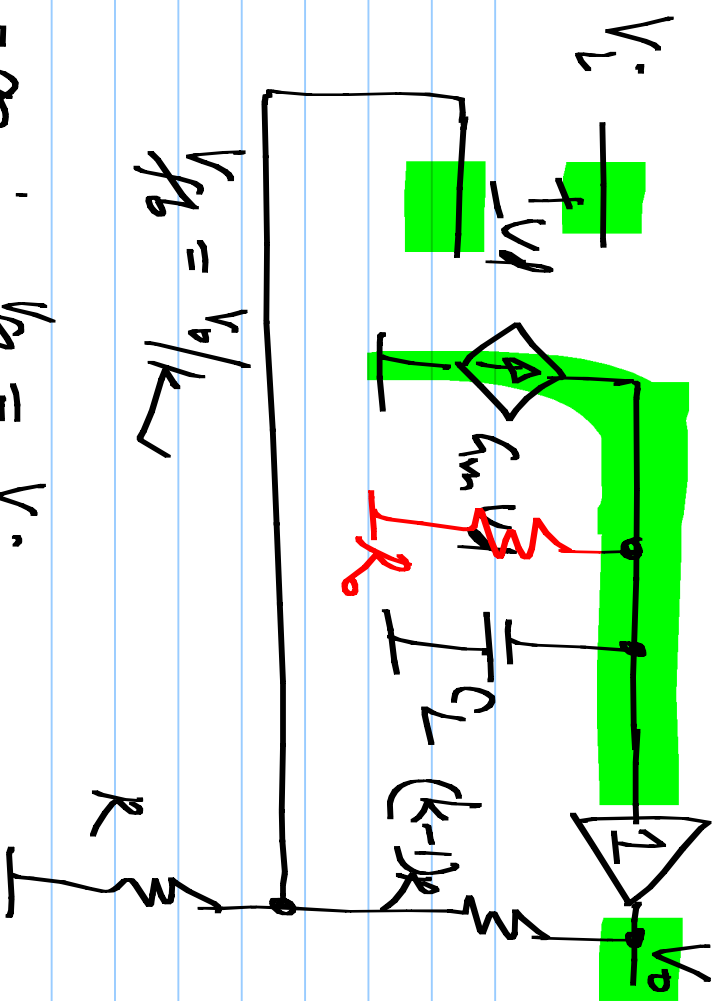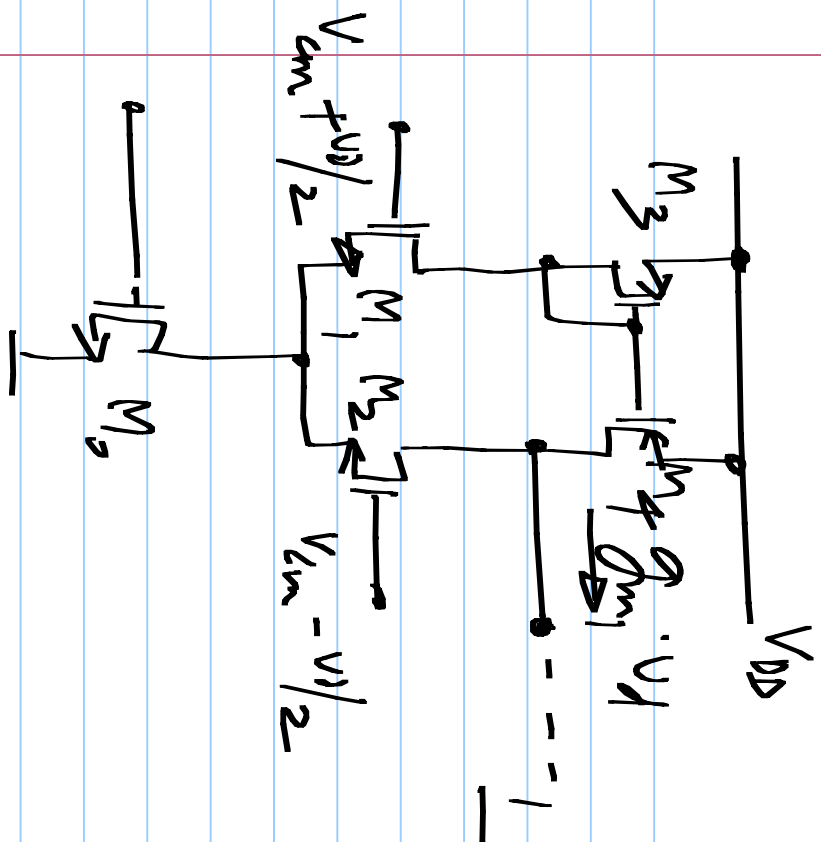

$$R_o = \infty ; \quad v_b = v_i$$

$$R_o < \infty ; \quad v_i - v_b = \frac{v_o}{g_m R_o}$$

Steady state error

With $R_o < \infty$;

$$\frac{V_o}{V_i} = k \cdot \frac{1}{1 + \frac{k}{A_m R_o}}$$

$$\frac{1}{1 + \frac{k}{A_m R_o}} \text{ — dc loop gain}$$

$$\frac{V_o}{V_i} = k \cdot \frac{1}{1 + \frac{k}{A(s)}}$$

$$= k \cdot \frac{1}{1 + \frac{k}{A(s)}}$$


opamp's dc gain

$$V_o = k V_i$$

$$\frac{1}{1 + \left(\frac{k}{A_m R_o} \right)}$$

$$\approx k V_i \left[1 - \frac{k}{A_m R_o} \right]$$


rel. error

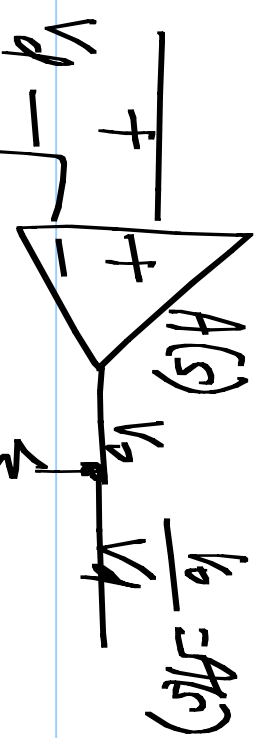

$$k \cdot \frac{L}{1+L} = \frac{1}{\frac{1}{k} + \frac{1}{L}}$$

$$\frac{L}{1+L} = \frac{1}{1 + 1/L}$$
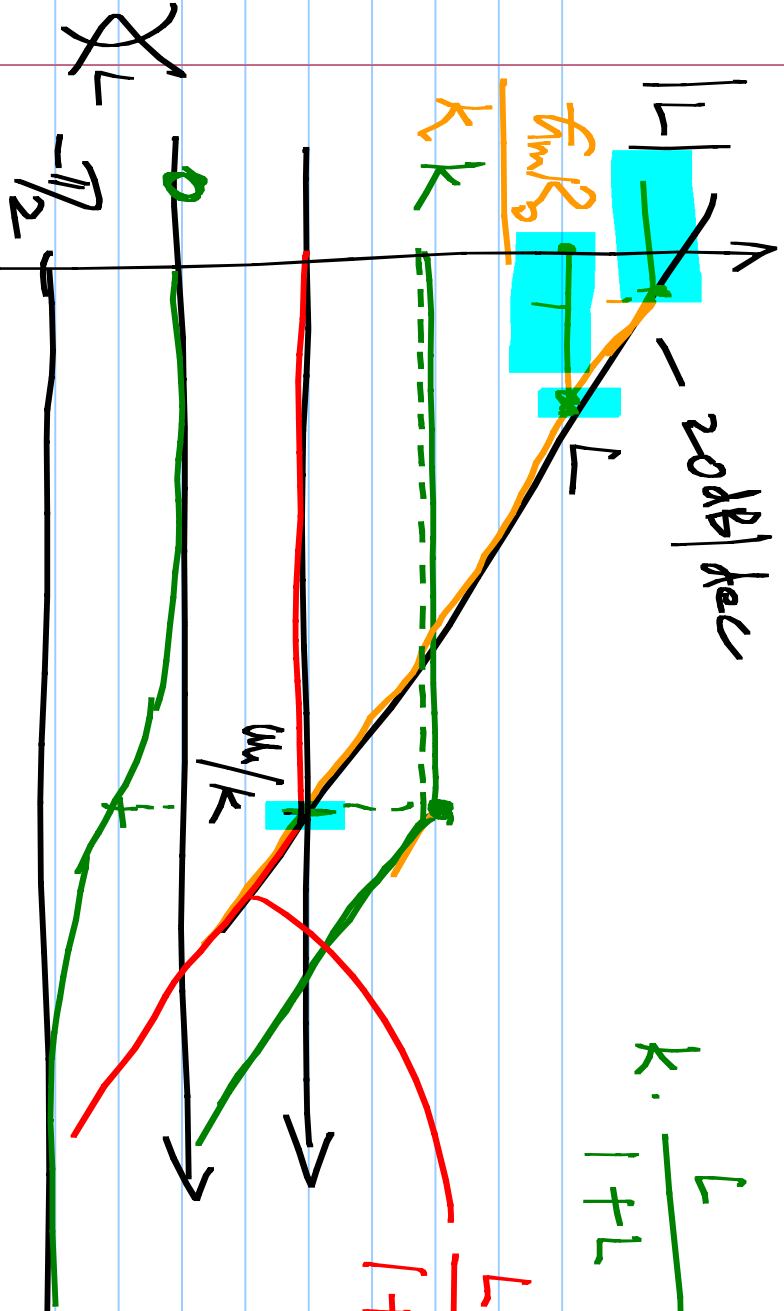
$$\frac{L}{1+L} = \frac{1}{1 + \frac{s}{\omega_n/k}}$$




$$A(s) = \frac{\omega_n}{s} = \frac{g_m}{sC_L}$$

$$A(s) = \frac{g_m}{sC_L + G_o}$$

$$A(s) = \frac{g_m}{sC_L + g_m} = \frac{1}{\frac{sC_L}{g_m} + \frac{g_o}{g_m}} \approx \frac{g_m}{sC_L}$$

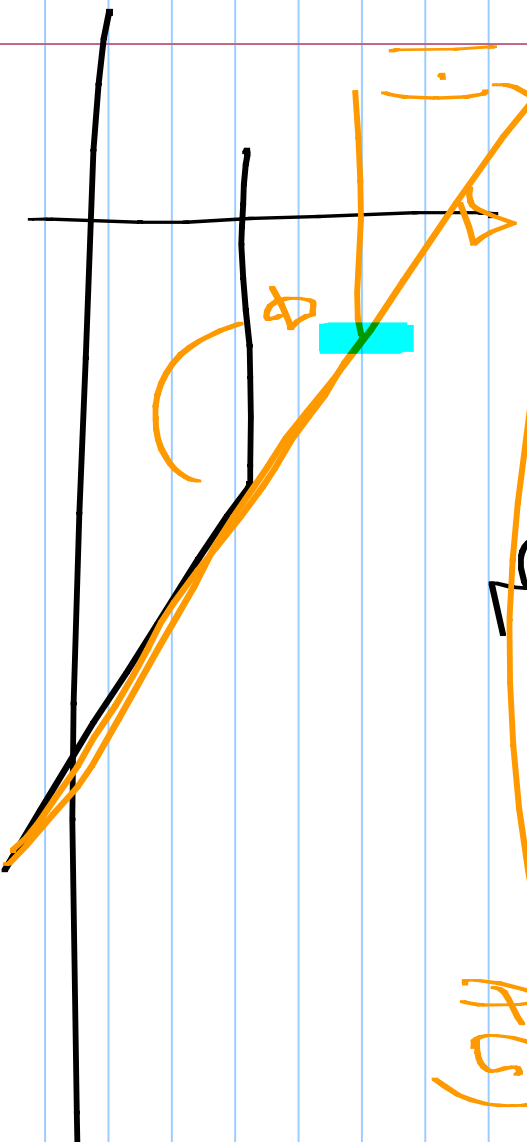
orig: $A(s) = \frac{g_m}{sC_L} = \sqrt{\frac{sC_L}{g_m} + \frac{g_o}{g_m}} \quad \text{!} \quad s = j\omega$





$$\frac{1}{\frac{s}{\omega_n} + 1} \quad \omega_n = \frac{g_m}{C_L}$$

$\omega \rightarrow \infty$

$$V_0 = \frac{f}{\dots}$$

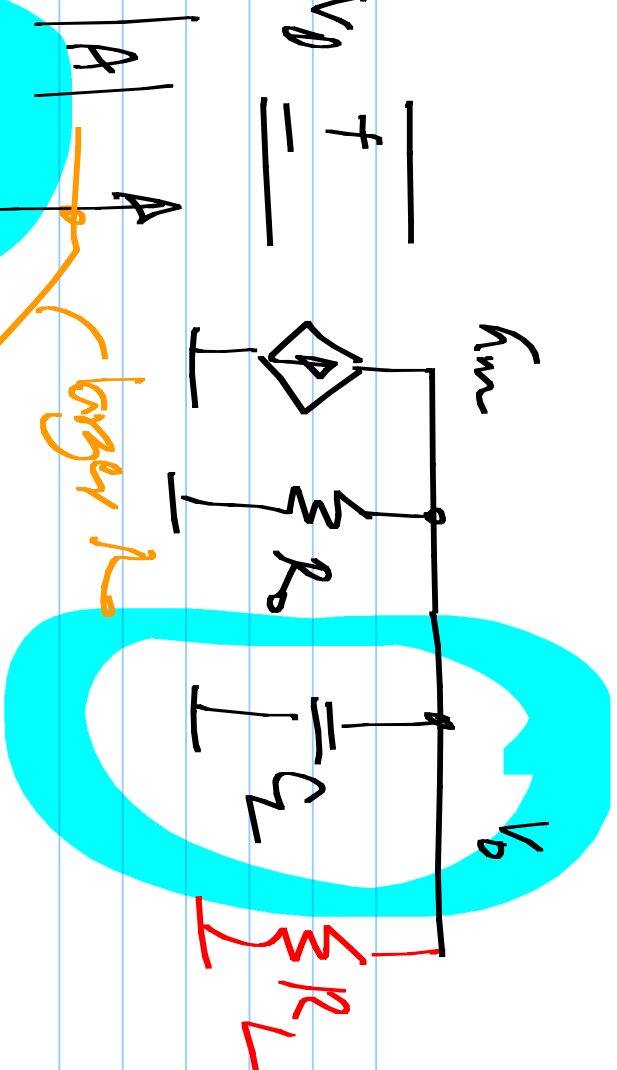

$$C_{in} R_0 (1/12)$$

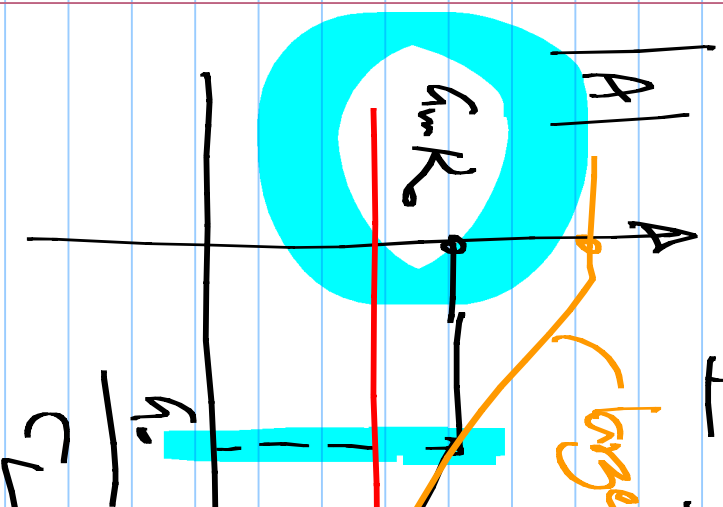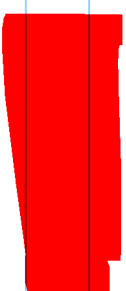

$$v_{in} = \frac{C_{in}}{C_L}$$

Single-stage opamp: $DC \text{ gain} = g_m R_o$

* Increase dc gain by increasing R_o

(Cascode opamp)

↓
Doesn't work if there is a resistive load

(dc gain = $g_m R_L$) $R_L < R_o$

