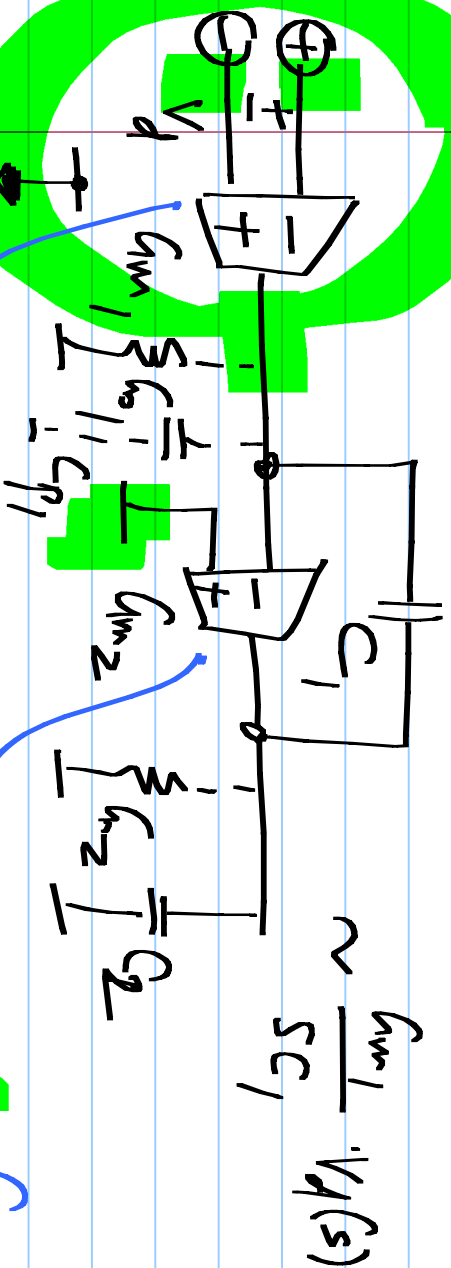



Lecture 29 16/3/2016

# Two-stage miller compensated opamp.



differential pair

Common source amplifier

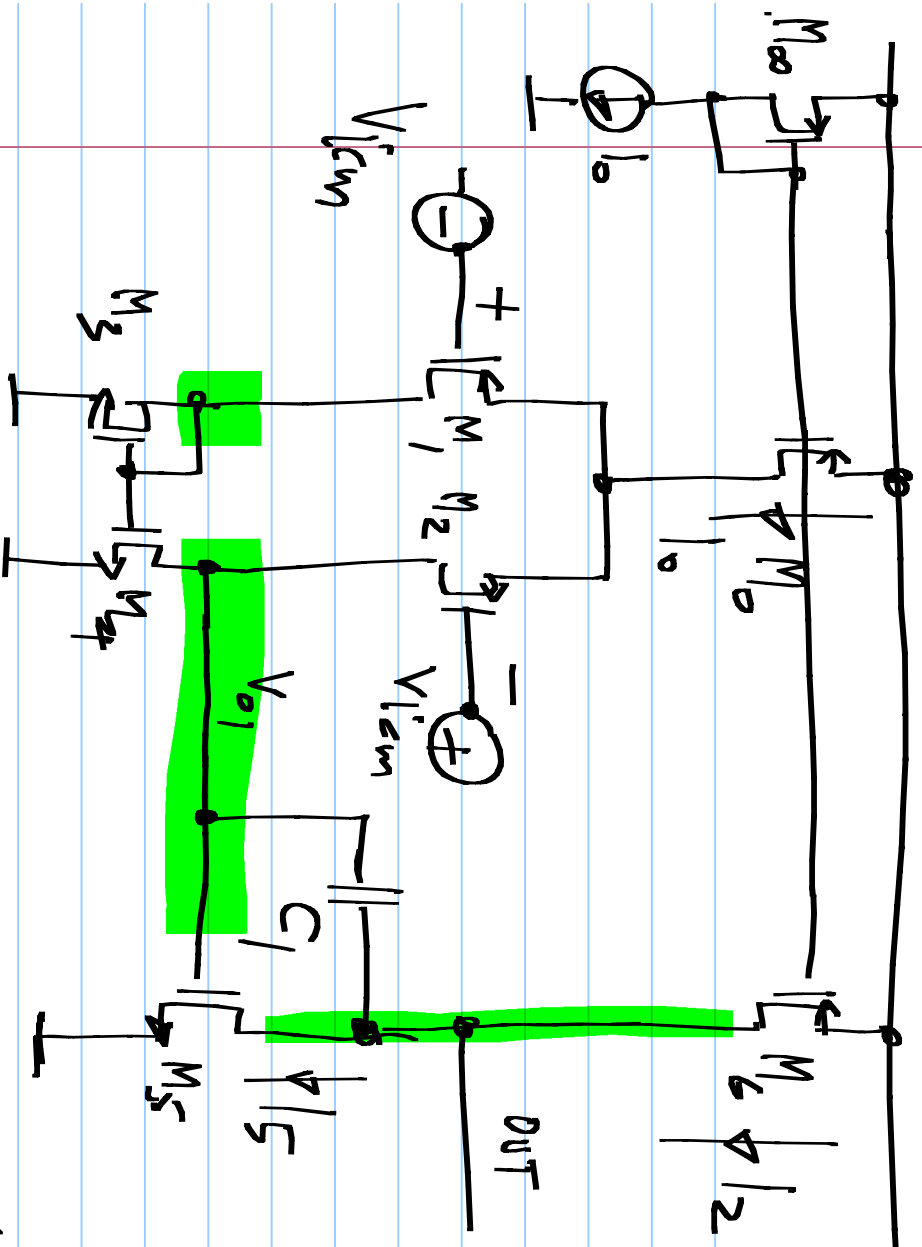


Two stage opamp


$$w_1 = \frac{g_{m1}}{C_1}$$

$$g_{m2} = g_{m5} = \sqrt{2 \cdot \mu_p C_{ox} \frac{W_5}{L_5} I_5}$$

$$g_{m1} = \sqrt{I_0 \cdot \mu_p C_{ox} \frac{W_1}{L_1}}$$
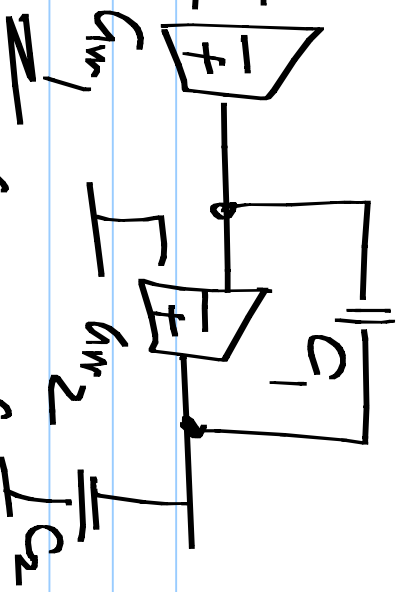
$$\frac{g_{m2}}{C_2} > \frac{g_{m1}}{C_1}$$




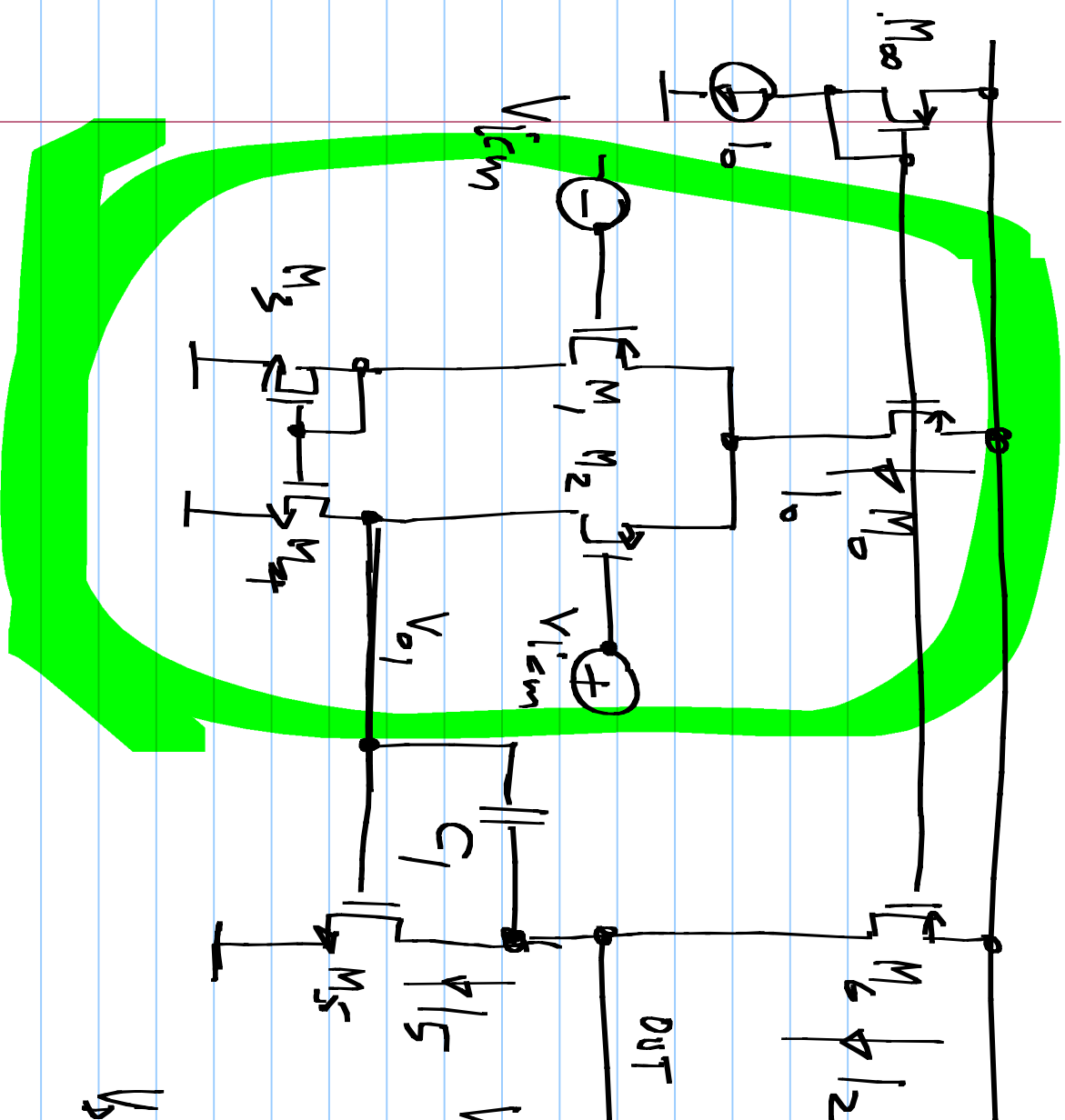



$$A_o = \frac{g_{m1}}{g_{m1} + g_{m3}} \cdot \frac{g_{m5} + g_{m6}}{g_{m5}}$$

$$V_{ds3}/2 \leq V_{in} \leq V_{DD} - (V_{ds10}/2 + V_{ds11}/2 + V_{t1})$$
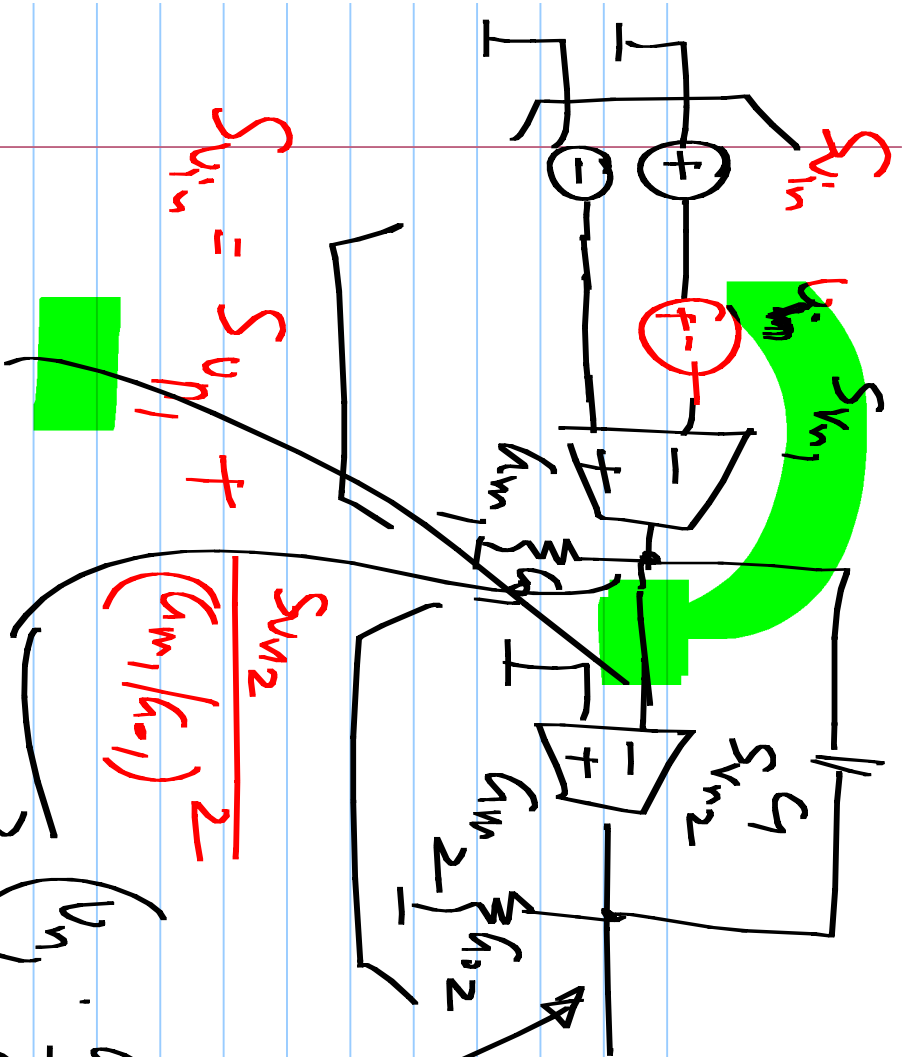
$$V_{ds2}/2 \leq V_D \leq V_D - V_{ds12}/2$$


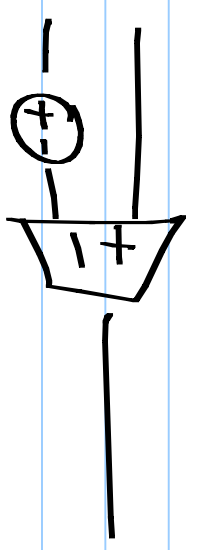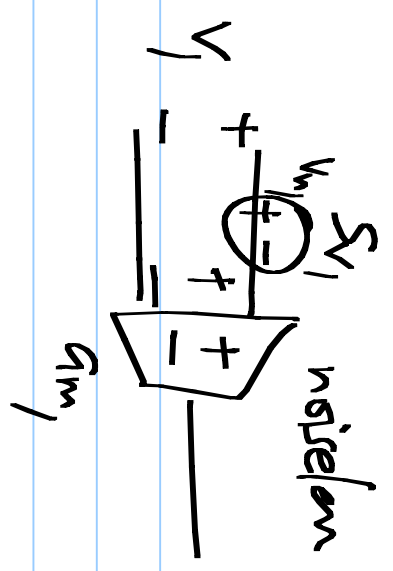
$$S_{V_{in}} = S_{V_{n1}} + \frac{S_{V_{n2}}}{(G_{m1}/G_{o1})^2}$$



$$S_{V_{on}} = S_{V_{n1}} \left( \frac{G_{m1}}{G_{o1}} \cdot \frac{G_{m2}}{G_{o2}} \right)^2 + S_{V_{n2}} \left( \frac{G_{m2}}{G_{o2}} \right)^2 \left( -\frac{G_{m2}}{G_{o2}} \right)^2$$