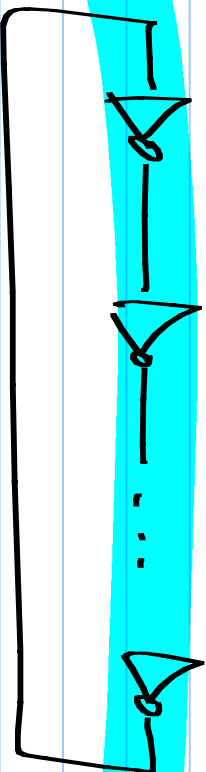





Lecture 19

Jitter / Phase noise in VCOs





VCOs :




ring oscillators

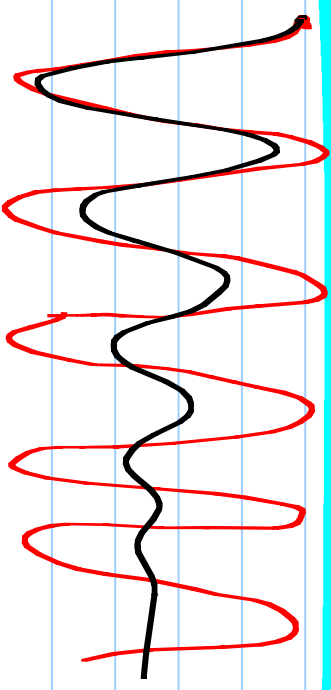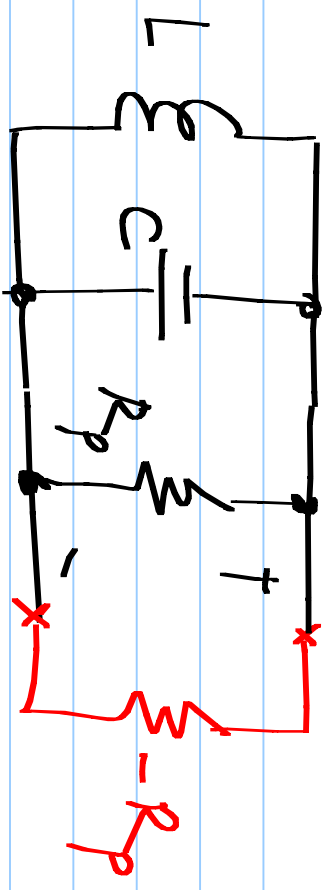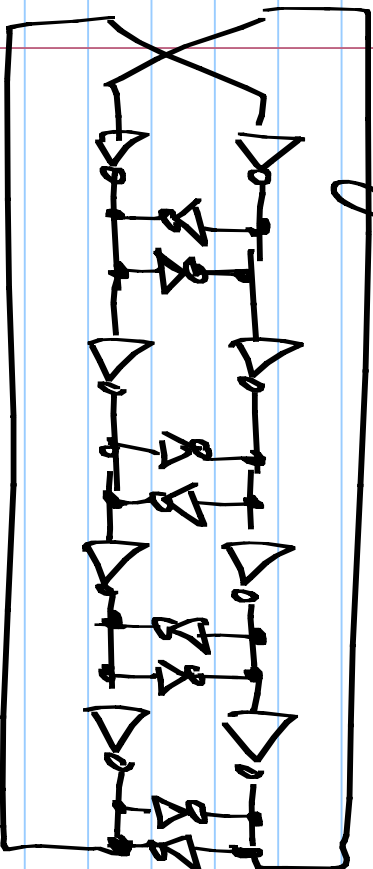

$$\frac{1}{2\pi\sqrt{LC}}$$

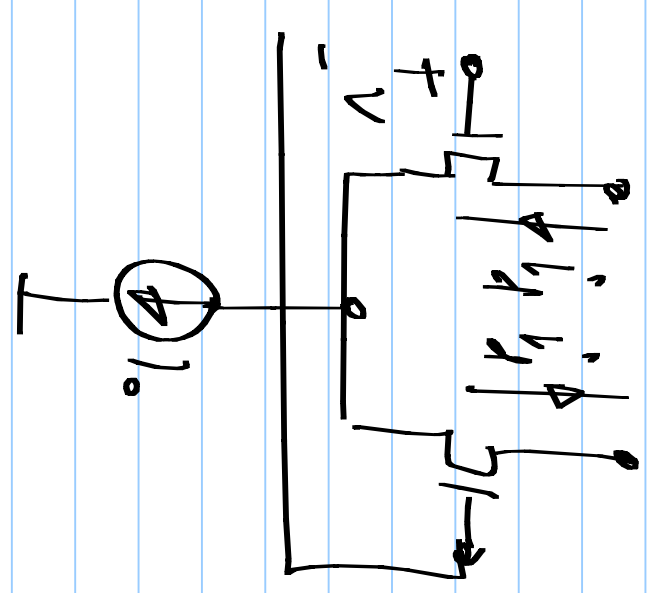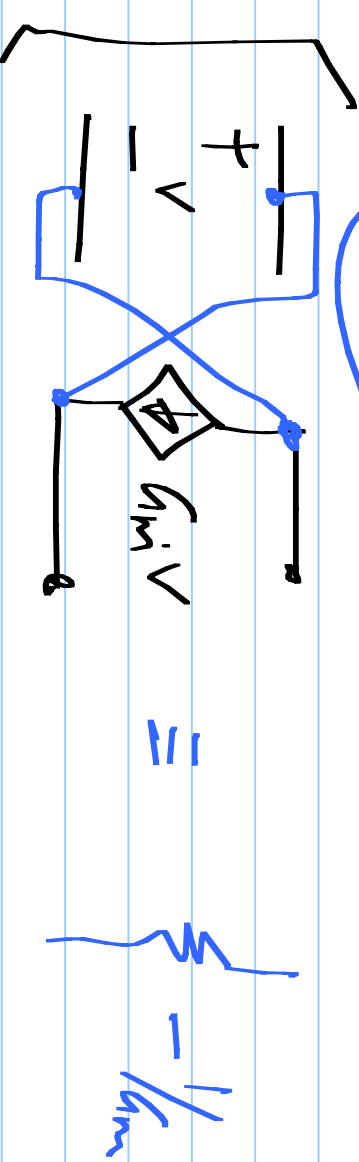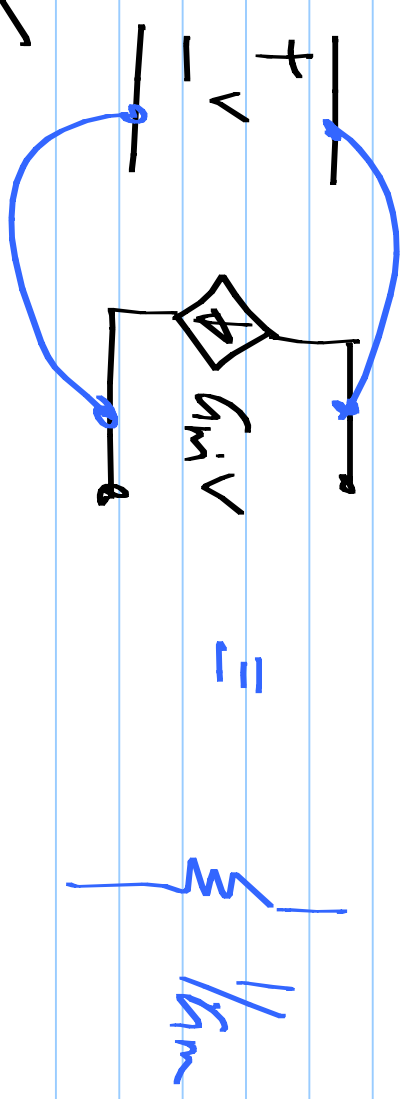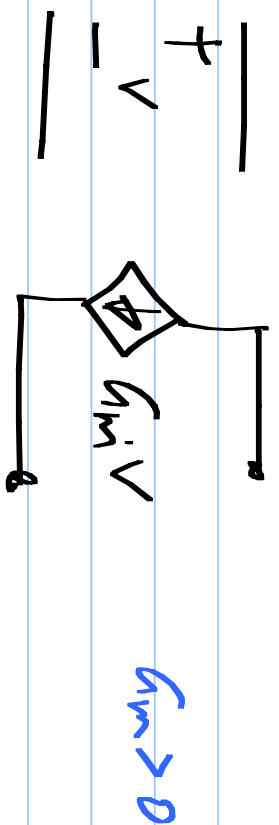

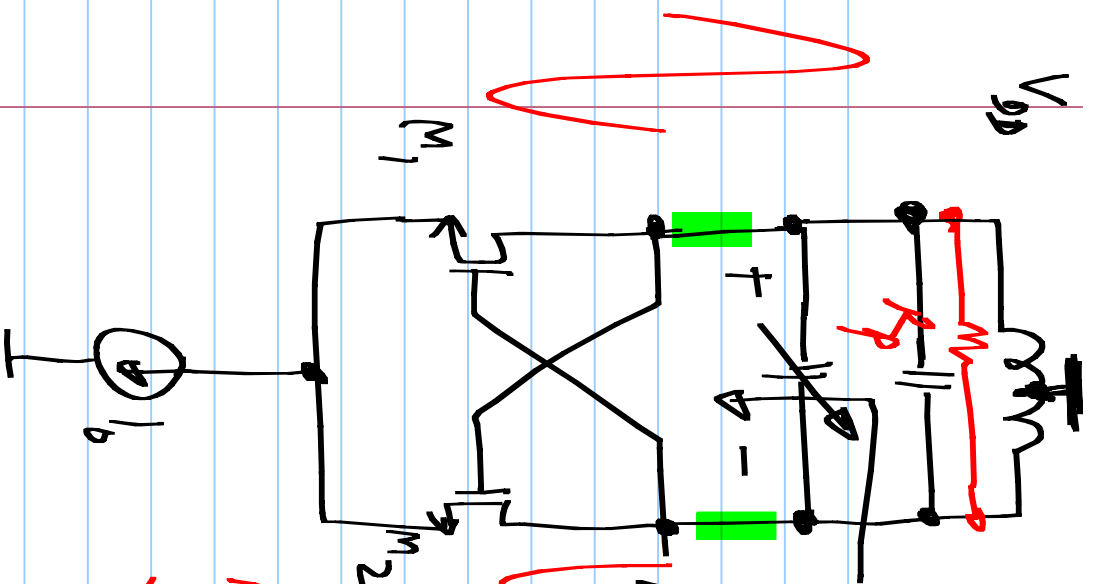

— on L on —

$$R_{in} = \frac{-2}{g_{m1}}$$

Transconductance of M_1 & M_2

$$\omega = 1/\omega/2 = g_{m1}$$



LC oscillator

Small signal resistance

$$Q = CV$$

$$\sqrt{\frac{2}{g_{m1}}} < R_p \quad Q = Q(V)$$

for oscillation

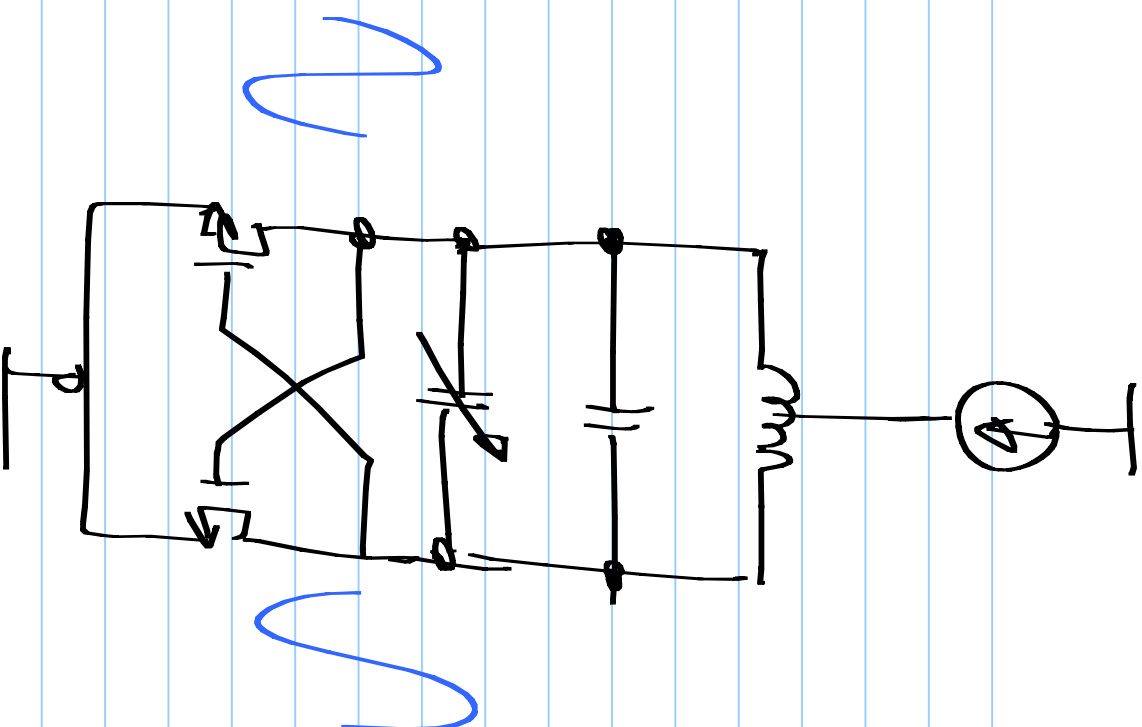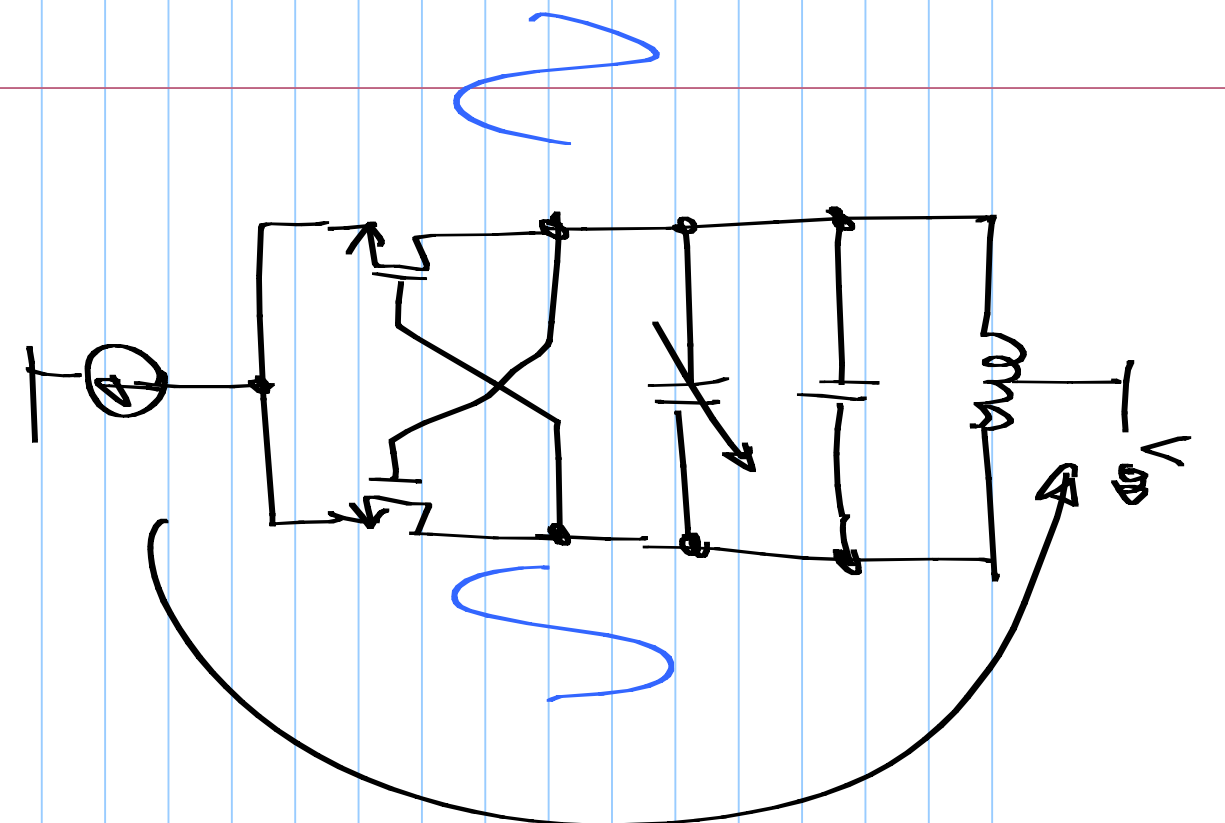

* Ring oscillators: Active elements & C

- High phase noise (MOS)

- Very compact (small area)

* LC oscillators: L, C & active elements

- Low phase noise

- Large area

Phase noise / Jitter

Inherent noise of oscillators

Ideal periodic waveform : $\cos(2\pi f_0 t)$

w/ phase disturbance : $\cos(2\pi f_0 t + \phi_n)$

$$\phi_n \ll 1 \text{ rad}$$

— zero —

$$\cos(2\pi f_0 t) \cdot \cos(\phi_n) - \sin(2\pi f_0 t) \cdot \sin(\phi_n) \quad \text{average}$$

1

$\approx \phi_n$

modulator

$$\cos(2\pi f_0 t)$$

$$- \phi_n \sin(2\pi f_0 t)$$

$$\sin(2\pi f_0 t)$$

by ϕ_n

$$\phi_n = a \cdot \cos(2\pi f_n t)$$


$$| \text{ideal} : \cos(2\pi f_c t) |$$

$$\cos(2\pi f_c t)$$

$$w/ \text{ phase } - \phi_n \sin(2\pi f_c t)$$

disturbance :
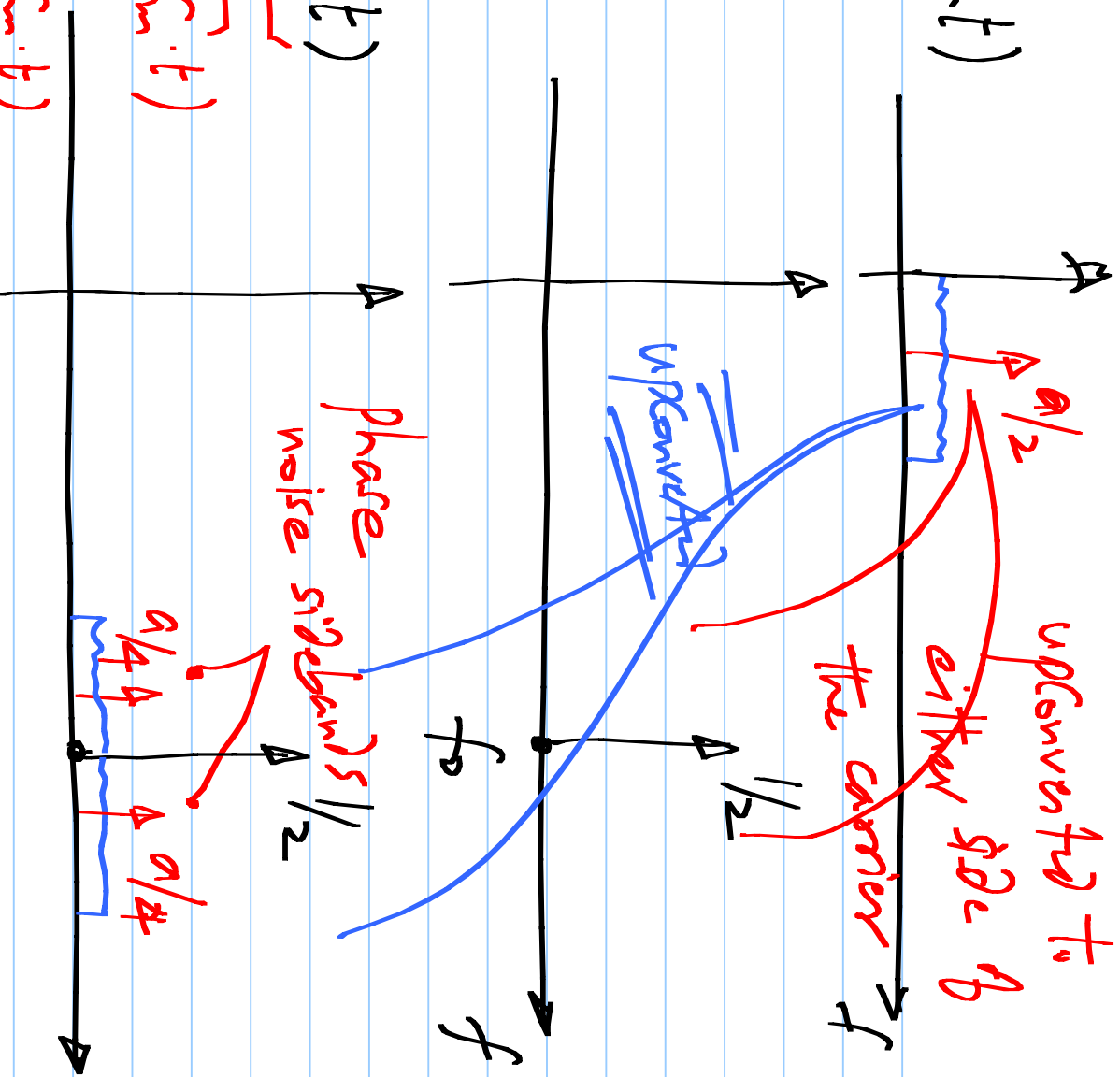
$$\frac{a}{2} \sin(2\pi f_c + f_n \cdot t) + \frac{a}{2} \sin(2\pi f_c - f_n \cdot t)$$



Real oscillators:

Amplitude limited
(steady state solution has
a particular amplitude)