
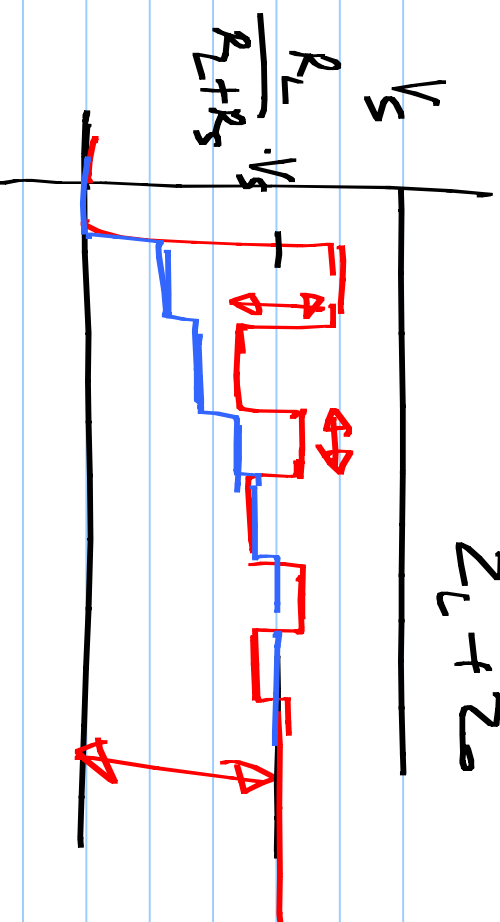


Lecture 30

$$L_0, C_0, R_0, G_0$$


$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

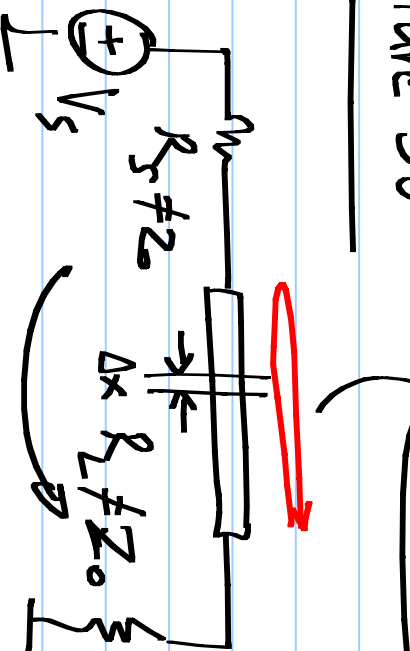


- * Ideal, lossless T-line, w/ mis-termination
- $Z_0 = \sqrt{\frac{L}{C}}$: real number

- * Series resistance — transfer fn. diagram

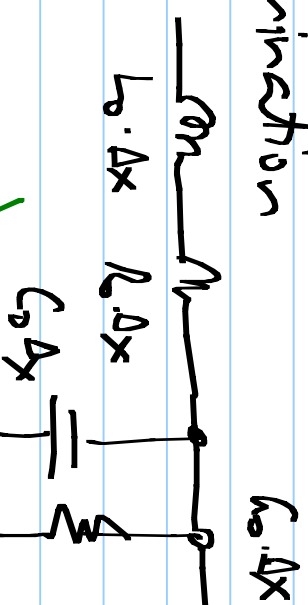skin effect $\rightarrow$ resistance $\uparrow$ freq. the response spread out




Lossy transmission line:

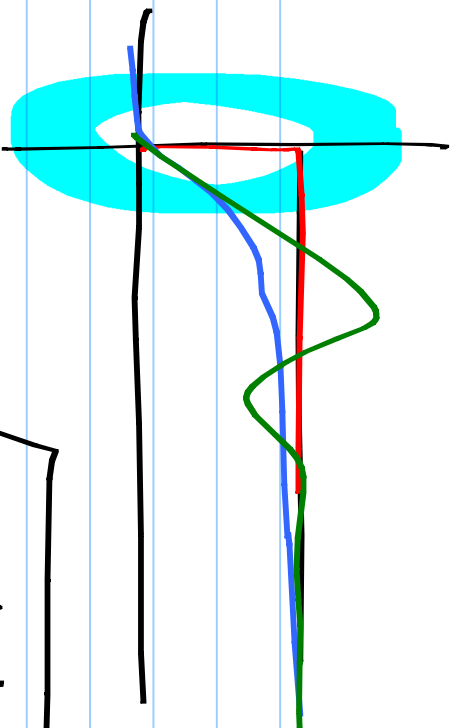


$$Z_0 = \sqrt{\frac{R_0 + j\omega L_0}{G_0 + j\omega C_0}}$$

Z_{real}

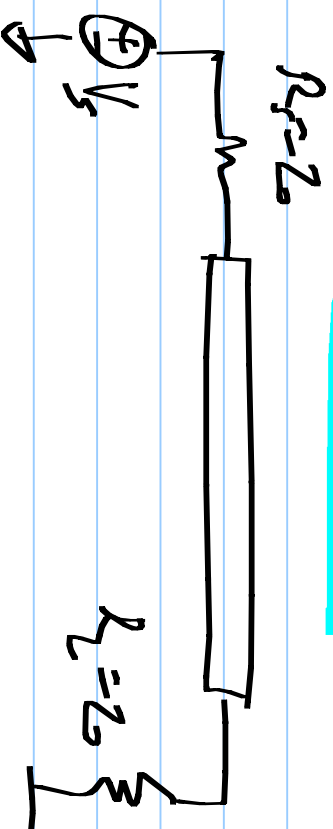
$$\frac{L_0}{R_0} < \frac{C_0}{G_0} \quad \text{Distortionless}$$




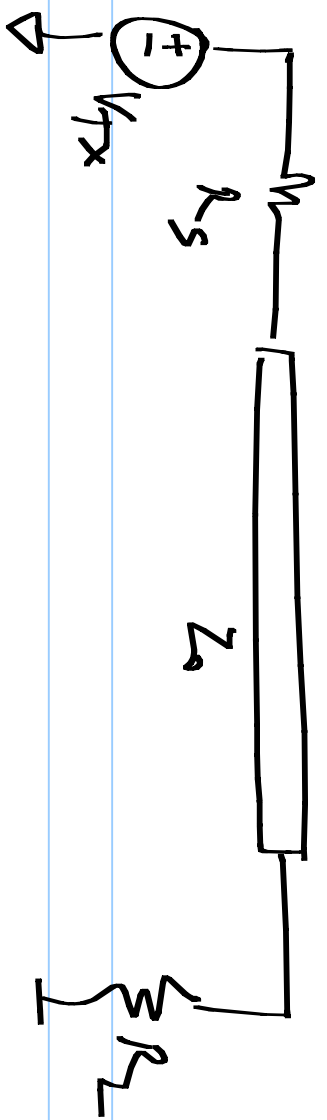


T_x


R_x

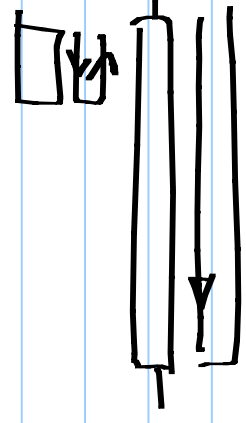


T_x chip

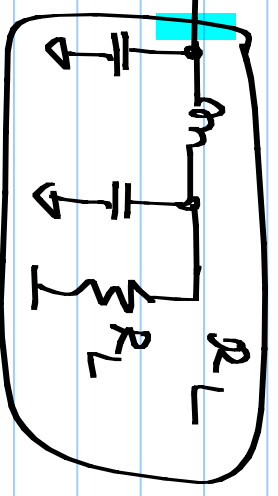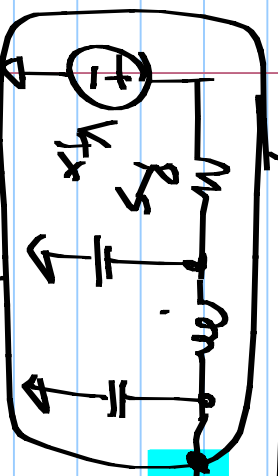

R_x

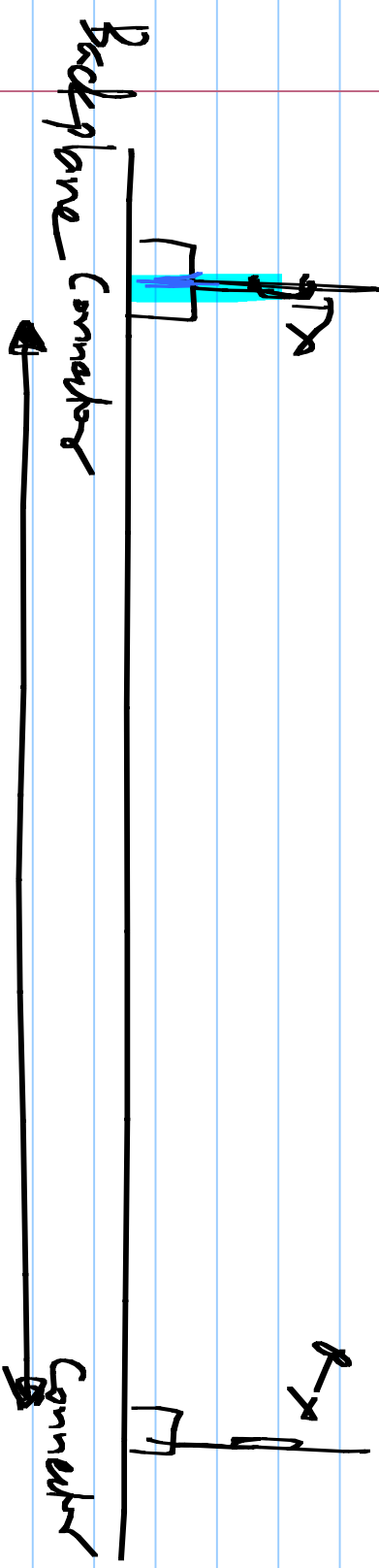


1.1

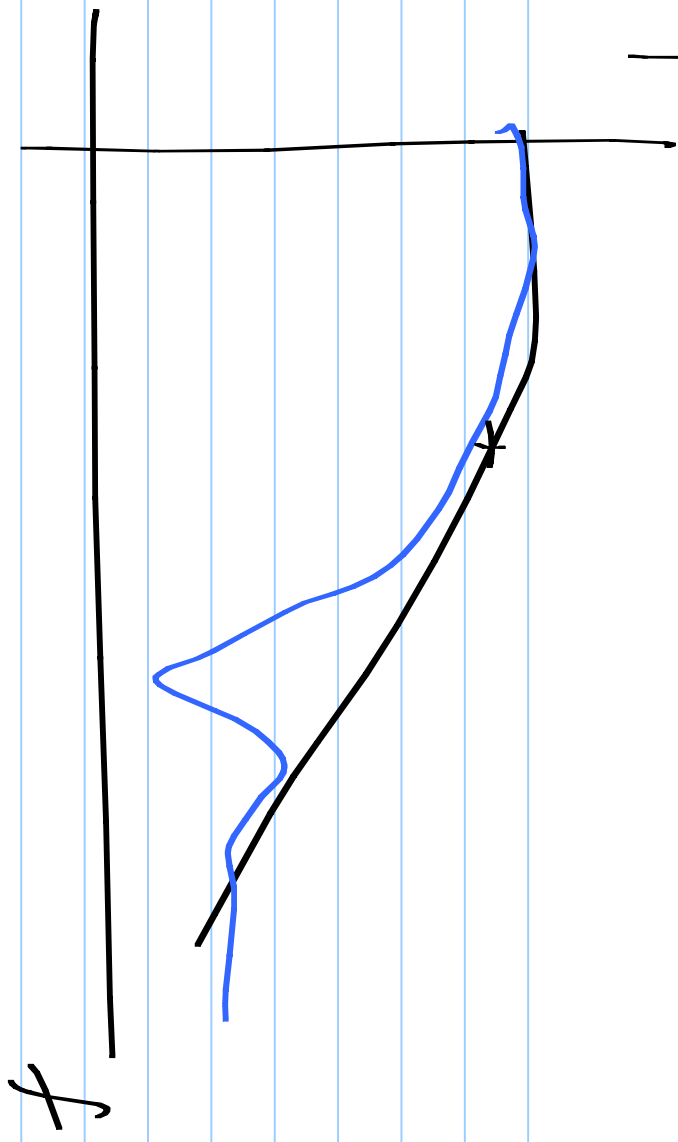


Crosstalk:


$R_{X1} + R_{X2}$

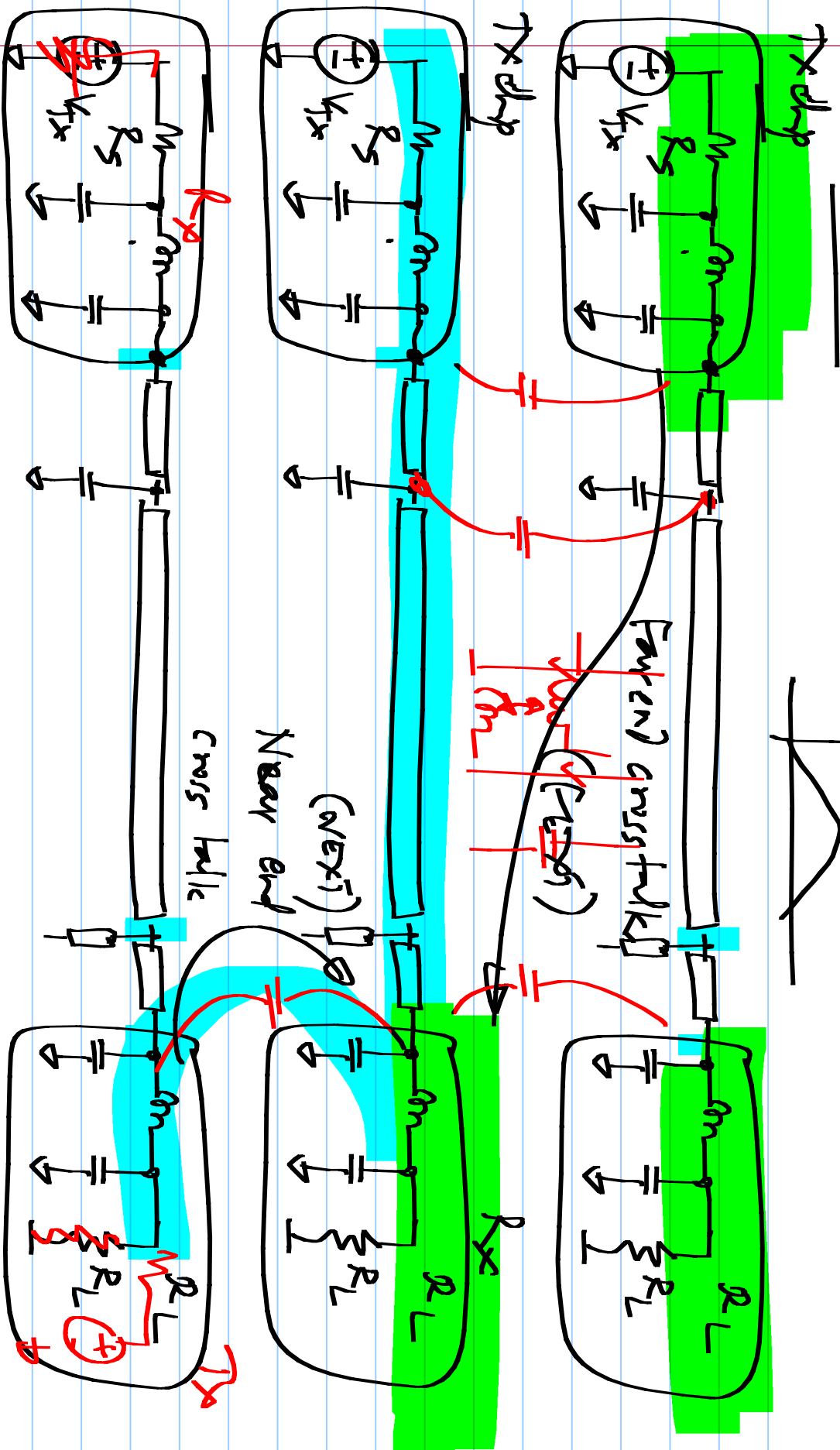


$$T_{x_1 - p_{x_1}}$$

$$T_{x_2 - p_{x_2}}$$

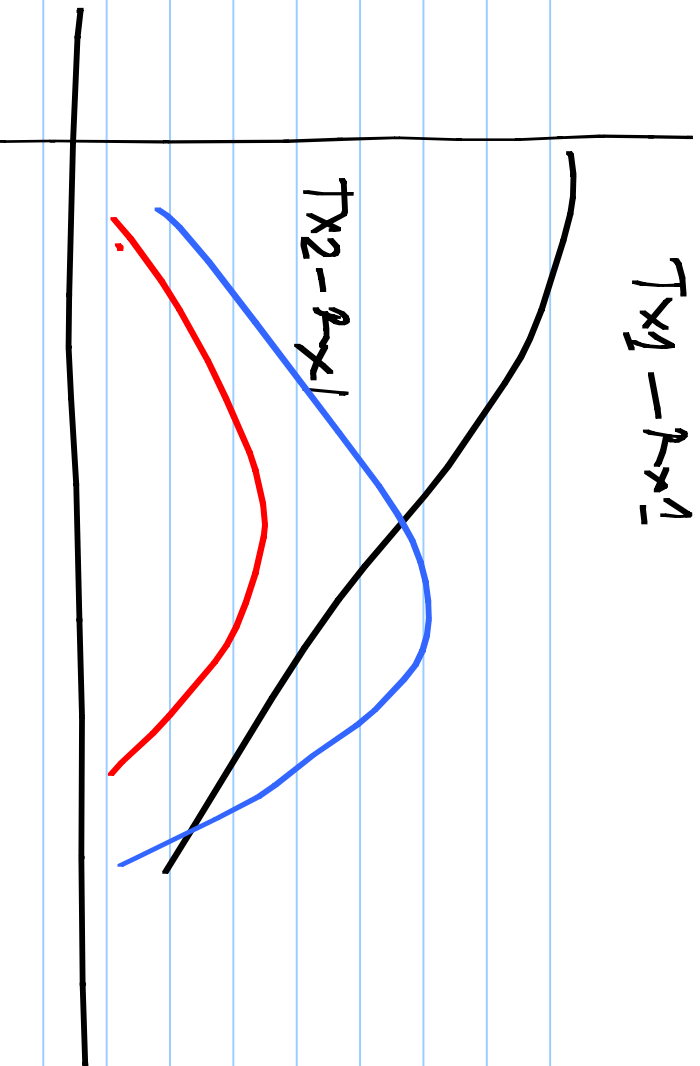

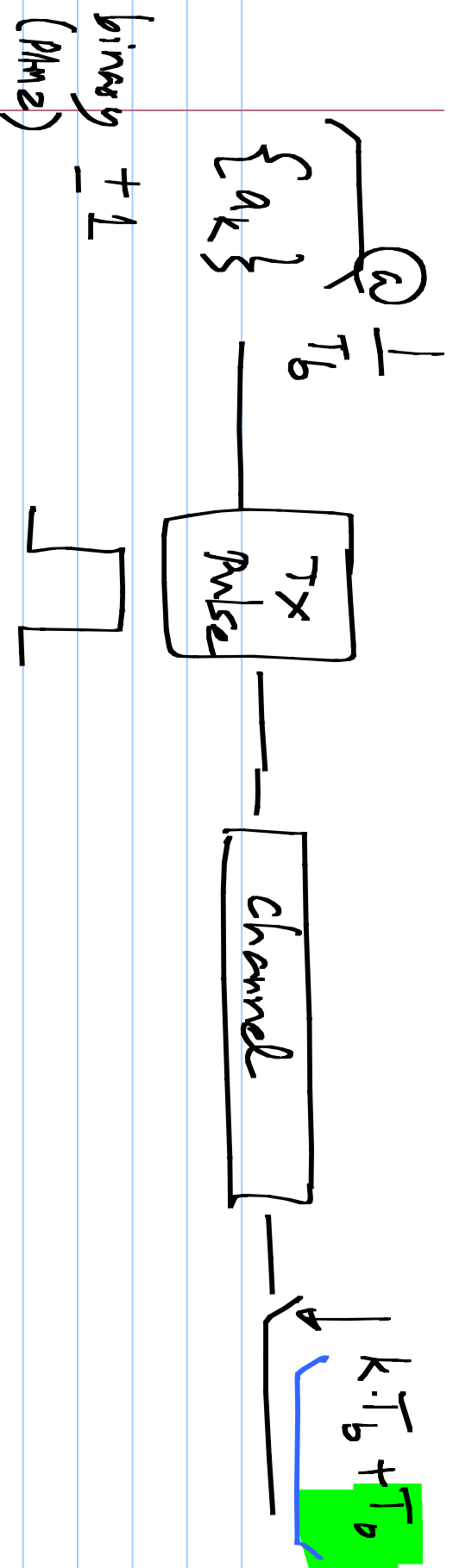


PAM4 $\pm 1, \pm 3$

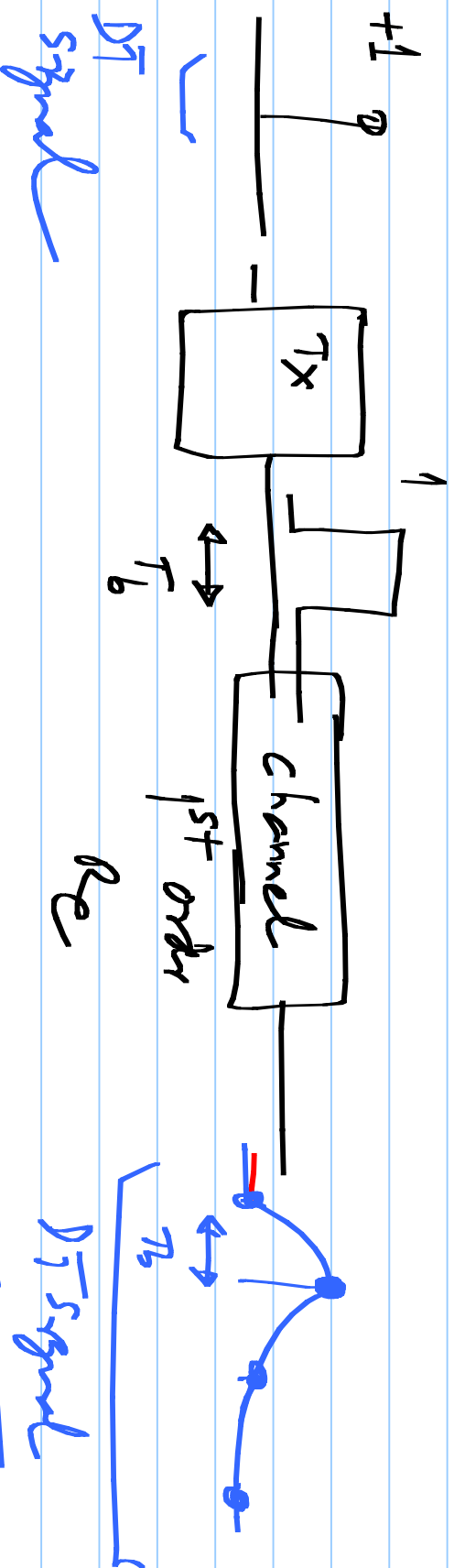

1st order RC

$$1 - 1/e$$

$$T = T_b$$


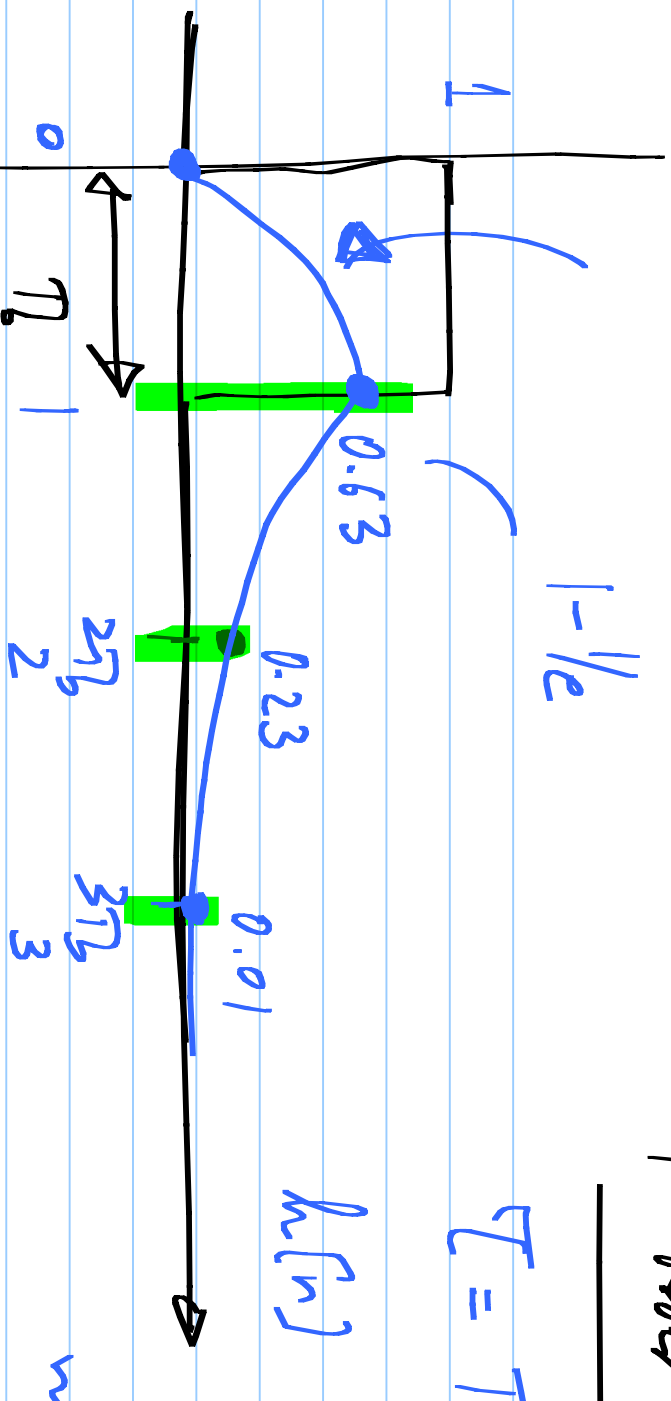


$$\{a_k\}$$

$$\sum_k a_k h[n-k]$$

CT response to a single "1"

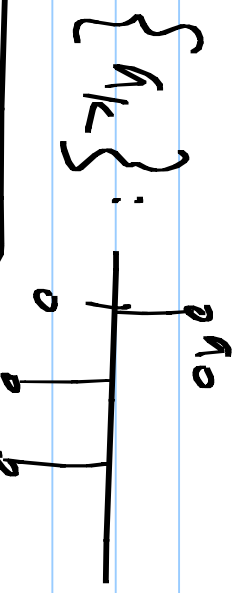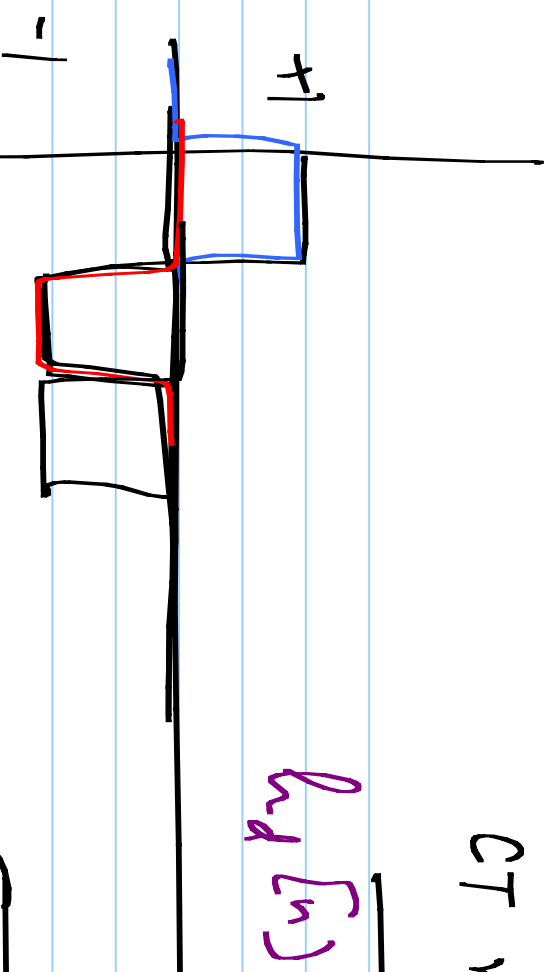$h_d[n]$ sampled at $T_0 + kT_b$
 $h_c(t)$



$\sum_k a_k h_c(t - kT_b)$

$a_0 \cdot h_c(t)$

$a_1 h_c(t - T_b)$

$a_2 h_c(t - 2T_b)$

$\sum_k a_k h_d[n - k]$

