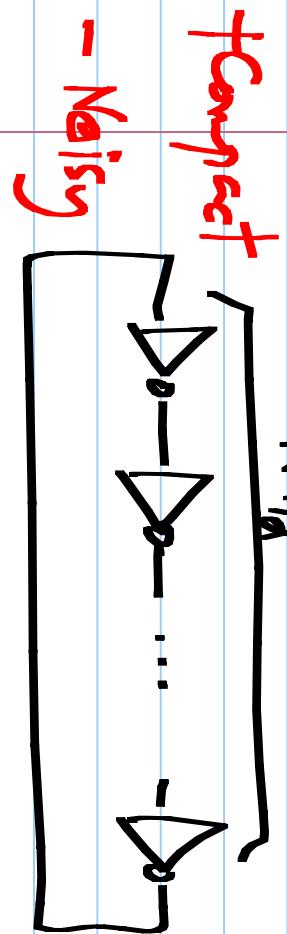


EE 6322


VCO phase noise

16/2/2018



+ Widely tunable period \Rightarrow inc. $= 2N \cdot T_d$

Ring oscillator

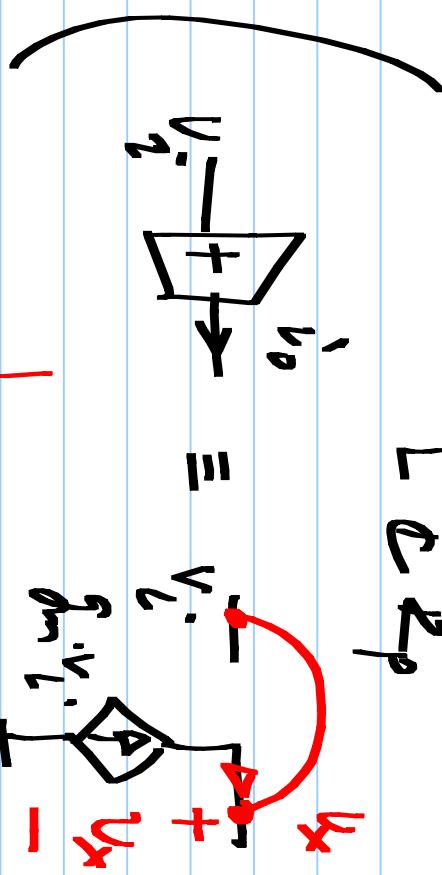

+ lower noise


- occupying a large area
- Narrow tuning range

LC oscillator

$$f_0 \sim \frac{1}{2\pi\sqrt{LC}}$$

$\frac{1}{f_m}$

$\frac{1}{f_m}$

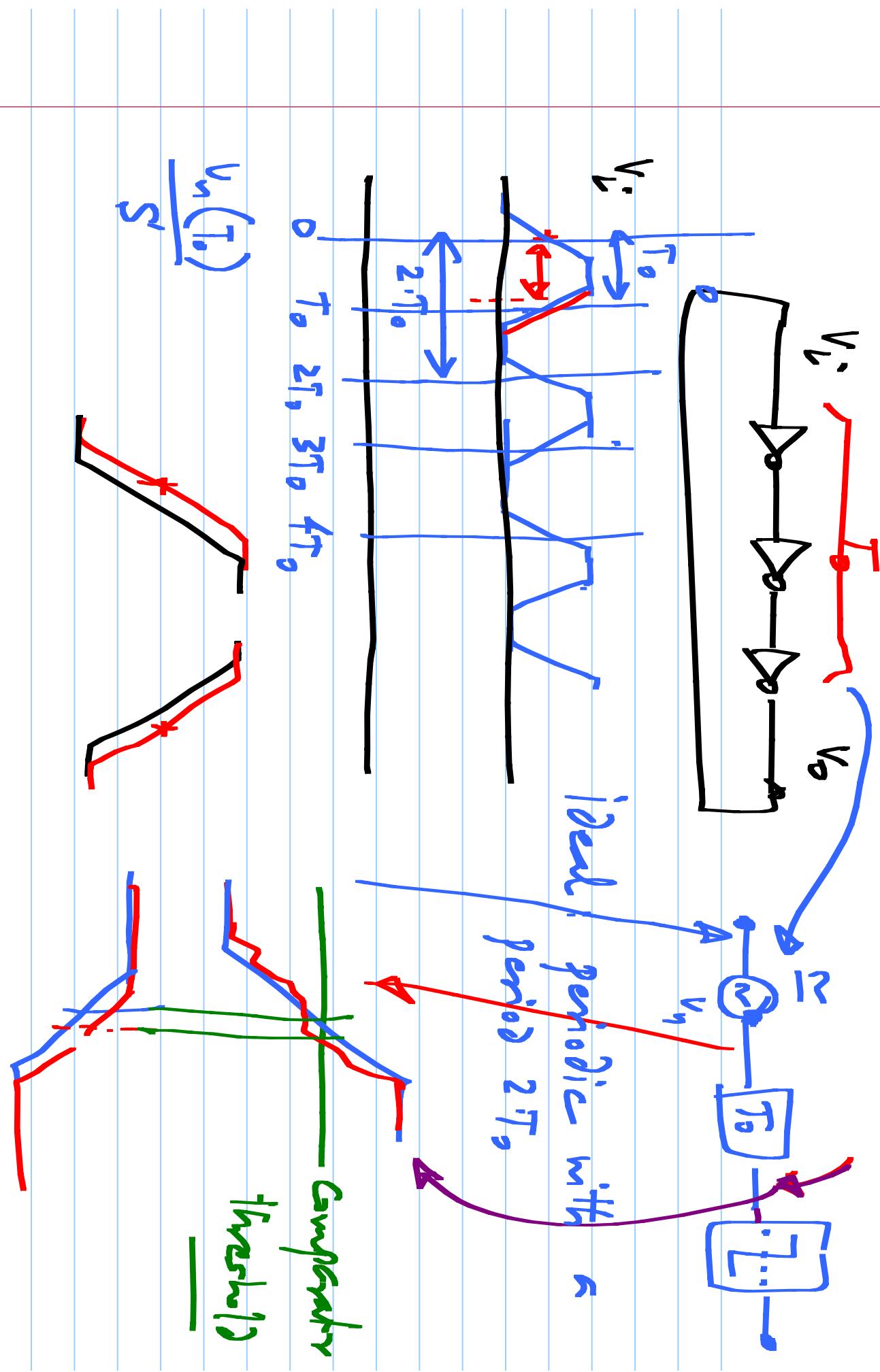


First transition at $t=0$ (by defn.)

$$\text{Second transition at } T_0 + \frac{v_n(t_0)}{\sum} \times \frac{2\pi}{2T_0}$$

$$T_{\text{min}} = 2T_0 + \frac{v_n(T_0)}{\sum} - \frac{v_n(2T_0)}{\sum}$$

$$T_{\text{max}} = 3T_0 + \frac{v_n(t_0)}{\sum} - \frac{v_n(2T_0)}{\sum} + \frac{v_n(3T_0)}{\sum}$$

$$T_{\text{min}} = " "$$

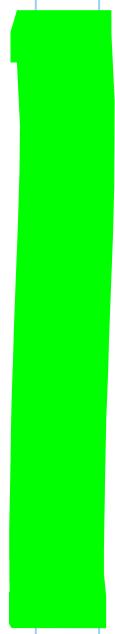

v_n : Input ref. noise of amplifier/delay line/comparator

Sample of v_n every T_0


$$f_{sc} = \frac{1}{2 \cdot T_0}$$

PSD of v_n

$$v_n(kT_0) : \sigma_{v_n}^2$$

white

$$2T_0 \sigma_{v_n}^2$$

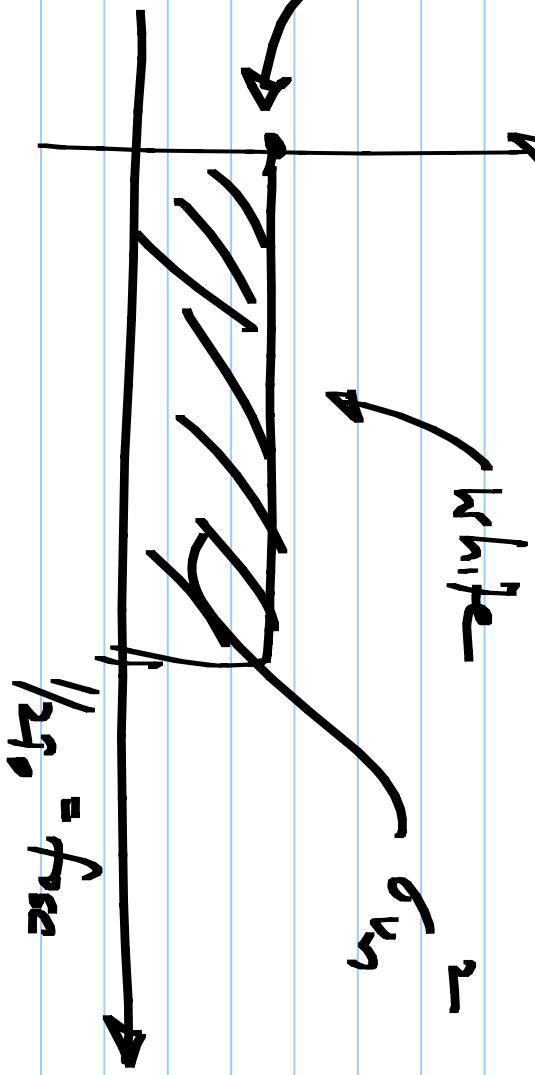

$$\frac{1}{2\pi} f_{sc}$$

Cont. time noise


$$\int_0^{\infty} S_x(f) df = \sigma_x^2$$

Discrete-time noise

$$(\text{Samples} @ f_s)$$

$$\int_{f_s/2}^{\infty} S_x(f) df = \sigma_x^2$$

One-sided spectral density

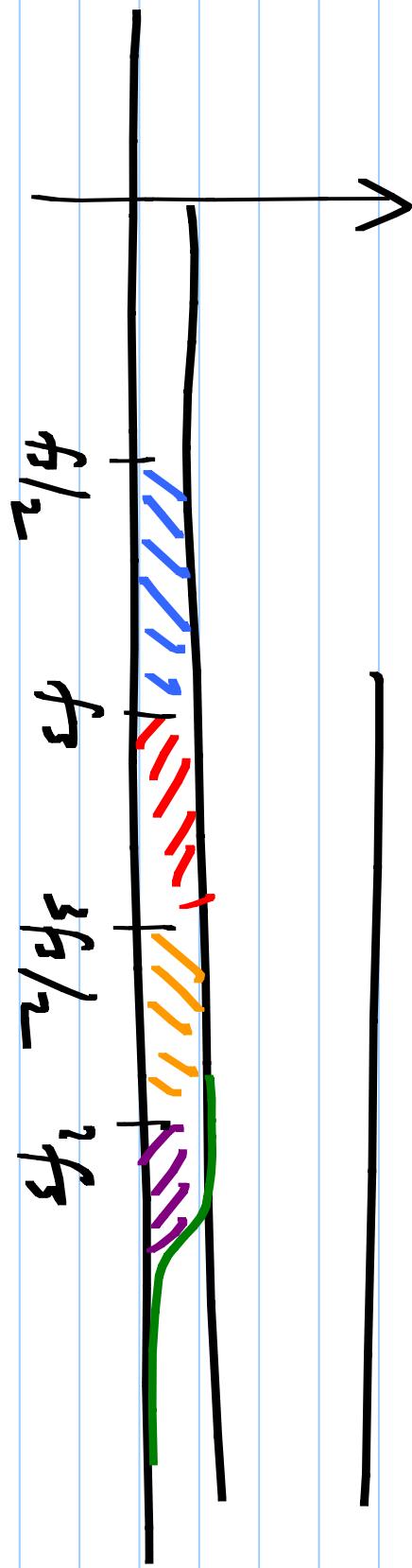


$f_l/2$

f_s


$3f_s/2$

f_h

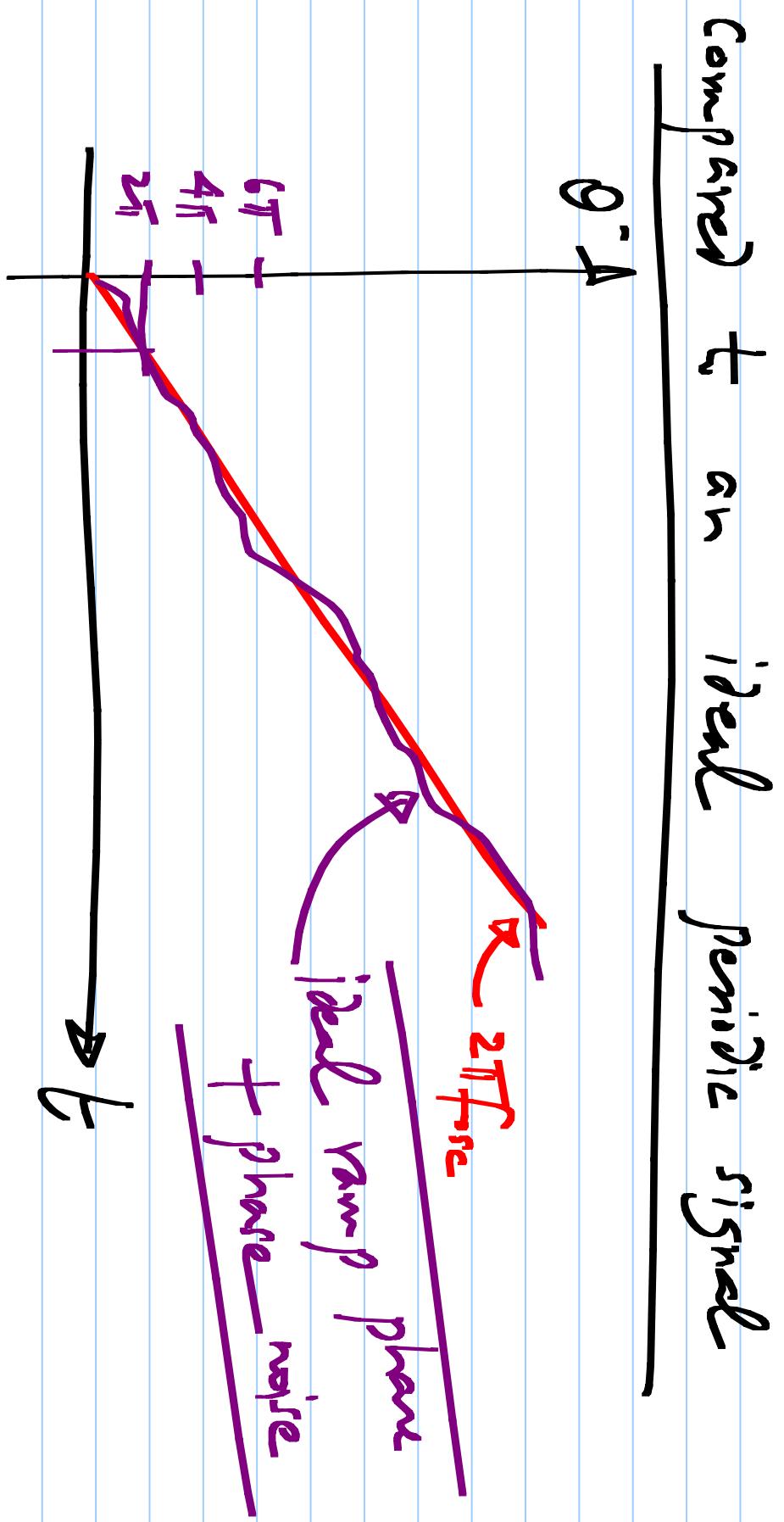Phase noise: shift in transition instants
(zero-crossing)



Actual Deviation (phase) | Ideal zero-crossings

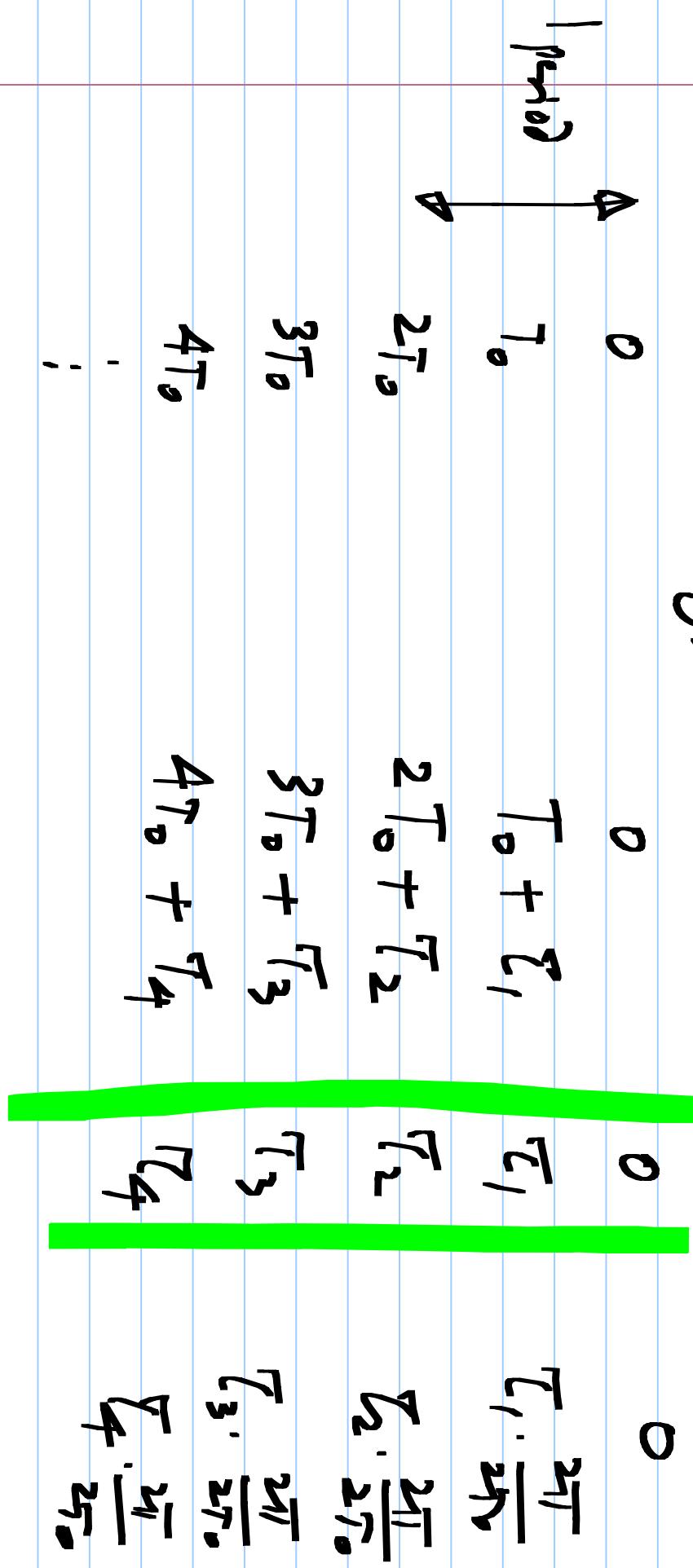

$$v_n(\tau_0)$$

$$\sum_{j=1}^k =$$

$$\tau_2 = \frac{v_n(\tau_0)}{\zeta} - \frac{v_n(2\tau_0)}{\zeta}$$

$$\tau_3 = \frac{v_n(\tau_0)}{\zeta} - \frac{v_n(2\tau_0)}{\zeta} + \frac{v_n(3\tau_0)}{\zeta}$$

if ζ is

$$v_n(k\tau_0)$$

same

$$\tau_k = \frac{v_n(k\tau_0)}{\zeta}$$

$$\tau_k - \tau_{k-1}$$

$$\tau_k - \tau_{k-1} = \frac{v_n'(kT)}{s}$$

width of k^{th} half-period = $(\tau_0 + \tau_k) - (\tau_0 + \tau_{k-1})$



$$= \tau_0 + \tau_k - \tau_{k-1}$$

$\rightarrow k^{\text{th}}$ half-period jitter: uncorrelated white

$$v_n'(z) = \frac{s}{(1-z^{-1})}$$